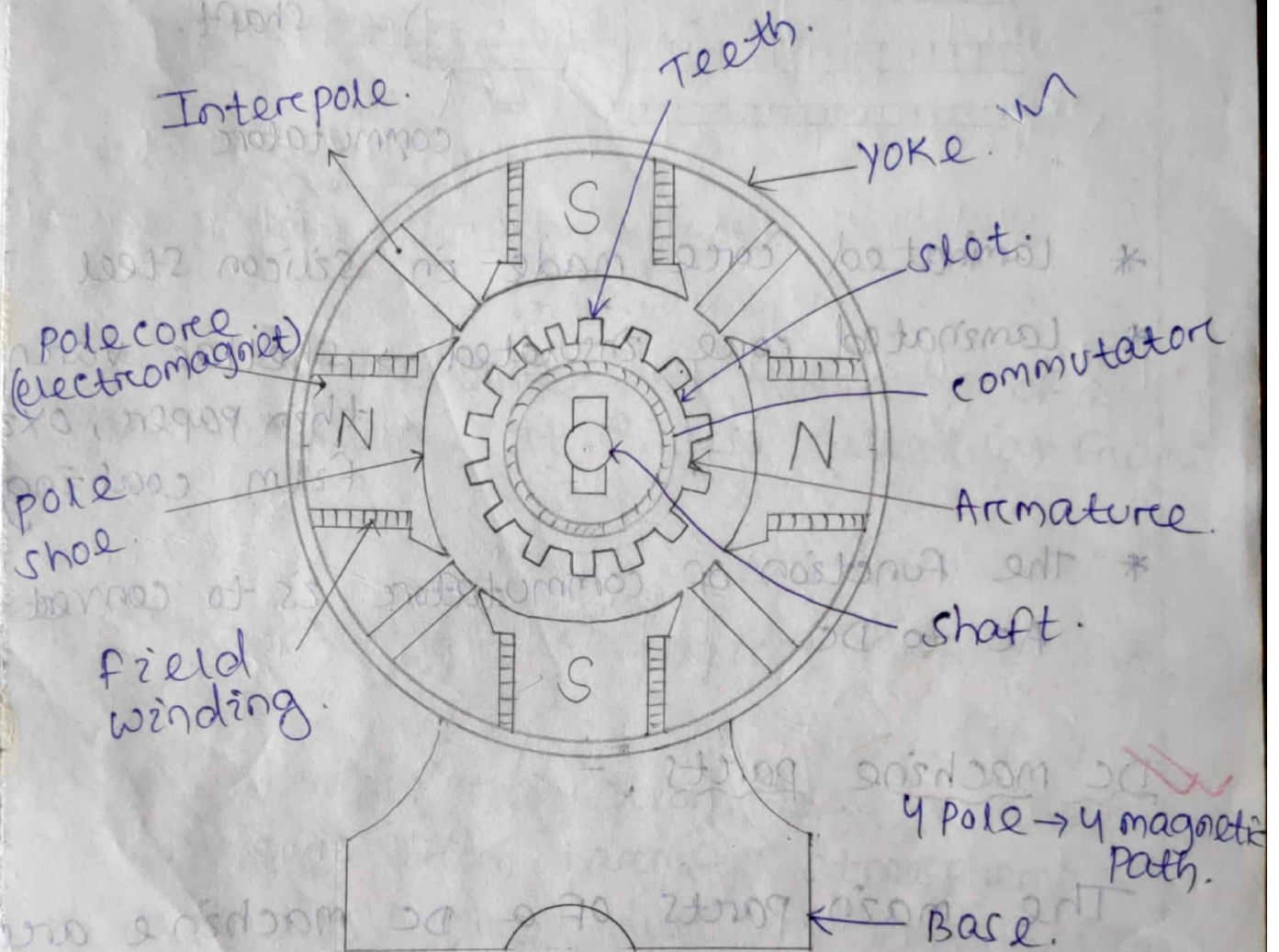


## Chapter - 1. (DC Generator.)


### Dc generator
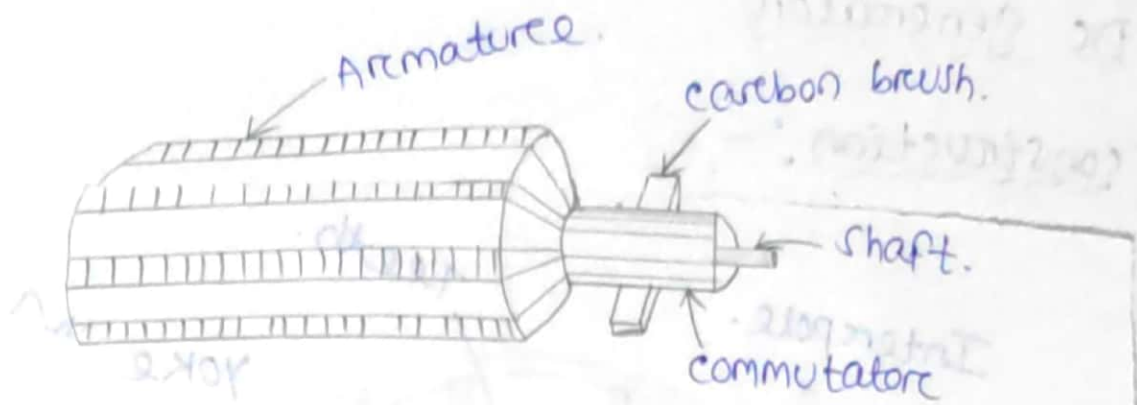
#### construction:-



- \* pole core and pole shoe made in laminated silicon steel
- \* Yoke made in cast iron or silicon steel, depending upon size.
  - small size  $\rightarrow$  cast iron.
  - big size  $\rightarrow$  silicon steel.
- \* The working function of interpole to reduce the armature reaction.





\* Laminated core made in silicon steel.

\* Laminated core insulated  $\rightarrow$  shellac varnish, then paper, oxide film coating.


\* The function of commutator is to convert AC to DC.

### ✓ DC machine parts :-

The main parts of a DC machine are

- (1) Yoke.
- (2) pole core and pole shoe.
- (3) Field winding.
- (4) Armature core.
- (5) Armature winding or conductor.
- (6) commutator.
- (7) brushes and bearings.
- (8) Interpole.
- (9) shaft. (10) base. (11) slot.

YOKE:-

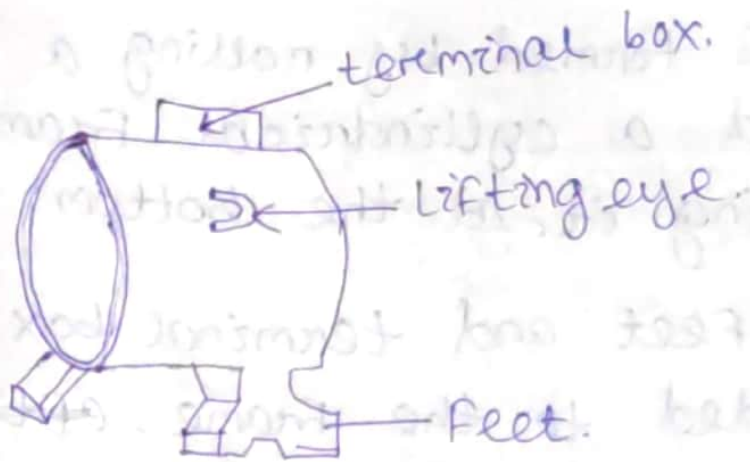

(i) Yoke is the outermost covering of a DC machine. It is also called as frame.

function:-

- (i) It provides mechanical support for poles.
- (ii) It provides protection to whole machine from harmful atmospheric elements like dust, moisture,  $SO_2$ , Acid, etc.
- (iii) It also provide protection against mechanical injury.
- (iv) It carry the magnetic flux produced by the poles or it provides path for the magnetic flux.

Material used and construction:-

For small machine yoke is made of cast iron and for large machine




it is made of silicon steel or cast steel.

(ii) It is formed by rolling a steel slab around a cylindrical frame, then welding it at the bottom.

(iii) <sup>Then</sup> The feet and terminal box, etc are welded to the frame.

✓ Pole core and pole shoe :-

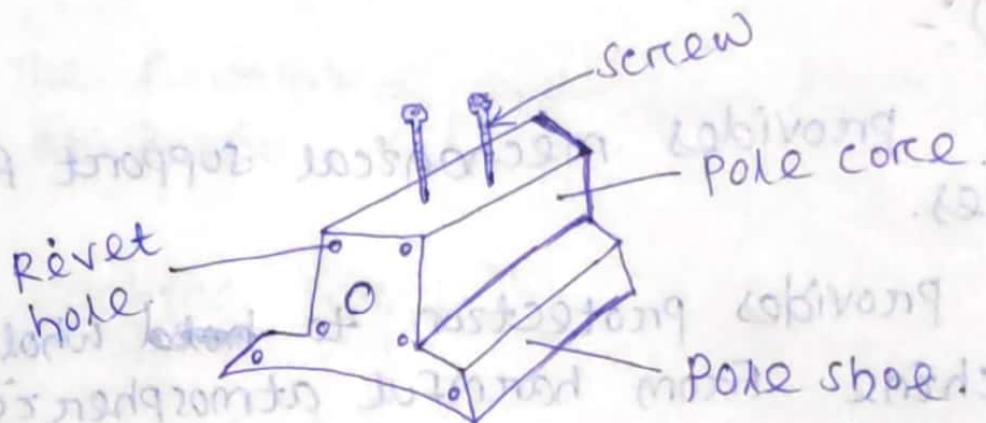

(i) The field magnet consists of pole core and pole shoe.

(ii) The pole cores are fixed to the magnetic frame or yoke by screw/bolt.

(iii) Each pole core has a curved surface which is called as pole shoe.

### Function :-

- (i) It supports and hold the field winding.
- (ii) Pole shoe increases the cross sectional area of magnetic ckt. as a result the magnetic path is reduced.
- (iii) Due to pole shoe, the magnetic flux spread in the air gap uniformly.

### Material used and construction :-

- (i) The pole core and pole shoe are made of thin lamination of cast steel which are rivetted together under hydraulic pressure.  
rivet  $\rightarrow$  passing metal pins through holes in two or more metal plates to held them together.
- (ii) The thickness of the lamination varied from 0.25 mm to 1mm.
- (iii) Lamination of core is required to reduce eddy current loss.



## Field winding :-

(i) Field windings are used to form electromagnet and wound on the pole core with a definite direction.

(ii) Field windings carry current to form electromagnet <sup>and</sup> to produce necessary flux.

(iii) Field coils are connected series with each other and in such a direction around pole core so that alternate 'N' pole and 'S' pole are formed.

(iv) Generally field winding is made of copper.

## Armature core :-

(i) It is the rotating part of a DC machine and connected to the shaft.

(ii) A prime mover is connected to the shaft to move the armature.

## Function :-

(i) It holds the armature conductors and causes them to rotate.

so the armature conductors cut the magnetic field and an emf is induced in them.

(ii) It provides a path of very low reluctance to the flux through the armature from N-pole to S-pole

material used and construction:-

(i) It is cylindrical or drum shape and made of circular laminated silicon steel sheet or disc.

(ii) The thickness of the lamination varied from 0.25 mm to 1 mm.

(iii) The slots are punched on the outer periphery of the disc.

(iv) The laminations are perforated for air ducts which permits axially flow of air through the armature for cooling purpose.

(v) The purpose using lamination is to reduce eddy current loss.

(vi) If the laminations are thinner, then resistance offered to the current is greater. hence  $I^2R$  loss in core is less.



## ✓ Armature winding :-

(i) Armature winding is interconnection of armature conductors placed in the slots.

(ii) Armature winding are made of copper and insulated from each other and from armature core.

(iii) Armature winding can be done by two methods.

(1) Wave winding.

(2) Lap winding.

✓ In lap winding number of parallel path is equal to no. of pole. But in wave winding no. of parallel path is equal to two.

## ✓ Commutator :-



(i) The function of commutator is to collect current from the armature conductors.

(ii) It convert AC induced in the armature conductor into unidirectional current.

(iii) It is of cylindrical structure and made of wedge shaped segment of hard drawn copper.

(iv) These segments are insulated from each other by thin layers of mica.

brushes and bearings:

(i) The function of brush is to collect current from the commutator and supplied it to the external ckt.

(ii) Brushes are placed in brush holders which rest on the commutator.





(iii) Brushes are usually made of carbon and are in the shape of a rectangular box.

(i) The function of bearings are to reduced friction between rotating and stationary parts of the machine.









## Shaft:

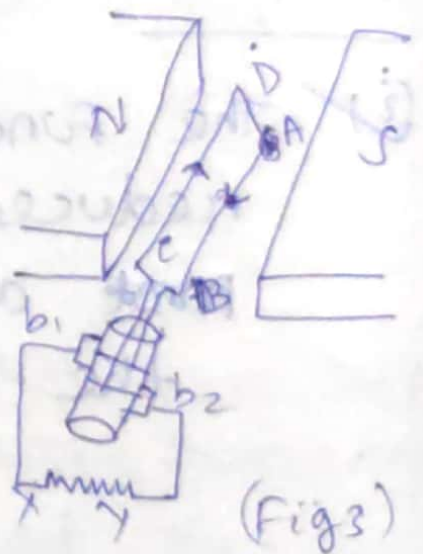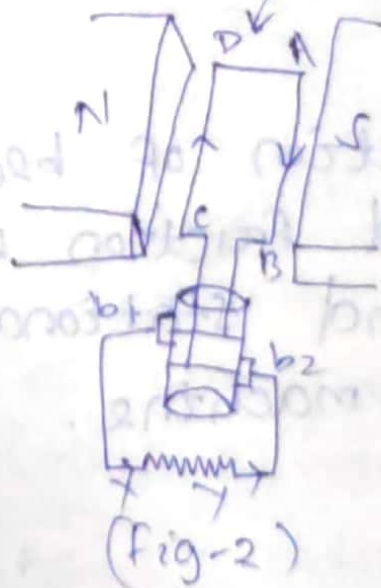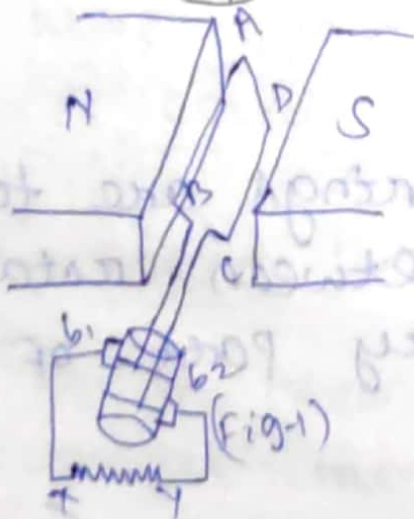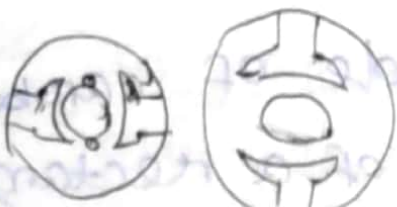- (i) Rotating Parts like armature core, commutator, cooling fans are mounted on the shaft.
- (ii) The shaft is made of mild steel with a maximum breaking strength or mechanical strength.
- (iii) The shaft is used to transfer mechanical energy from armature to load or from prime mover to armature.



(Fig-4)

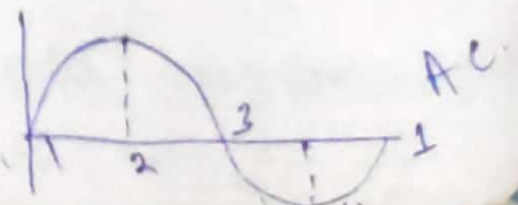

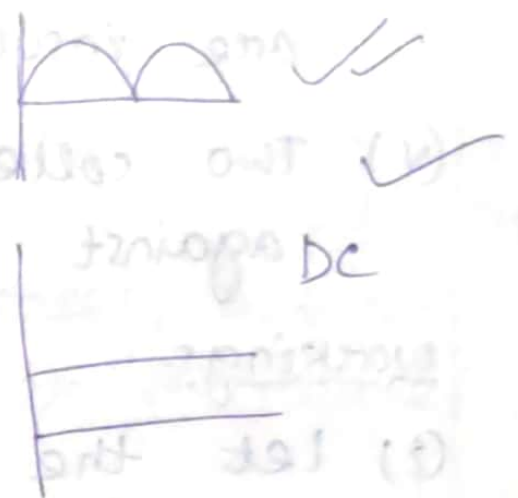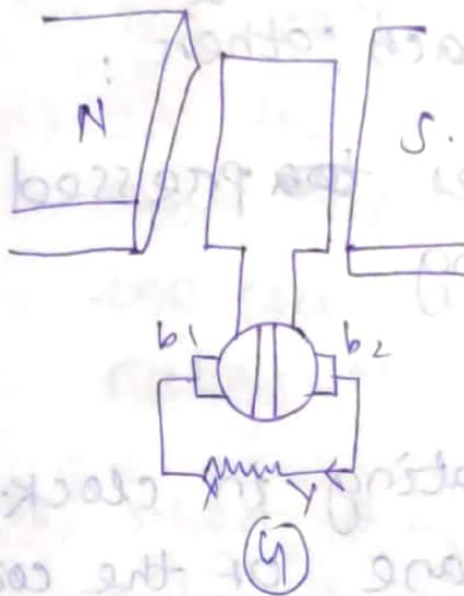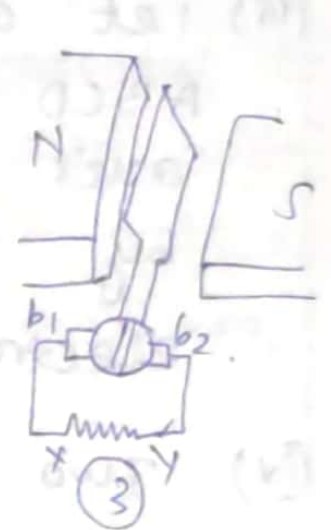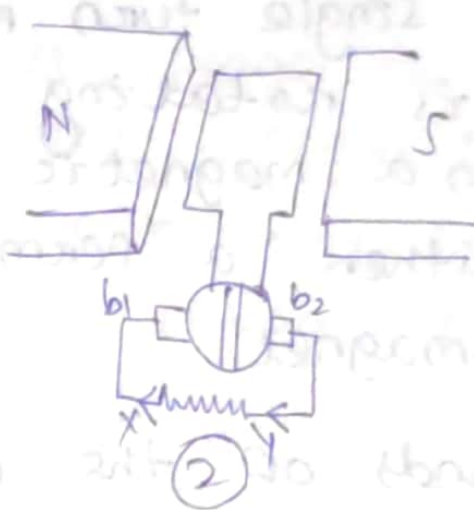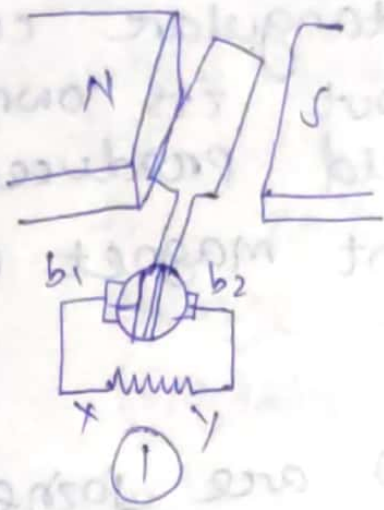

## Working principle of DC generator :-

(i) Working of a DC generator based on the principle of Faraday's law of electromagnetic induction. According to Faraday's law of electromagnetic induction whenever a conductor cuts magnetic flux induced emf is produced.

(ii) This emf causes a current to flow if the conductor the circuit is closed.



(iii) Let a single turn rectangular coil ABCD is rotating about its own axis in a magnetic field produced by either a permanent magnet or electromagnet.

(iv) Two ends of the coils are joined to two slip-rings  $S_1$  and  $S_2$  which are insulated from each other.

(v) Two collecting brushes pressed against the slip ring.

working:-

(i) Let the coil is rotating in clock-wise direction, when the plane of the coil is at right angle to lines of flux (Fig-1). Then the flux linked with coil is maximum but rate of change of flux is minimum.

(ii) Because in this position the coil sides AB and CD do not cut the flux. They move parallel to the flux. Hence there is no induced EMF in the coil.

(iii) As the coil continued rotating further the rate of change of

Flux linkage increases.

(iv) When the coil plane is horizontal to the line of flux, flux linked with the coil is minimum, but rate of change of flux linkage is maximum. (fig-2)

(v) Hence maximum EMF is induced in the coil in this position.

(vi) In the next quarter revolution i.e. from  $90^\circ$  to  $180^\circ$ , the flux linked with the coil gradually increases, but the rate of change of flux decreases.

(vii) When  $\theta = 180^\circ$  (fig-3), the emf induced in the coil is reduced to zero value.

(viii) In the first <sup>half</sup> revolution of the coil we find that no emf is induced when  $\theta = 0^\circ$  and  $\theta = 180^\circ$  and maximum emf is induced, when  $\theta = 90^\circ$ . The direction of current can be found by Fleming's right hand rule.

(ix) According to Fleming's right hand rule, Here the direction of current flow is  $AB \rightarrow XY \rightarrow CD$ .



(x) The current through the load resistance are flow from X to Y during the first half revolution of the coil.

(xi) In the next half revolution i.e. from  $180^\circ$  to  $360^\circ$ , the variation of in the magnitude of emf are similar to those in the first half revolution.

(xii) The value of emf induced is maximum when  $\theta = 270^\circ$  (Fig-4).

But in this half revolution the direction of flow of current is DC - YX - BA. The current through the load resistance are flow from Y to X during the second half revolution of coil i.e. just reverse of first half revolution.

(xiii) It is clear that the output current is alternating in nature. For making the flow of current unidirectional in the external ckt the slip-rings are replaced by split-rings or

commutator.

(xiv) The commutator are made of conducting cylinder which is cut into two half insulated from each other by a thin sheet of mica.

(xv) The coils ends are connected to these segments such that when the coil rotates this segments also move with them.

(xvi) In the first half revolution, conductor AB is connected with segment  $c_1$  and segment  $c_1$  is contact with brush  $b_1$ . so the current flow will along the path AB - XY - CD. but

in the next half revolution segment  $c_2$  will be in contact with brush  $b_1$ . so current will flow along the path DC - XY - BA.


(xvii) current in the load resistance flow from X to Y in both half revolution, so this output current is unidirectional but not continuous like pure <sup>direct</sup> current.



## Armature winding :-
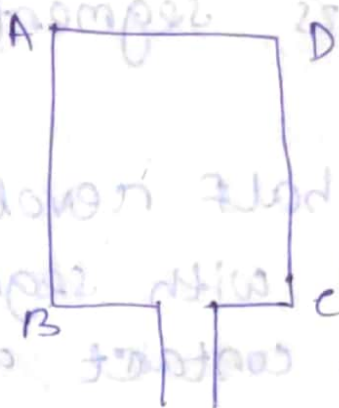
### Conductor :-

The length of a wire laying in the magnetic field and in which an emf is induced is called a conductor.



$AB = CD = \text{conductors}$ .

### Coil :-


(i) Two conductors  $AB$  and  $CD$  along with their end connection constitute one coil of the armature winding.

(ii) coil may be of two types.

(1) single turn.  $\rightarrow$




(2) multi turn.  $\rightarrow$

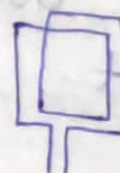

aw

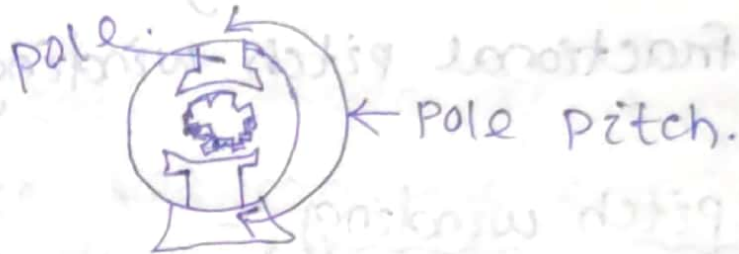Pole Pitch :- The distance between two adjacent poles is called pole pitch.





(ii) It is equal to the no. of armature conductors or armature slots per pole.

e.g. → If there are 48 conductors and 4 poles in a generator, then pole pitch.

$$\text{pole pitch} = \frac{48}{4} = 12$$

Coil Pitch / Coil Span :-

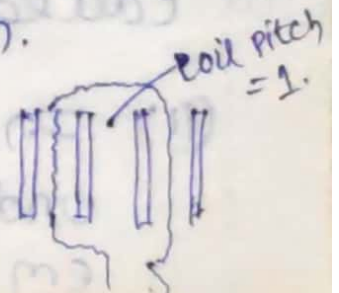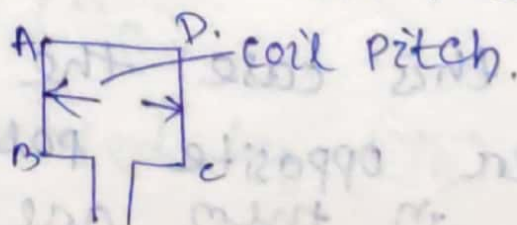(i) The distance between two sides of a coil is called coil pitch.







(i) According to length of coil pitch, winding of armature is divided into two types.

(1) Full pitch winding.

(2) fractional pitch winding.


full pitch winding

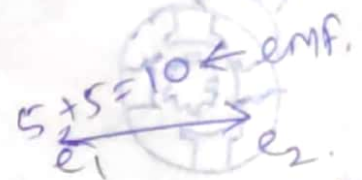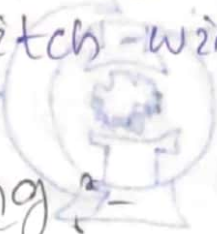

pole pitch = coil pitch. [emf induced maximum]

Fractional pitch winding

coil pitch < pole pitch.

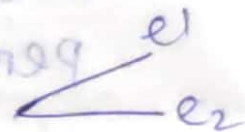

emf induced is less than full pitch winding

$$\sqrt{5^2 + 5^2 + 2 \times 5 \times \cos 50^\circ} = 7.29 \text{ emf}$$

Full-pitch winding :-

(i) If coil pitch is equal to pole pitch, then winding is called full-pitch winding.

(ii) In this case the coil sides lie under opposite pole, Hence induced emf in them are additive in nature.


## Fractional pitch winding: -

(i) If coil pitch is less than pole pitch, then the winding is called fractional pitch winding.

(ii) In this case, there is a phase difference between the emf in two sides of the coil. Hence total emf around the coil is the vector sum of emf in the two coil sides.

(iii) The main advantage of is saving of copper at the end connection.

## Back pitch $\gamma_B$ : -

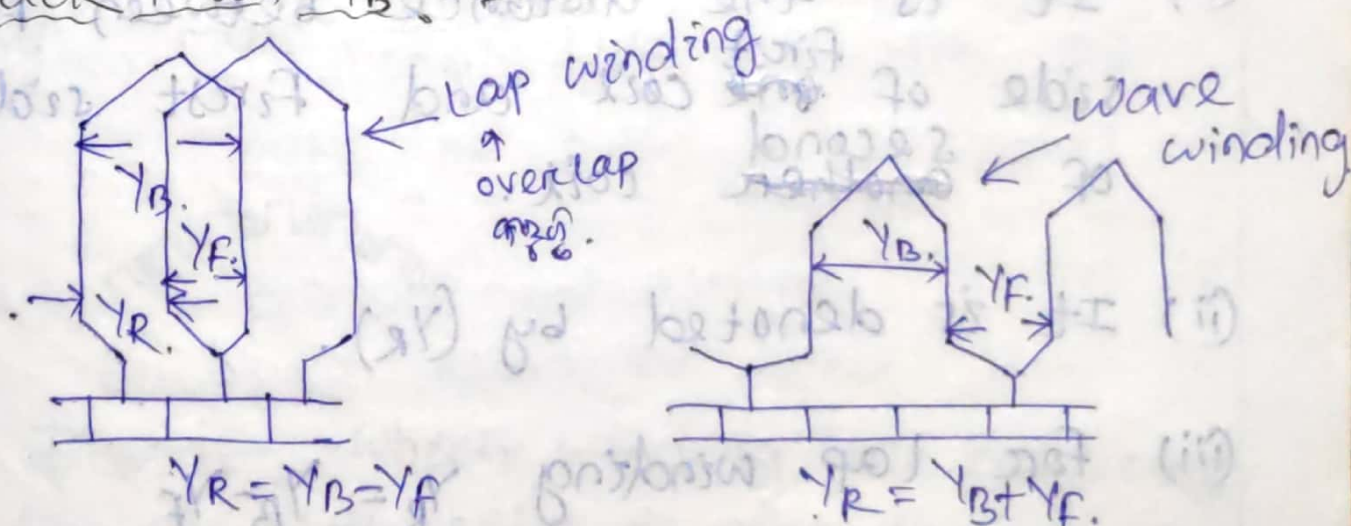

(i) The distance covered by a coil on the back side of the armature is called back pitch ( $\gamma_B$ ).

(ii) It is denoted by ( $\gamma_B$ ).



## Front pitch :-

(i) The number of armature conductor covered by a coil on the front end of the armature is called front pitch.

(ii) It is denoted by  $(Y_F)$ .

(iii) Front pitch may be defined as the distance between second conductor of one coil and the first conductor of an other coil.

## Resultant pitch :-


(i) It is the distance between first side of first coil and first side of second coil.

(ii) It is denoted by  $(Y_R)$ .


(iii) For lap winding  $Y_R = Y_B - Y_F$

For wave winding  $Y_R = Y_B + Y_F$

## Commutator pitch :-

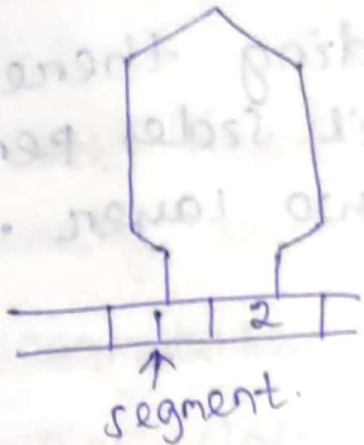

$$Y_c = 2 - 1 = 1$$

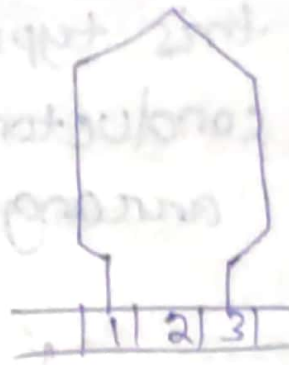


$$Y_c = 3 - 1 = 2 \quad \checkmark$$

(i) It is the distance between the segments to which the two ends of a coil are connected.

(ii) It is denoted by ' $Y_c$ '

## Single Layer winding :-


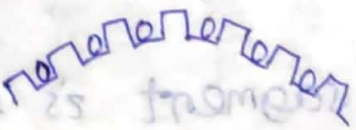


(i) In which winding, one conductor or one coil side is placed in each armature slot is called single layer winding.



## Two layer winding :-

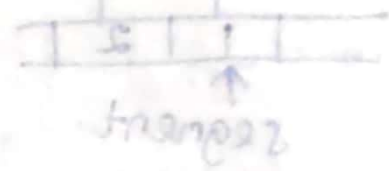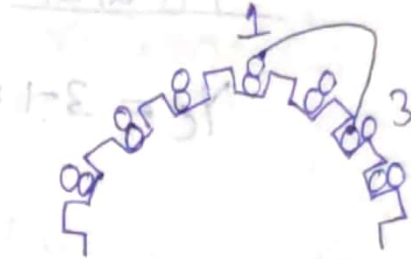(i) In this type of winding there are two conductors or coil sides per slot arranged in two layers.



$$L = 1 - 6 = 5$$

Simplex lap winding :-

rules :-

- (1) Both front pitch and back pitch should be odd, otherwise it would be difficult to place the coil properly on the armature.
- (2) No. of commutator segment is equal to no. of slots or coils, because the front end of the conductors are joined to the segment in pairs.
- (3) The back pitch and front pitch can not be equal, they differ by two or some multiple of two.

$$Y_B = Y_F \pm 2m \quad (m = 1, 2, 3, \dots)$$

$\uparrow$  simplex       $\uparrow$  duplex       $\uparrow$  multiplex

(4) Both front pitch and back pitch should be nearly equal to pole pitch.

(5) commutator pitch ( $Y_c$ ) is equal  $\pm 1$ .

(6) NO. OF slots for a two layer winding is equal to the no. of coils

(7) The no. of parallel path in the armature is equal no. of poles.

(8) Progressive winding.

$$Y_F = \frac{Z}{p} - 1 \quad Y_B = \frac{Z}{p} + 1$$

$$Y_B > Y_F$$

(ii) Retrgressive winding.

$$Y_F = \frac{Z}{p} + 1 \quad Y_B = \frac{Z}{p} - 1$$

$$Y_F > Y_B$$

$Z \rightarrow$  no. of conductor.

$p \rightarrow$  pole



Wave winding -

Rule 1 -

$$\beta_1 = (P + F) \leftarrow F$$

$$\beta_1 = (P + P) \leftarrow P$$

(1) Both back pitch and front pitch are odd.

$$\beta_1 = (P + \beta_2) \leftarrow \beta_2$$

$$\beta_2 = (P + \beta_1) \leftarrow \beta_1$$

(2) Back pitch and front pitch are nearly equal to pole pitch, they may be equal or differ by two.

$$\beta_1 = (P + \beta_2) \leftarrow \beta_2$$

$$\beta_2 = (P + \beta_1) \leftarrow \beta_1$$

(3) Resultant pitch  $\gamma_R = \beta_B + \beta_F \leftarrow \beta_2$

(4) Commutator pitch  $\gamma_c = \gamma_A \leftarrow \beta_2$

(5)  $\gamma_c = \frac{\text{No. of commutator bars} \pm 1}{\text{No. of pairs of poles}}$

(6) Average pitch  $\gamma_A = \frac{Z \pm 2}{\dots}$

$$\beta_2 = (F - \beta_1) \leftarrow \beta_1$$

$$\beta_1 = (P + \beta_2) \leftarrow \beta_2$$

$$\beta_2 = (F - \beta_1) \leftarrow N \text{ or}$$


$$\frac{\text{No. of commutator bars} \pm 1}{\text{No. of pairs of poles}}$$

## Classification of DC generator

Depending upon the excitation of field DC generator is divided into two types

- (1) separately excited DC generator
- (2) self excited DC generator

### Separately excited DC generator

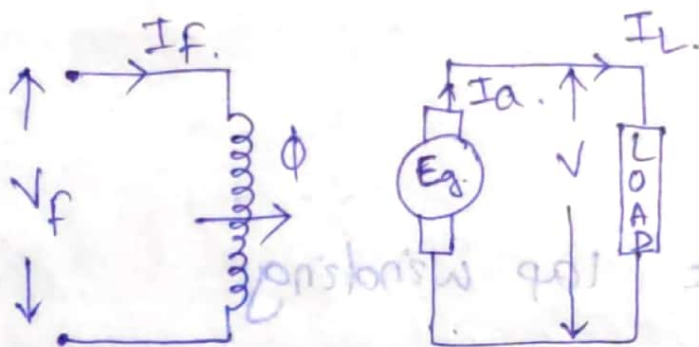

- (i) In separately excited DC generator a separate voltage source is used to excite the field

$$E_g = I_a R_a + V + V_B$$

$$I_a = I_L$$

- (ii) The field and armature ckt are electrically isolated and magnetically coupled



uses :-

- (i) Because of their ability of giving wide range of voltage output, they are used as source of DC motors.
- (ii) used for testing purpose in laboratories.

self excited DC generator :-

- (i) In self excited generator the field winding is excited by the current produced by the generator itself.
- (ii) A part of current or entire current produced can be used for exciting the field winding.
- (iii) Due to residual magnetism, some magnetic flux always remains present in the coil of magnetic poles to start the generator.
- (iv) There are three types of self excited generator.
  - (1) series generator.
  - (2) shunt generator.
  - (3) compound generator.

(1) A separately excited DC generator running at 1200 rpm, supplies 200 A at 125 V. to a ckt of constant resistance. what will be the generated emf when the speed is drop to 1000 rpm and the field current is reduced to 80%, armature resistance is  $0.04 \Omega$  and total drop at brushes is 2 V.

Given data:-

$$N = 1200 \text{ rpm,}$$

$$I_a = 200 \text{ A}$$

$$V = 125 \text{ V.}$$

$$V_B = 2 \text{ V.}$$

$$(i) E_g = I_a R_a + V + V_B$$

$$= (200 \times 0.04) + 125 + 2$$

$$= 135 \text{ V.}$$



$$E_{g1} = \frac{\phi Z N P}{60 A}$$

$$\begin{aligned} I_f &\propto \phi \\ I_{f1} & \quad I_{f2} = \frac{80}{100} = 0.8 I_{f1} \\ \phi_1 & \quad \phi_2 = 0.8 \phi_1 \end{aligned}$$

$$\Rightarrow 135 = \frac{PZ}{60 A} \times 1200 \times \phi_1 \quad \text{--- (1)}$$

$$E_{g2} = \frac{PZ}{60 A} \times 1000 \times 0.8 \phi_1 \quad \text{--- (2)}$$


Dividing eqn (1) & (2).

$$\Rightarrow \frac{135}{E_{g2}} = \frac{1200 \times \phi_1}{1000 \times 0.8 \phi_1}$$

$$\Rightarrow E_{g2} = \frac{135 \times 1000 \times 0.8}{1200}$$

$$\Rightarrow E_{g2} = 90 \text{ V.}$$

Series Generator:

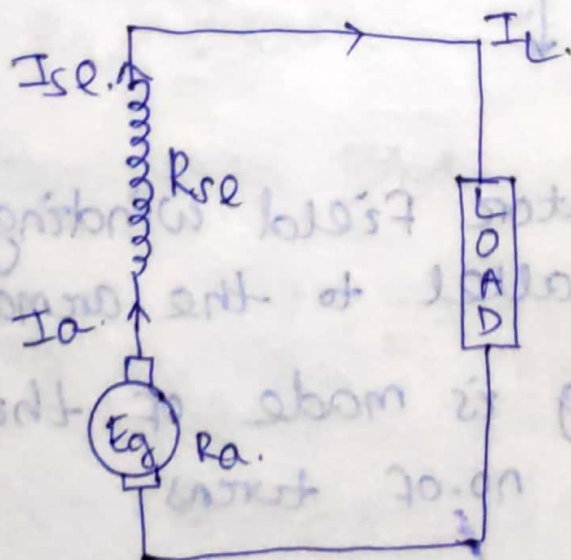

$$E_g = I_a R_a + V_b + R_{se} I_{se} + V.$$


(i) In series generator field winding is connected in series with the armature.

(ii) field winding is made of thick wire with less number of turns.

(iii) It is used where constant load at constant speed is required.

(iv) It is used as booster in transmission line to compensate voltage drop.

Shunt Generator :-

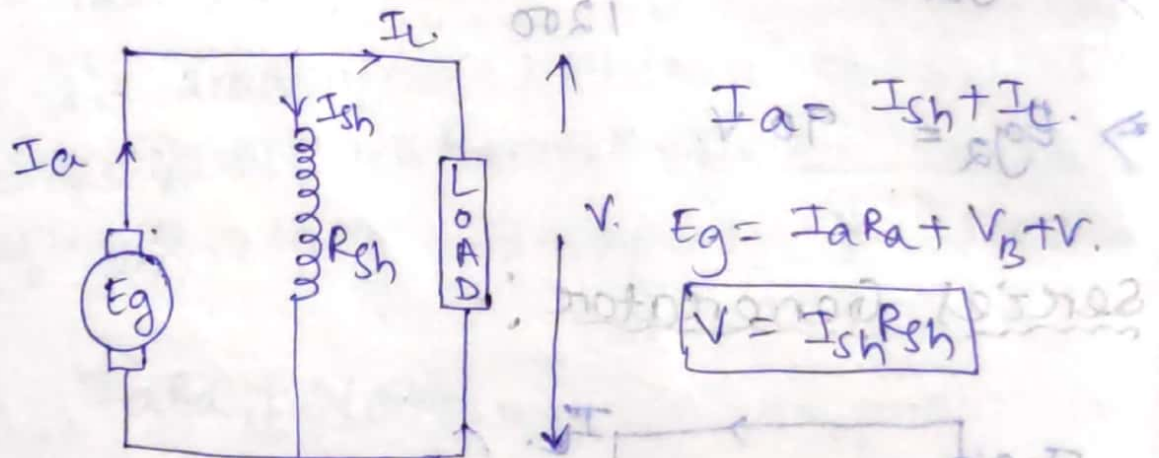

(i) In shunt generator field winding is connected in parallel to the armature.

(ii) The field winding is made of thin wire with more no. of turns.



use) :-

- (i) They are used to charge battery, because they can be made to give constant output voltage.
- (ii) They are used for giving excitation to alternator.

- (1) A shunt generator delivers 450 A at 230V at the resistance of the shunt field and armature are  $50\ \Omega$  and  $0.03\ \Omega$  respectively. calculate the generated emf.

Given data

$$I_L = 450\text{ A.}$$

$$V = 230\text{ V.}$$

$$R_{sh} = 50\ \Omega.$$

$$R_a = 0.03\ \Omega.$$

~~Find~~  $I_a$  ~~to~~  $I_{sh}$

$$I_{sh} = \frac{V}{R_{sh}} = \frac{230}{50} = 4.6\text{ A.}$$


$$I_a = I_{sh} + I_L = 4.6 + 450 = 454.6\text{ A.}$$

$$E_g = I_a R_a + V = (454.6 \times 0.03) + 230 = 243.63\text{ V.}$$

## compound generator :-

- (i) In a generator if both series and shunt windings are present, then it is called as compound generator.
- (ii) In a compound generator, series winding has less number of turns and shunt winding has more no. of turns.
- (iii) There are two types of compound generator.
- (1) Short shunt compound generator.
  - (2) Long shunt compound generator.

### Short shunt compound generator :-

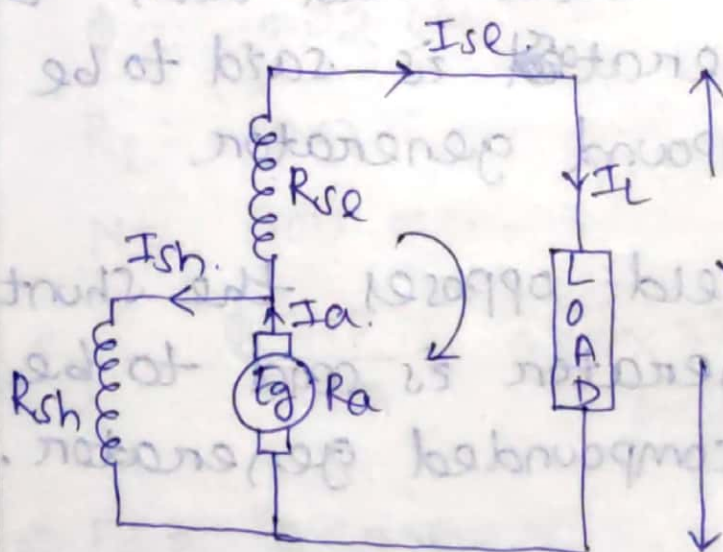


$$I_a = I_{sh} + I_{se} \quad (I_{se} = I_L)$$

$$E_g = I_a R_a + I_{se} R_{se} + V + V_b$$



## Long shunt compound generator

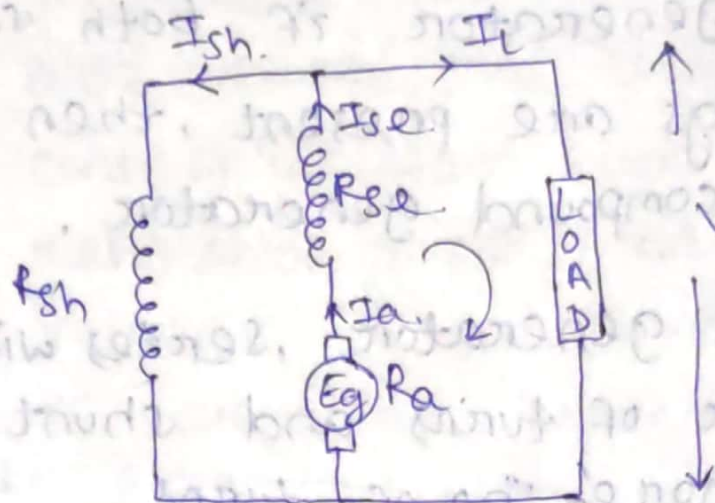

$$I_{se} = I_{sh} + I_L \quad (I_{se} = I_a)$$

$$E_g = I_a R_a + I_{se} R_{se} + V + V_B$$

$$V = I_{sh} R_{sh}$$

→ When the series field aids the shunt field, the generator is said to be cumulatively compound generator.

→ If series field opposes the shunt field, the generator is said to be differentially compounded generator.

$$(I = 2I) \quad \checkmark \quad I_a = I_{sh} + I_L = 2I$$

$$E_g = I_a R_a + I_{se} R_{se} + V + V_B$$

## E.M.F equation of DC Generator:

Let,

$p$  = No. of pole.

$Z$  = Total no. of armature conductor.

$\phi$  = FLUX per pole.

$N$  = speed of the armature in R.P.M.

$A$  = No. of parallel path.

According to Faraday's Law of electromagnetic induction induced EMF

$$E = \frac{d\phi}{dt}$$

— ①

Since the flux per pole is  $\phi$ , each conductor cut's flux in one revolution equal to  $p \times \phi$

$$d\phi = p \times \phi$$

$N$  revolution

$$\text{in } \frac{1 \text{ min}}{60 \text{ sec}}$$

1

1

$$= \frac{60}{N} \text{ sec}$$

$$\text{so } dt = \frac{60}{N} \text{ sec.}$$

Now putting the value of  $d\phi$  and  $dt$  in eqn ①.

$$\text{induced emf} = \frac{d\phi}{dt}$$




$$E = \frac{d\phi}{dt}$$

$$\Rightarrow E = \frac{P\phi}{60 \times N}$$

$$\Rightarrow E = \frac{P\phi N}{60}$$

$$Z = 16, P = 4$$

Wave

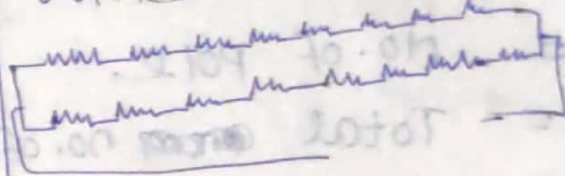

$$Emf \text{ total} = 8 \times emf / \text{conductor} = \frac{Z}{A}$$

Total generated emf will be determined from no. of armature conductors in series in any one path between the brushes

$$\Rightarrow E = \frac{P\phi N}{60} \times \frac{Z}{A}$$

$$\Rightarrow E_g = \frac{\phi Z N P}{60 A}$$

For wave winding  $\phi \times 9 = \phi \times 16$

$$\Rightarrow E_g = \frac{\phi Z N P}{60 \times 2} = \frac{\phi Z N P}{120}$$

For Lap winding

$$A = P$$

$$\Rightarrow E_g = \frac{\phi Z N P}{60 \times P}$$

$$\Rightarrow E_g = \frac{\phi Z N}{60}$$

(1) An 8 pole DC generator has 500 armature conductors and a useful flux of 0.05 Wb/pole. What will be the emf generated if it is lap connected and runs at 1200 rpm. What must be the speed at which it is to be driven produced the same emf. Given data :- if it is wave wound.

$$p = 8$$


$$A = 8 \text{ (Lap)}$$

$$\phi = 0.05$$

$$N = 1200$$

$$Z = 500$$
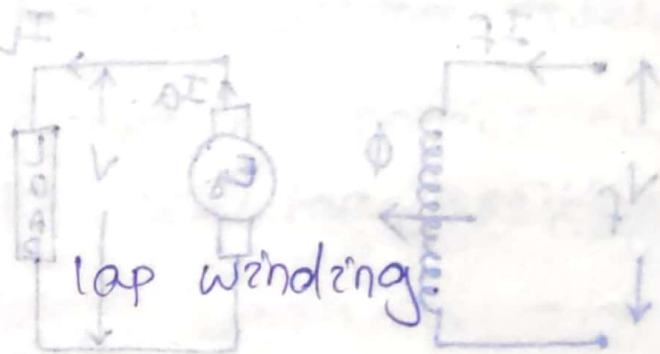
$$E_g = \frac{\phi Z N P}{60 A} \text{ for lap winding}$$



$$= \frac{0.05 \times 500 \times 1200 \times 8}{60 \times 8}$$

$$= 500 \text{ V}$$

for wave winding.


$$E_g = \frac{\phi Z N P}{60 A}$$

$$\Rightarrow 500 = \frac{0.05 \times 500 \times N \times 8}{60 \times 2}$$

$$\Rightarrow N = \frac{500 \times 60 \times 2}{0.05 \times 500 \times 8} = 300 \text{ RPM}$$



## Losses in a DC machine :-

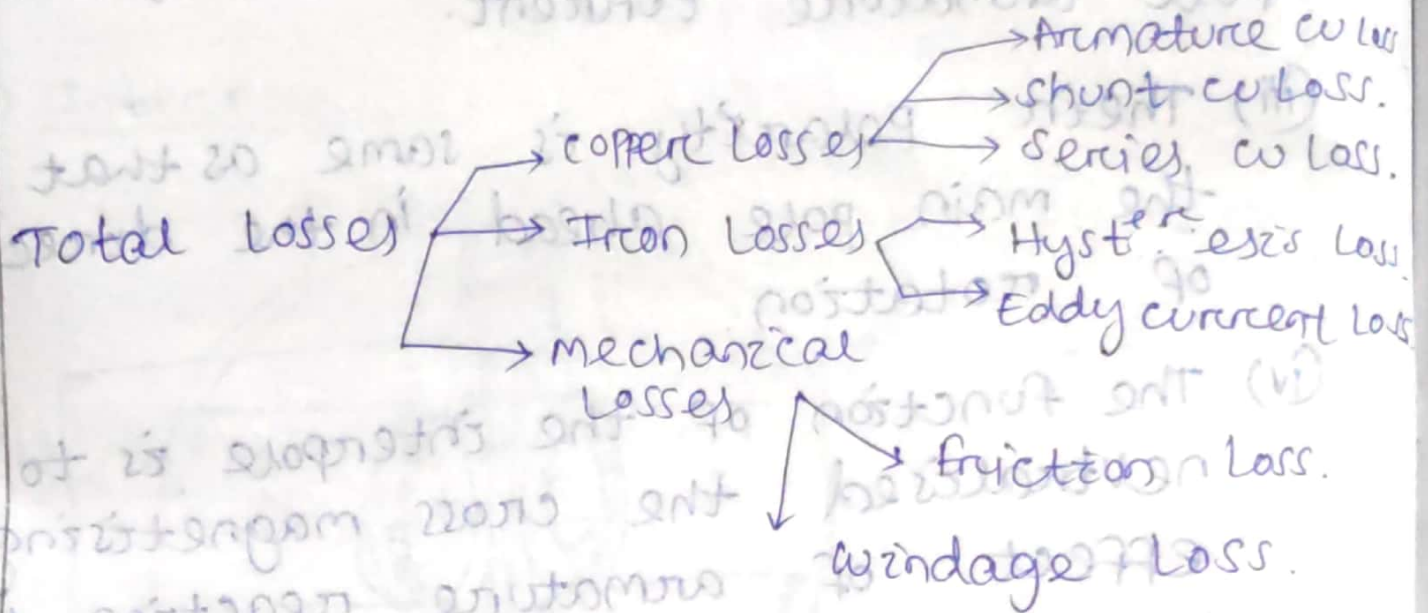

### Iron Loss :-

(i) Due to the rotation of the armature core of the armature in the magnetic flux of the field poles, there are some losses taking place continuously in the core, and are known as iron loss or iron loss.

(ii) There are two types of iron loss.

① Hysteresis Loss.

(ii) Eddy current Loss.

## Hysteresis Loss :-

- (i) Hysteresis loss is due to reversal of magnetisation of armature core.
- (ii) Every portion of the rotating core passes under N-pole and S-pole alternately.
- (iii) This core undergoes one complete cycle of magnetic reversal after passing under one pair of pole.
- (iv) If,  $P$  is no. of pole and  $N$  is armature speed in rpm, then frequency of magnetic reversal is 
$$f = \frac{PN}{120}$$
- (v) The loss depends upon the volume and grade of iron maximum value of flux density  $B_{max}$  and frequency of magnetic reversal.

$$\text{Hysteresis Loss (W}_h\text{)} = K B_{max}^{1.6} f v \text{ watts.}$$

where,

$v$  = volume of core.

$B_{max}$  = maximum flux density.



## Eddy current loss :-

- (i) when a armature core rotates it also cuts the magnetic flux, hence an emf is induced in the body (surface) of the armature core. According to Faraday's Law of Electromagnetic induction.
- (ii) This emf is small but can set-up large current on the body of core. This circulating current is known as eddy current.
- (iii) The power loss due to flow of this current is known as eddy current loss.
- (iv) In order to reduce this loss the core is build up of thin-laminations. These core laminations are insulated from each other by a thin coating of varnish.
- (v) when the core body is a single continuous solid iron piece, magnitude of the eddy current is large, because the armature area is large and resistance is very small.
- (vi) But when the core is laminated, the cross-sectional area decreases and resistance increases as a result the eddy current loss gets reduced.
- (vii) Eddy current losses raise the temperature of the core and reduce the efficiency of the generator.

$$\text{eddy current loss} = K B_{\max}^2 t^2 v^2 f^2 \text{ watt.} \\ (W_e / P_e).$$

where,

$B_{\max}$  = Flux density.

$v$  = volume of the core.

$f$  = frequency.

$t$  = thickness of lamination.



## Copper Loss :-

(i) armature copper loss.

$$I_a^2 R_a$$

where,

$I_a$  = armature current

$R_a$  = armature resistance

(\*) It is about 30-40% full load losses.

(ii) shunt copper loss.

$$I_{sh}^2 R_{sh}$$

$I_{sh}$  = shunt field current.

$R_{sh}$  = shunt field resistance.

(iii) series copper loss.

$$I_{se}^2 R_{se}$$

$I_{se}$  = series field current

$R_{se}$  = series field resistance

## Mechanical Losses :-

Mechanical loss consists of

(i) friction loss at bearing & at commutator

(ii) Air friction or windage loss of rotating armature.

Stray Loss :-

Mechanical Loss + iron Loss.

- (i) usually iron loss and mechanical losses are collectively known as stray loss. These are also known as rotational loss.

constant Loss :-

Armature copper loss.  
series field copper loss ]  $\rightarrow$  variable.

All losses  $\rightarrow$  constant  $\rightarrow$  shunt field loss.

- (i) The shunt field copper loss is constant for shunt and compound generators.

- (ii) Shunt copper loss and stray loss together known as constant loss.

~~Total loss = armature copper loss~~

Total loss = variable loss + constant loss.



condition for maximum efficiency:-

Generator output =  $VI$  watt.

Generator input = output + losses  
 $= VI + W_c + I_a^2 R_a$  ← For shunt

$$\text{efficiency } (\eta) = \frac{O/P}{I/P}$$

$$= \frac{VI}{VI + W_c + I_a^2 R_a}$$

$$\frac{VI}{VI \left( 1 + \frac{W_c}{VI} + \frac{I_a^2 R_a}{VI} \right)}$$

$$= \frac{1}{1 + \frac{W_c}{VI} + \frac{I_a^2 R_a}{VI}}$$

For shunt generator.

$$I_a = I_L + I_{sh}$$

$$\Rightarrow I_a = I + I_{sh}$$

$$\Rightarrow \boxed{I_a = I} \quad [I_{sh} \text{ very small}]$$

$$I_{sh} \approx 0$$

$$\Rightarrow \eta = \frac{1}{1 + \frac{W_c}{VI} + \frac{I_a^2 R_a}{VI}}$$

$$\Rightarrow \eta = \frac{1}{1 + \frac{W_c}{VI} + \frac{I^2 R_a}{VI}}$$

$$\Rightarrow \eta = \frac{1}{1 + \frac{W_c}{VI} + \frac{I R_a}{V}}$$

Now, efficiency is maximum, when denominator is minimum.

i.e. when:

$$\Rightarrow \frac{d}{dI} \left[ \frac{I R_a}{V} + \frac{W_c}{VI} \right] = 0$$

$$\Rightarrow \frac{R_a}{V} = \frac{W_c}{I^2}$$

$$\Rightarrow \boxed{W_c = I^2 R_a} \quad \left[ \text{constant loss} = \text{variable loss} \right]$$



(1)

A shunt generator has a full load current of 196 Amp at 220V. The stray losses are 720 watt and the shunt field resistance is  $55 \Omega$ . It has a full load efficiency of 88%. Find the armature resistance. Also find the load current corresponding to maximum efficiency.

Given data

$$I_L = 196 \text{ Amp}$$

$$V = 220 \text{ V}$$

$$\text{stray loss} = 720 \text{ watt}$$

$$R_{sh} = 55 \Omega$$

$$\eta_L = 88\% = 0.88$$

$$\text{output power} = VI \text{ watt}$$

$$= (220 \times 196)$$

$$= 43120 \text{ watt}$$

$$\eta = \frac{\text{output power}}{\text{input power}}$$

$$\Rightarrow 0.88 = \frac{43120}{\text{input power}}$$

$$\Rightarrow \text{input power} = \frac{43120}{0.88} = 49000$$

$$I_{sh} = \frac{V}{R_{sh}}$$

$$\Rightarrow I_{sh} = \frac{220}{55}$$

$$\Rightarrow I_{sh} = 4 \text{ A}$$

$$I_a = I_L + I_{sh}$$

$$\Rightarrow I_a = 196 + 4$$

$$\Rightarrow I_a = 200 \text{ A}$$

Variable loss = Armature Cu. loss.

$$\Rightarrow I_a^2 R_a = 4280$$

$$\Rightarrow (200)^2 R_a = 4280$$

$$\Rightarrow R_a = \frac{4280}{(200)^2}$$

$$\Rightarrow R_a = 0.107 \Omega \quad \underline{\underline{\text{Ans}}}$$

$$\text{Total loss} = \text{Input Power} - \text{output power}$$

$$= 49000 - 43120$$

$$= 5880 \text{ watt.}$$

$$\text{Total loss} = \text{constant loss} + \text{variable loss}$$

$$\Rightarrow 5880 = (\text{stray loss} + \text{shunt field loss}) + \text{variable loss}$$

$$\Rightarrow 5880 = [720 + (I_{sh}^2 R_{sh})] + \text{variable loss}$$

$$\Rightarrow 5880 = 720 + (4^2 \times 55) + \text{variable loss}$$

$$\Rightarrow 5880 = 1600 + \text{variable loss}$$

$$\Rightarrow \text{variable loss} = 4280 \text{ watt.}$$



for maximum efficiency.

Constant loss = variable loss.

$$\Rightarrow I_a^2 R_a = 1600$$


$$\Rightarrow I_a^2 \times 0.107 = 1600$$

$$\Rightarrow I_a = \sqrt{\frac{1600}{0.107}}$$


$$\Rightarrow I_a = 122.28 \text{ A.}$$

(Ans).

## Armature Reaction :-

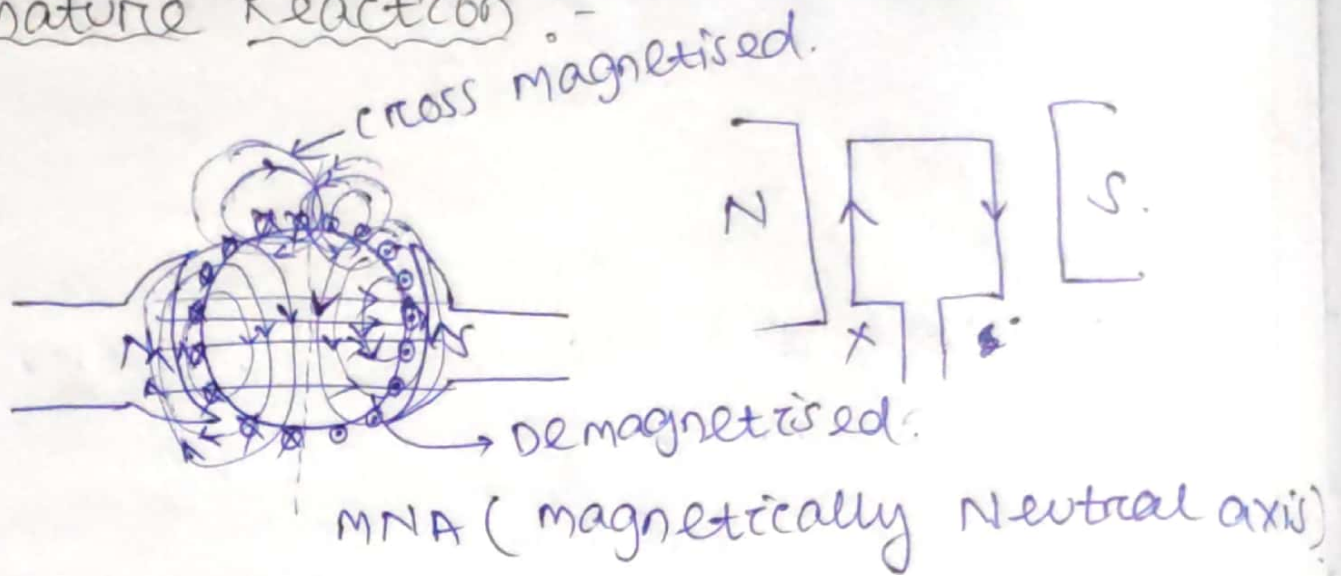

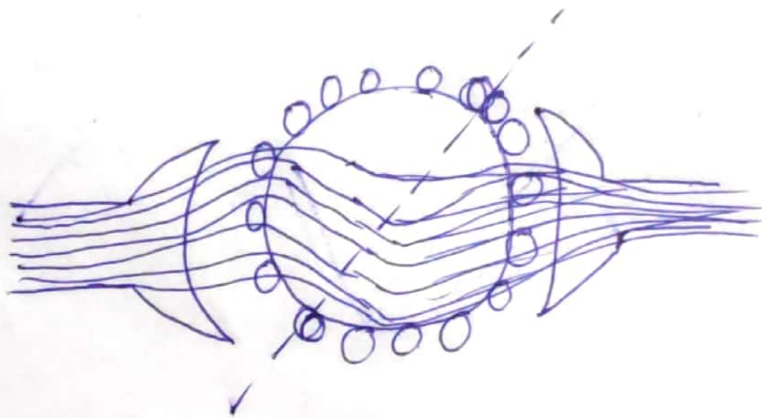magnetic field direction  $\rightarrow$  Right hand screw rule.  
Direction of current  $\rightarrow$  Fleming's Right hand rule.



- (i) Armature reaction is the effect of magnetic field setup by the armature current on the main flux of a generator.
- (ii) Armature magnetic field has two effects...
  - (1) ~~It~~ demagnetised ~~flux~~ or weakens the magnetic ~~flux~~.



(2) ∴ It cross magnetised the main flux.

### Armature reaction:-

(i) In a DC machine two kinds of magnetic flux are present, the armature flux and main field flux.

(ii) The effect of armature flux on the main field flux is called armature reaction.

MNA & GNA :-

MNA : (Magnetically Neutral axis). :-

✓ EMF is induced in the armature conductors, when they cuts the magnetic field lines but there is an axis along which armature conductors move parallel to the flux lines and there is no induced emf along that axis. This axis is known as magnetically neutral axis.

(ii) So MNA may be defined as the axis along which no emf is generated in the armature conductors.

(iii) Brushes are always placed along MNA because reversal of current

in the armature conductor takes place along this axis.


GNA (Geometrical Neutral axis) :-

(i) GNA is defined as the axis which is perpendicular to the main field axis.

→ consider no current is flowing in the armature conductor and only field winding is energized.

→ in this case magnetic flux lines due to the field pole are uniform.

→ so MNA coincides with GNA.

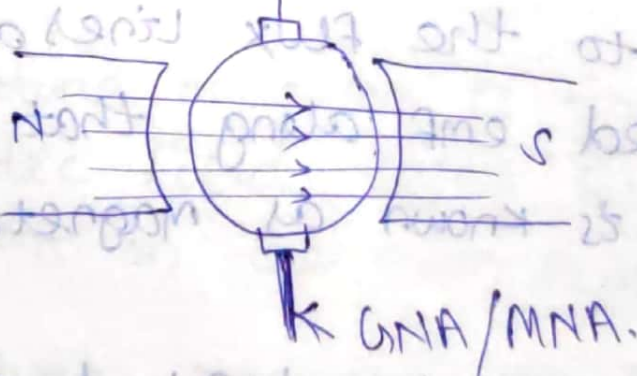

→ when the machine is running both the flux will present at a time.

→ Now the armature flux superimposed



with the main field flux and disturbs it.

→ This armature magnetic field has two effect.

(i) It demagnetised or weakens the main flux.

(ii) It cross-magnetised the main flux.

cross magnetizing effect:-


(i) At first MNA is coincide with GNA.

(ii) When the generator starts, current starts flowing through the armature conductor. Their direction found by Flemings right hand rule. So the current direction is inward in the conductors under N-pole and outward under S-pole.

(iii) The direction of lines of force around the armature conductors can be found by applying Right hand screw rule.

(iv) Now it is seen that the flux through the armature is no longer uniform.

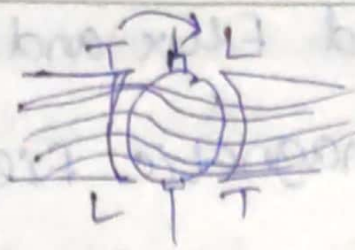
(v) The flux is seen to be crowded at the trailing pole tips but ~~are~~ ~~can~~ weaken or thin Leading pole tips (LPT).



\* When conductors move, if it cross the first side of a pole is called leading and then trailing.

(vi) Now the MNA will shift to a new position.

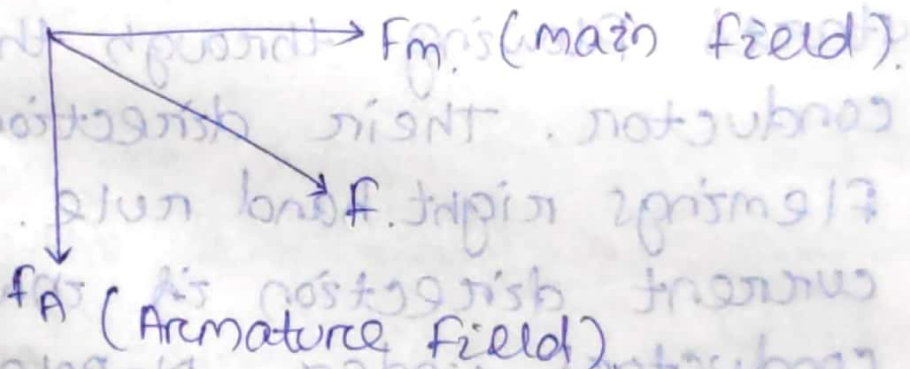(vii) Hence the angle between main field and armature field is  $90^\circ$ .




(viii) So the resultant field is found by vector addition of main field and armature field.


(ix) As MNA shift its original position spark produced in armature.



## Demagnetizing effect :-

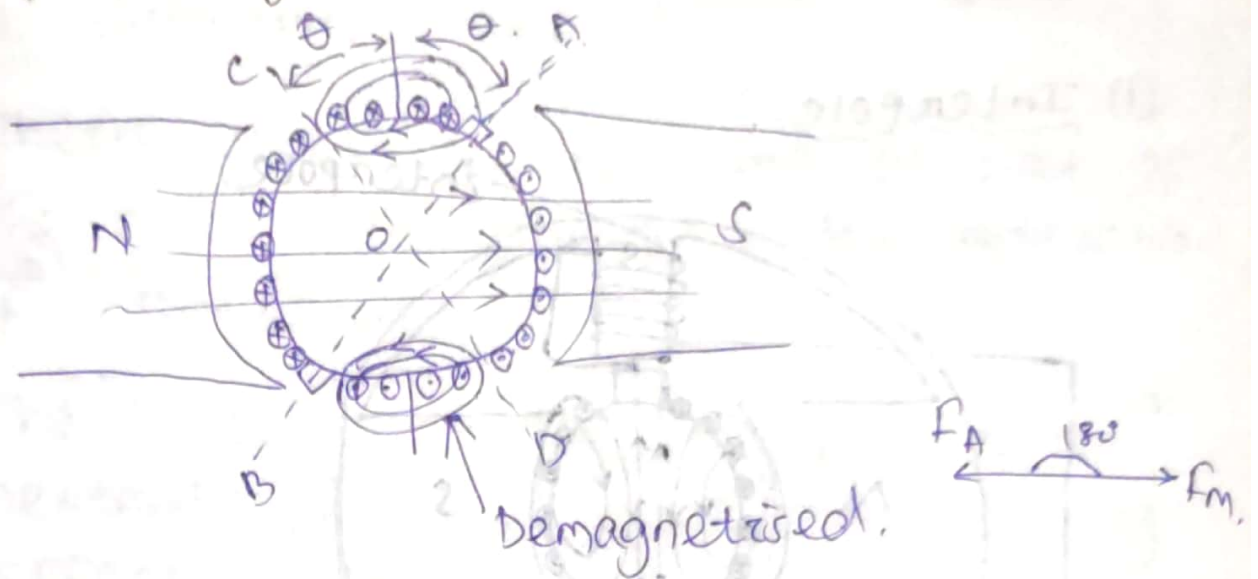

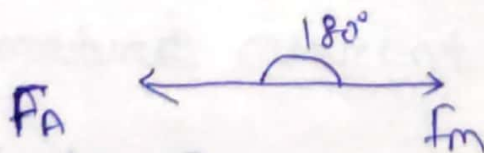
- (i) Hence the MNA is shift to a new position which is at angle  $\theta$  from GNA.
- (ii) The conductors in region  $AOC = BOD = 2\theta$  at the top and bottom of the armature are carrying current in such a direction to create flux an armature from right to left.
- (iii) So the main flux get reduced.




$$F = F_m - F_A$$

## How to reduce armature reaction.

### (1) Interpole.

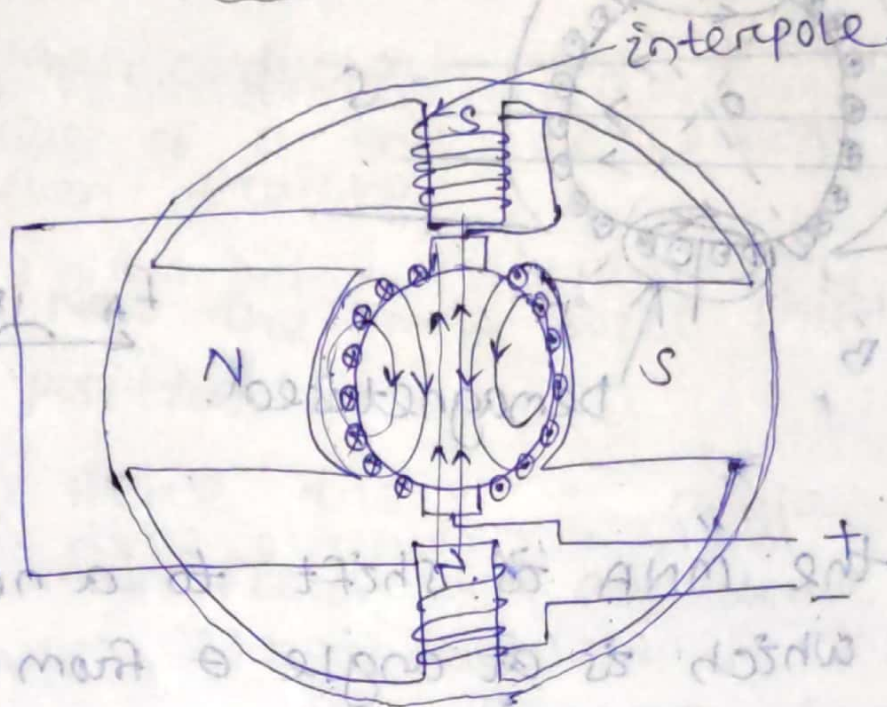

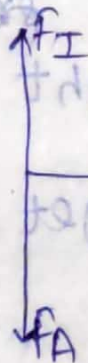\* Inter pole winding connected in series with armature winding.



$F_m$

$F_a$

(i) These are small poles fixed to the yoke and placed in between the main poles.

(ii) They are wound with copper wire and connected in series



with the armature, so that they carry full armature current.


(iii) Their polarity is same as that of the main pole ahead in the direction of rotation.

(iv) The function of the interpole is to neutralised the cross magnetising effect of armature reaction. Hence brushes are not to be shifted from the original position.

(v) Here the flux produced by the interpole is just opposite to the armature flux. Hence they cancel each other.

(vi) This cancellation of cross magnetisation is automatic and for all loads because both are produced by the same armature current.


(a) By using compensating winding.

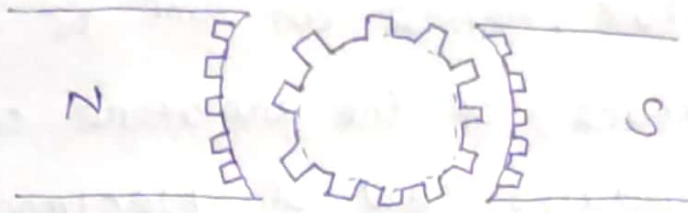


- (i) These are used for large DC machine which are subjected to large fluctuation in load that is rolling, meal motor, turbo generator, etc.
- (ii) The function of compensating winding is to neutralize the cross magnetising effect of armature reaction.
- (iii) In absence of compensating winding arc can strike between consecutive commutator segment.
- (iv) These winding are placed in slots in the pole shoes and are connected in series with armature in such a way that the current in them flows in opposite direction to that of armature conductor directly placed below the poles.




# commutation Process :-

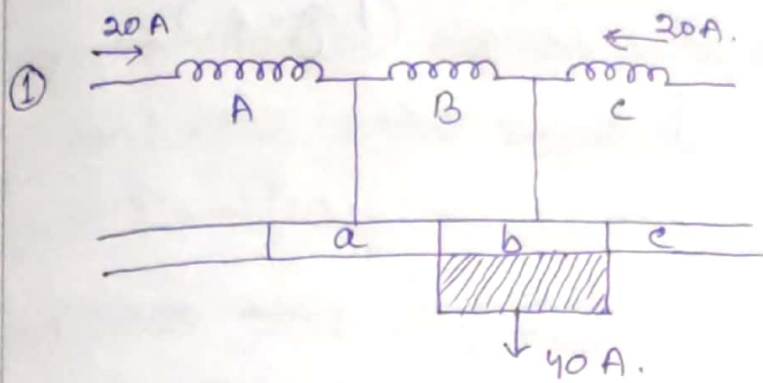


(fig-A.)

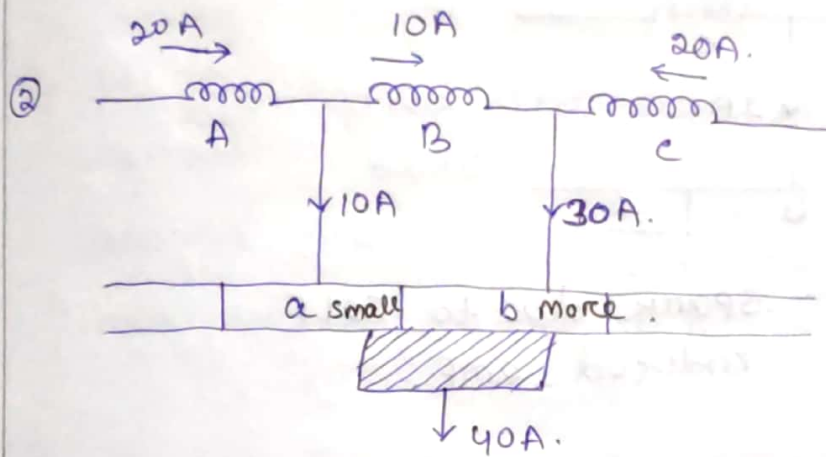



(fig-B.)

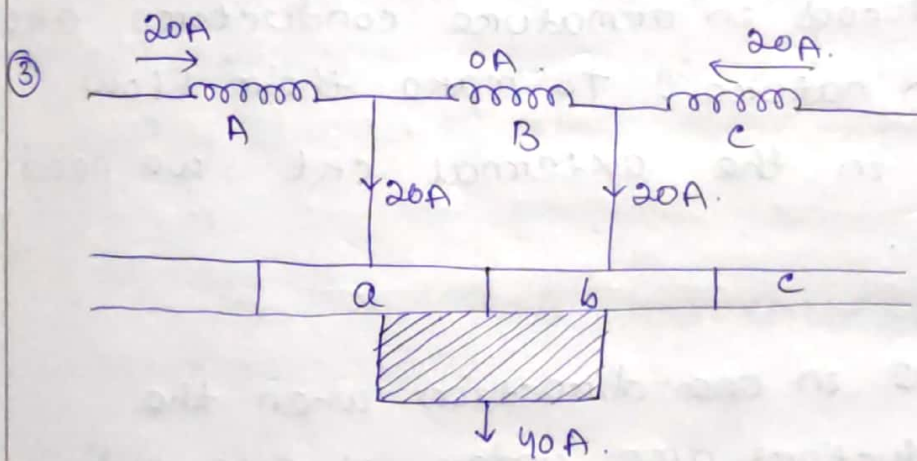

(fig-c.)

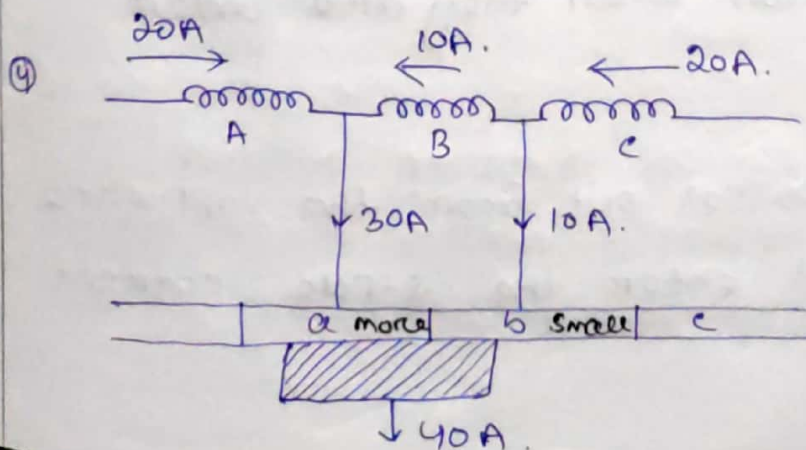

(fig-D.)

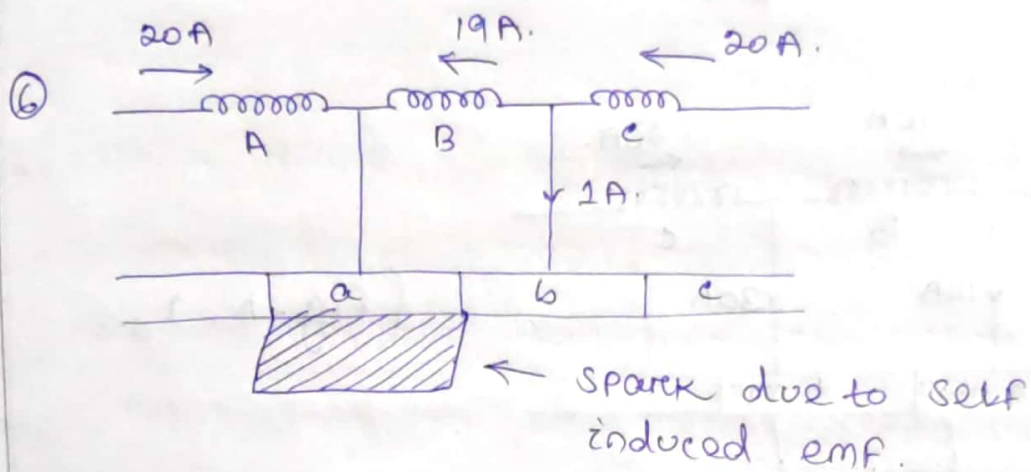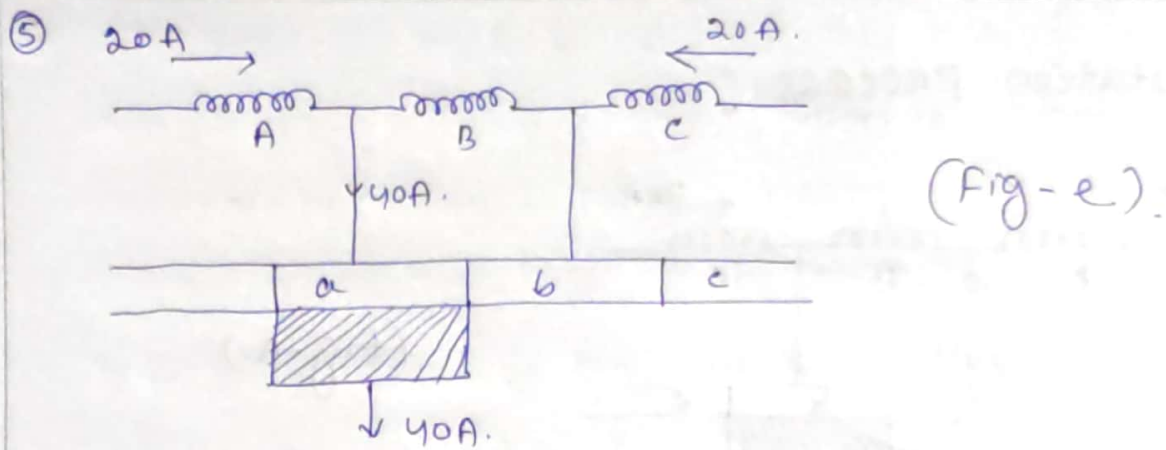

(i) current induced in armature conductors are alternating in nature. To make their flow uni-directional in the external ckt, we need a commutator.

(ii) current flows in one direction when the armature conductors are under N-pole and in opposite direction when they are under S-pole.

(iii) As a conductor passes out from the influence of a N-pole and enter the S-pole, current in them reversed.



- (iv) This reversal of current takes place along the MNA.
- (v) The process by which current is reversed in a conductor while crossing the MNA axis is called commutation.
- (vi) Total time required for this process is known as commutation period.
- (vii) It is assumed that size of each commutator segment is equal to size of brush and each coil carries  $20\text{ A}$  current so that total current output from the brush is  $40\text{ A}$ .
- (viii) In Fig-A, coil-B is about to be ~~short~~ short ckt because brush is about to come in contact with commutator segment 'A'. Here the brush current is  $40\text{ A}$ .
- (ix) In Fig-B coil-B has entered, its period of short ckt current through coil 'B' has reduced from  $20\text{ A}$  to  $10\text{ A}$ . Because,  $10\text{ A}$  current flows via segment 'a'.
- (x) As area of contact of the brush is more with segment 'b' than with segment 'a'. It receives  $30\text{ A}$ . So, the total current is again  $40\text{ A}$ .

(xi) In fig-c, coil-B is in the middle of its short ckt period. Now, current through it has reduce to zero. Two currents of value  $20\text{A}$  each passes to the brush directly from coil A & 'c'. Because the brush contact areas with the two segments A and B are equal.

(xii) In fig-D, it is seen that brush contact area with segment 'B' is decreasing rapidly and with segment 'A' is increasing. coil-B now carries  $10\text{A}$  in reverse direction. The other  $10\text{A}$  supplied by coil-c passes through segment 'B' to the brush.

(xiii)  $10\text{A}$  current of coil 'B' combines with  $20\text{A}$  of coil 'A'. As a result total  $30\text{A}$  current passes through commutator segment to the brush. Again the total current at the brush is  $40\text{A}$ .



(xiv) In fig-e, the coil 'B' is almost at the end of commutation period (short ckt period). For ideal commutation current in coil B should be completely reversed that is  $20\text{A}$  in opposite direction.



- (xiv) If current in coil 'B' can not reverse with in the commutation period, remaining current will try to jump from commutator segment 'B' to the brush. As a result spark is produced.

### characteristic's of separately excited generator.

open ckt characteristics. ∴

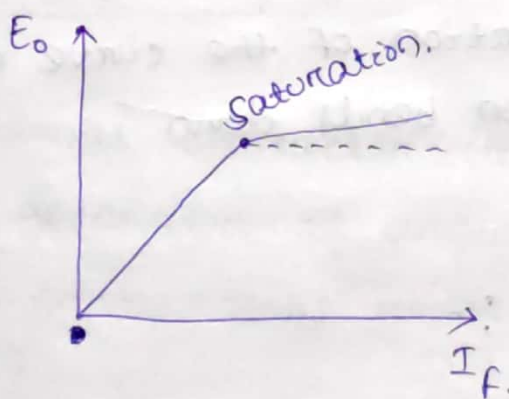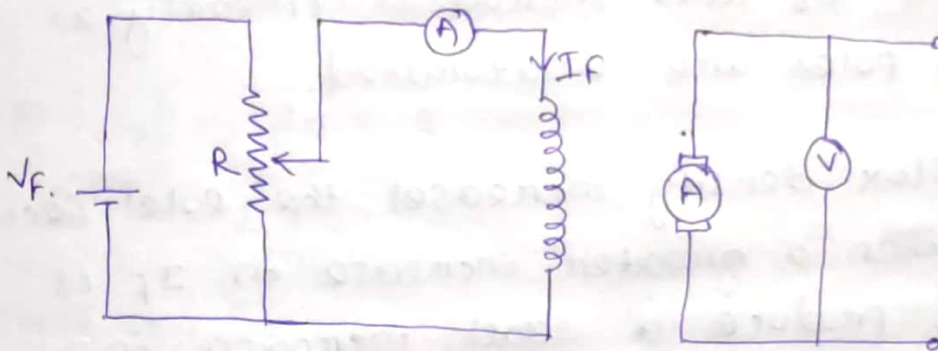

- (i) In a separately excited DC generator field current is obtained from an external independent DC source.

- (ii) Its value can be changed from 0 to upward by using a rheostat.

(ii) we know that the voltage equation of DC generator is  $E_g = \frac{P\phi ZN}{60A}$ , hence if

speed is constant,  $E_g \propto \phi$


(iv) when field current is zero. Flux is also zero. As a result the generated emf is also zero. Therefore the graph starts from initial position.

(v) when  $I_f$  is increased from its initial zero value, generated emf ' $E_o$ ' also increases linearly as long as the poles are unsaturated.


(vi) when the flux density increases the poles become saturated, then a greater increase in  $I_f$  is required to produce a small increase in voltage.

(vii) Therefore the lower portion of the curve is almost linear and upper portion bends down.

Internal characteristics.

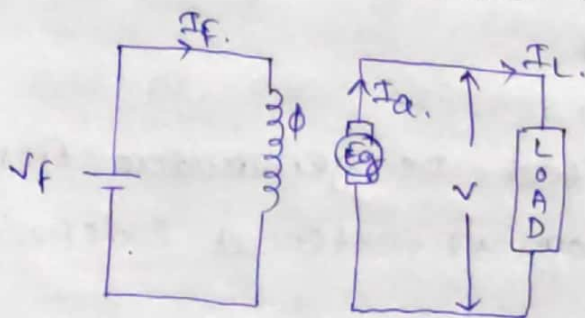



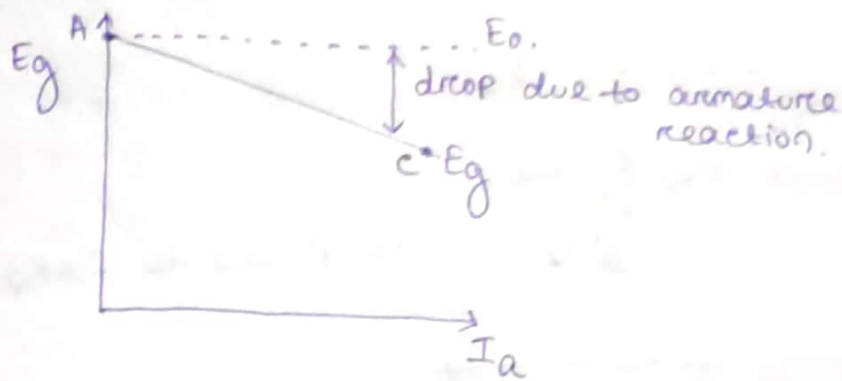

let,

$$\text{Load} = 0, I_a = 0.$$

$$\text{Armature reaction} = 0.$$

$$\text{Load} = \uparrow, I_a = \uparrow$$

$$\text{armature reaction} = \uparrow$$

$$\text{Total Flux} = \phi_m = \phi_A$$


$$\boxed{\phi_A \propto I_a.}$$

(i) Internal characteristics of a separately excited DC generator is obtained by subtracting the drop due to armature reaction from no load voltage ( $E_0$ ).

(ii) This curve is slightly dropping as armature current increases, voltage drop due to armature reaction also increases gradually.

(iii) The 'Ac' line in the diagram indicates the actual generated voltage ' $E_g$ ' w.r.t armature current.

## External characteristics

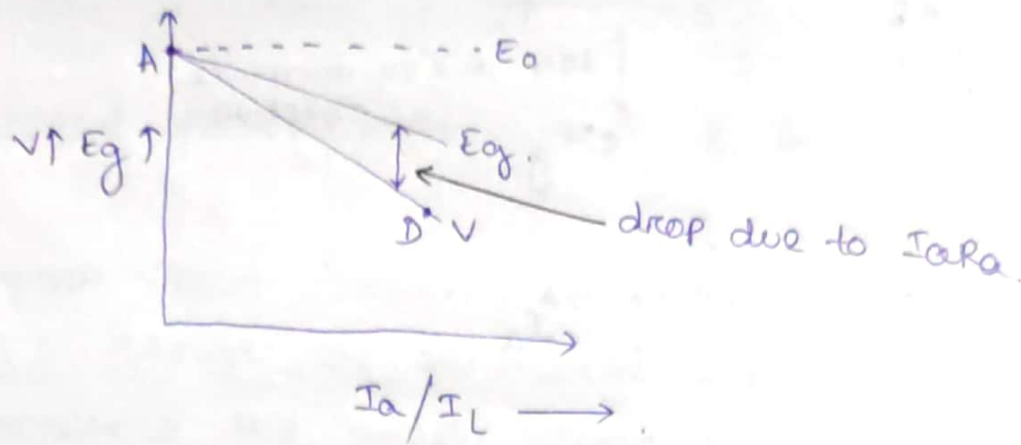

$$E_g = I_a R_a + V.$$

$$V = E_g - I_a R_a$$

(i) External characteristics of a separately excited DC generator is obtained by subtracting the voltage drop due to armature resistance ( $I_a R_a$ ) from the generated voltage ' $E_g$ '.

i.e

$$V = E_g - I_a R_a$$

(ii) The external lies below the internal characteristics curve.

(iii) Here 'AD' line in the diagram indicates the characteristics curve.

(iv) It can be seen from the curve that when load current increases terminal voltage



(v) This decrease in voltage can be maintain easily by increasing field current .


(vi) This type of generator can operate in stable condition with any field excitation and give wide range of output voltage .


(vii) The main disadvantage of this type of generator is that it is very expensive to provide a separately excited source.

Separately excited generator has slightly drooping characteristics.

Dc series Generator.

open ckt characteristic :-

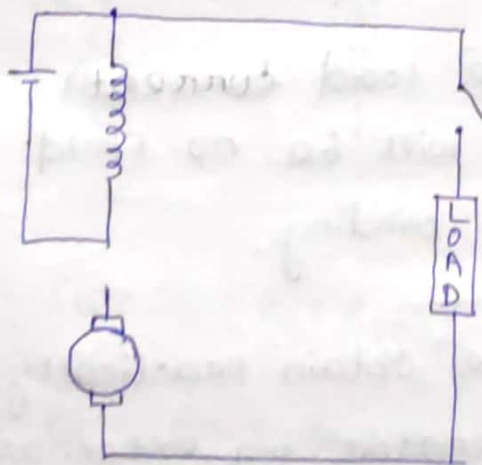

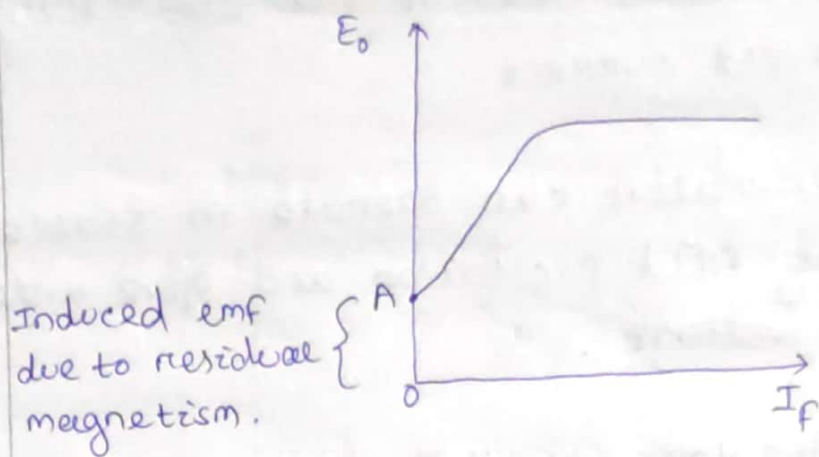

(i) In series generator the armature winding, field winding and external load ckt., all are connected in series with each other.

(ii) Therefore, the same current flow through all parts of the ckt i.e.  $I_a = I_f = I_L$

(iii) The curve which shows the relation between no load voltage and field current is called OCC (Open ckt characteristics).

(iv) As during no load the load terminals are open ckt, there will be no field current in the field winding.

(v) So this curve can be obtained practically by exciting the DC generator by external source.

(vi) Due to residual magnetism there will be a small initial voltage across the armature





that is why the curve started from a point 'A' which is above the origin 'O'.

(vii) when field current is increased, generated emf ' $E_g$ ' increases directly as long as the poles are unsaturated.

(viii) when the flux density increases the poles become saturated, then a greater increase in  $I_f$  is required to produce a small increase in voltage.

(ix) Therefore, the lower portion of the curve is almost linear and upper portion bends down.

### Internal characteristics.

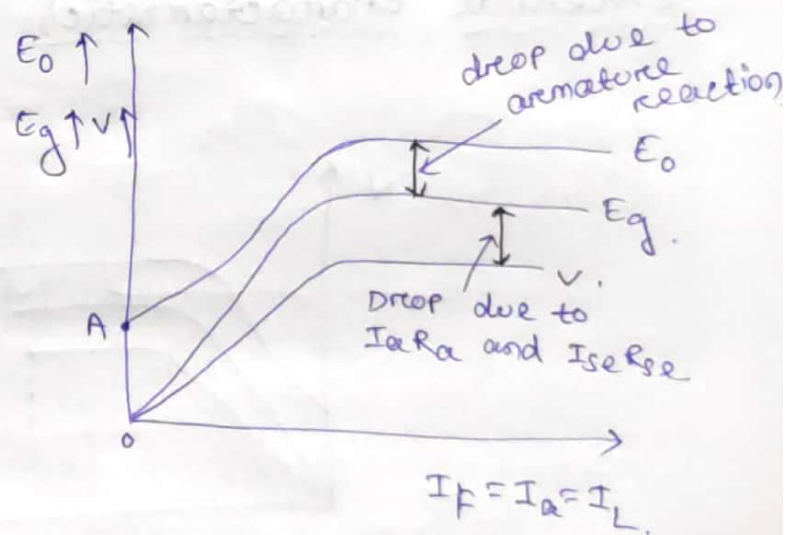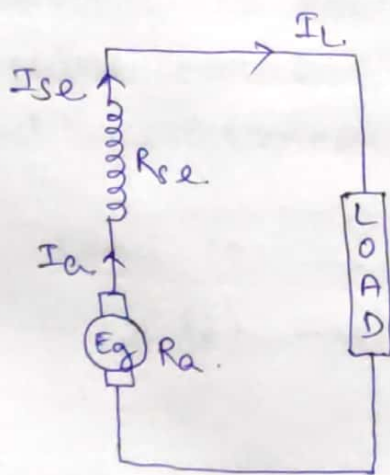

$$V = E_g - I_a (R_a + R_{se}).$$

$$E_g = E_0 - \text{drop due to armature reaction.}$$

$$E_g < E_0.$$

$$V = E_g - I_a (R_a + R_{se}).$$

$$V < E_g.$$


(\*) Dc series generator has rising characteristics.

(i) The internal characteristics curve gives the relation between generated voltage in the armature current ' $I_a$ '.

(ii) This curve is obtain by subtracting the drop due to demagnetizing effect of armature reaction from the no load voltage.

(iii) So, the actual generated voltage  $E_g$  will be less than no load voltage  $E_0$  that is why the curve is slightly dropping from the o.c.c curve.

External characteristics :-

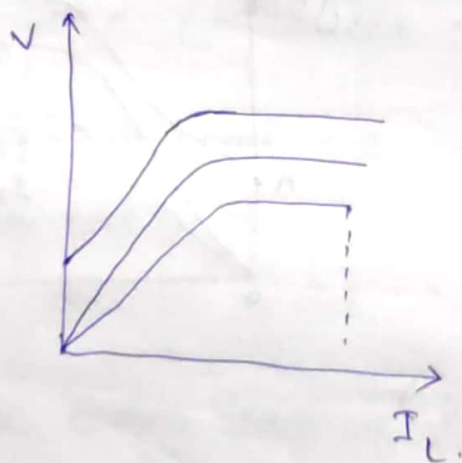

(i) This curve shows the variation of terminal voltage ' $V$ ' with the load current ' $I_L$ '.

(ii) Terminal voltage of this type of generator



is obtain by subtracting the ohmic drop or resistive drop due to armature resistance ' $R_a$ ' and series field resistance ' $R_{se}$ ' from the actual generated voltage ' $E_g$ '.

$$V = E_g - I_a (R_a + R_{se}).$$

- (iii) The external characteristics curve lie below the internal characteristics curve because the value of ' $V$ ' is less than ' $E_g$ '.
- (iv) But after reaching it's maximum value it starts to decrease due to excessive demagnetising effect of armature reaction.
- (v) Dotted portion of the characteristics gives decrease in terminal voltage and approximately constant current irrespective of the external load resistance.


$$\begin{aligned} \text{Load } (\uparrow) &\rightarrow I_L (\uparrow), \\ V (\downarrow) &\rightarrow I_L (\downarrow). \end{aligned}$$

- (vi) Because increase in load tends to increase the load current but decrease in load voltage tends to decrease load current (ohm's law).
- (vii) Due to these two simultaneous effect there will be no significant in the load current.

DC series generator has constant current characteristics.



## Shunt Generator.

### open ckt characteristics.

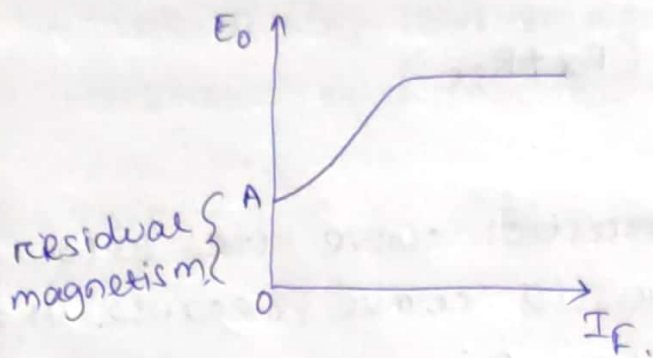

\* Same as OCC of series generator.

### Internal characteristics.

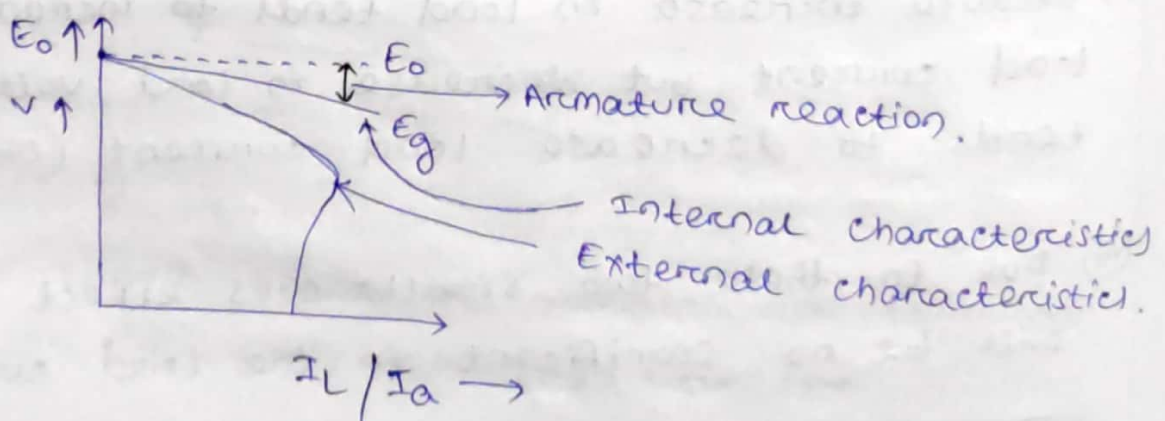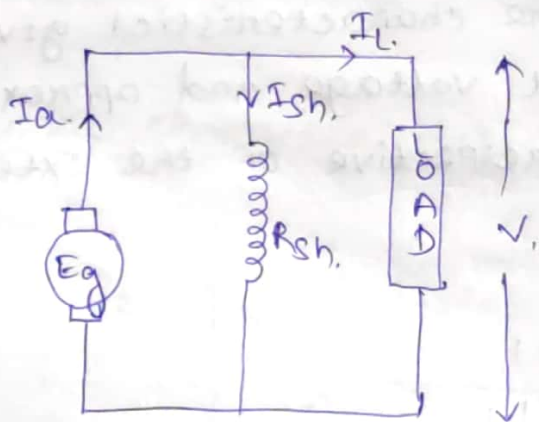



(i) It shows the variation of generated voltage  $E_g$  with the armature current  $I_a$ .

(ii) When the generator is loaded, the generated voltage is decreased due to armature reaction.

(iii) So, the internal characteristics curve will be below the no load induced emf  $E_0$ .

(iv) The drop will increase with increase in armature current.

External characteristics :-

$$V = E_g - I_a R_a$$

↑ constant                      ↑ Increase with increase in load.

(i) It shows the relation between terminal voltage 'V' and load current  $I_L$ .

(ii) This curve is obtained by subtracting the ohmic drop due to armature resistance from the generated voltage.

$$V = E_g - I_a R_a$$

(iii) When load is increased terminal voltage will decrease with increase in load current.

(iv) Therefore the external curve always lies below the internal curve.


(v) But after a certain point, terminal voltage start to decrease drastically due to excess armature reaction and ohmic drop.

(vi) Just like series generator here also two factor acts simultaneously. Increase in load will try to increase the load current and decrease in load voltage will try to decrease the load current.

(vii) But here the effect of decrease in load voltage is more. As a result the load current will start to decrease.

Compound Generator.

External characteristics.

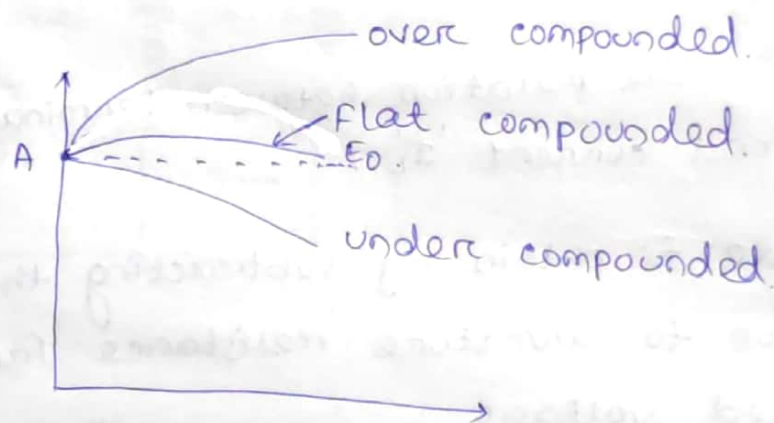

(i) If series and shunt winding ampere turns are adjusted, so that, increase in load current causes increase in terminal voltage, then the generator is called over compounded generator.



(i) If the series and shunt winding ampere turns are adjusted, so that terminal voltage remains constant even when load current is increased, then the generator is called as Flat compounded generator.


(ii) If the series winding has Less no. of turns. Increase in load current causes decrease in terminal voltage. This type of generator is called under compounded Generator.

critical resistance :-

$$I_f = 0$$

$$E_o = \downarrow$$

[only due to residual magnetism]

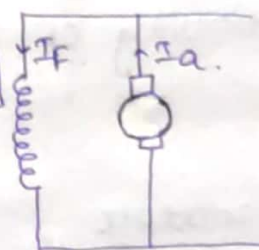

Rotate the armature.

$$I_f = \uparrow \quad \phi = \uparrow \quad E_o = \uparrow$$

$$I_f = \uparrow\uparrow \quad \phi = \uparrow\uparrow \quad E_o = \uparrow\uparrow$$

(i) critical resistance is the value of shunt field resistance above which if it is increased, then voltage build up in a shunt generator is not possible or zero.

(ii) The speed of the shunt generator when its field resistance is equal to critical resistance is called critical speed.

## Voltage build up of a shunt generator:

- (i) Before loading a shunt generator, it is allowed to build up its voltage.
- (ii) Usually there is always present some residual magnetism in the poles. Hence a small EMF is produced initially.
- (iii) This emf circulates a small current in the field circuit which increases the pole flux.
- (iv) When the flux is increased, generated emf is increased which further increases the flux and so on.
- (v) Now the generated emf in the armature has two functions:
  - (1) To supply the ohmic drop  $I_{sh} R_{sh}$  in the winding
  - (2) To overcome the opposite self induced emf in the field coil.



$$E_g = I_{sh} R_{sh} + L \frac{dI_{sh}}{dt}$$

condition for voltage build up of a shunt generator

(i) There must be some residual magnetism in the generator poles.

(ii) For the given direction of rotation the shunt field coils should be correctly connected to the armature.

(iii) If excited on open ckt its shunt field resistance should be less than critical resistance.

(iv) If excited on load, then its shunt field resistance should be more than a certain minimum value of resistance.

## Parallel operation of DC generator :-

→ It is economical to install no. of smaller rated generators in parallel than installing a bigger rated DC generator.

### Advantages :-

→ Easy to increase generating plant capacity. The demand of electricity is increasing day by day. To meet the requirement of extra load or demand extra generators are connected in parallel with the running generator.

### → Continuity of Power supply :-

In case of breakdown of one generator, the power supply will not interrupt, because of supply can be maintained by the healthy generator.


### → Easy to maintain :-

The routine maintenance of generator is required time to time. If the generators are connected parallelly routine maintenance can be done by one without interrupting the power supply.



→ Increases system efficiency :-

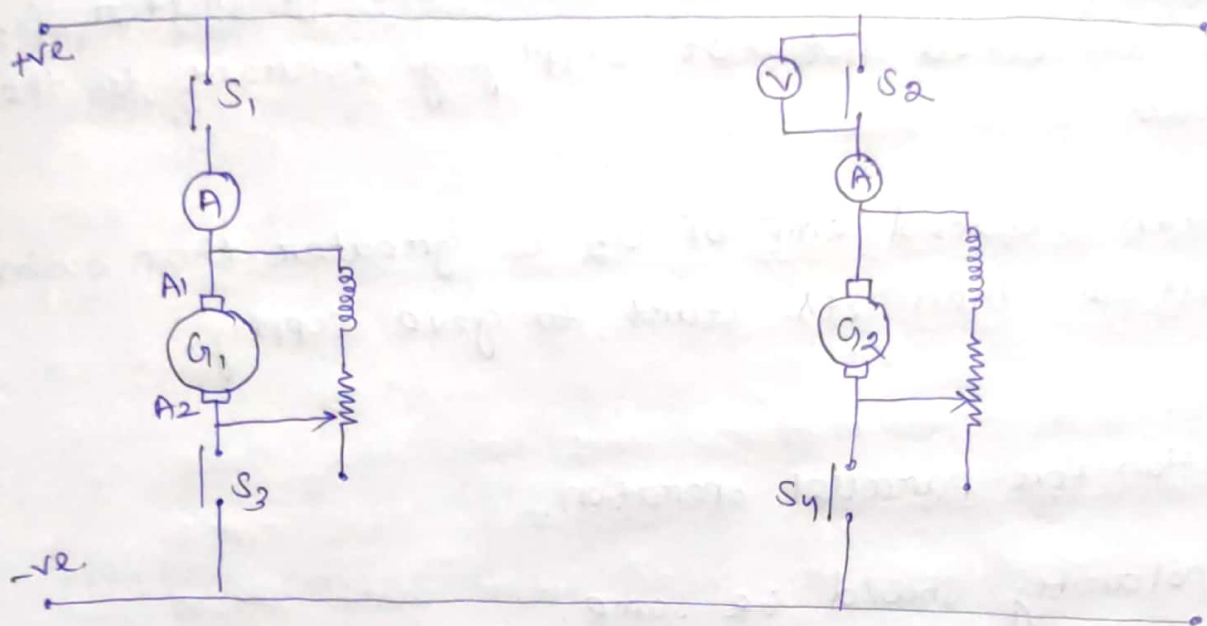If generators are connected parallelly we can turn on the amount of generator according to demand. If the load is less, one or more generator can be shutdown. As a result efficiency of the system increases.



(i) Generators are connected by heavy thick copper bar called busbar which acts as +ve and -ve. terminals, positive terminal of the generator are connected to +ve terminal of busbar and negative terminal of the generator are connected to -ve busbar.

(ii) Let generator-1 ( $G_1$ ), is already connected.

(iii) To connect generator-2 parallelly with  $G_1$ , we have to first bring the speed of prime mover of second generator to rated speed.

Then switch -4 is closed.

(iv) Excitation of generator-2 is increase with the help of field rheostat, till it's generate voltage is equal to the busbar voltage.

(v) when voltmeter 'V' indicates 0 (zero) reading, switch  $S_2$  is closed. This condition is called floating condition, that means the generator  $G_2$  is connected but not supplying current to the load.

(vi) when induced emf of  $G_2$  is greater than busbar voltage then it start to give supply.

condition for parallel operation.

(i) polarity should be same.

(ii) voltage should be same.



## uses of DC Generator

### Series generator :-

- (i) These are not used for power supply because of their rising characteristics.
- (ii) Their rising characteristics makes them suitable for being used as boosters.

### Shunt generator :-

Shunt Generator with field regulators are used for ordinary lighting and power supply purpose.

### Compound Generator :-

(i) Cumulatively compounded generator is the most widely used DC generator because its external characteristics can be adjusted.

(ii) Hence such generators are used for heavy power service such as Electric railways.

(iii) lamp loads, for motor which required DC supply and constant voltage.

(iv) The differentially compound generator widely used in arc welding where large voltage drop is desirable with increase in current.





## Chapter-2 (DC MOTOR)

Motor is a device or machine which converts electrical energy to mechanical energy.

Working Principle :-

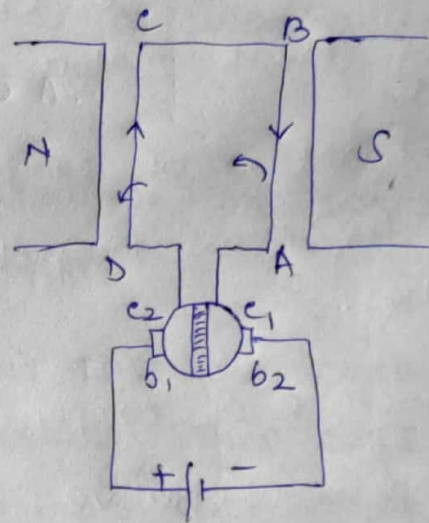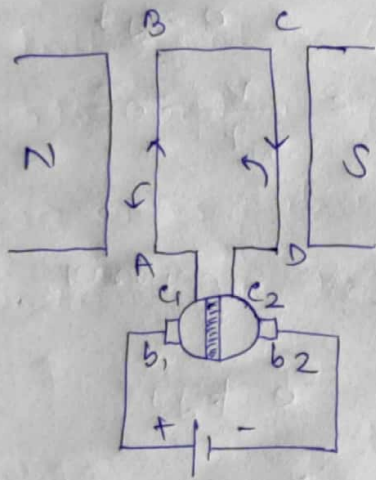Electrical energy  $\rightarrow$  Motor  $\rightarrow$  Mechanical energy.



(i) whenever a current carrying conductor placed in a magnetic field it will experience a force (Lorenz law).

(ii) The direction of force experienced is given by Fleming's left hand rule. According to Fleming's left hand rule, if we stretch middle finger, forefinger and thumb of our left hand perpendicular to each other, then middle finger

will indicate the direction of current in the conductor, fore finger indicate the direction of magnetic flux and thumb will indicate the direction of force.

Back emf :-

→ when the motor starts to rotate the armature conductor cuts the flux and emf is induced in the conductors according to Faraday's law of electro magnetic induction,

→ Polarity of the induced emf is such that it always opposes the supply voltage.

→ This induced emf is called as back emf ( $E_b$ ),

$$E_b \propto \phi N$$

$$N \propto \frac{E_b}{\phi}$$


At starting  $E_b = 0$ ,

At rated speed  $E_b = \text{maximum}$ .

$$V = I_a R_a + E_b$$

$$\Rightarrow I_a R_a = V - E_b$$
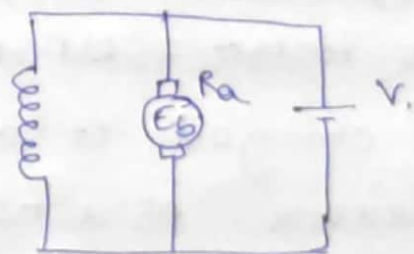
$$\Rightarrow I_a = \frac{V - E_b}{R_a}$$



Here  $V$  and  $R_a$  is constant

So,

$$I_a \propto E_b$$



$$E_b \propto N$$

then,

$$I_a \propto N$$

$\therefore$  So current depends upon speed of motor.

At starting,

$$E_b = 0$$

$$I_a = \frac{V}{R_a} = \frac{230}{0.2} = 1150 \text{ A.}$$

At running

$$E_b \neq 0$$

$$I_a = \frac{V - E_b}{R_a}$$

Significance of Back EMF. :-

- (i) Significance of Back emf is that it makes the motor self regulating. If load of motor is changed it automatically change the input current. As a result it draws i/p power as the requirement of the load. It draws less input power, if the load is less and it draws more input power, if the load is large.

$N = N_1$     load  $\uparrow\uparrow$      $N_1 \downarrow\downarrow$      $E_b \downarrow\downarrow$      $I_a \uparrow\uparrow$      $P_{i/r} \uparrow\uparrow$   
                  load  $\downarrow\downarrow$      $N_1 \uparrow\uparrow$      $E_b \uparrow\uparrow$      $I_a \downarrow\downarrow$      $P_{i/r} \downarrow\downarrow$

(ii) magnitude of back emf is directly proportional to speed of the motor.


$$E_b \propto N.$$

(iii) Let, load on a dc motor is suddenly reduce, speed of the motor will increase due to excess torque. As a result back emf will increase which decreases the armature current as well as load current, so the input power reduce according to the load.


(iv) on the other hand If a dc motor load is suddenly increase, speed of the motor will decrease. Due to decrease in speed back emf will also decrease, as a result armature current and load current and input power increases. so the increased armature current increases the torque to rotate the motor. Hence, presence of back emf makes a dc motor self regulating.



Torque :-

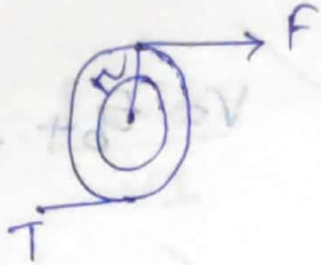

$$T = F \times r$$

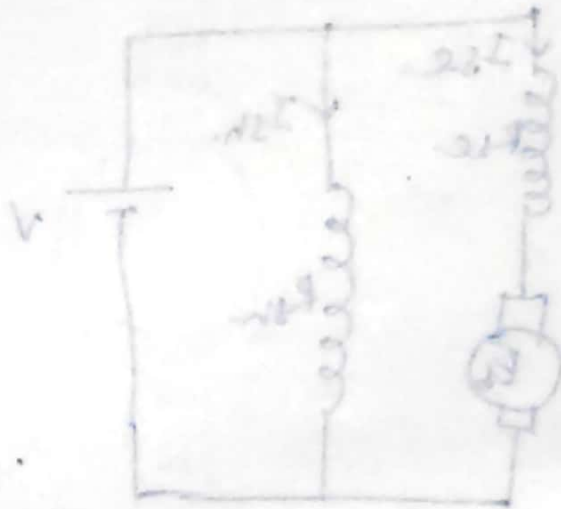

(i) Torque is a measure of how much force acting on an object to rotate it or the turning or twisting movement of a force about an axis is known as torque.

(ii) It is measured by the product of force and the radius at which the force acts.

(iii) Consider a pulley of radius  $r$ -meter. A force of  $F$  newton is acting upon

it to rotate it at rpm.

$$\text{Torque (T)} = f \times r$$

unit = N-m.

work done by this force on one revolution.

$$W = f \times \text{distance}$$

$$= f \times 2\pi r$$

$$P = \frac{W}{t}$$

$$= \frac{f \times 2\pi r}{\frac{60}{N}}$$

$$= \frac{f \times 2\pi r}{60/N}$$

$$= \frac{2\pi r f N}{60}$$

$$= (f r) \times \frac{2\pi N}{60}$$

$$= \left[ \frac{1}{N} \times \frac{2\pi N}{60} \right] = \frac{2\pi}{60} \quad (\omega - \text{omega})$$

$$\left[ \frac{1}{N} \times \frac{2\pi}{60} \times T N \right] = \frac{2\pi}{60} \times T$$

$$= 0.104 \text{ N.T watt}$$



✓ Armature torque :- ( $T_a$ ).

let,

$T_a$  be the torque developed by the armature of a motor running at  $N$  rpm. then mechanical power developed

$$P_m = T_a \times \frac{2\pi N}{60} \text{ watt.}$$

$$\frac{W}{T} = 9$$

Electrical power at armature

$$P_e = E_b I_a \text{ watt.}$$

$$\boxed{P_m = P_e}$$

$$\Rightarrow T_a \frac{2\pi N}{60} = E_b I_a$$

$$\Rightarrow T_a = \frac{E_b I_a \times 60}{2\pi N}$$

$$T_a = 9.55 \frac{E_b I_a}{N} = \left[ \frac{4.71}{0.02} T \propto \frac{1}{N} \right] \checkmark$$

$$\Rightarrow T_a = 9.55 \frac{I_a}{N} \times \phi Z \frac{P}{A} \left[ E_b = \frac{\phi Z N}{60} \times \frac{P}{A} \right]$$

$$\Rightarrow T_a = 9.55 \frac{I_a}{60A} \times \phi Z P$$

$$\Rightarrow \boxed{T_a = 0.159 \phi Z \frac{P}{A} I_a}$$

shaft torque :-

$$\text{output power of motor} = T_{\text{shaft}} \frac{2\pi N}{60}$$

$$T_{\text{sh}} = \frac{\text{o/p power}}{N} \times 9.55$$

$$\Rightarrow T_{\text{sh}} = \frac{\text{output power of motor}}{2\pi N} \times 60$$

$$= 9.55 \frac{\text{o/p}}{N} \text{ N-m.}$$

$$T_a = 9.55 \frac{E_b I_a}{N}$$



(1) A 4-pole 240 V wave connected shunt motor gives 11.19 kW, when running at 1000 rpm. and drawing armature and field currents of 50 A and 1 A respectively. The armature has 540 conductors and its resistance is  $0.1 \Omega$ . Assuming a drop of 1 V per brush. Find

(i) armature torque

$$\frac{9450}{400} = 23.625$$

(ii) shaft torque

(iii) flux per pole

$$\frac{240 \times 1000 \times 0.01}{2 \times 540} = 2.22 \text{ Wb}$$

(iv) rotational losses

$$\frac{240 \times 1000 \times 0.01}{2 \times 540} = 2.22 \text{ Wb}$$

(v) efficiency

$$\frac{240 \times 1000 \times 0.01}{2 \times 540} = 2.22 \text{ Wb}$$

Given data :-

$$P = 4$$

wave wound.

$$A = 92$$

$$V = 240 \text{ V.}$$

$$Z = 540$$

$$I_a = 50 \text{ A}$$

$$R_a = 0.1 \Omega$$

$$I_{sh} = 1 \text{ A}$$

$$V_B = 2 \text{ V.}$$

$$P = 11.19 \text{ kW.} = 11.19 \times 10^3 \text{ watt.}$$

$$N = 1000$$

$$V = E_b + I_a R_a + V_B$$

$$E_b = V - I_a R_a - V_B$$

$$E_b = 240 - (50 \times 0.1) - 2$$

$$E_b = 233 \text{ V.}$$

$$E_b = \frac{\phi Z N P}{60 A}$$

$$233 = \frac{\phi \times 540 \times 1000 \times 4}{60 \times 2}$$

$$\phi = \frac{233 \times 60 \times 2}{540 \times 1000 \times 4} = 0.012 \text{ wb.}$$



$$T_a = 9.55 \times \frac{E_b I_a}{N}$$

$$= 9.55 \times \frac{233 \times 50}{1000}$$

$$= 111.257 \text{ N-m.}$$

$$\text{i/p Power} = V \times (I_a + I_{sh})$$

$$= 240 \times 51$$

$$= 12,240 \text{ watt}$$

$$\text{o/p Power} = 11.19 \times 10^3 \text{ watt}$$

$$T_{sh} = \frac{\text{o/p Power}}{N} \times 9.55$$

$$= \frac{11.19 \times 10^3}{1000} \times 9.55$$

$$= 1067.86 \text{ N-m.}$$

$$\text{efficiency} = \frac{\text{o/p}}{\text{i/p}} = \frac{11.19 \times 10^3}{12,240} = 0.9142$$

$$(91.42\%)$$

$$\begin{aligned}
 \text{Total Losses} &= \text{Input} - \text{Output} \\
 &= 12240 - (11.19 \times 10^3) \\
 &= 1050 \text{ watt.}
 \end{aligned}$$

$$\begin{aligned}
 \text{Copper Loss} &= (I_a + I_{sh})^2 R_{sh} \\
 &= I_a^2 R_a + I_{sh}^2 R_{sh} \\
 &= (50^2 \times 0.1) + (1^2 \times \frac{240}{1}) \\
 &= 490 \text{ watt.}
 \end{aligned}$$





$$\text{Brush contact losses} = \frac{V_b \times I_a}{22.7 \times 10^3} = \frac{2 \times 50}{22.7 \times 10^3} = 100 \text{ watt}$$

$$\text{rotational losses} = 1050 + (490 + 100) = 1640 \text{ watt}$$

$$\text{P.O} = \frac{E_b \times I_a}{E_g \times I_a} = \frac{950}{950} = 1.0$$

## characteristics of DC series motor

(1)  $T_a$  Vs.  $I_a$  :-

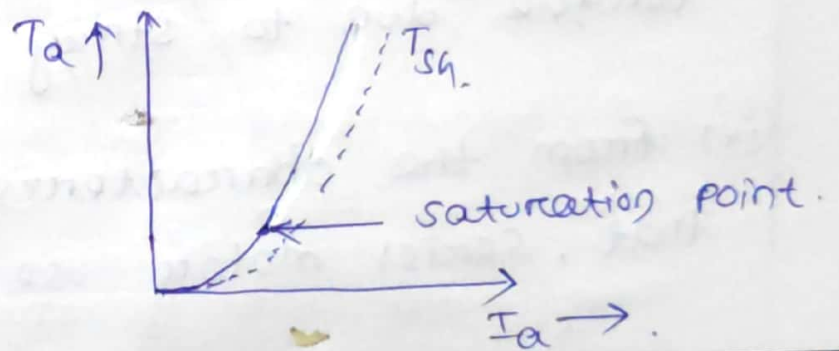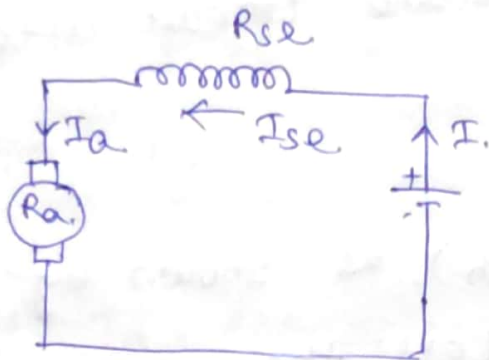



$$T \propto \phi I_a$$

$$\phi \propto I_{se}$$

$$\phi \propto I_a$$

$$\Rightarrow \boxed{T \propto I_a^2} \leftarrow \text{before saturation.}$$

$$\boxed{T \propto I_a} \leftarrow \text{After saturation.}$$

(i) Before saturation torque  $\propto I_a^2$ . At light load  $I_a$  is small, hence Flux is small. As  $I_a$  increases, armature torque  $T_a$  also increases as square of the armature current.


(ii) Hence, initially the torque is parabolic but after saturation the flux is almost independent of  $I_a$ , hence torque ( $T_a$ )  $\propto I_a$ . So, the characteristics become linear after saturation.

(iii) The shaft torque ( $T_{sh}$ ) is shown by the dotted line. It is less than armature torque due to stray loss.

(iv) From the characteristics we can conclude that, series motor use where <sup>huge</sup> starting torque.

is required for accelerating heavy masses like electric train.

(2)  $N$  vs.  $I_a$  :-

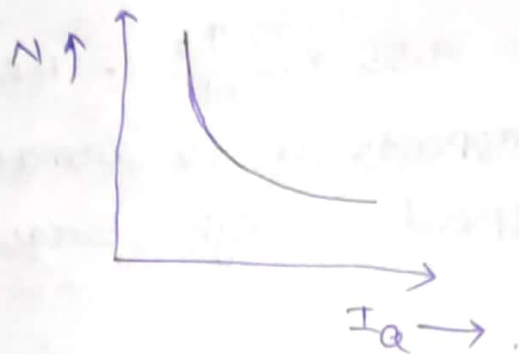

$$\left\{ \begin{array}{l} E_b \propto \phi N \\ \downarrow N \propto \frac{E_b \downarrow}{\phi \uparrow} \\ E_b = V - I_a R_a \end{array} \right.$$

(i) variation of speed can obtain from the formula


$$N \propto \frac{E_b}{\phi}$$

(ii) As load increase  $I_a$  increase, with increases the flux. Hence change in  $E_b$  for various load current is very small.

(iii) Hence the speed varies inversely as the armature current. when load is heavy,  $I_a$  is large and speed will be low.

(iv) when load is small  $I_a$  falls to a very small value. As a result speed become very high.

(3)  $N$  vs.  $T_a$  characteristics :-

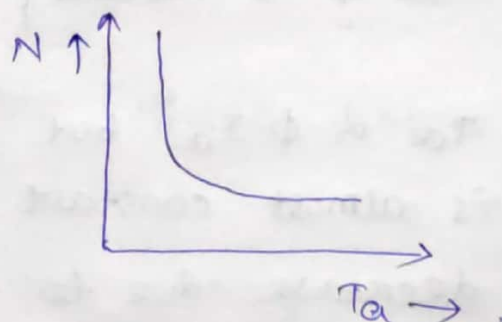

$$T_a \propto \frac{1}{N}$$



$$T_a = 9.55 \times \frac{E_b I_a}{N}$$


$$N \propto \frac{E_b}{T_a} \quad \text{because } \phi \propto I_a$$

→ we know that  $T_a = 9.55 \times \frac{E_b I_a}{N}$ . Here speed is inversely proportional to armature torque. so, when speed is high, torque is low.

→ when speed is low, torque is high.

Shunt Motor.

$T_a$  Vs  $I_a$  characteristics.

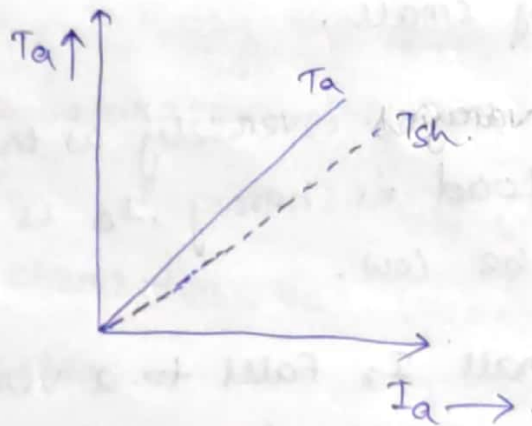

$$T_a \propto \phi I_a$$


$$\boxed{T_a \propto I_a} \quad \left\{ \text{because } \phi \text{ is constant} \right\}$$

(i) we know that  $T_a \propto \phi I_a$  but in shunt motor the flux is almost constant only of heavy load.  $\phi$  decrease due to increase

in armature reaction.

- (i) Therefore, In a shunt motor  $T_a \propto I_a$ . So the characteristics is a straight line passing through the origin (linear).


$N$  vs  $I_a$  characteristics. :-

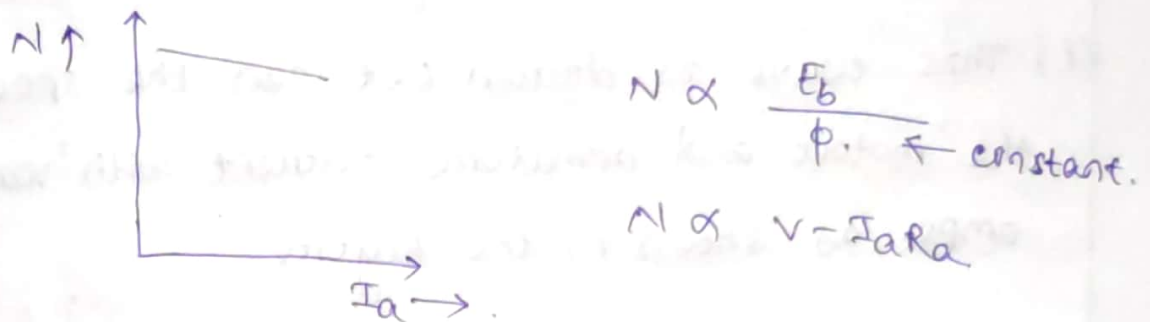

- (i) In a shunt motor, Flux is almost constant, therefore  $N \propto E_b$ . But practically both  $E_b$  and Flux decreases with increase in load.
- (ii) However, decrease in  $E_b$  is more than the flux, as a result there is some decrease in speed.
- (iii) From the characteristics we can notice that there is no appreciable change in the speed of DC shunt motor from no load to full load.
- (iv) Therefore these motor are used where sudden change in the load takes place like wood cutting, Lathe machine, etc.



$N$   $V_s$   $T_a$  characteristic. :-

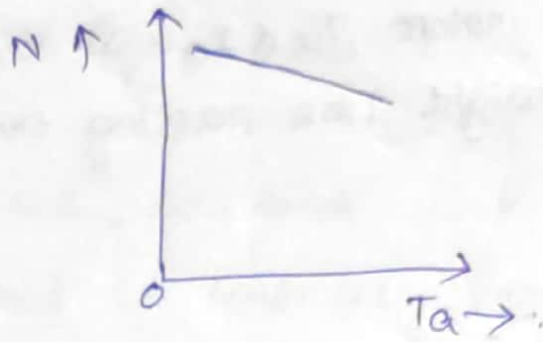

(i) This curve is drawn between the speed of the motor and armature current with various amps. as shown in the figure.

(ii) From the curve it is understood that the speed reduces when the load torque increases.


(iii) With the above three characteristics, it is clearly understood that when the shunt motor runs from no load to full load there is slight change in speed. Thus, it is essentially a constant speed motor.

Since the armature torque is directly proportional to the armature current, the starting torque is not high.

## compound Motore. :-

- (i) These motores have both series and shunt winding
- (ii) If Series Field flux is in the same direction with shunt field flux, then motore is said to be cumulative compound motore.
- (iii) If the series field opposes the shunt field, then the motore is said to be differential compound motore.

## N vs Ia characteristics :-

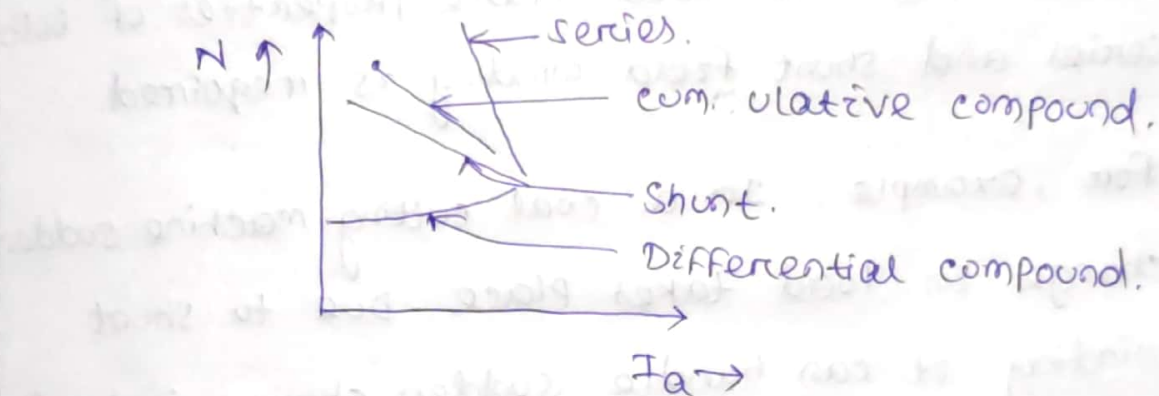

## cumulative compound.

$$\phi_t = \phi_{sh} + \phi_{se}$$

$$\text{Load} \uparrow \quad I_a \uparrow \quad \phi_{se} \uparrow \quad \phi_t \uparrow \quad N \downarrow$$


## Differential compound

$$\phi_t = \phi_{sh} - \phi_{se}$$

$$\text{Load} \uparrow \quad I_a \uparrow \quad \phi_{se} \uparrow \quad \phi_t \downarrow \quad N \uparrow$$



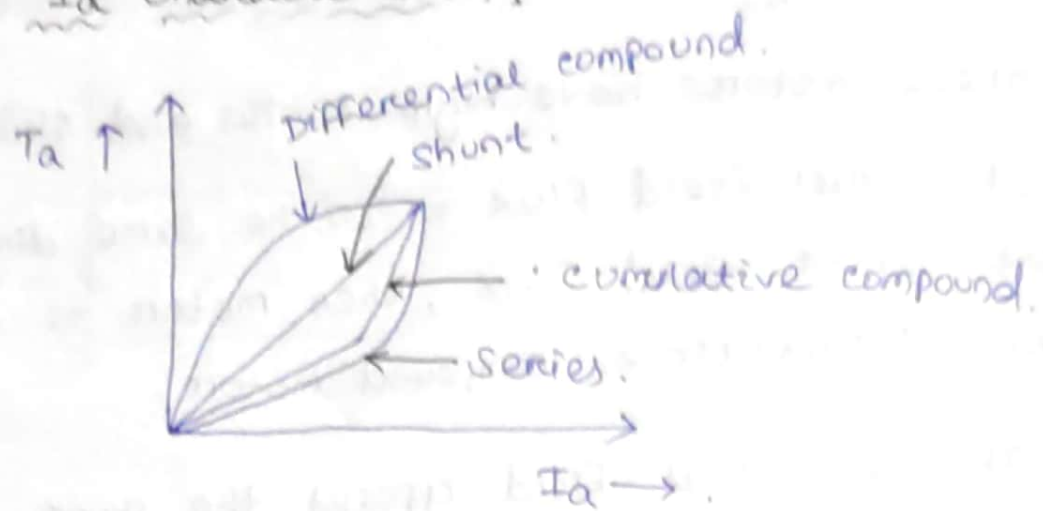$T_a$   $V_s$   $I_a$  characteristics :-



cumulative compound Motor :-

- (i) These motor are used where properties of both series and shunt field winding is required.
- (ii) For example, In a coal cutting machine sudden change in load takes place. Due to shunt winding it can handle sudden change in load and due to series field it will be able to take heavy load.
- (iii) cumulative compound motor are used where high starting torque is required with pulsating loads.

Differential compound Motor :-

- (i) As series field opposes the shunt field, if load is increased, total flux will decrease.

(ii) Therefore speed of differential compound motor is constant when load is less, but speed increases with increase in load.


(iii) Therefore, these motors are not commonly used.



## Speed control of DC series motor :-

### 1) Flux control method :-

#### (a) field diverter :-

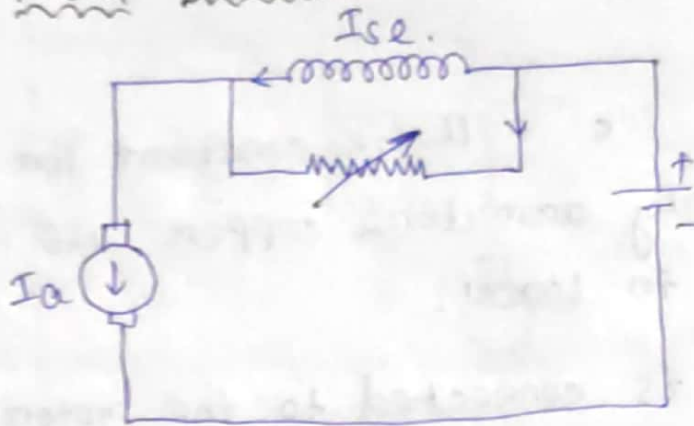


$R = \text{max}$  ,  $I_{se} = \text{max}$  ,  $\phi = \text{max}$  ,  $N = \text{minimum}$

$R = \downarrow$  ,  $I_{se} = \downarrow$  ,  $\phi = \downarrow$  ,  $N = \uparrow$

$$N \propto \frac{E_b}{\phi}$$

→ In this method series field winding is shunted by a variable resistance known as field diverter. By adjusting the variable resistance, we can vary the field current. As a result flux changes. We know that flux is inversely proportional to speed ( $\phi \propto \frac{1}{N}$ ). Therefore the speed also changes.


(b) Armature Diverter :-

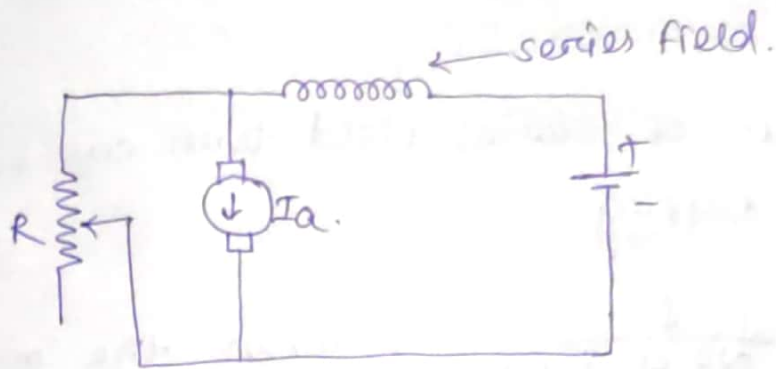

$$I_a \downarrow \quad I_{se} \downarrow \quad \phi \uparrow \quad N \downarrow$$

- (i) A diverter across the armature can be used for giving speed below rated speed.
- (ii) For a given constant load torque, if  $I_a$  reduced due to the armature diverter, the torque decrease for a given constant torque.
- (iii) To maintain constant torque the motor draw more amount of current as a result,  $I_{se}$  increase which increase the flux. Therefore the speed of the motor decrease.

(2) Tapped field Method :-

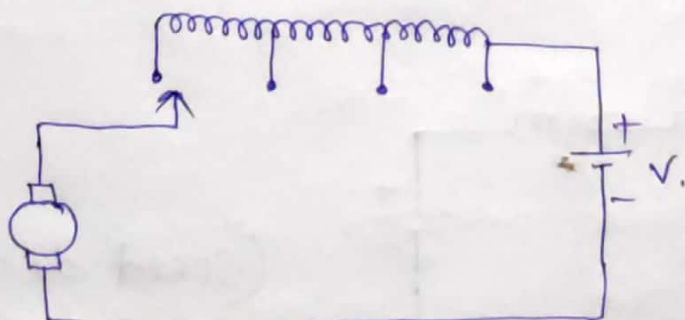




(i) This method is mostly used in electric traction.

(ii) Here number of series field turns can be changed by tapping.

(iii) As,  $f \propto \frac{1}{\text{No. of turns}}$ , when the motor runs with full turns, field flux will be maximum. As a result its speed will be minimum.


(iv) when the no. of turns decreased, flux decreased with increase in speed.

Series-parallel control method.

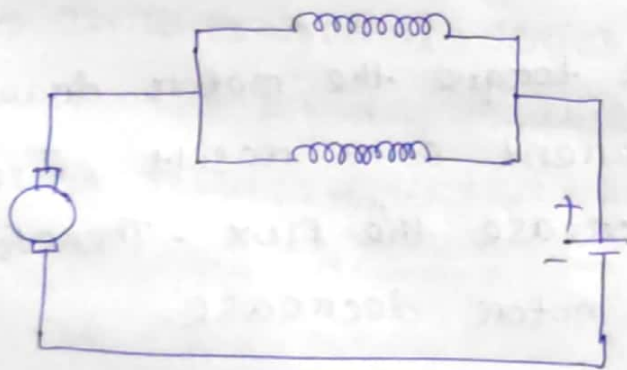

(speed increase).

(Parallel field coil.)

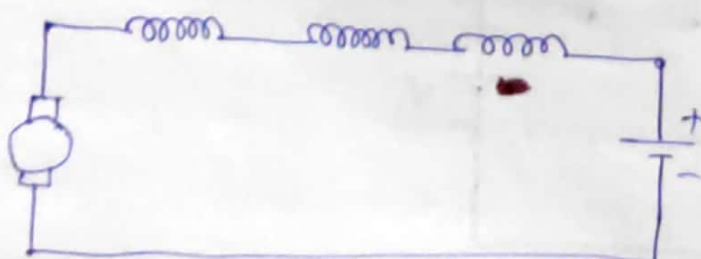

(speed decrease)

(series field coil.)

(i) This system is widely used in electric traction, where two or more mechanically coupled series motors are employed.

(ii) For low speed, the motors are connected in series and for higher speeds, the motors are connected in parallel.


(iii) when in series, the motors have the same current passing through them, although voltage across each motor is divided.

(iv) when in parallel, the voltage across each motor is same although the current gets divided.



## Speed control of DC shunt motor.
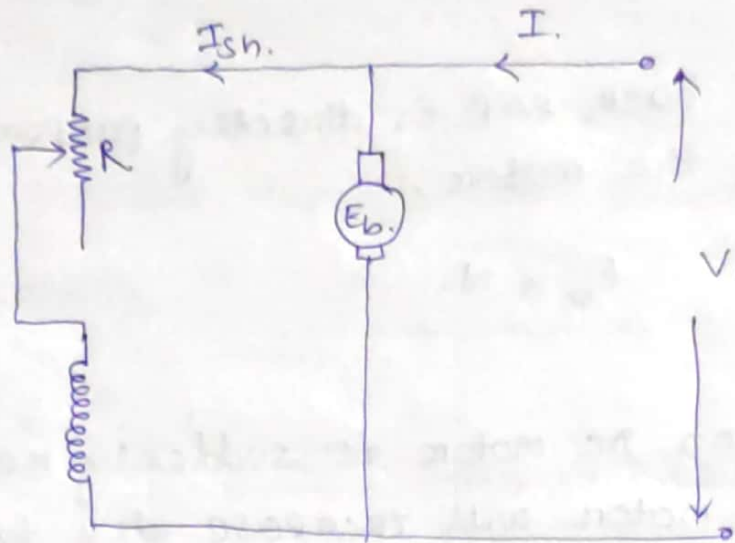
### (1) Variable Flux or Flux control method.



$$R = 0 \quad I_{sh} = \max. \quad N(\text{rated.})$$

$$R = \uparrow \quad I_{sh} = \downarrow \quad \phi = \downarrow \quad N = \uparrow$$

$$R = \uparrow\uparrow \quad I_{sh} = \downarrow\downarrow \quad \phi = \downarrow\downarrow \quad N = \uparrow\uparrow$$

(i) we know that,  $N \propto \frac{1}{\phi}$

By decreasing the field flux speed can be increase or vice versa.

(ii) The Flux of a DC motor can be changed by changing  $I_{sh}$  with the help of a shunt field rheostat.


(iii) when resistance of the field rheostat is increased  $I_{sh}$  decreases. As a result flux

decreases which results in increase of speed.

(iv) In the field control method speed of the motor can be increased above the rated speed. It can't be decreased below rated speed.

(v) As magnitude of  $I_{sh}$  is small power loss in the rheostat ( $I_{sh}^2 R_{sh}$ ) is small. Therefore, this method is very effective.

(a) Armature voltage control Method.

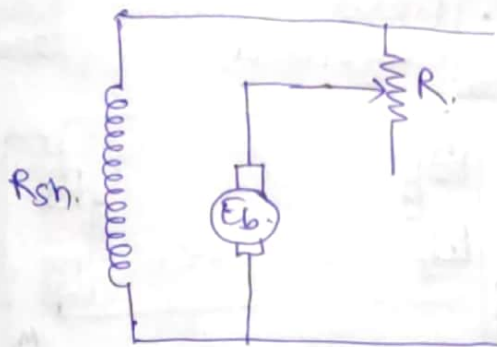

$$N \propto \frac{V - I_a (R_a + R)}{\phi}$$

(i) This method is used to decrease the speed below the rated speed.

(ii) As the supply voltage is constant voltage across the armature can be changed by inserting a rheostat in series with the armature circuit.


(iii) As the variable resistance is increased potential difference across the armature ( $E_b$ ) is decreased. As a result speed of the motor decreases.



(iv) In this method losses will be more because value of  $I_a$  is more as compare to  $I_{sh}$ .

(3) supply voltage control method.

OR. ward Leonard method. :-

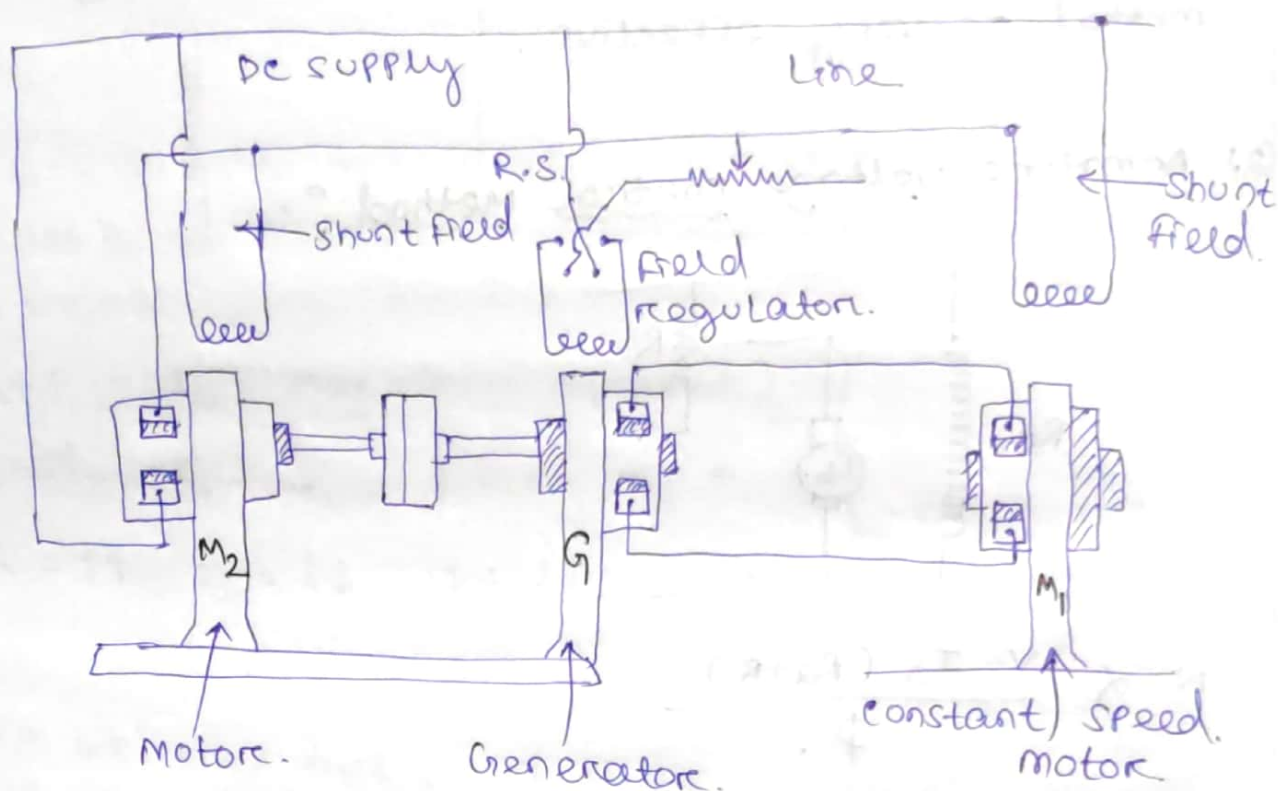

$$N \propto \frac{V - I_a R_a}{\phi}$$

$$N \propto \frac{E_b}{\phi}$$


$$V \uparrow \quad E_b \uparrow \quad N \uparrow$$

$$V \downarrow \quad E_b \downarrow \quad N \downarrow$$

(2) This system is used where a wide and sensitive speed control is required.

- (i) Let  $M_1$  is the main motor whose speed control is required.
- (ii) By changing the supply voltage of  $M_1$ , any desired speed can be obtained.
- (iv) This variable voltage is supplied by a motor generator set which consists of a DC motor  $M_2$  and a DC generator 'G'.
- (v) The motor  $M_2$  runs at approximately constant speed. output of the motor  $M_2$  is given to the generator and output voltage of the generator is directly fed to the main motor  $M_1$ .
- (vi) output voltage of the generator 'G' can be vary from '0' to maximum by using a rheostat.
- (vii) This process of speed control is very expensive and losses will be more.

### Brake test method (Direct method.)

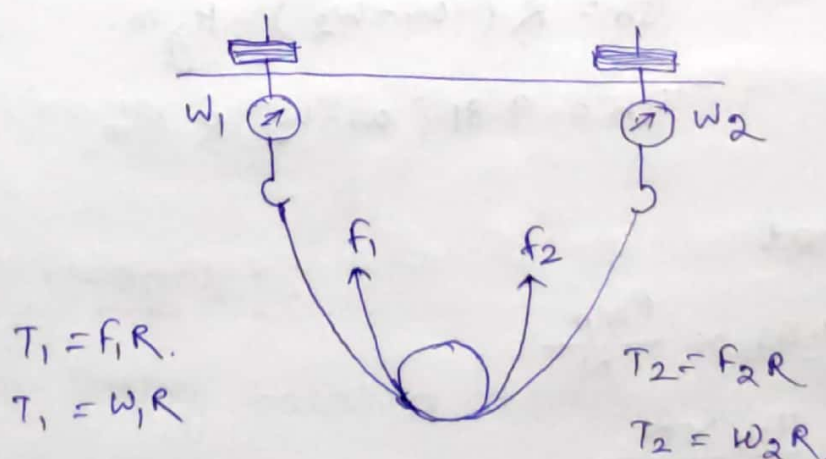



(i) This is the direct method for testing a DC motor from this test we can determine efficiency of a motor.

(ii) A belt is fixed around a pulley and its two ends are attached to the spring balance  $w_1$  and  $w_2$ . The pulley is coupled with shaft of a DC motor.

(iii) using belt tightening hand wheels  $H_1$  and  $H_2$ , load of the motor is adjusted to its rated value.

(iv) Here two forces  $F_1$  and  $F_2$  are acting on the pulley. Torque because of these two forces are opposing each other. Hence the net torque will be subtracting of the two torque.

So,

$$\text{shaft torque} = (T_1 - T_2)$$

$$= (w_1 R - w_2 R)$$

$$T_{sh} = R (w_1 - w_2) \text{ Kg.m.}$$

$$T_{sh} = 9.81 (w_1 - w_2) R \text{ Nm.}$$

we know that

$$T_{sh} = 9.55 \times \frac{P_{o/p}}{N}$$

$$P_{o/p} = \frac{T_{sh} \times N}{9.55}$$

Now, putting the value of  $T_{sh}$  in above equation we get,

$$P_{o/p} = \frac{9.81 (w_1 - w_2) R \times N}{9.55}$$

$$P_{o/p} = 1.02 (w_1 - w_2) NR$$

Input power can be calculated from the formula

$$P_{i/p} = VI$$

The input voltage and current can be measure by using voltmeter and ammeter

Now, we can easily calculate  $\eta$  (efficiency) of the motor.

$$\eta = \frac{P_{o/p}}{P_{i/p}}$$

$$\eta = \frac{1.02 (w_1 - w_2) NR}{VI}$$


( $\eta$  = efficiency.)

Disadvantages :-

- (i) The spring balance reading are not stable.
- (ii) The o/p power is wasted.
- (iii) It can be use for only small motors.



## Swinburnes Test. (Indirect method).

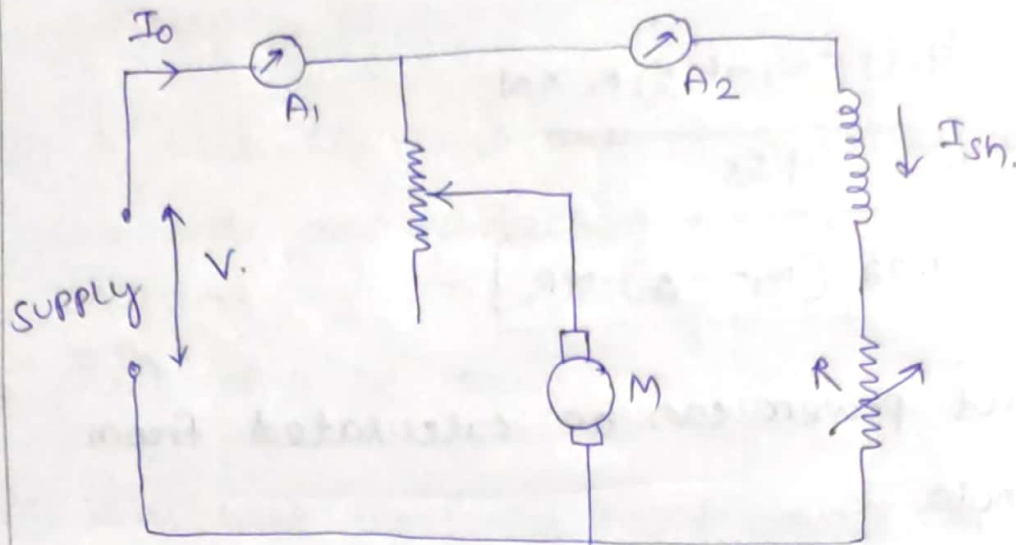

- (i) Swinburnes test is an indirect method for determining the efficiency ( $\eta$ ) of DC machine.
- (ii) In this test no load losses are constant, losses are determined. From these losses we can calculate efficiency of DC motor at any load.
- (iii) Here the machine is run at rated voltage and speed without load.
- (iv) 2 ammeters are connected to measure field current  $I_{sh}$  and total current  $I$ .
- (v) As there is no load.

$$P_{o/p} = 0$$

So,

$$P_{i/p} = \text{Losses.}$$

$$\Rightarrow P_{i/p} = W_{\text{const.}} + \text{Armature copper loss.}$$

$$W_{\text{const.}} = P_{i/p} - \text{Armature copper loss.}$$

constant loss ' $W_c$ ' will be constant for any change in load. only armature copper loss will vary with change in load.

Let, a load is connected to the motor such that it draws  $I_1$  amount of current from the source.

$$\text{Losses} = W_c + (I_1 - I_{sh})^2 R_a$$

$$\eta = \frac{P_{o/p}}{P_{i/p}}$$


$$= \frac{P_{i/p} - \text{Losses}}{P_{i/p}}$$

$$= \frac{V I_1 - W_c + (I_1 - I_{sh})^2 R_a}{V I_1}$$



## Power stages

motor  
i/p  
 $= VI$  Watt

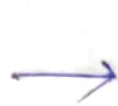

cu.  
Loss




Power  
in armature  
 $= E_b I_a$  Watt

$$0.025 + (-20.0 \times 20.88) + (1.0 \times 20.88) =$$

→ Iron and  
friction loss

→ motor  
output  
in watt

$$\eta_e = \frac{E_b I_a}{VI}$$

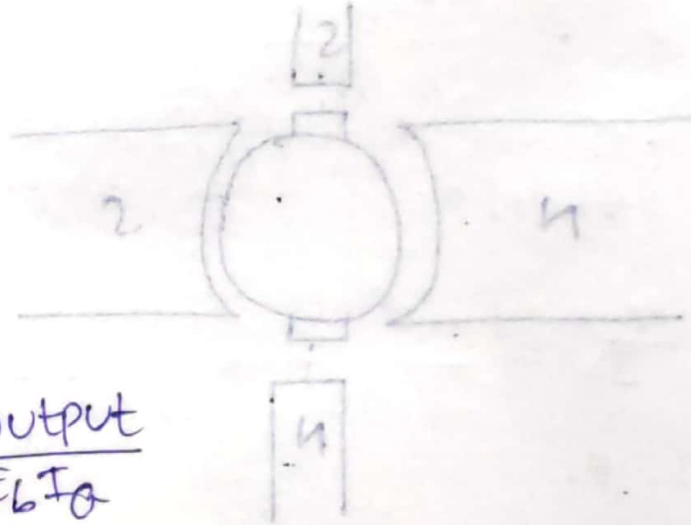

$$\eta_m = \frac{\text{motor output}}{E_b I_a}$$

$$\eta_o = \frac{\text{motor output}}{\text{motor input}(VI)}$$

2) A 220V DC shunt motor has an armature resistance of  $0.73 \Omega$ , shunt field resistance of  $110 \Omega$  and no load the speed is 1200 rpm and armature current is 2.4A. on rated load the speed drops to 1100 rpm. determine the line current and input power, when the motor delivers rated load.

Given data :-

$$V = 220$$

$$R_a = 0.73 \Omega$$

$$R_{sh} = 110 \Omega$$

$$\text{at no load } N = 1200 \text{ rpm}$$

$$I_a = 2.4 \text{ A}$$

$$\text{at load } N = 1100 \text{ rpm}$$

$$I = ?$$


$$\text{i/p power} = ?$$

$$I_{sh} = \frac{V}{R_{sh}}$$

$$= \frac{220}{110}$$

$$= 2 \text{ A}$$
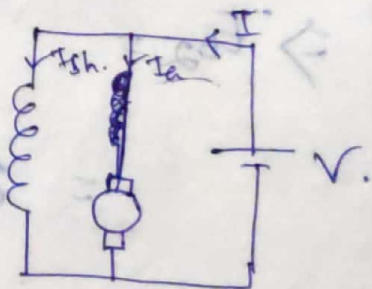
$$I = I_a + I_{sh} = 2 + 2.4 = 4.4 \text{ A}$$





Q.20

$$E_{b1} = V - I_a R_a$$

$$= 220 - (2.4 \times 0.73)$$

$$= 218.248 \text{ V.}$$

$$E_{b1} \propto N_1 \text{ --- ①}$$

$$E_{b2} \propto N_2 \text{ --- ②}$$


$$E_{b1} = K N_1$$

$$E_{b2} = K N_2$$

$$\Rightarrow \frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2}$$

$$\Rightarrow \frac{218.248}{E_{b2}} = \frac{1200}{1100}$$
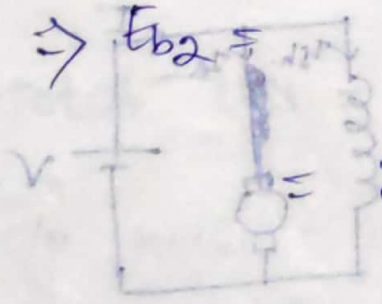
$$\Rightarrow E_{b2} = \frac{218.248 \times 1100}{1200}$$



$$= 200.06 \text{ V.}$$

$$E_{b2} = V - I_a R_a$$

$$\Rightarrow 200.06 = 220 - I_a (0.73)$$

$$\Rightarrow I_a = \frac{220 - 200.06}{0.73} = 27.31 \text{ A.}$$

$$I_L = I_a + I_{sh}$$

$$= 27.31 + 2$$

$$= 29.31 \text{ A}$$

$$\text{i/p power} = V \times I_L$$

$$= 220 \times 29.31$$

$$= 6448.2 \text{ watt}$$

$$= 6.448 \text{ kW}$$



Q. The speed of a 37.3 kW series motor working on 500 V supply is 750 rpm at full load and 90% efficiency. If the load torque is made 350 N-m and a  $5\Omega$  resistance is connected in series with the machine, calculate the speed at which the machine will run. Assume the magnetic ckt to be unsaturated and the armature and field resistance which is  $0.5\Omega$ .

Given data

$$R_a + R_{se} = 0.5\Omega$$

$$\text{o/p } P = 37.3 \text{ kW} = 37.3 \times 10^3 \text{ W}$$

$$N_1 = 750 \text{ rpm}$$

$$\text{efficiency } (\eta) = 90\% = 0.90$$

$$T_{sh_2} = 350 \text{ N-m}$$


$$R = 5\Omega$$

$$V = 500 \text{ V}$$

$$T_{sh_1} = 9.55 \times \frac{\text{o/p Power}}{N}$$

$$= 9.55 \times \frac{37.3 \times 10^3}{750}$$

$$= 474.95 \text{ N-m}$$

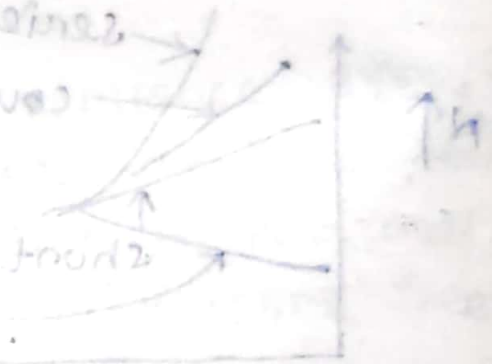

$$\eta = \frac{o/p}{i/p}$$

$$\Rightarrow i/p = \frac{37.3 \times 10^3}{0.90}$$

$$\Rightarrow i/p = 41444.44 \text{ watt}$$

$$= 41.44 \text{ kW.}$$

$$\text{Input power} = V \cdot I_a$$

$$\Rightarrow 41444.44 = 500 \times I_a$$

$$\Rightarrow I_a = 82.88 \text{ A.}$$

$$T_{sh} \propto I_a^2$$

$$\left[ T_a \propto I_a^2 \text{ for series motor} \right]$$

$$\Rightarrow \frac{T_{sh1}}{T_{sh2}} = \frac{I_{a1}^2}{I_{a2}^2}$$

$$\Rightarrow \frac{474.95}{350} = \frac{82.88^2}{I_{a2}^2}$$

$$\Rightarrow I_{a2}^2 = \frac{82.88^2 \times 350}{474.95}$$

$$\Rightarrow I_{a2} = \sqrt{\frac{82.88^2 \times 350}{474.95}}$$

$$\frac{88.68 \times 22.82}{11.15 \times 22.82} = \frac{71.14 \times 22.82}{22.82}$$



(1) A 400 V series motor runs at 500 rpm, taking a current of 40 A. Calculate the speed and percentage change in torque if the load is reduced, the motor is taking 30 A. Total resistance of armature and field is  $0.8 \Omega$ .

Given data: -

$$V = 400 \text{ V.}$$

$$N_1 = 500 \text{ rpm.}$$

$$I_{a1} = 40 \text{ A.}$$

$$I_{a2} = 30 \text{ A.}$$

$$R_a + R_{se} = 0.8 \Omega$$

$$E_{b1} = V - I_{a1} (R_a + R_{se})$$

$$\Rightarrow E_{b1} = 400 - 40(0.8)$$

$$\Rightarrow E_{b1} = 368 \text{ V.}$$

$$E_{b2} = V - I_{a2} (0.8)$$

$$= 400 - 30(0.8)$$

$$= 376 \text{ V.}$$

$$\frac{E_{b1}}{E_{b2}} = \frac{N_1 I_{a1}}{N_2 I_{a2}}$$

$$\Rightarrow \frac{368}{376} = \frac{500 \times 40}{N_2 \times 30}$$

$$\Rightarrow N_2 = \frac{500 \times 376 \times 40}{368 \times 30}$$

$$\Rightarrow N_2 = 510.86 \text{ rpm,}$$

$$\Rightarrow N_2 = 681.15 \text{ rpm,}$$

$$T_{a1} = \frac{E_{b1} I_{a1} (9.55)}{2\pi N_1}$$

$$= \frac{368 \times 40 (9.55)}{500}$$

$$= 281.152 \text{ N-m.}$$



$$\frac{T_{a1}}{T_{a2}} = \frac{I_{a1}^2}{I_{a2}^2}$$

$$\Rightarrow \frac{281.152}{T_{a2}} = \frac{(40)^2}{30^2}$$

$$\Rightarrow T_{a2} = \frac{281.152 \times 30^2}{40^2}$$

$$\Rightarrow T_{a2} = 158.14 \text{ N-m.}$$

$$\begin{aligned} \text{change in torque} &= T_{a1} - T_{a2} \\ &= 281.152 - 158.14 \\ &= 123.012 \end{aligned}$$

$$\begin{aligned} \% \text{ of change in torque} &= \frac{123.012}{281.152} \times 100 \\ &= 43.75 \% \end{aligned}$$

$$I_a = I_o - I_{sh}$$

$$\text{i/p power} = VI_o$$

$$\text{Armature i/p power} = VI_a$$

$$\begin{aligned} \text{Total Losses} &= \text{i/p power} \\ &= VI_o \end{aligned}$$

$$\begin{aligned} \eta &= \frac{\text{i/p} - \text{losses}}{\text{i/p}} \\ &= \frac{VI - (I_o - I_{sh})^2 R_a - W_c}{VI} \end{aligned}$$

$$\begin{aligned} \text{Total Losses} &= W_c + \text{Armature copper loss} \\ &= W_c + I_a^2 R_a \end{aligned}$$

$$\Rightarrow \boxed{W_c = \text{Total Loss} - I_a^2 R_a}$$

Let, load is connected,  $I$  current flow

$$\text{i/p} = VI$$

$$\text{Losses} = W_c + I_a^2 R_a$$

$$\boxed{\eta = \frac{\text{i/p} - \text{loss}}{\text{i/p}}}$$



## Application of DC shunt motor :-

The various applications of DC shunt motor are in.

- (i) lathe machines.
- (ii) centrifugal pumps.
- (iii) Fans.
- (iv) Blowers.
- (v) conveyors.
- (vi) Lifts.
- (vii) weaving machine.
- (viii) Spinning machines, etc.
- (ix) Shapers.
- (x) Elevators.
- (xi) Rolling mills.
- (xii) Heavy presses.

→ The shunt motors are used where constant speed is required.

## Application of series motor :-

- (i) Traction system. <sup>Trains, Trolleys</sup>
- (ii) cranes.
- (iii) air compressors.
- (iv) vacuum cleaner
- (v) Hair dryer

→ The series DC motors are used where high starting torque is required and variation in speed are possible.

## Application of compound motor :-

- (i) presses.
- (ii) Shears.
- (iii) Elevators.
- (iv) Rolling mills
- (v) Heavy planners.

→ The compound motors are used where higher starting torque and fairly constant speed is required.


## Application of separately excited DC motor :-

→ By separately varying the field current variable speed can be achieved. So due to this reason this type motor are used.



## Chapter-3 Single phase Transformer.

### Single Phase Transformer

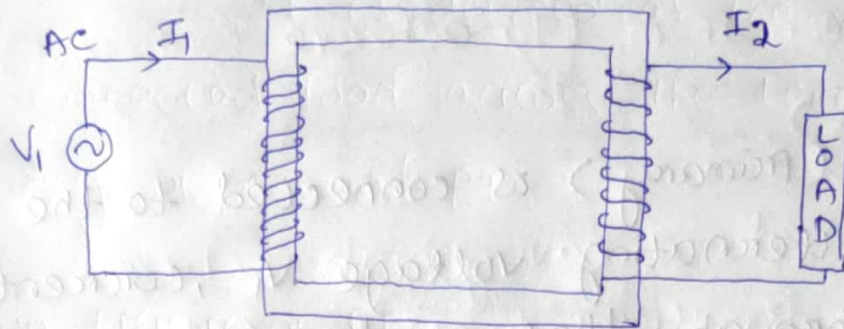

(i) It is a device which transform voltage from one level to another at constant frequency and constant power, through mutual induction process.

Q (ii) Transformer is a static device that transfer electric power from one ckt to another with same frequency through the process of mutual induction.

(iii) It is most commonly used to increase and decrease the voltage level between the circuits.

### Working Principle of Transformer :-

(i) The basic working principle of transformer is mutual induction between two ckt linked by a common magnetic field.

(ii) Let two inductive coils which are electrically

separated but magnetically linked through the path of low reluctance that is transformer core as shown in the above figure.

(iii) If one coil (Primary) is connected to the source of alternating voltage  $V_1$ , current  $I_1$  flows through that winding. As a result alternating flux is set up in the laminated core.


(iv) This alternating flux linked with the coil and according to Faraday's law of electromagnetic induction emf is induced in both coils. ( $E_1$  in the primary coil and  $E_2$  in the secondary coil).

(v) when the secondary coil is connected to a load current  $I_2$  will start to flow to the load and power will transfer to it. voltage drop across the load is  $V_2$ .

(vi) The induced voltage ( $E_2$ ) in the secondary coil will depend upon the no. of turns.



## Basic construction of Transformer.

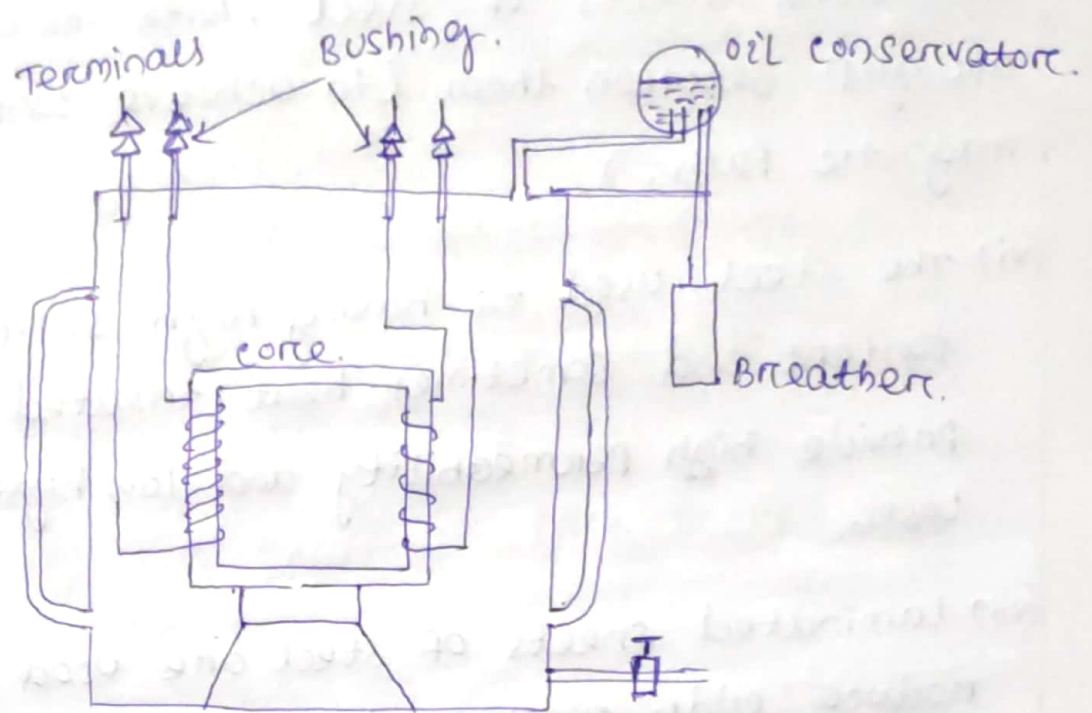

(Transformer.)

- (i) Basically a transformer consists of two inductive winding and a laminated steel core.
- (ii) The coils are insulated from each other as well as from the steel core.
- (iii) A Transformer may also consist of a container for winding and core assembly (called as tank) suitable bushing to take out the terminals.
- (iv) oil conservator to provide oil in the transformer tank for cooling purpose etc.
- (v) The figure shows the basic construction of

a transformer. In all types of transformers core is constructed by assembling (stacking) laminated sheets of steel, with minimum air gap between them (to achieve continuous magnetic path).

(vi) The steel used is having high silicon content and sometimes heat treated, to provide high permeability and low hysteresis loss.

(vii) Laminated sheets of steel are used to reduce eddy current loss. The sheets are cut in the shape as 'E', 'I' and 'L' to avoid high reluctance at joints.

Main Parts of transformer :-

- (1) Laminated Iron core,
- (2) winding of the Transformer,
- (3) Insulating material.
- (4) Tap changer.
- (5) Transformer tank.
- (6) oil conservator tank.
- (7) Breather
- (8) Buchholz Relay
- (9) Bushing.



- (10) cooling tube and radiator
- (11) explosion vent.

### 1. Laminated iron core :-

- (i) Transformer core is made up of iron or silicon steel or ferromagnetic material.
- (ii) core provides support's to the winding. It also provide a low reluctance path to the magnetic flux to flow.

### (a) winding of the transformer :-

- (i) Two sets of winding are wound over the transformer core and insulated from each other.
- (ii) According to the connection of source and load it is classified into two types.

#### ① Primary winding :-

This type of winding to which source is connected.

#### ② secondary winding :-

This is the winding to which load is connected.

→ According to the voltage level winding is classified into two types.

① High voltage winding (H.V).

In this winding magnitude of the induced emf is high.

② Low voltage winding (L.V). :-

In this winding magnitude of the induced emf is less.

3. Insulating material :-

(i) Insulating papers, cardboard are used in the transformer to isolate the primary and secondary winding from each other and from the transformer core.

(ii) Transformer oil is used in transformer to provide insulation and cooling to the core and coil assembly.

(iii) The transformer core and winding must be completely immersed in the oil.

Normally hydrocarbon mineral oil is used as transformer oil.



#### 4. Tap changer :-

- (i) Tap changers are used to change the output voltage by increasing or decreasing no. of turns in the high voltage side.
- (ii) There are 2 types of tap changer.

##### ① off-load Tap changer :-

Tap changing is done when the transformer is disconnected from both source and load.

##### ② ON load Tap changer :-

Here tap changing is done when the transformer is connected to both source and load.

#### 5. Transformer tank :-

- (i) laminated core and windings are placed in transformer tanks.
- (ii)  $\frac{3}{4}$ th part of the transformer tank is filled with transformer oil (mineral oil).
- (iii) Transformer tank is made up of cast steel.

## 6. Oil conservatore tank :-

- (i) The oil conservatore tank look like a rectangular tank. It stores the extra oil and directly connected with the transformer tank.
- (ii) The oil conservatore tank is played an important role in the transformer.
- (iii) The purpose of the conservatore tank is to protect the expansion of oil in the main tank of the transformer.
- (iv) The oil used in the transformer two purposes.
  - ① insulation,
  - ② cooling.
- (v) when the oil level reduces due to losses or leakage, the conservatore will be delivering oil to the transformer. Thus it acts as a reservoir oil.

## 7. Breathere :-

- (i) Breathere is connected with the conservatore tank.
- (ii) It is a cylindrical vessel which filled



blue coloured silica gel.

- (i) They have two purposes - remove the moisture from the air and to have the capacity to absorb the moisture in a transformer.
- (ii) It plays a role to act as the air filter and provide the free moisturizing air to the conservator tank.
- (iv) Initially the colour of silica gel is blue. When the silica gel soaks a lot of moisture it turns to pink. Once the silica gel turns pink it can not absorb more moisture.

#### 8. Buchholz's Relay :-

- (i) It is a protective device placed on the connecting pipe from main tank to conservator tank.
- (ii) It senses the fault which occurs in the transformer.

#### 9. Bushing :-

- (i) The bushing is an insulating device that is made up of porcelain materials.
- (ii) The terminal of the bushing is provided a path of the conductors to the transformer tank.

(iii) with the help of the terminal, the transformer gives and provides the supply to another system.

#### 10. cooling Tube and Radiator :-

(i) The cooling tube is necessary for maintaining the temperature and circulating cooling oil in the transformer.

(ii) The radiator is connected with the transformer tank. It is also made of a number of metal strips or pipes.

(iii) Both the cooling tube and the radiator provide the same function in a different way.

(iv) It is divided into two types of cooling system

① Natural cooling system.

② forced cooling system.

#### (ii) Explosion vent :-

(i) The explosion vent is located at the top-most position on the transformer. The conservator tank is directly connected to the explosion tank with the help of a pipe.



- (ii) The main purpose to prevent damage transformer oil tank by expelling boiling oil during an internal fault. and it is necessary to remove heated oil (in the form of gas). in the transformer.
- (iii) This explosion tank use only for emergency purpose. It mostly works when a breather and Buchholz relay will not doing work properly.

### Classification of Transformer :-

(i) According to phase, T/F are two types.

- ① Single phase Transformer.
- ② Three phase Transformer.

(ii) According to voltage level it is 2 types.

- ① Step up transformer.
- ② Step down transformer.

(iii) According to use, it is 3 types.

- ① Power Transformer (used in transmission line).
- ② Distribution Transformer (used in distribution line).
- ③ Instrument T/F (used to measure 'V' and 'I')

(iv) According to construction it is divided into 3 types.

① core type.

② shell type.

③ Berry type.

cooling methods of A Transformer :-

Different cooling methods of transformers are

① For dry type transformers.

① Air Natural.

② Air Blast.

② For oil immersed transformers

① oil Natural Air Natural.

② oil Natural Air forced.

③ oil forced Air forced.

④ oil forced water forced.

Air Natural or Self Air cooled transformer :-

This method of transformer cooling is generally used in small transformers

(upto 3 MVA). In this method the transformer is allowed to cool by natural air



flow surrounding it.

### Air Blast cooling :-

- (i) For transformers rated more than 3 MVA, cooling by natural air method is inadequate.
- (ii) In this method, air <sup>is</sup> forced on the core and windings with the help of fans or blowers.
- (iii) The air supply must be filtered to prevent the accumulation of dust particles in ventilation ducts. This method can be used for transformers up to 15 MVA.

### Oil Natural Air Natural :-

- (i) This method is used for oil immersed transformer.
- (ii) In this method, the heat generated in the core and winding is transferred to the oil.
- (iii) According to the principle of convection, the heated oil flows in the upward direction and then in the radiator.
- (iv) The vacant place is filled up by cooled oil from the radiator. The heat from the oil will dissipate in the atmosphere due to the natural air flow around the transformer.

(v) In this way, the oil in transformer keeps circulating due to natural convection and dissipating heat in atmosphere due to natural conduction.

(vi) This method can be used for transformers up to about 30 MVA.

### Oil Natural Air Forced (ONAN) :-

(i) The heat dissipation can be improved further by applying forced air on the dissipating surface.

(ii) Forced air provides faster heat dissipation than natural air flow.

(iii) In this method, fans are mounted near the radiator and may be provided with an automatic starting arrangement, which turns on when temperature increases beyond certain value. This transformer cooling method is generally used for large transformers up to about 60 MVA.

### Oil Forced Air Forced (OFAF) :-

(i) In this method, oil is circulated with the help of pump.



(i) The oil circulation is forced through the heat exchangers. Then compressed air is forced to flow on the heat exchanger with the help of fans.

(ii) The heat exchangers may be mounted separately from the transformer tank and connected through pipes at top and bottom.

(iv) This type of cooling is provided for higher rating transformers at substation or power station.

oil forced water forced :-

(i) This method is similar to OFAF method, but here forced water flow is used to dissipate heat from the heat exchangers.

(ii) The oil is forced to flow through the heat exchanger with the help of a pump, where the heat is dissipated in the water which is also forced to flow.

(iii) The heated water is taken away to cool in separate coolers. This type of cooling is used in very large transformers having rating of several hundreds MVA.

## Maintenance of Transformer :-

A power transformer is most costly and essential equipment of an electrical transformer. So for getting high performance and long functional life of the transformer, it is desired to perform various maintenance activities.

### Monthly Basis maintenance of transformer :-

- (i) The oil level in oil cap under silica gel breather must be checked in one month interval. If it is found the transformer oil inside the cup comes below the specific level, oil to be top up as per specified level.
- (ii) Breathing holes in silica gel breather should be checked monthly and properly cleaned if required, for proper breathing action.

### Daily Basis maintenance and checking :-

- (i) Reading of MOG (magnetic oil gauge) of main tank and conservator tank.
- (ii) colour of silica gel in breather.



(iii) leakage of oil from any point of a transformer.

### Yearly Basis Transformer Maintenance Schedule


- (i) The auto, remote, manual function of cooling system that means, oil pumps, air fans and other items engaged in cooling system of transformer, along with their control ckt to be checked in the interval of one year.
- (ii) All the bushings of the transformer to be cleaned by soft cotton cloths yearly.
- (iii) Mechanical inspection of Buchholz relays to be carried out on yearly basis.
- (iv) All the relay, alarms and control switches along with their ckt, in R and C panel (Relay and control panel), and RTCC (Remote Tap changer control panel) to be cleaned by appropriate cleaning agent.
- (v) Insulation resistance and polarization index of transformer must be checked with battery operated megger of 5KV range.
- (vi) Resistive value of earth connection and rizer must be measured annually with clamp on earth resistance meter.

### Half yearly Basis maintenance of transformer

- (i) The transformer oil must be checked half yearly basis that means once in 6 month, for dielectric strength, water content, acidity, sludge content, Flash point, resistivity for transformer oil.



## ✓ EMF equation of a transformer:

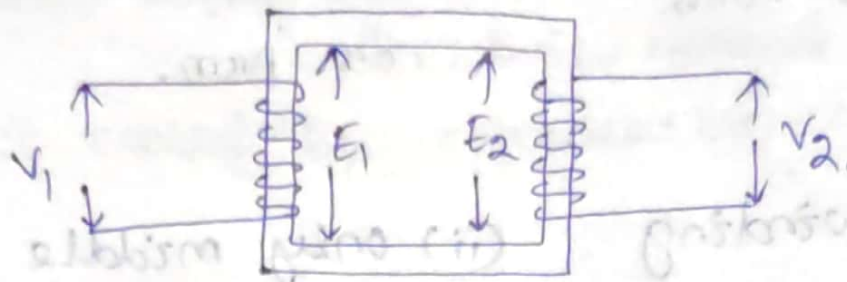


Let,

$N_1$  = No. of turns in primary

$N_2$  = No. of turns in secondary

$\phi_m$  = maximum flux in core

$f$  = frequency of AC input in Hz.

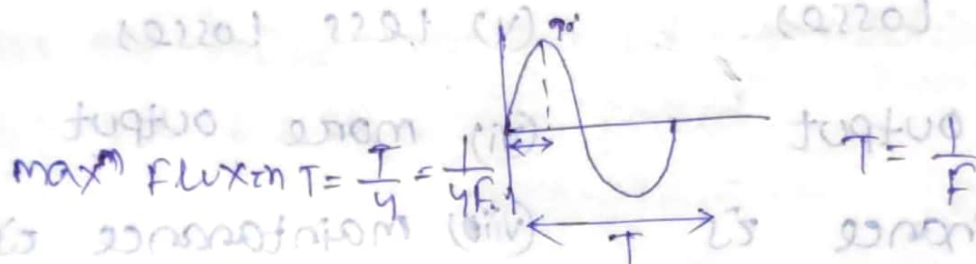

Flux increases from its zero value to maximum value in one quarter of cycle i.e.  $\frac{1}{4f}$  second.

So the average rate of change of flux

$$\text{Avg emf/turn} = \frac{\phi_m}{\frac{1}{4f}} = 4f\phi_m \text{ Volt}$$

→ If flux  $\phi$  vary sinusoidally then rms value of induced emf is obtained by multiplying the average value with form factor.

→ rms value of emf per turn =  $1.11 \times 4 f \phi_m$  volt  
 $= 4.44 f \phi_m$  volt.


Now rms value of induced emf in whole primary winding is = induced emf per turn  $\times$  no. of primary turns.

$$\boxed{E_1 = 4.44 f \phi_m \times N_1} \text{ volt} \quad \text{--- ①}$$

Similarly rms value of emf induced in ( $E_2$ ) =  $4.44 f \phi_m \times N_2$  volt secondary

$$\Rightarrow \boxed{E_2 = 4.44 f \phi_m \times N_2} \text{ --- ②}$$

Ideal Transformer:

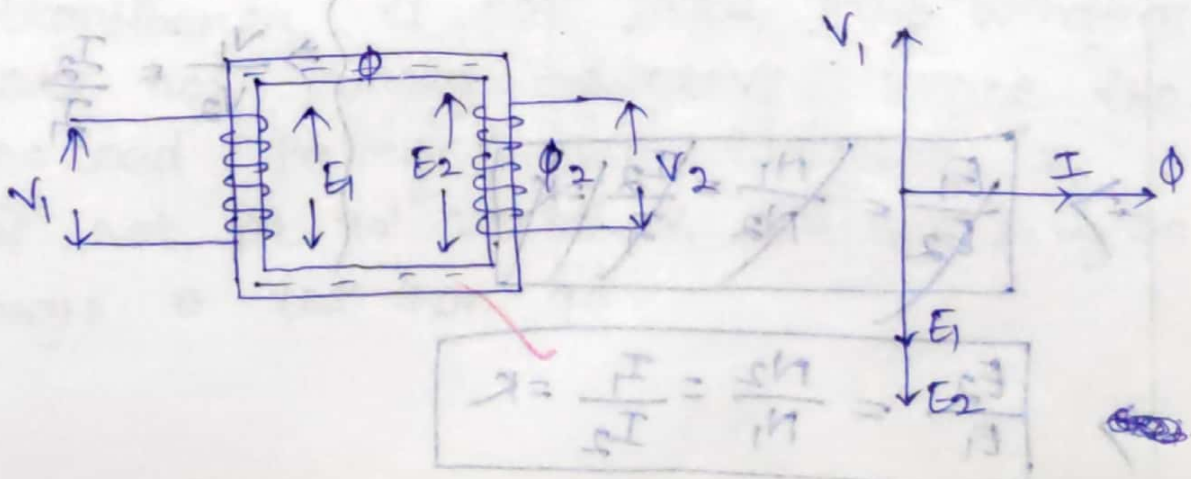



(i) An ideal t/f is one which has no losses. i.e. it's winding have no ohmic resistance.

(ii) In other words an ideal transformer consists of two purely inductive coils wound on a loss free core.

Voltage Transformation ratio (K) :-

$$E_1 = 4.44 \phi_m f N_1 \quad \text{--- (1)}$$

$$E_2 = 4.44 \phi_m f N_2 \quad \text{--- (2)}$$

$$\frac{E_1}{N_1} = 4.44 \phi_m f, \quad \frac{E_2}{N_2} = 4.44 \phi_m f.$$

$$\frac{E_1}{N_1} = \frac{E_2}{N_2} = 4.44 \phi_m f = K$$

$$\Rightarrow \frac{E_1}{E_2} = \frac{N_1}{N_2} = K$$

$$\frac{E_2}{E_1} = \frac{N_2}{N_1} = K$$

eq 2  
eq 1



$$V_1 I_1 = V_2 I_2$$

$$\Rightarrow \frac{V_1}{V_2} = \frac{I_2}{I_1}$$

$$\frac{E_1}{E_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1} = K$$

$$\Rightarrow \frac{E_2}{E_1} = \frac{N_2}{N_1} = \frac{I_1}{I_2} = K$$

## Transformer on No-load :-

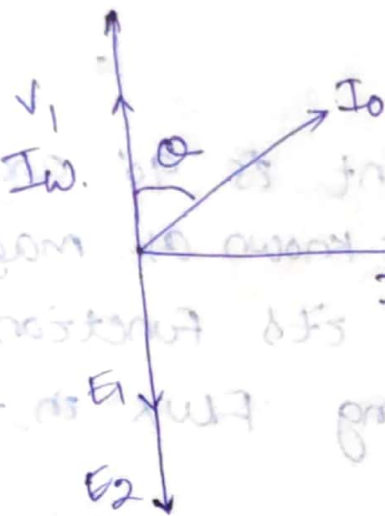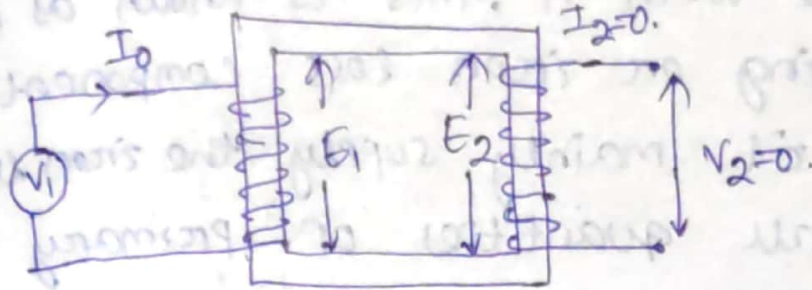

(i) In ideal transformer there are no ~~core~~ core losses and copper losses, so the windings are purely inductive in nature, and primary current lags behind the supply voltage by  $90^\circ$ . But when the transformer is not ideal, the windings are not purely inductive. Hence the no load primary i/p current ' $I_0$ ' is not at  $90^\circ$  behind  $V_1$  but lags it by an angle  $\theta$  less than  $90^\circ$ .



(ii) The primary current  $I_0$  has two components

- (1)  $I_w$  in phase with  $V_1$ , this is known as active or working or iron loss component.  $I_w$  because it mainly supply the iron loss plus small quantities of primary copper loss.


$$I_w = I_0 \cos \theta$$

- (2) The other component is  $90^\circ$  angle with  $V_1$  (lagging). It is known as magnetising component. because its function is to maintain alternating flux in the core.


$$I_m = I_0 \sin \theta$$

on no load transformer the core loss and copper loss are negligible. The primary current  $I_0$  is the sum of the working component  $I_w$  and the magnetising component  $I_m$ .

Transformer on load :-

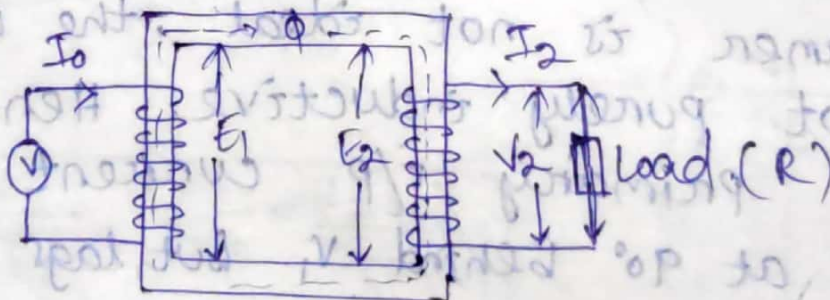

2. Construction of phasor diagram

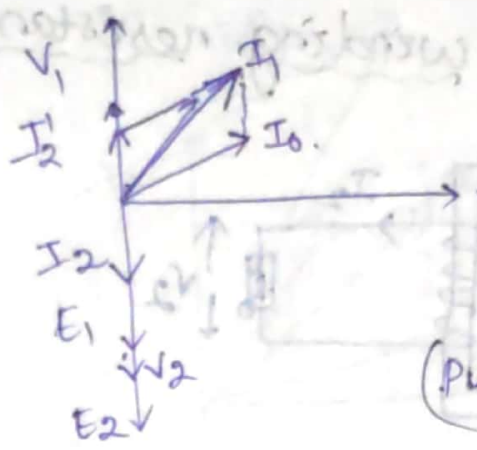

$$\phi = \phi_m \sin \omega t$$

$$e = \frac{d\phi}{dt} = \frac{d}{dt} \phi_m \sin \omega t$$

$$= -\phi_m \omega \cos \omega t$$


$$= \phi_m \omega (-\cos \omega t)$$

$$= \phi_m \omega \sin(\omega t - 90^\circ)$$

(Purely resistive load)



$$V_1 = I_1 R_1 + E_1$$

$$E_1 = -I_1 R_1 + V_1$$

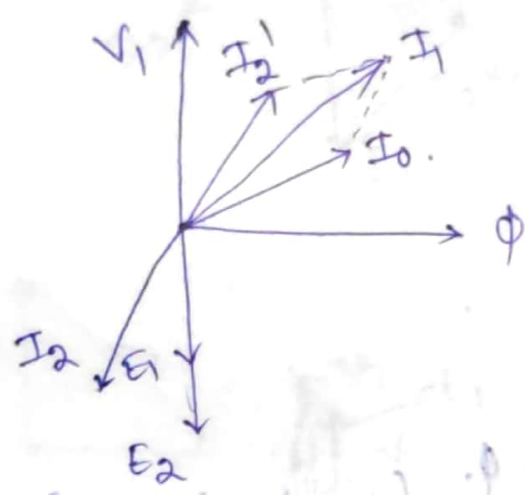

(Load is inductive)


(Inductive load)

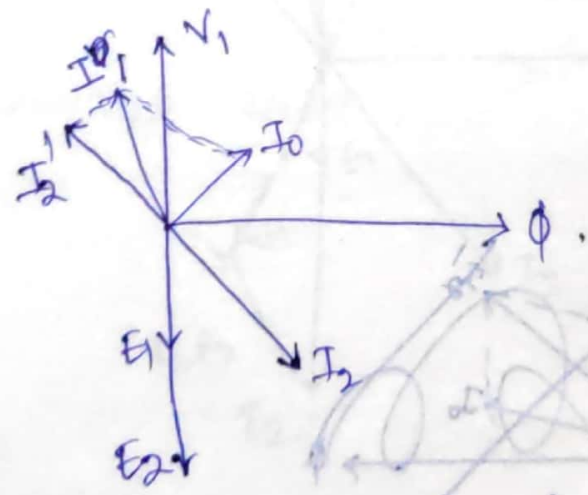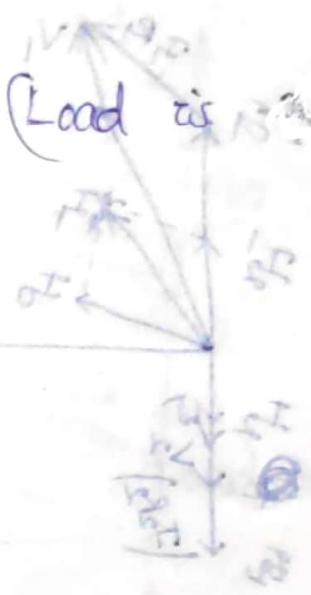

(Load is capacitive)





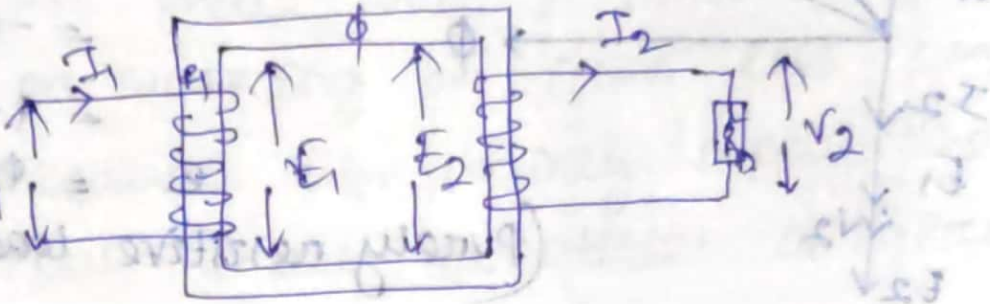
## Transformer with winding resistance :-



$$E_1 = V_1 - I_1 R_1$$


$$E_2 = V_2 + I_2 R_2$$

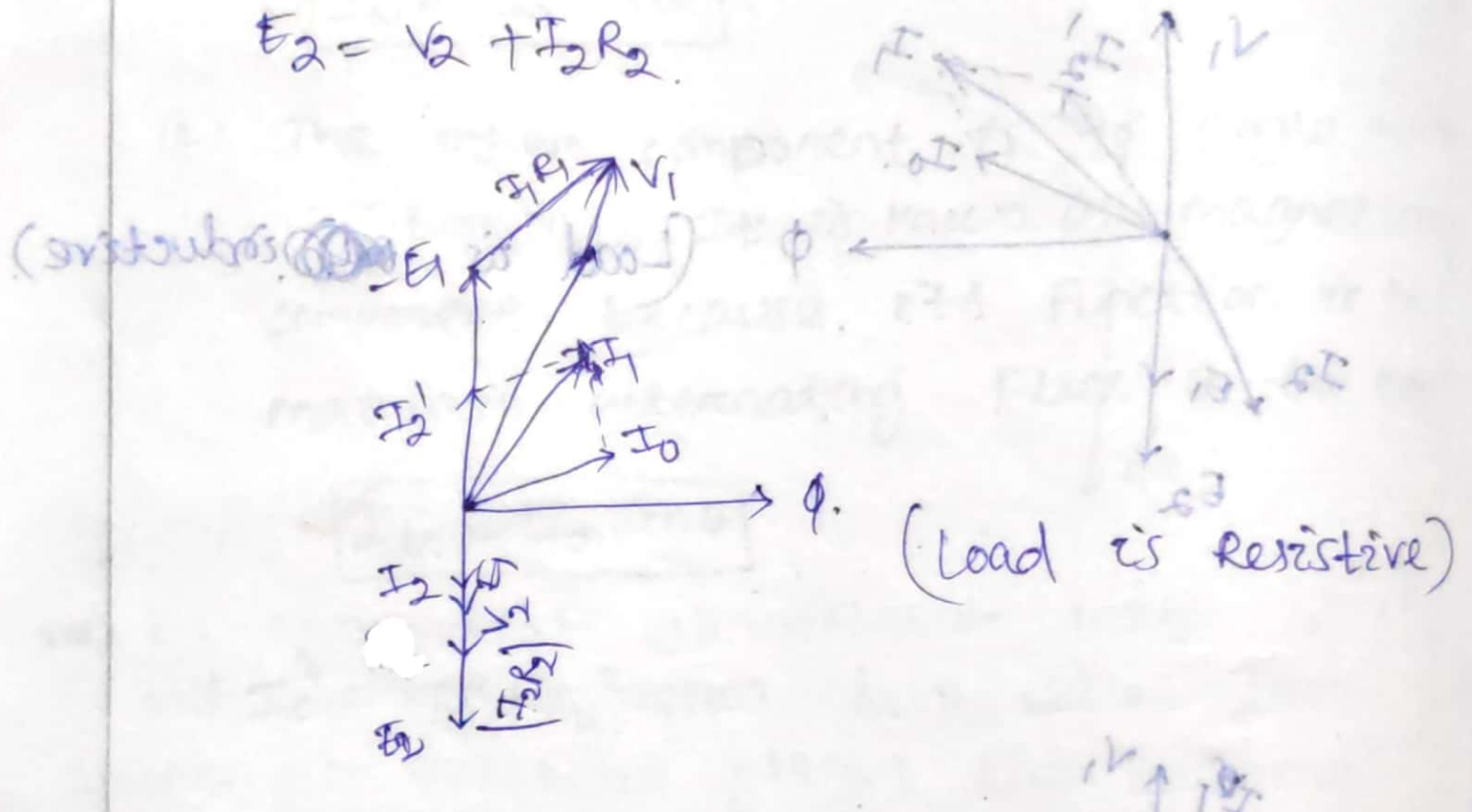

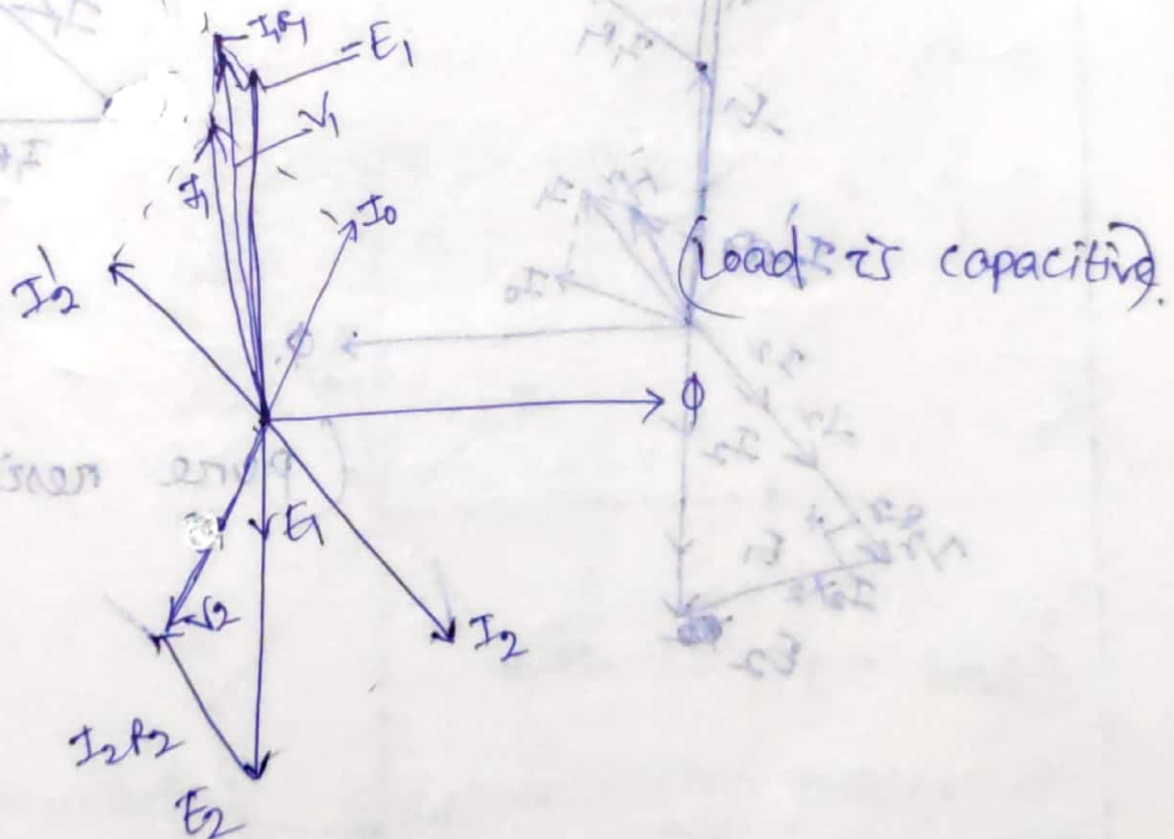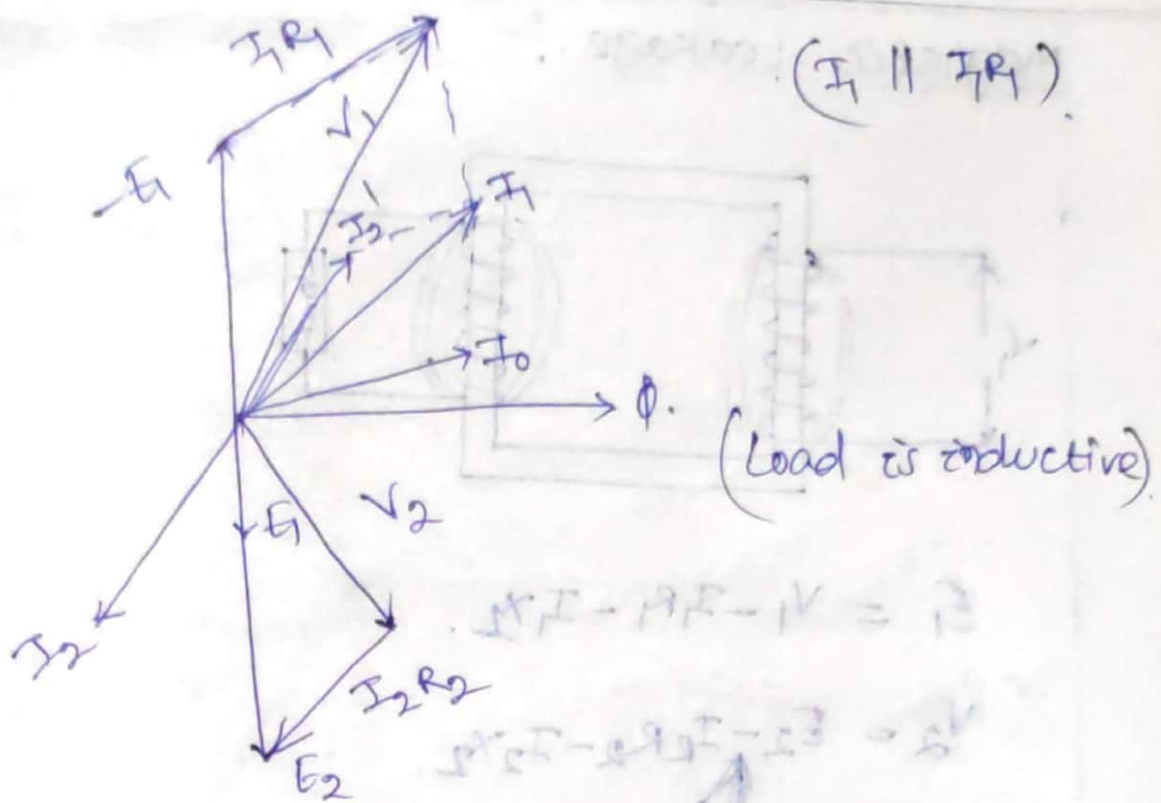





# Magnetic Leakage :-

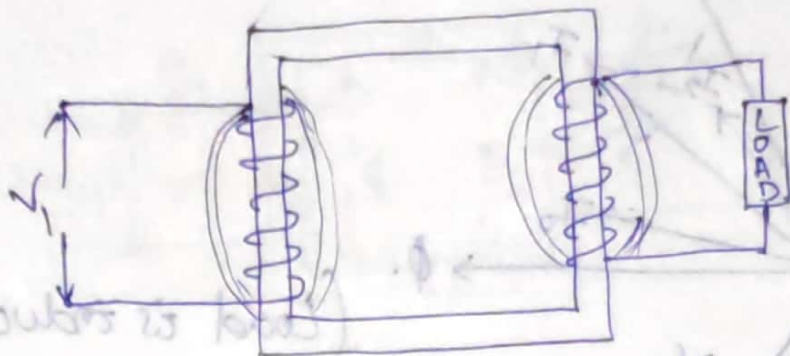


$$E_1 = V_1 - I_1 R_1 - I_1 X_1$$

$$V_2 = E_2 - I_2 R_2 - I_2 X_2$$

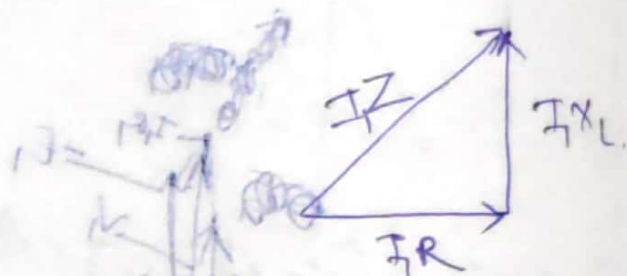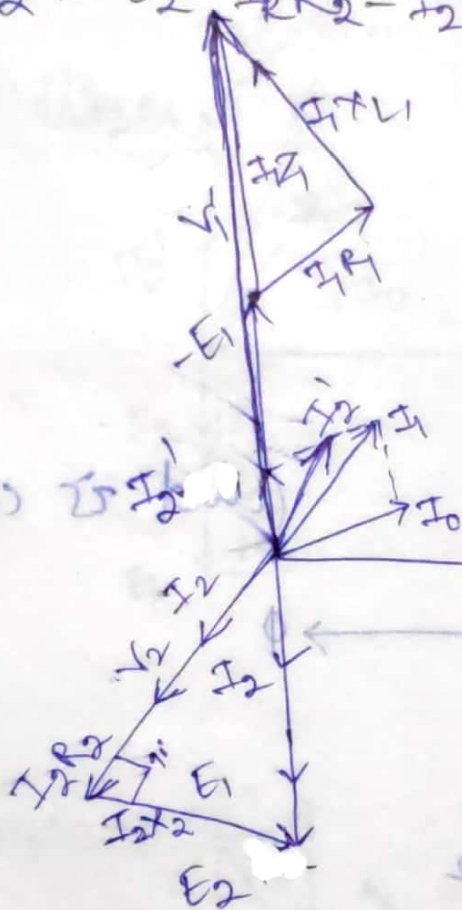

(pure resistive load)

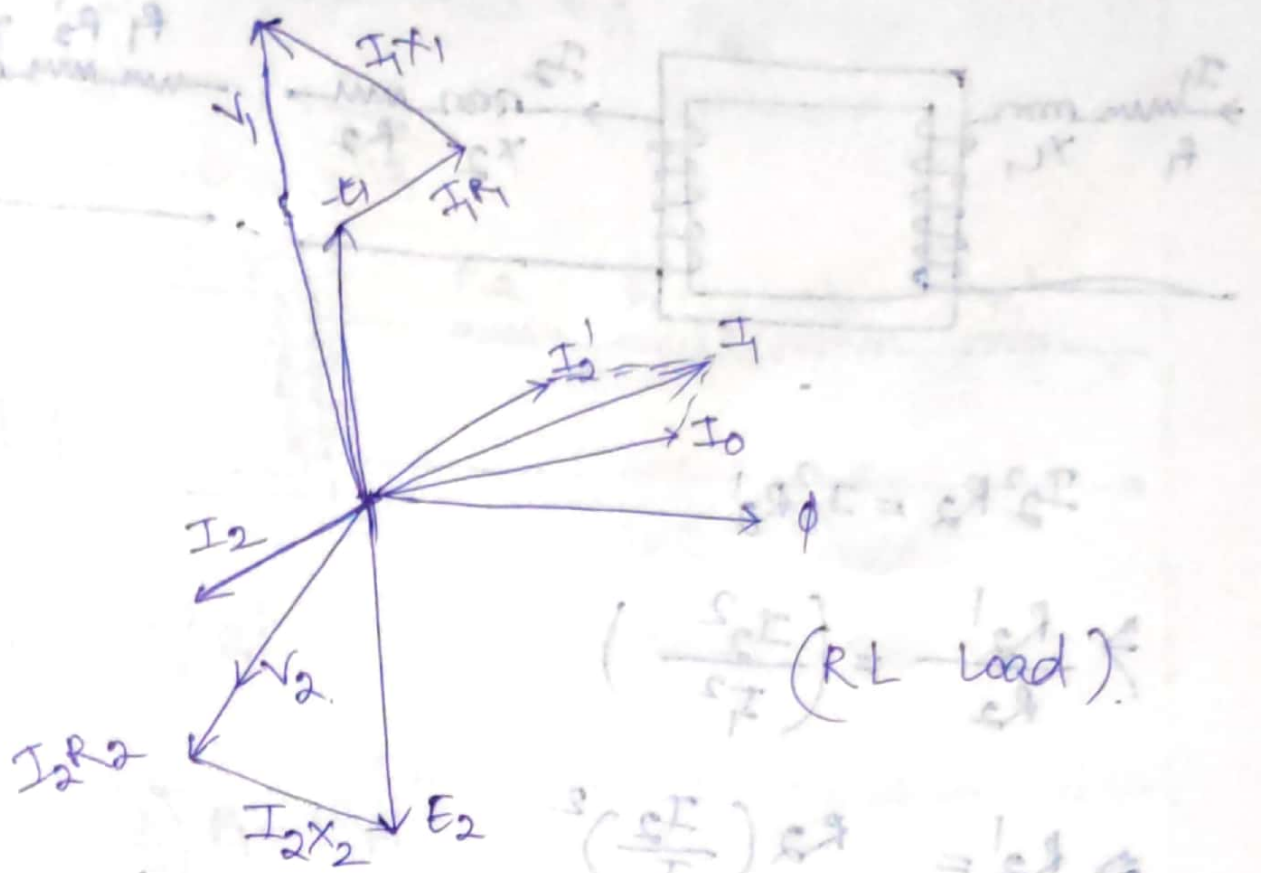


$$\left( \frac{E_2}{E_1} \right) (R_L \text{ load})$$

$$\left( \frac{E_2}{E_1} \right) \cos \phi = \cos \phi$$

$$\left( \frac{E_2}{E_1} \right) \sin \phi = \sin \phi$$

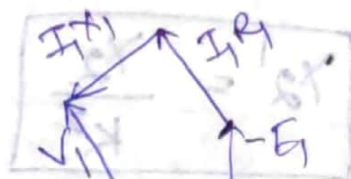
$$\left( \frac{E_2}{E_1} \right) = \cos \phi$$



$$\cos \phi + \sin \phi = \cos \phi + \sin \phi = \cos \phi$$

$$\left( \frac{E_2}{E_1} \right) + \sin \phi = \cos \phi + \sin \phi = \cos \phi$$


(RC load).

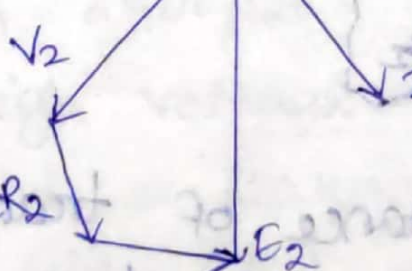

$$\left( \frac{E_2}{E_1} \right) + \sin \phi = \cos \phi + \sin \phi = \cos \phi$$


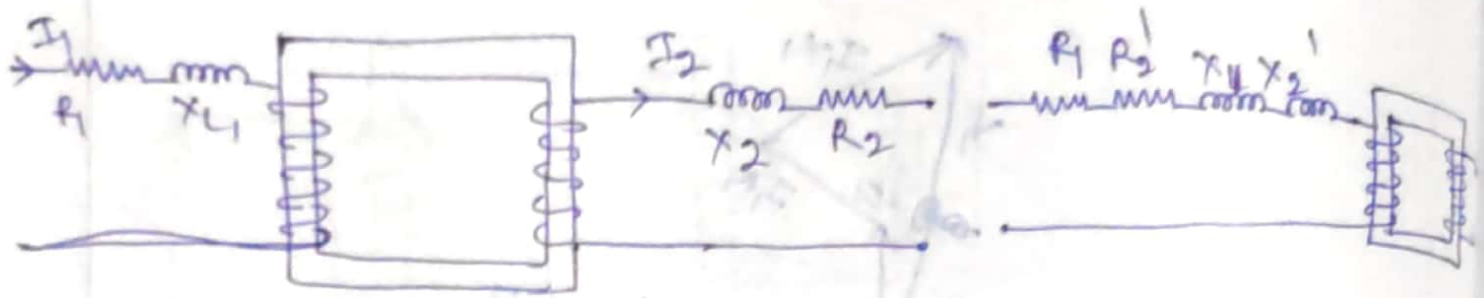
## Equivalent resistance and reactance of T/F



$$I_2^2 R_2 = I_1^2 R_2'$$

$$\Rightarrow \frac{R_2'}{R_2} = \left( \frac{I_2}{I_1} \right)^2$$

$$\Rightarrow R_2' = R_2 \left( \frac{I_2}{I_1} \right)^2$$

$$\Rightarrow R_2' = R_2 \left( \frac{1}{K} \right)^2$$

$$\Rightarrow \boxed{R_2' = \frac{R_2}{K^2}}$$

$$\boxed{X_2' = \frac{X_2}{K^2}}$$

$$\checkmark R_{01} = R_1 + R_2' = R_1 + \frac{R_2}{K^2}$$


$$X_{01} = X_1 + X_2' = X_1 + \frac{X_2}{K^2}$$

equivalent resistance of transformer as refer to primary is denoted by  $R_{01}$

$$R_{01} = R_1 + R_2' = R_1 + \frac{R_2}{K^2}$$

equivalent reactance of transformer is refer to primary is denoted by  $X_{01}$
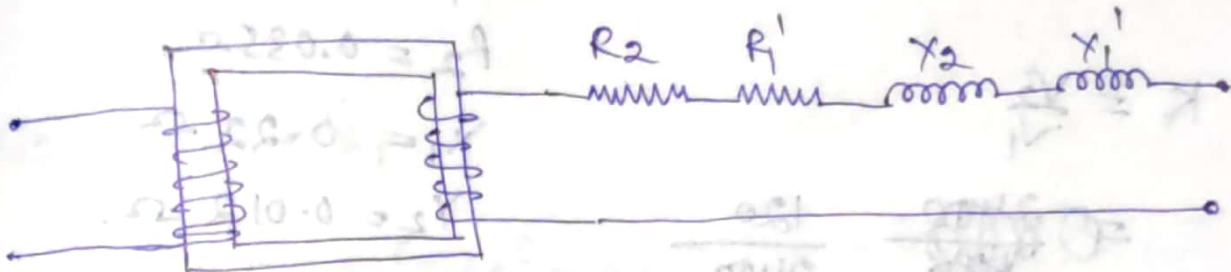
$$X_{01} = X_1 + X_2' = X_1 + \frac{X_2}{K^2}$$



$$I_1^2 R_1 = I_2^2 R_2'$$

$$\Rightarrow R_2' = \left( \frac{I_1}{I_2} \right)^2 R_2 = K^2 R_2$$

$$R_2' = K^2 R_2$$

$$X_2' = K^2 X_2$$


$$R_{02} = R_2 + R_2' = R_2 + K^2 R_1$$

$$X_{02} = X_2 + X_2' = X_2 + K^2 X_1$$

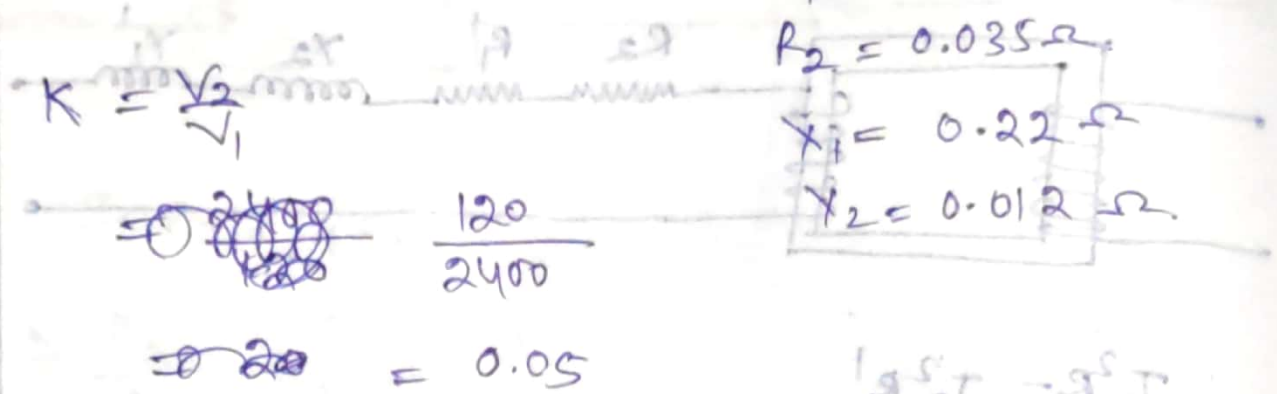- (1) A 30 KVA 2400/120 V 50 Hz transformer has a high voltage winding resistance of  $0.1 \Omega$  and a leakage reactance of  $0.22 \Omega$ . The low voltage winding resistance is  $0.035 \Omega$  and the leakage reactance is  $0.012 \Omega$ . Find the equivalent winding resistance, reactance, impedance refer



- to
- (1) High voltage side
  - (2) Low voltage side.



with reference to High voltage side

$$R_{01} = R_1 + \frac{R_2}{K^2}$$

$$= 0.1 + \frac{0.035}{0.05^2}$$

$$= 14.1 \Omega$$

$$X_1 = K^2 X_2$$

$$R_1 = K^2 R_2$$

$$R_1 + R_2 = R_1 + K^2 R_2 = 0.1 + 0.035 = 0.135$$

$$X_1 + X_2 = X_1 + K^2 X_2 = 0.22 + 0.012 = 0.232$$

$$X_{01} = X_1 + \frac{X_2}{K^2}$$

$$= 0.22 + \frac{0.012}{0.05^2}$$

$$= 5.02$$

$$Z_{01} = \sqrt{14.1^2 + 5.02^2}$$

$$= 14.96 \Omega$$

with reference to low voltage side.

$$R_{02} = R_2 + R_1 K^2$$

$$= 0.035 + \{0.1 \times (6.05)^2\}$$

$$= 0.035$$

$$X_{02} = X_2 + K^2 X_1$$

$$= 0.012 + (0.05^2 \times 0.22)$$



$$= 0.012$$

$$Z_{02} = \sqrt{0.035^2 + 0.012^2}$$

$$= 0.037 \Omega$$




Equivalent ckt diagram of Transformer :-

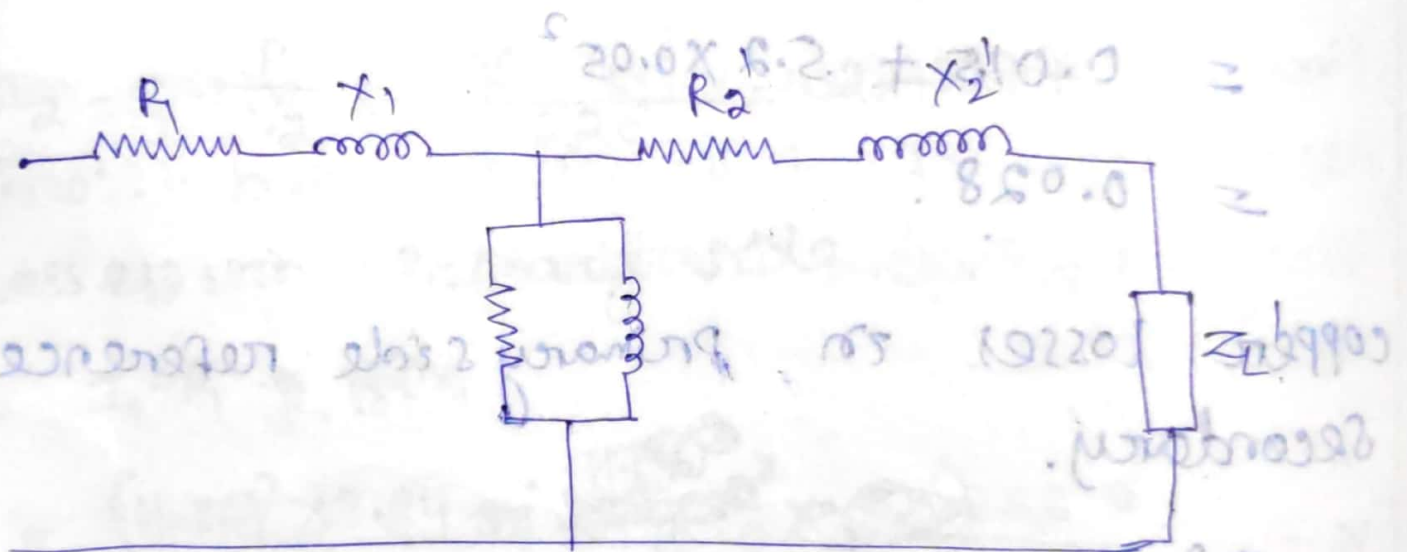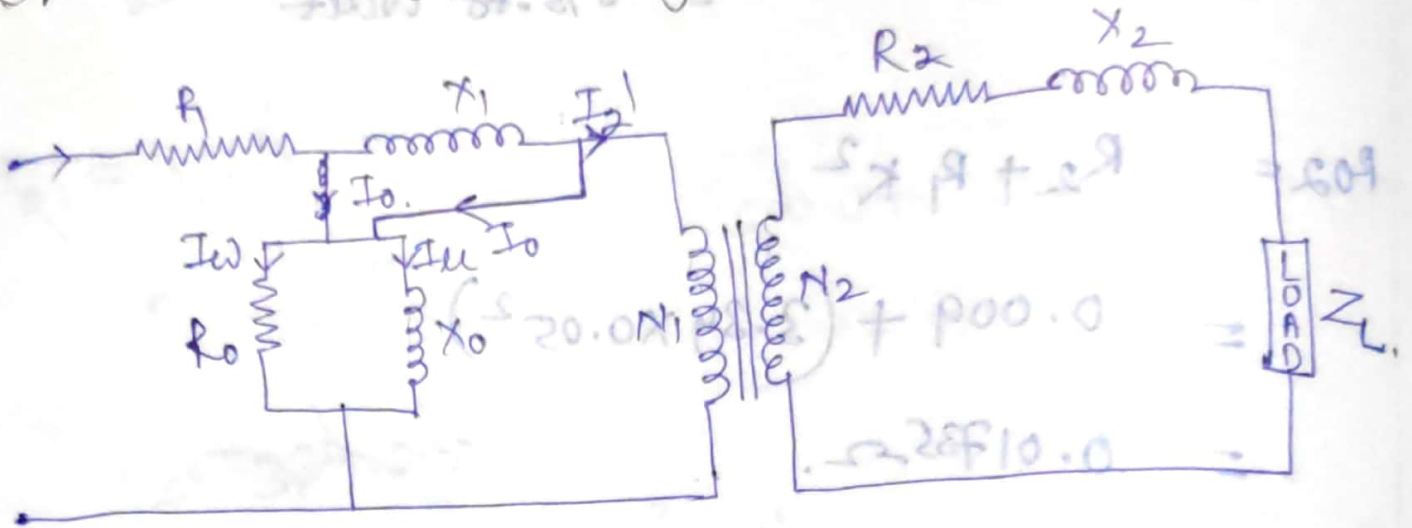

$$I_1 = I_0 + I_2'$$

$$R_2' = \frac{R_2}{K^2}, \quad X_2' = \frac{X_2}{K^2}, \quad Z_L' = \frac{Z_L}{K^2}$$

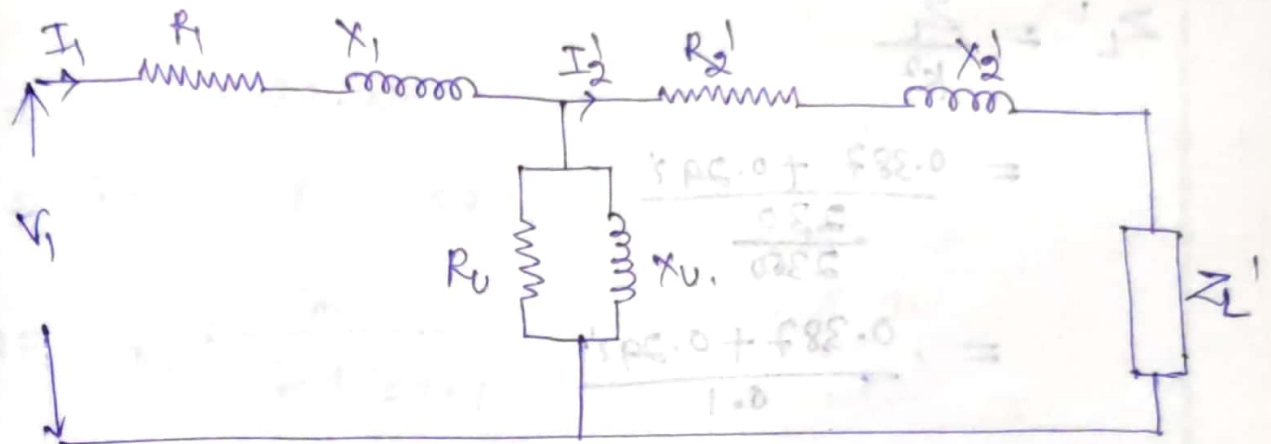1) A 2300/230V, 50Hz transformer has  $R_1 = 0.286 \Omega$ ,  $X_1 = 0.73 \Omega$ ,  $R_2' = 0.319 \Omega$ ,  $X_2' = 0.73 \Omega$ ,  $R_0 = 250 \Omega$ ,  $X_0 = 1250 \Omega$ . The secondary load impedance  $Z_L = 0.387 + 0.29j$ . Find input power, output power, primary copper loss, secondary copper loss and efficiency.



$$Z_L' = \frac{Z_L}{k^2}$$

$$\text{Primary cu. loss} = I_1^2 R_1$$

$$\text{Secondary cu. loss} = I_2'^2 R_2'$$

$$Z_{eq} = (Z_L' + Z_2') \parallel Z_m + Z_1$$

$$I_1 = \frac{V_1}{Z_{eq}}$$

$$I_2' = I_1 \times \frac{Z_m}{Z_m + Z_2' + Z_L'}$$

$$Z_1 = R_1 + jX_1$$

$$Z_m = R_0 \parallel X_0 = \frac{R_0 X_0}{R_0 + jX_0}$$

$$Z_2 = R_2 + jX_2$$



$$Z_1 = 0.286 + 0.73i$$

$$Z_2' = 0.319 + 0.73i$$

$$Z_m = 250 \parallel 1250i$$

$$= \frac{250 \times 1250i}{250 + 1250i}$$

$$= 240.38 + 48.07i$$

$$Z_1' = \frac{Z_1}{k^2}$$

$$= \frac{0.387 + 0.29i}{\frac{230}{2300}}$$

$$= \frac{0.387 + 0.29i}{0.1}$$

$$= 3.87 + 2.9i$$

$$Z_{eq} = \{(Z_1' + Z_2') \parallel Z_m\} + Z_1$$

$$= (3.87 + 2.9i) + (0.319 + 0.73i) \parallel (240.38 + 48.07i)$$

$$= (39.019 + 29.73i) \parallel (240.38 + 48.07i)$$

$$= \frac{(39.019 + 29.73i) \times (240.38 + 48.07i)}{(39.019 + 29.73i) + (240.38 + 48.07i) + (0.286 + 0.73i)}$$

$$= (34.751 + 22.614i) + (0.286 + 0.732i)$$

$$= 35.03 + 23.34i$$

$$= 42.10 \angle 33.67^\circ$$

$$I_1 = \frac{V_1}{Z_{eq}}$$

$$= \frac{2300}{35.03 + 23.34i}$$

$$= 45.47 - 30.29i$$

$$= 54.64 \angle -33.67^\circ$$

$$I_2 = I_1 \times \frac{Z_m}{Z_m + Z_2 + Z_1}$$

$$= 45.47 - 30.29i \times \frac{240.38 + 48.07i}{(240.38 + 48.07i) + (0.319 + 0.732i) + (38.7 + 29i)}$$

$$= 45.47 - 30.29i \times 0.84 - 0.06i$$

$$= 38.32 - 33.13i$$

$$= 46.01 \angle -37.75^\circ \text{ A}$$

$$\text{Primary copper loss} = I_1^2 R_1$$

$$= (54.64)^2 \times 0.286$$

$$= 853.86$$

$$\text{Secondary copper loss} = I_2^2 R_2$$

$$= (46.01)^2 \times 0.319 = 675.29$$




$$\begin{aligned}
 \text{Input power} &= V_1 I_1 \cos \phi \\
 &= 2300 \times 54.65 \times \cos(-33.68^\circ) \\
 &= 2300 \times 54.65 \times 0.83 \\
 &= 104326.85 \text{ watt} \\
 &= 104.32 \text{ KW}
 \end{aligned}$$

$$\begin{aligned}
 \text{o/p power} &= (46.01)^2 \times 0.387 \text{ watt} \\
 &= 0.81 \text{ KW}
 \end{aligned}$$

$$\begin{aligned}
 \eta &= \frac{\text{o/p power}}{\text{i/p power}} \\
 &= \frac{0.81}{104.328}
 \end{aligned}$$

$$\eta = 7.76 \times 10^{-3}$$

Approximate voltage drop Transformer

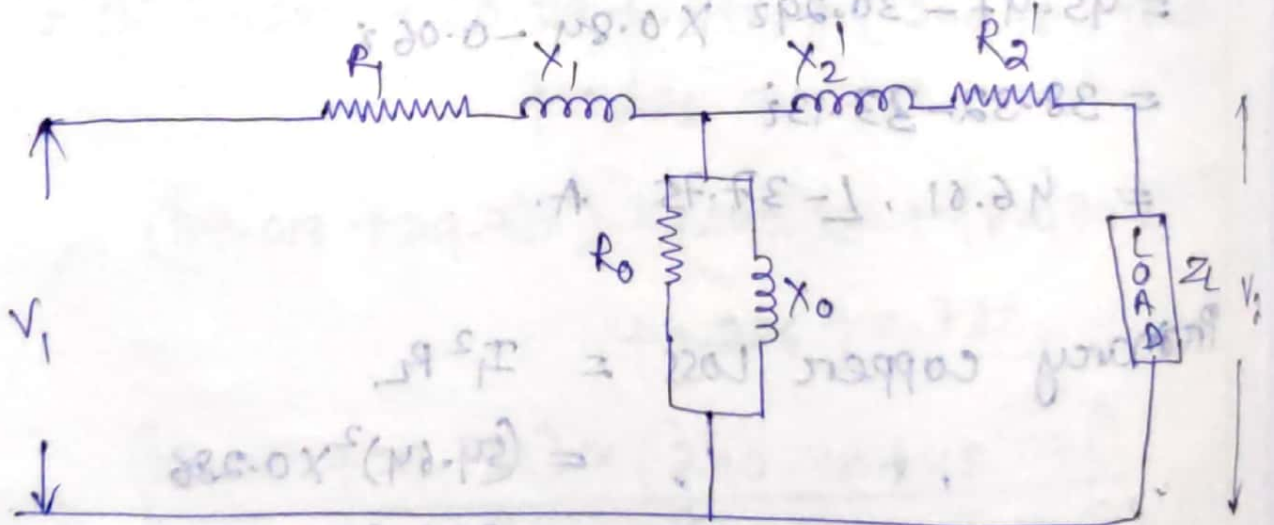

$$R_{eq} = R_1 + R_2 = R_{01}$$

$$X_{01} = X_1 + X_2$$

i/p voltage =  $V_1$

$$\text{drop} = I_1 R_{01}$$

$$= I_1 X_{01}$$

o/p voltage =  $V_2$

$$V_2 = V_1 - I_1 R_{01} - I_1 X_{01}$$

- Q) A Single Phase T/f has 1000 turns on primary 200 turns on secondary, the no-load current is 2.5 Amp and at a p.f of 0.25 lagging. calculate the primary current and power factor when the secondary current is 250 A at a p.f 0.9 lagging.

Given data

$$N_1 = 1000$$

$$N_2 = 200$$

$$I_0 = 2.50 \text{ A}$$

$$I_2' = 2.50 \text{ A}$$

p.f = 0.25 lagging.

angle between  $I_2'$  &  $I_0$

$$\phi = 75.52 - 25.84$$

$$= 49.68^\circ$$

$$\cos \phi = \cos (49.68^\circ)$$

$$= 0.64$$



$$I_1 = \sqrt{(I_2')^2 + I_0^2 + 2I_2' I_0 \cos \phi}$$

$$= \sqrt{50^2 + 2.5^2 + 2 \cdot 250 \cdot 2.5 \cos(40.68^\circ)}$$

$$= 51.63 \text{ Amp.}$$

- (2) A 1- $\phi$  T/F 400 primary and 1000 secondary turns the net cross-sectional area of the core is  $600 \text{ cm}^2$ . If the primary winding is connected to a 50 Hz supply and 520V, calculate the peak value of flux density in the core, voltage induced in the secondary winding.

Given data

$$N_1 = 400$$

$$N_2 = 1000$$

$$A = 60 \text{ cm}^2 = 0.6 \text{ m}^2$$

$$f = 50$$

$$V_1 = 520 \text{ V.}$$

$$E_2 = ? \quad B_m$$

$$E_2 = 4.44 \phi N_2 f.$$

$$\Rightarrow E_2 = 4.44 B_m A f N_2$$

$$K = 4.44 B_m A f N_2$$

$$K = \frac{N_2}{N_1} = \frac{V_2}{V_1}$$

$$= \frac{1000}{400} = \frac{V_2}{520} \Rightarrow V_2 = 1300$$

$$\frac{E_1}{N_1} = 4.44 \phi_m f \quad [V_1 \neq E_1] \quad A_1 = 0.1$$

$$\Rightarrow \phi_m = \frac{520}{400 \times 4.44 \times 50}$$

$$\Rightarrow \phi_m = 5.85 \times 10^{-3} \text{ wb.}$$

$$B_m = \frac{\phi_m}{A}$$

$$= \frac{5.85 \times 10^{-3}}{0.6}$$

$$= 9.75 \times 10^{-3} \text{ wb.}$$

$$E_2 = 4.44 \times f \times \phi_m \times N_2$$


$$= 4.44 \times 50 \times 5.85 \times 10^{-3} \times 10000$$

$$= 1298.7 \text{ V}$$


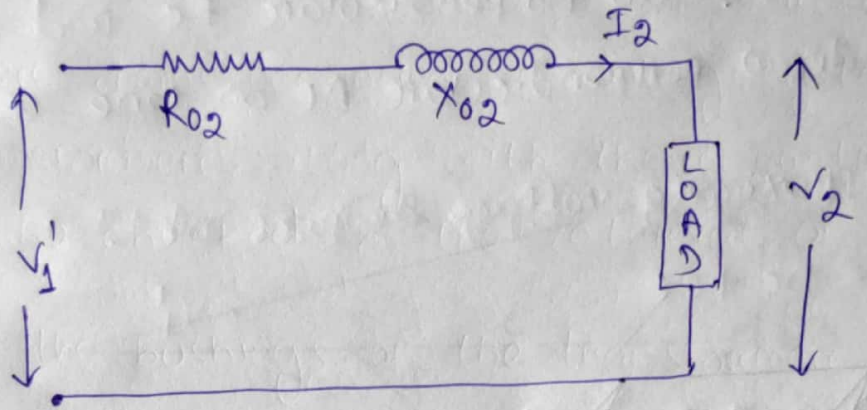
## Approximate voltage drop in a Transformer :-

Equivalent ckt of a transformer with reference to secondary is given below.



Here,

$R_{02}$  = Equivalent resistance of the transformer with respect to secondary

$X_{02}$  = Equivalent reactance of the transformer with respect to secondary.


Now, applying KVL on the ckt, we get

$$\begin{aligned}\vec{V}_1 &= \vec{I}_2 R_{02} + \vec{I}_2 X_{02} + \vec{V}_2 \\ &= \vec{I}_2 Z_{02} + \vec{V}_2\end{aligned}$$


Here  $\vec{I}_2 Z_{02}$  is the voltage drop in the transformer.

If we represent the above equation the form of phasor diagram, we get figure as below.

Let, Load is inductive.

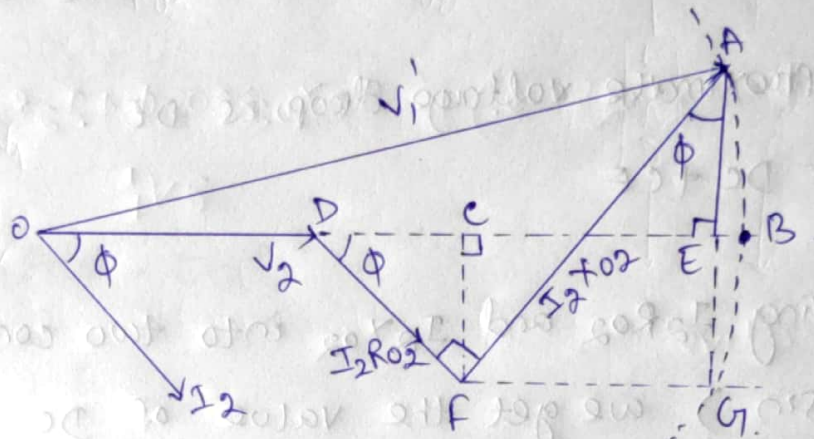

(fig-1)

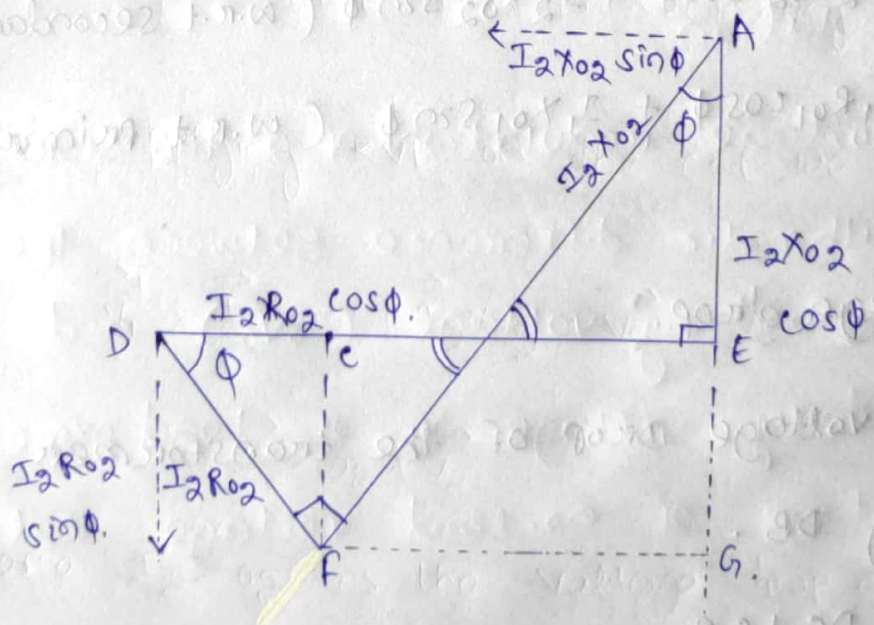

(fig-2)



→ with 'O' as centre and  $OA$  as radius as arc is drawn.

→ Extend  $OD$  with dotted line which cut the arc at point  $B$ .

→ From point  $F$ , draw perpendicular  $FC$  and from point  $A$  draw perpendicular  $AE$  on line  $OB$ .

→ Hence, Approximate voltage drop is  $DE$ .

$$DE = DC + CE$$

→ By resolving  $I_2 R_{02}$  and  $I_2 X_{02}$  into two component ( $\cos$  and  $\sin$ ) we get the value of  $DC$  and  $CE$

$$\rightarrow DE = I_2 R_{02} \cos \phi + I_2 X_{02} \sin \phi$$

Approximate voltage drop.

$$= I_2 R_{02} \cos \phi + I_2 X_{02} \sin \phi \quad (\text{w.r.t secondary})$$

$$= I_1 R_{01} \cos \phi + I_1 X_{01} \sin \phi \quad (\text{w.r.t primary})$$

Exact voltage drop:

The exact voltage drop of the transformer is given by  $DB$ .

$$DB = DC + CB$$

In  $\Delta AOB$  in Fig 1,

$$AE^2 = OA^2 - OB^2$$

$$= (OA + OB)(OA - OB)$$

$$= 2OA \times (OE + EB - OB)$$

$$= 2OA \times EB$$

$$\Rightarrow EB = \frac{AE^2}{2OA}$$

$$EB = \frac{(AG - EG)^2}{2OA}$$

$$= \frac{(I_2 X_{02} \cos \phi - I_2 R_{02} \sin \phi)^2}{2V_1}$$

Exact voltage drop = DB

$$= DE + EB$$

= Approximate voltage drop + EB

$$= (I_2 R_{02} \cos \phi + I_2 X_{02} \sin \phi)$$

$$+ \frac{(I_2 X_{02} \cos \phi - I_2 R_{02} \sin \phi)^2}{2V_1}$$

$$= \frac{V_1 - V_0}{V_0}$$



Load in capacitive.

Approximate voltage drop

$$= I_2 R_{02} \cos \phi - I_2 X_{02} \sin \phi.$$

Exact voltage drop

$$= (I_2 R_{02} \cos \phi - I_2 X_{02} \sin \phi) + \frac{(I_2 X_{02} \cos \phi + I_2 R_{02} \sin \phi)}{2V_1}$$

Load in Resistive :-

Exact voltage drop and approximate voltage drop  $= I_2 R_{02}$ .

Voltage regulation :-

voltage regulation of a transformer is the arithmetic difference between the no-load secondary voltage ( $V_2$ ) and the secondary voltage ' $V_2$ ' on load expressed as percentage of no-load voltage that is

$$\% \text{ voltage regulation} = \frac{V_2 - V_2'}{V_2} \times 100$$


$0V_2 =$  No-load secondary voltage.

$V_2 =$  secondary voltage on load.

$$0V_2 - V_2 = I_2 R_{02} \cos \phi_2 \pm I_2 X_{02} \sin \phi_2$$



## open circuit Test of T/F

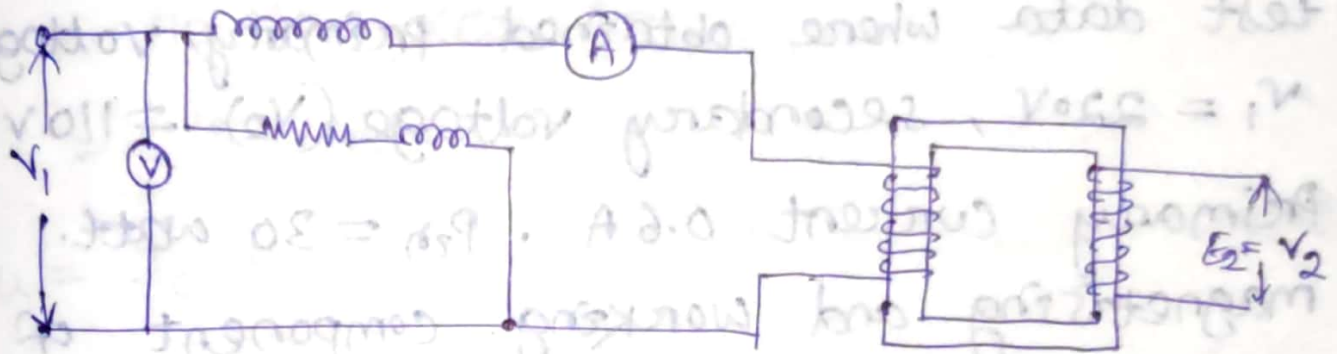

$$W = P_{in}$$

$$P = V I_0 \cos \phi$$

$$V = V_1$$

$$A = I_0$$

$$W = \text{Iron Loss} + \text{Primary cu. Loss}$$

$$\text{Primary cu. Loss} = I_0^2 R_L$$

$$\text{Iron Loss} = W - I_0^2 R_L$$

$$P = V_1 I_0 \cos \phi$$

$$\Rightarrow \cos \phi = \frac{P_{20}}{V_1 I_0}$$

$$\phi = \cos^{-1} \left( \frac{P_{20}}{V_1 I_0} \right)$$

$$I_{\mu} = I_0 \sin \phi$$

$$I_W = I_0 \cos \phi$$

$$R_0 = \frac{V_1}{I_W}$$

$$X_0 = \frac{V_1}{I_{\mu}}$$

- (1) In No-load test of 1- $\phi$  T/F the following test data were obtained primary voltage  $V_1 = 220V$ , secondary voltage ( $V_2$ ) = 110V. Primary current 0.6 A.  $P_{20} = 30$  watt. magnetising and working component of No-load current Iron loss  $R_0$  and  $X_0$  Resistance of primary winding = 0.6  $\Omega$ .

Given data

$$V_1 = 220V$$

$$V_2 = 110V$$

$$P_{in} = 30 \text{ watt}$$

$$I_0 = 0.5A$$

$$R_1 = 0.6 \Omega$$



$$P = VI \cos \phi = ?$$

$$\phi = \cos^{-1} \left( \frac{P}{VI} \right)$$

$$= \cos^{-1} \left( \frac{30}{220 \times 0.5} \right)$$

$$= 74.17$$

$$P_1 = V_1 I_0 \cos \phi$$

$$= 220 \times 0.5 \times \cos(74.17)$$

$$= 30 \text{ watt.}$$

$$P_2 = V_2 I_0 \cos \phi$$

$$= 110 \times 0.5 \times \cos(74.17) =$$

$$= 15 \text{ watt.}$$

$$I_u = I_0 \sin \phi$$

$$= 0.5 \times \sin(74.17)$$

$$= 0.48$$

$$I_w = I_0 \cos \phi$$

$$= 0.5 \times \cos(74.17)$$

$$= 0.13$$

$$R_0 = \frac{V_1}{I_w}$$

$$= \frac{220}{0.13}$$

$$= 1692.30 \Omega$$

$$= 1.69 \text{ k}\Omega$$

$$X_0 = \frac{V_1}{I_u}$$

$$= \frac{220}{0.48}$$

$$= 458.33 \Omega$$

$$= 0.45 \text{ k}\Omega$$

$$P = \phi 200 I V = 9$$

$$\left( \frac{9}{2.0} \right) \cos \phi = 0$$

$$\left( \frac{0.8}{2.0 \times 0.85} \right) \cos \phi = 0$$

$$51.14 \text{ PF} =$$

$$\text{Primary Iron Loss} = W - I_0^2 R \quad \phi 200 \text{ of } I V = 9$$

$$= 30 - 0.5^2 \times 0.6$$

$$= 29.85$$

$$\text{Copper Loss} = I_0^2 R$$

$$= (0.5)^2 \times 0.6$$

$$= (0.155) \quad 200 \times 2.0 \times 0.11 =$$



## Short circuit test of T/F.

total loss.

$W = \text{Total cu. loss} + \text{Iron loss.}$

$\Rightarrow W = \text{total cu. loss.}$

$$\Rightarrow W = I_1^2 R_{01}$$


$$Z_{01} = R_{01} + jX_{01}$$

$$= (R_1 + R_2') + j(X_1 + X_2')$$

$$R_{01} = \frac{W}{I_1^2}$$

$$Z_{01} = \frac{V_{sc}}{I_1}$$

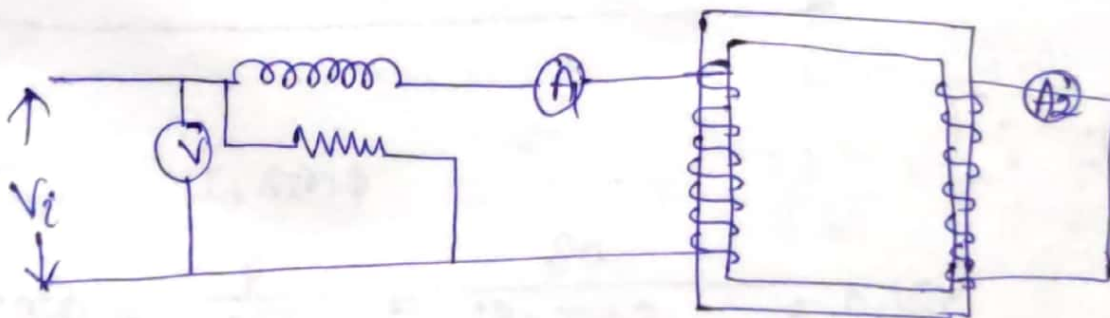Total iron loss is neglected as the input voltage is very small.



with reference to primary  $0.852 \text{ of } I = 11$

$$V_1 = V_{se}$$

$$Z_1 = \frac{V_{se}}{I_1}$$

$$Z_{01} = R_{01} + jX_{01}$$

$$= (R_1 + R_2) + j(X_1 + X_2)$$

$$Z_{01} = \frac{V_{se}}{I_1}$$

$$R_{01} = \frac{W}{I_1^2}$$

$$X_{01} = \sqrt{Z_{01}^2 - R_{01}^2}$$



(1) The instrument readings obtain from open and short ckt test on 10 KVA, 450/120 V, 50 Hz Transformer.

Open ckt Test:  $V_1 = 120V$ ,  
 $I_1 = 4.2A$   
 $W_1 = 80W$ .

Short ckt Test:  $V_1 = 9.65V$ ,  
 $I_1 = 22.2A$ ,  
 $W_1 = 120W$ .

With reference to primary

$$I_1$$

$$R_{01} = R_1 + R_2'$$

$$\text{Copper Loss} = I_1^2 (R_1 + R_2').$$

With reference to secondary

$$I_2$$

$$R_{02} = R_2 + R_1'$$

$$\text{Copper Loss} = I_2^2 (R_2 + R_1').$$

calculate equivalent impedance, reactance, with respect to primary

(ii) Efficiency for an 80% lagging P.F Load.

$$I_\mu = I_0 \sin \phi$$

$$\cos \phi = \frac{P}{\sqrt{I}} = \frac{80}{120 \times 4.2} = 0.158$$

$$\phi = \cos^{-1}(0.158) = 80.90$$

$$\sin \phi = \sin(80.90) = 0.98$$

$$I_\mu = I_0 \sin \phi = 4.2 \times 0.98 = 4.116 A.$$

$$I_w = I_0 \cos \phi$$

$$= 4.2 \times 0.158$$

$$= 0.66 \text{ A}$$

$$R_0 = \frac{V_1}{I_w}$$

$$= \frac{120}{0.66}$$

$$= 181.81 \Omega$$

$$X_0 = \frac{V_1}{I_w}$$

$$= \frac{120}{4.11}$$

$$= 29.19 \Omega$$

$$R_0 = \frac{W}{I^2}$$

$$= \frac{120}{22.2^2}$$

$$= 0.24 \Omega$$

$$Z_{01} = \frac{V_{se}}{I_1} = \frac{9.65}{22.2} = 0.43 \Omega$$

$$\cos \phi = \frac{P}{IV} = \frac{821.0}{8.4 \times 120} = \frac{9}{10} = 0.9$$

$$Z_{01}^2 = R_{01}^2 + X_{01}^2$$

$$\Rightarrow X_{01} = \sqrt{Z_{01}^2 - R_{01}^2}$$

$$= \sqrt{(0.43)^2 - (0.24)^2}$$

$$= 0.356 \Omega$$

$$V_{se} = 120 \text{ V}$$

$$A.S.P = 8.4$$

$$W = 80 \text{ W}$$

primary of generator with reference to primary

$$I_1 + I_2 = 10 \text{ A}$$

$$(I_1 + I_2) \cdot I = 220 \text{ A}$$

secondary of generator with reference to secondary

$$I_1 + I_2 = 10 \text{ A}$$

$$(I_1 + I_2) \cdot I = 220 \text{ A}$$



(ii)  $\cos \phi = 0.8$  (80% lagging).

Total loss = o.c loss + s.c loss.

$$= 80 + 120$$

$$= 200 \text{ W.}$$

o/p power =  $VI \cos \phi$ .

$$= 10 \times 10^3 \times 0.8 \times I$$

$$= 8000 \text{ W.}$$

$$\eta = \frac{\text{o/p power}}{\text{o/p} + \text{losses}} \times 100$$

$$= \frac{8000}{8000 + 200} \times 100$$

$$= 97.56 \%$$

## Core type

(i) It has two Limb or Arm.

(ii) It has winding in both arm.

(iii) It has one path for the flux.

(iv) maximum leakage flux.

(v) more losses.

(vi) Less output.

(vii) maintenance is simple.

(viii) It is used for high voltage transformer.

## Shell type

(i) It has 3 Limb or Arm.

(ii) only middle arm has winding.

(iii) It has two path for the flux.


(iv) Less leakage flux.

(v) Less losses.

(vi) more output.

(vii) maintenance is complex.

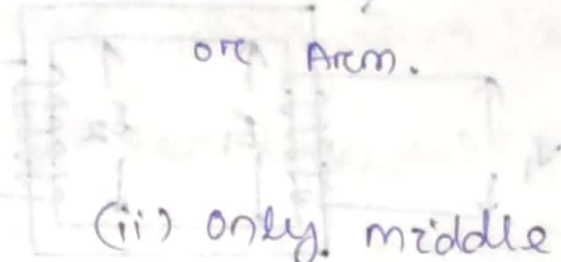(viii) It is used for low and medium voltage transformer.



## Efficiency of a Transformer

The efficiency of a T/F at a particular load and power factor is defined as

a) o/p power divided i/p power being measured in the same unit.

$$\eta = \frac{\text{o/p}}{\text{i/p}} = \frac{\text{o/p}}{\text{o/p} + \text{losses}}$$
$$= \frac{\text{i/p} - \text{losses}}{\text{i/p}}$$

## Condition for maximum efficiency

$$\text{i/p} = V_1 I_1 \cos \phi$$

$$\text{Losses} = W_i + W_c$$

with reference to primary

$$W_c = I_1^2 R_{01}$$

$$\eta = \frac{I_1 V_1 \cos \phi - (W_i + I_1^2 R_{01})}{I_1 V_1 \cos \phi} \quad \left\{ \frac{\text{i/p} - \text{loss}}{\text{i/p}} \right\}$$

$$= 1 - \left( \frac{W_i + I_1^2 R_{01}}{I_1 V_1 \cos \phi} \right)$$

$$= 1 - \frac{W_i}{I_1 V_1 \cos \phi} - \frac{I_1^2 R_{01}}{I_1 V_1 \cos \phi}$$



for maximum efficiency.

$$\frac{d(\eta)}{dI} = 0$$

$$\Rightarrow 0 + \frac{W_i}{I_1^2 V \cos \phi} - \frac{R_{01}}{V_1 \cos \phi} = 0$$

$$\Rightarrow \frac{W_i}{I_1^2 V \cos \phi} = \frac{R_{01}}{V_1 \cos \phi}$$

$$\Rightarrow \frac{W_i}{I_1^2} = R_{01}$$

$$\Rightarrow \boxed{W_i = I_1^2 R_{01}}$$

for maximum efficiency  $\boxed{W_i = W_c}$

All day efficiency

(i) The ordinary or commercial efficiency of the transformer is given by the ratio  $\frac{\text{o/p in watt}}{\text{i/p in watt}}$ .

(ii) But There are certain types of T/F whose performance can not be judged


by this efficiency.

(iii) for example distribution T/F have their p/m winding energized all the 24 hours.

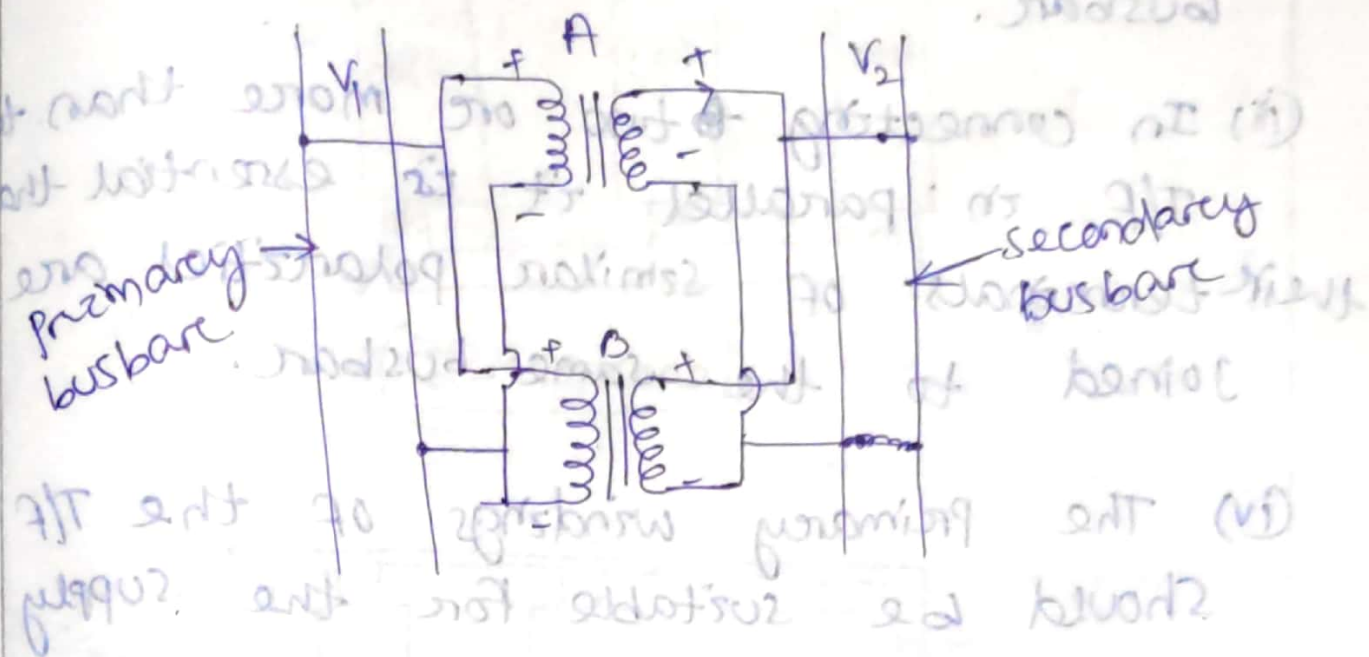(iv) But Load connected in the secondary changes through out the day, therefore in this case all day efficiency of the T/F is calculated.

$$\eta_{\text{all day}} = \frac{\text{o/p } \text{Wh}}{\text{i/p } \text{Wh}} \quad (\text{for 24 hour}).$$

Parallel operation of T/F : Transformers are connected in parallel to the load and at the same time to the supply.



condition for parallel operation:

- (i) Polarity should be same
- (ii) Percentage of impedance should be same.
- (iii) Rating should be same.

(iv) If load connected to a T/F increases beyond its rating, a second T/F may be connected in parallel with it to supply the extra load.

(v) The p/m windings are connected to the supply busbar or p/m busbar



and secondary windings are connected to the load busbar or secondary busbar.

(iii) In connecting two or more than two T/F in parallel it is essential that their terminals of similar polarities are joined to the same busbar.

(iv) The primary windings of the T/F should be suitable for the supply voltage and frequency.


(v) The voltage rating of both P/m and secondary should be identical. In other words the T/F should have same transformation ratio.

(vi) The percentage impedance of the T/F should be equal in magnitude to avoid circulating current and operation at different power factor.

## Chapter - 4 Auto Transformer.
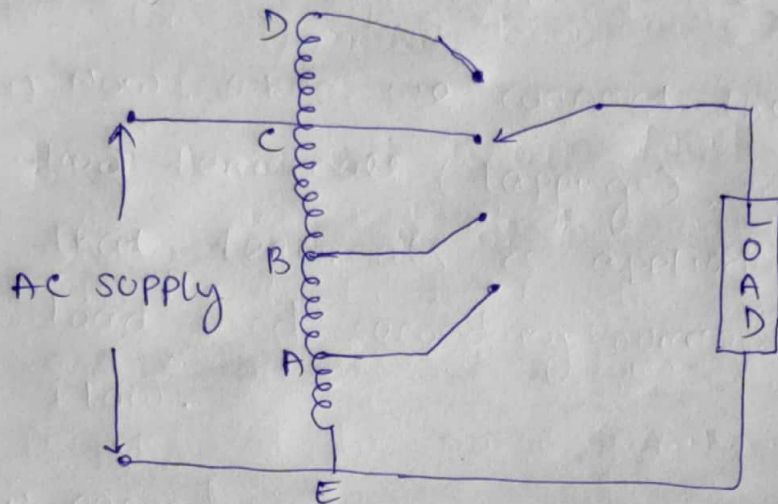
### Auto Transformer :-

An auto transformer is an electrical transformer having one winding with more than two terminals.



### Advantages :-

- (i) They are smaller in size.
- (ii) Cheap in cost.
- (iii) low leakage reactance.
- (iv) low exciting current.

### construction :-

- (i) An auto transformer consists of a single copper wire, which is common in both primary as well as secondary circuit.
- (ii) The copper wire is wound on a laminated silicon steel core with more than two tapping.



both primary and secondary circuit share the same neutral point.

- (iii) The above figure shows ckt diagram of a Auto transformer. we can see that variable turns on the secondary can be obtained by tapping of the winding.
- (iv) Here the primary and secondary circuits are connected electrically as well as magnetically.
- (v) The same transformer can be used as step down or step-up transformer due to presence of tapping. For example, if the load is connected to tapping 'D', then the transformer will act as step-up transformer. Because, here primary turns are 'CE' where as secondary turns are 'DE'. we can clearly see that  $CE < DE$ . So secondary voltage will be greater than primary. But if load is connected to tapping B or A, then it will act as a step down transformer.

Working principle of Auto transformer :-

- (i) It's working principle and operation is similar to a two winding transformer.
- (ii) when supply is given to the primary circuit



AC current flows through the winding. Therefore an alternating flux is created around the conductors or winding.

(iii) According to Faraday's law of electromagnetic induction emf will induce in the coil.

(iv) Now, when we connect the load between two terminals (tappings), induced emf between that terminals is applied across the load and secondary current starts to flow.

(v) secondary voltage will depend on the number of turns and no. of turns depends upon tapping on winding.

Comparison between two winding T/F and Auto Transformer. :-

| <u>Two winding T/F.</u>  | <u>Auto T/F.</u>   |
|--|--|
| (i) It has two winding i.e. primary and secondary.                 | (i) It has one winding only.                                   |
| (ii) Primary and secondary circuits are electrically separated but | (ii) Primary and secondary circuits are connected electrically |

magnetically coupled

(ii) size is large

(iv) copper requirement is more

(v) cost is more.

(vi) Losses are more and efficiency is less.

(vii) Poor voltage regulation.

(viii) output is constant.

as well as magnetically.

(iii) size is small.

(iv) copper requirement is less.


(v) cost is less.

(vi) Losses are less and efficiency is more.

(vii) Better voltage regulation.

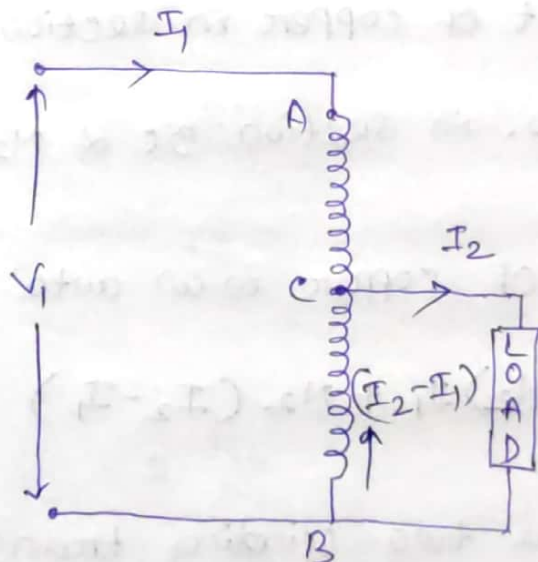(viii) output is variable.

Saving of copper in an Auto Transformer. :-



Here AB is the primary winding having  $N_1$  turns and BC is secondary winding having  $N_2$  no. of turns. So,

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = \frac{I_1}{I_2} = K.$$

current in section BC is vector difference of  $I_2$  and  $I_1$ . As it is a step down transformer  $V_2 < V_1$  and  $I_2 > I_1$ . So current in section 'BC' is  $I_2 - I_1$ .

We know that weight of copper is proportional to the length and area of cross-section of the conductors. Again length is proportional to no. of turns and cross-sectional area depends on current. Hence weight is proportional to the product of current and number of turns.

So, weight of copper in section AC  $\propto (N_1 - N_2)I_1$   
weight of Cu. in section BC  $\propto N_2(I_2 - I_1)$ .

$\therefore$  Total weight of copper in an auto transformer  

$$= (N_1 - N_2)I_1 + N_2(I_2 - I_1)$$

Let, we take a two winding transformer.

Here weight of copper in primary  $\propto N_1 I_1$

Similarly weight of copper in secondary  $\propto N_2 I_2$



$$\therefore \text{Total weight of copper in a two winding} \\ = N_1 I_1 + N_2 I_2.$$

$$\frac{\text{weight of cu. in auto T/F.}}{\text{weight of cu. in two winding Transformer}} = \frac{(N_1 - N_2) I_1 + N_2 (I_2 - I_1)}{N_1 I_1 + N_2 I_2}$$

$$\Rightarrow \frac{W_a}{W_o} = \frac{N_1 I_1 - N_2 I_1 + N_2 I_2 - N_2 I_1}{N_1 I_1 + N_2 I_2}$$

$$\Rightarrow \frac{W_a}{W_o} = \frac{N_1 I_1 + N_2 I_2 - N_2 I_1 - N_2 I_1}{N_1 I_1 + N_2 I_2}$$

$$= 1 - \frac{N_2 I_1 - N_2 I_1}{N_1 I_1 + N_2 I_2}$$

$$= 1 - \frac{\frac{2 N_2 I_1}{N_1 I_1}}{\frac{N_1 I_1}{N_1 I_1} + \frac{N_2 I_2}{N_1 I_1}} \quad \left[ \text{dividing by } N_1 I_1 \right]$$

$$= 1 - \frac{2 \frac{N_2}{N_1}}{1 + \frac{N_2}{N_1} \times \frac{I_2}{I_1}}$$

$$= 1 - \frac{2 \times K}{1 + \frac{1}{K} \times K}$$

$$\Rightarrow \frac{W_a}{W_0} = 1 - \frac{2K}{2}$$

$$\Rightarrow \frac{W_a}{W_0} = 1 - K$$

$$\Rightarrow W_a = (1 - K) W_0$$

$$\text{Saving of copper} = W_0 - W_a$$

$$= W_0 - (1 - K) W_0$$

$$= W_0 (1 - 1 + K)$$

$$= K W_0$$

Saving =  $K \times$  weight of ordinary or two winding transformer.

Here, Power transferred inductively =  $(1 - K) P_{i/p}$ .

Power transferred conductively =  $K P_{i/p}$ .

Uses of Auto Transformer :-

(i) To adjust AC supply voltage. By using it we can vary the AC voltage (voltage-regulator).

(ii) It is used as a starter for squirrel cage induction motor.

(iii) It is used in power transmission and distribution system.

(iv) It is also used in audio system and railway.


Tap changer :-

Mechanism used to change the tapping of a transformer is called tap changer. Tap changer is mainly classified into two types.

(1) Off Load tap changer.

(2) ON-Load Tap changer.

1. Off Load Tap changer :-

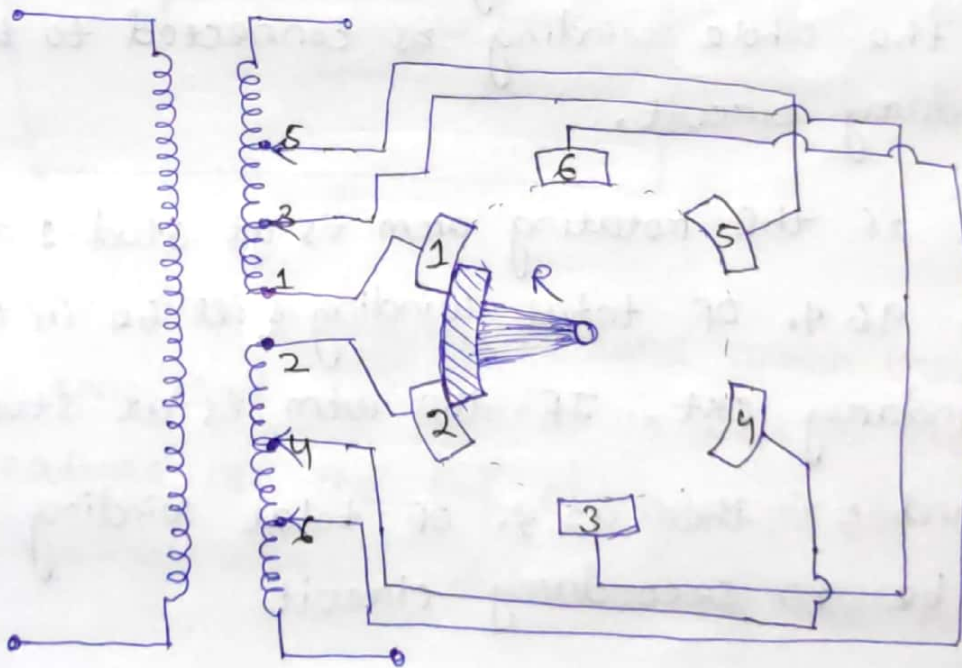




- (i) Here tap changing is done when the transformer is disconnected from the main supply. This tap changing is usually done manually.
- (ii) The above fig. shows on off-load tap changer. The secondary winding is tapped from six location.
- (iii) These tappings are connected to six studs arranged along a periphery of a circle.
- (iv) The rotatable arm R can be rotated by a hand wheel mounted outside the transformer tank.
- (v) Let, the tappings are at an interval of 2%. If position of rotating arm is at stud 1 and 2, the whole winding is connected to the secondary circuit.
- (vi) But if the rotating arm is at stud 1 and 6 then 96% of total winding will be in the secondary ckt. If the arm is at stud 6 and 5, then 92% of total winding will be in secondary circuit.
- (vii) In the process by moving the rotating arm, no. of turns in the secondary winding

changes. As a result secondary voltage also changes.

(iii) This tap changer is only used in off condition of transformer. If we use it in on condition, then huge spark will produce.

### ON-Load Tap changer :-

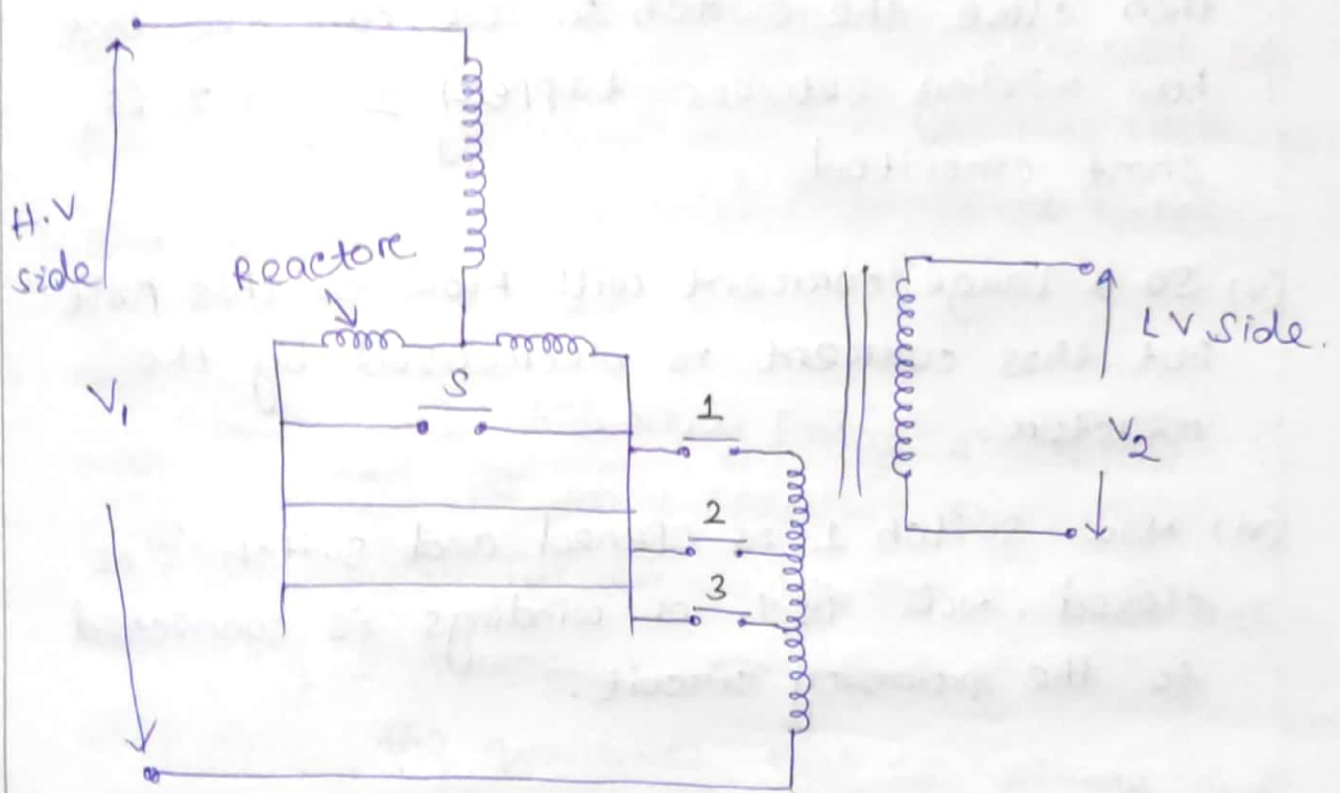

(i) Here Tap changing is done, when transformer is connected to source as well as load. Main feature of the tap changer is to change tapping without discontinuing the power supply.

(ii) In this type of tap changer a centre tapped reactor provided to prevent short circuit

of the tap winding. During normal operation switch 'S' remainly closed.

(iii) Let initially switch of tapping one is closed. So whole windings is connected. Now if I required less voltage, the tappers 2 is to be connected.

(iv) For this we have to first open the switch 'S', then close the switch 2. we can see that how winding between tapping 1 and 2 is short circuited.

(v) So a large current will flow to this part. But this current is decreased by the reactor.

(vi) Now switch 1 is opened and switch 'S' is closed. Now 98% of windings is connected to the primary circuit.




## (Chapter-5) Instrument Transformers

### Instrument transformers:-

- (i) Instrument transformers are used in AC system for measurement of electrical quantities like current, voltage, power, energy etc.
- (ii) Generally measuring instruments are of low ratings. So by using this instruments we can not measure high electrical quantities. It is very costly to design the measuring instrument for measurement of such high level voltage and current.
- (iii) measurement of such very large electrical quantities can be made possible by using instrument transformers with these small rating measuring instruments. Instrument transformers step down the quantities that is voltage and current, so that they can be measured by low rating instruments.
- (iv) Mainly there are two types of instrument transformers
  - (1) current transformer (C.T).
  - (2) Potential transformer (P.T).

## current Transformer :-

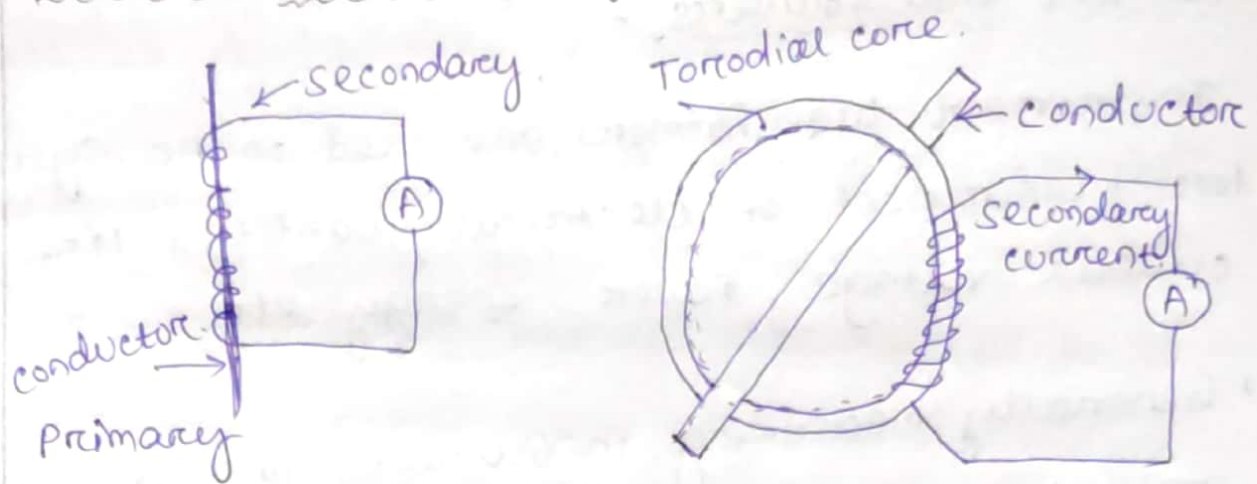

- (i) current transformer is used to step up the voltage or step down the current so that this stepped down current can be easily measured by measuring instruments.
- (ii) Primary of C.T is having very few turns and secondary has large no. of turns. Secondary winding is connected to measuring instrument.
- (iii) current transformers are often constructed by passing a single primary turn (either an insulated cable or an uninsulated busbar) through a well insulated ring shaped (toroidal) core wound with many no. of turns.
- (iv) one terminal of the secondary is earthed to avoid the chance of insulation breakdown




and also protect the operators against high voltage

(v) Turns ratio of the transformer is

$$\text{Turns ratio} = \frac{N_p}{N_s} = \frac{I_s}{I_p} = \frac{V_p}{V_s}$$

Potential Transformer (PT) :-

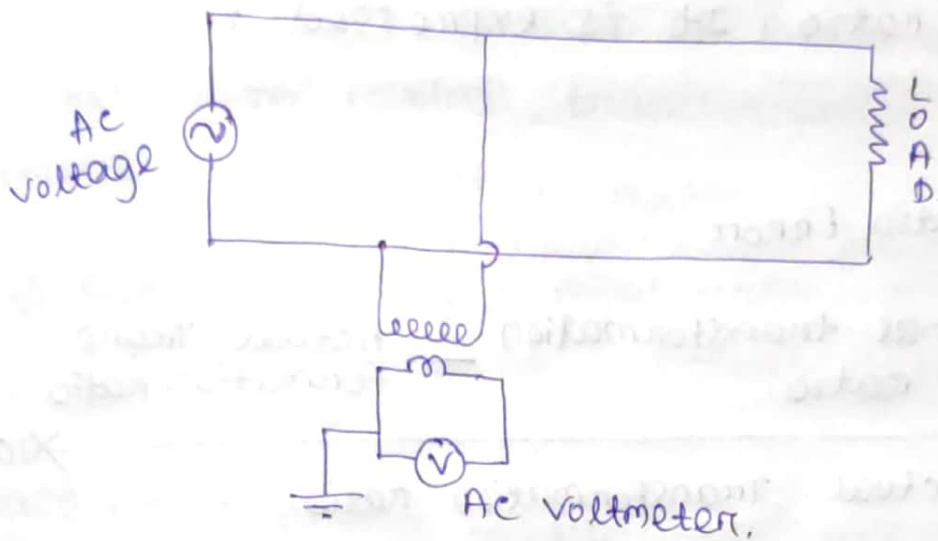

(i) Potential transformers are also known as voltage transformers and they are basically step down transformers.

(ii) They step down the voltage of high magnitude to a lower value, which can be measured with standard measuring instrument.

(iii) These transformers have large number of primary turns and less number of secondary turns.



- (iv) secondary winding is connected to a voltmeter.
- (v) one terminal of the secondary is connected to each for safety of operator.

### Ratio Error of C.T. :-

Ratio error of C.T is defined as the per unit deviation in transformation ratio from nominal ratio. It is expressed in Percentage.

Percentage Ratio Error

$$= \frac{\text{Nominal transformation ratio} - \text{Actual Transformation ratio}}{\text{Actual Transformation ratio}} \times 100$$

Nominal transformation ratio = rated transformation ratio.

### Phase angle error of CT :-

Ideally the angle between primary and secondary current should be 180 degree. But there is some deviation from 180°. This deviation is called phase angle error.

OR

It is defined as the phase difference between primary current and reversed

Secondary current.

Burden of CT or PT. ° -

It is defined as the volt ampere (VA) of connected load across the terminals of secondary winding of CT and PT.

Ratio Error of PT. ° -

Ratio error of PT is defined as the variation in nominal transformation ratio to actual transformation ratio.

$$\% \text{ Ratio Error} = \frac{\text{Nominal ratio} - \text{Actual ratio}}{\text{Actual ratio}} \times 100$$

Phase angle error of PT. ° -

Ideally angle between primary and secondary voltage should be  $180^\circ$ . But practically there is some deviation from  $180^\circ$ .

OR.

It is defined as the phase difference between the primary voltage and reversed secondary voltage.



### uses of current T/F :-

current transformers are used in a wide variety of applications ranging from power system control to the precise current measurement in industrial, medical, automotive and telecommunication system.

Some of the application are,

- (1) Extending the range of measuring instruments such as ammeter, energy meter, wattmeter etc.
- (2) over current fault protection.
- (3) Distance protection in <sup>Power</sup> transmission system.

### uses of Potential Transformer :-

Like C.T., potential transformers are also used in power system control, industrial, medical, automotive and telecommunication system.

- ① Extending the range of measuring instruments like voltmeter, energy meter, wattmeter, etc.
- ② Electrical Protection system.
- ③ Distance protection of feeders
- ④ Impedance protection of generator.



## Th2. Analog Electronics and OP-AMP

|   |         |                           |                 |
|---|---------|---------------------------|-----------------|
| Name of the Course: Diploma in Electrical Engineering |         |                           |                 |
| Course code:  |         | Semester                  | 4 <sup>th</sup> |
| Total Period:   | 60      | Examination               | 3 hrs           |
| Theory periods:                                       | 4P/week | Internal Assessment :     | 20              |
| Maximum marks:  | 100     | End Semester Examination: | 80              |

### A. Rationale:

Electrical Engineers use electronic devices and circuits in various fields. The modern electrical plants need help of solid state electronic circuits for control, starting etc. So it was felt to provide a subject having electronic devices and circuits for the electrical students. Study of practical circuits and components have been dealt here with in the theoretical approach.

### B. Objectives:

1. To develop knowledge on the characteristics of different types of diodes, transistors, UJT, FET and to draw a comparison in their characteristics and application.
2. To develop knowledge of their application.
3. To develop knowledge of different oscillator circuits and to identify the difference between them and their frequency relation.
4. To develop knowledge of operational amplifiers and their application in the field.

### C. TOPIC WISE DISTRIBUTION OF PERIODS

| Sl No.       | Name of the Topic                   | Periods   |
|--------------|-------------------------------------|-----------|
| 1            | P-N JUNCTION DIODE                  | 6         |
| 2            | SPECIAL SEMICONDUCTOR DEVICES       | 5         |
| 3            | RECTIFIER CIRCUITS & FILTERS        | 7         |
| 4            | TRANSISTORS                         | 7         |
| 5            | TRANSISTOR CIRCUITS                 | 7         |
| 6            | TRANSISTOR AMPLIFIERS & OSCILLATORS | 13        |
| 7            | FIELD EFFECT TRANSISTOR             | 6         |
| 8            | OPERATIONAL AMPLIFIERS              | 9         |
| <b>Total</b> |                                     | <b>60</b> |

## **D. Course Content:**

### **1. P-N JUNCTION DIODE:**

1 . 1 P-N Junction Diode

1 . 2 Working of Diode

1 . 3 V-I characteristic of PN junction Diode.

1 . 4 DC load line

1 . 5 Important terms such as Ideal Diode, Knee voltage

1 . 6 Junctions break down.

1.6.1 Zener breakdown

1.6.2 Avalanche breakdown

1 . 7 P-N Diode clipping Circuit.

1 . 8 P-N Diode clamping Circuit

2. **SPECIAL SEMICONDUCTOR DEVICES:**

2 . 1 Thermistors, Sensors & barretters

2 . 2 Zener Diode

2 . 3 Tunnel Diode

2 . 4 PIN Diode

3. **RECTIFIER CIRCUITS & FILTERS:**

3.1 Classification of rectifiers

3.2 Analysis of half wave, full wave centre tapped and Bridge rectifiers and calculate:

3.2.1 DC output current and voltage

3.2.2 RMS output current and voltage

3.2.3 Rectifier efficiency

3.2.4 Ripple factor

3.2.5 Regulation

3.2.6 Transformer utilization factor

3.2.7 Peak inverse voltage

3.3 Filters:

3.3.1 Shunt capacitor filter

3.3.2 Choke input filter

3.3.3  $\pi$  filter

4. **TRANSISTORS:**

4.1 Principle of Bipolar junction transistor

4.2 Different modes of operation of transistor



- 4.3 Current components in a transistor
- 4.4 Transistor as an amplifier
- 4.5 Transistor circuit configuration & its characteristics
  - 4.5.1 CB Configuration
  - 4.5.2 CE Configuration
  - 4.5.3 CC Configuration

5. **TRANSISTOR CIRCUITS:**

- 5.1 Transistor biasing
- 5.2 Stabilization
- 5.3 Stability factor
- 5.4 Different method of Transistors Biasing
  - 5.4.1 Base resistor method
  - 5.4.2 Collector to base bias
  - 5.4.3 Self bias or voltage divider method

6. **TRANSISTOR AMPLIFIERS & OSCILLATORS:**

- 6.1 Practical circuit of transistor amplifier
- 6.2 DC load line and DC equivalent circuit
- 6.3 AC load line and AC equivalent circuit
- 6.4 Calculation of gain
- 6.5 Phase reversal
- 6.6 H-parameters of transistors
- 6.7 Simplified H-parameters of transistors

6.8 Generalised approximate model

6.9 Analysis of CB, CE, CC amplifier using generalised approximate model

6.10 Multi stage transistor amplifier

6.10.1 R.C. coupled amplifier

6.10.2 Transformer coupled amplifier

6.11 Feed back in amplifier

6.11.1 General theory of feed back

6.11.2 Negative feedback circuit

6.11.3 Advantage of negative feed back

6.12 Power amplifier and its classification

6.12.1 Difference between voltage amplifier and power amplifier

6.12.2 Transformer coupled class A power amplifier

6.12.3 Class A push – pull amplifier

6.12.4 Class B push – pull amplifier

6.13 Oscillators

6.13.1 Types of oscillators

6.13.2 Essentials of transistor oscillator

6.13.3 Principle of operation of tuned collector, Hartley, colpitt, phase shift, wein-bridge oscillator (no mathematical derivations)

## 7. **FIELD EFFECT TRANSISTOR:**

7.1 Classification of FET

7.2 Advantages of FET over BJT

7.3 Principle of operation of BJT

7.4 FET parameters (no mathematical derivation)

7.4.1 DC drain resistance

7.4.2 AC drain resistance

7.4.3 Trans-conductance

7.5 Biasing of FET

8. **OPERATIONAL AMPLIFIERS:**

8.1 General circuit simple of OP-AMP and IC – CA – 741 OP AMP

8.2 Operational amplifier stages

8.3 Equivalent circuit of operational amplifier

8.4 Open loop OP-AMP configuration

8.5 OPAMP with fed back

8.6 Inverting OP-AMP

8.7 Non inverting OP-AMP

8.8 Voltage follower & buffer

8.9 Differential amplifier

8.9.1 Adder or summing amplifier

8.9.2 Sub tractor

8.9.3 Integrator

8.9.4 Differentiator

8.9.5 Comparator



**Syllabus coverage up to Internal assessment**


Chapters: 1, 2, 3, 4 and 5.

| <b>Learning Resources:</b> |                        |                                    |                              |
|----------------------------|------------------------|------------------------------------|------------------------------|
| <b>Sl.No</b>               | <b>Name of Authors</b> | <b>Title of the Book</b>           | <b>Name of the publisher</b> |
| 1                          | Sanjeev Gupta          | Electronic Devices and<br>Circuits | Dhanpat Rai<br>Publications  |
| 2                          | R.S SEDHA              | Electronics circuit                | S.CHAND                      |

## Rectifier circuits & Filters

Two rectifier circuits :-


(i) Half Wave Rectifier →

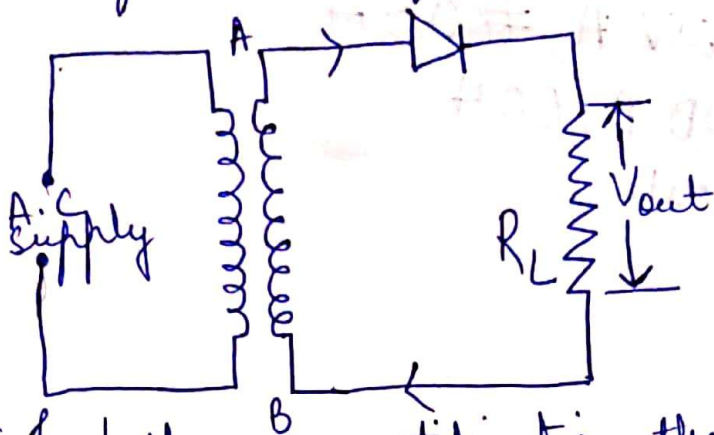

\* In half wave rectification, the rectifier conducts current only during the +ve half cycle of s/p a.c supply.

\* The negative half cycles of a.c supply are suppressed i.e during negative half cycles, no current is conducted & hence no voltage appears across the load.

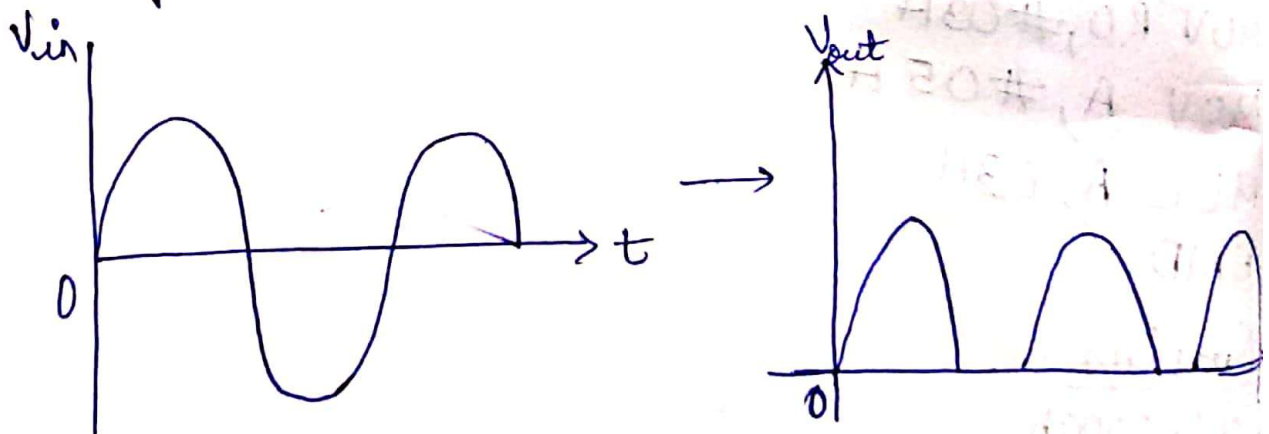\* Therefore current always flows in one direction through the load



### Circuit Details

\* It has a single crystal diode which acts as a half-wave rectifier.

\* The a.c supply to be rectified is applied in series with the diode and load resistance  $R_L$ .

\* A.C supply is given through a transformer.

\* Transformer used permits two advantages:  
Firstly, it allows to step up or step down the a.c s/p voltage  
Secondly, it isolates the rectifier circuit from power line and thus reduces the risk of electric shock.

### Operation

- \* The AC voltage across the secondary winding AB changes polarities after every half-cycle.  
During the +ve half cycle of i/p ac voltage, end A becomes +ve w.r.t end B.  
\* This makes diode forward biased and hence it conducts current.
- \* During -ve half cycle, end A is -ve w.r.t end B. The diode is reverse biased and it conducts no current.
- \* Therefore current flows through the diode during +ve half-cycles of i/p a.c voltage only and it is blocked during -ve half cycle.
- \* In this way current flows through load  $R_L$  always in same direction.
- \* Hence d.c o/p is obtained across  $R_L$ .
- \* o/p obtained is pulsating d.c

### Disadvantages

- \* It requires an elaborate filtering to produce steady ~~out~~ direct current
- \* A.C supply delivers power only half the time.  
Therefore, ~~out~~ o/p is low.



## Calculate Analysis of half wave rectifier

### DC current

$$I_{DC} = \frac{I_{max}}{\pi} \quad I_{DC} = \frac{V_m}{\pi R_L} = 0.318 \frac{V_m}{R_L}$$

~~$I_{max}$~~  = maximum DC load current

~~o/p DC voltage~~  $V_m$  = max<sup>m</sup> o/p supply voltage

$R_L$  = load resistance

\* It is the voltage appeared at the load resist<sup>n</sup>  
 $R_L$

\* This is obtained by multiplying the o/p DC current with load resistance  $R_L$

$$V_{DC} = I_{DC} R_L$$

$$\Rightarrow V_{DC} = \frac{I_{max} R_L}{\pi} \quad \frac{V_m}{\pi}$$

$$\frac{I_{max} R_L}{\pi} = V_{smax}$$

$V_{smax}$  = Maximum secondary voltage

### Ripple Factor

\* The DC produced by a half wave rectifier is not a pure DC but a pulsating DC.

\* In the o/p pulsating DC signal, we find ripples.

\* These ripples can be reduced by using filters such as capacitors & inductors.

\* These ripples can be measured by a factor known as ripple factor.

\* Ripple factor tells us the amount of ripples present in the o/p DC signal.

\* Ripple factor can be simply defined as ratio of ripple voltage to the DC voltage.

$$r = \sqrt{\left(\frac{V_{rms}}{V_{DC}}\right)^2 - 1}$$

$V_{rms}$  = rms value of AC component of the o/p voltage  
 $V_{DC}$  = DC component of o/p voltage

### Peak Inverse Voltage

\* It is the maximum reverse bias voltage upto which a diode can withstand.

\* If the applied voltage is greater than the PIV, the diode will be destroyed.

$$PIV = V_s \max$$

$V_s \max = \max^{\text{m}} \text{secondary voltage}$

### Efficiency

\* Ratio of o/p DC power to i/p AC power.

\* efficiency of half wave rectifier is 40.6%.

### RMS value of load current $I_{rms}$

~~$$I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{I_m}{\sqrt{2}} = \frac{I_m}{\sqrt{2}}$$~~

$I_m = \text{peak value of o/p current}$

$$I_{rms} = \frac{I_m}{2}$$

### RMS value of o/p load voltage

~~$$V_{rms} = I_{rms} R_L = \frac{I_m}{\sqrt{2}} R_L$$~~

$$V_{rms} = I_{rms} R_L = \frac{I_m}{2} R_L$$

~~$$V_{rms} = \frac{I_m}{\sqrt{2}} \times R_L = \frac{V_m \times R_L}{\sqrt{2} (R_s + R_L)}$$~~



## Percentage of Regulation

It is a measure of the variation of DC o/p voltage for variations in the load.

$$= \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$

$V_{FL}$

$V_{NL}$  = Voltage at no load

$V_{FL}$  = Voltage at full load

## Form Factor

$$F = \frac{\text{rms Value}}{\text{average Value}} = \frac{I_m/2}{I_m/\pi} = 1.57$$

## Peak Factor

$$\text{Peak Factor} = \frac{\text{Peak Value}}{\text{r.m.s value}} = \frac{V_m}{V_m/2} = 2$$

## TU F

$$\frac{2\sqrt{2}}{\pi^2} = 0.287$$





# Full Wave Rectifier

\* In full wave rectifier, both half cycle of the input are utilized with the help of two diodes working alternately.

\* Therefore in full wave rectifier circuit, current flows through load resistor in the same direction for both half cycles of input a.c voltage.

## Centre-Tap full wave rectifier

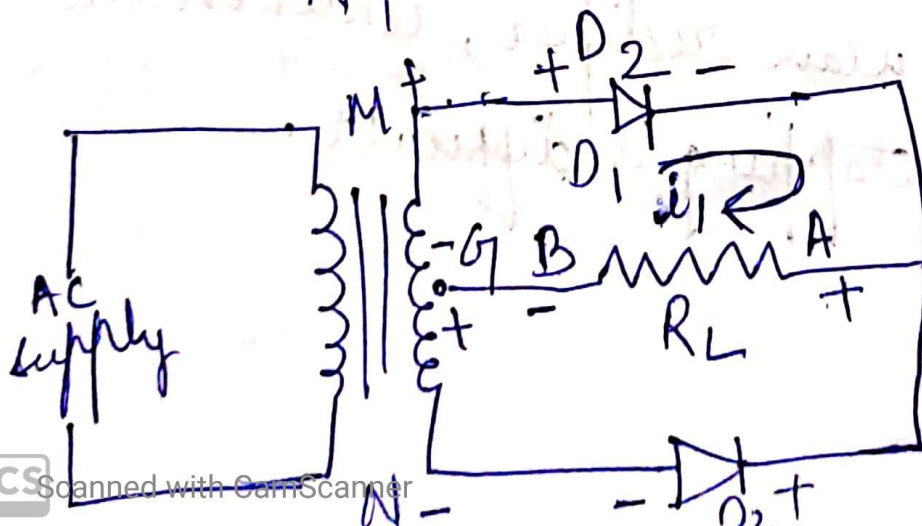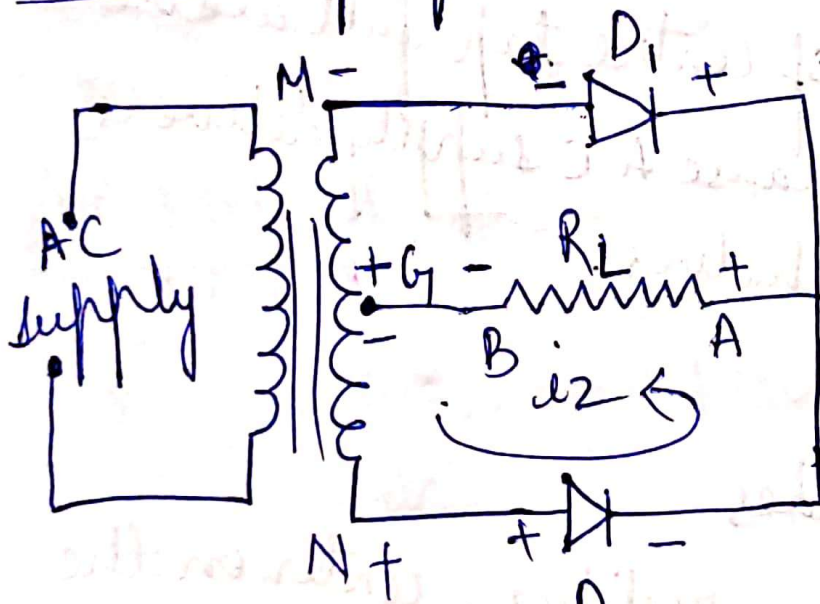

\* When 1/2 a.c supply is switched on, the ends M & N of the transformer secondary becomes positive & negative alternately.

\* During +ve half of a.c input; terminal N is positive and M is at -ve potential.

\* Now, diode  $D_1$  is forward biased i.e. it conducts and causes a current  $i_1$  in load resistor  $R_L$ .

\* Diode  $D_2$  remains non conducting being reversed biased.

\* During the -ve half cycle, terminal N becomes +ve and M becomes -ve.

\* During this cycle, diode  $D_2$  conducts and current  $i_2$  flows in the circuit through load resistor  $R_L$ . Diode  $D_1$  is non conducting.

### Advantages

\* The o/p and efficiency of centre tap full wave rectifier are high because A.C supply delivers power during both the halves.

### Disadvantages

\* It requires two diodes

\* In center tap full wave rectifier, center on the secondary winding for tapping is difficult.



## Analysis of centre tap full wave rectifier

### 1) o/p d.c current

$$I_{dc} = \frac{2I_m}{\pi}, \quad I_m = \text{peak value of o/p current}$$

### 2) DC o/p voltage

$$V_{dc} = \frac{2I_m R_L}{\pi}$$

### 3) RMS current

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

### 4) Efficiency

$$\eta = \frac{P_{dc}}{P_{ac}}$$

\* The efficiency of a full wave rectifier is 81.2%.

### 5) Ripple factor

$$\gamma = \sqrt{\left(\frac{I_{rms}}{I_{dc}} - 1\right)^2 - 1}$$

### 6) Form Factor

$$F = \frac{I_{rms}}{I_{dc}} = \frac{I_m/\sqrt{2}}{2I_m/\pi}$$



### 7) PIV

$$PIV = 2V_m$$

$V_m = \text{max}^m \text{ supply voltage.}$

### 8) TUF (Transformer Utilization Factor)


$$TUF = 0.573$$

### 9) Voltage Regulation

$$\frac{2V_m}{\pi} - I_{dc} R_f$$

$R_f = \text{Diode resistance in ON condition.}$

### Full Wave Bridge Rectifier

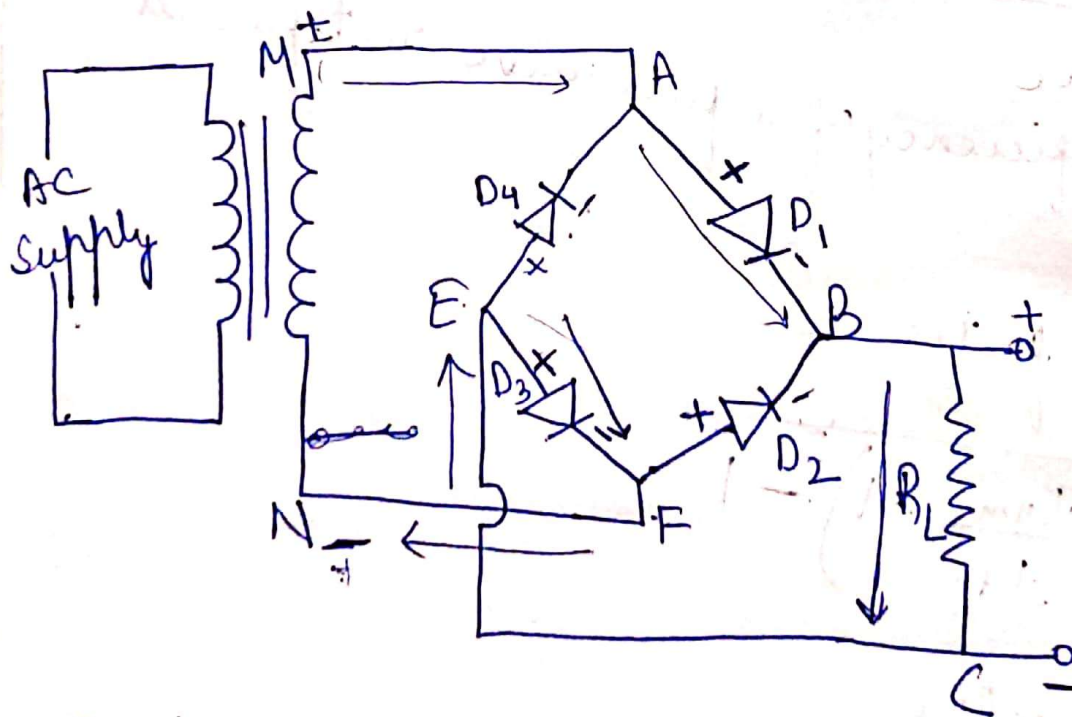


\* During +ve input half cycle, terminal M of the secondary of the transformer is +ve while the terminal N is negative. In this

situation diodes  $D_1$  &  $D_3$  are forward biased (ON position) i.e they conduct whereas diodes  $D_2$  &  $D_4$  are reverse biased (OFF position) i.e they do not conduct.

\* So current flows through M A B C E F N.

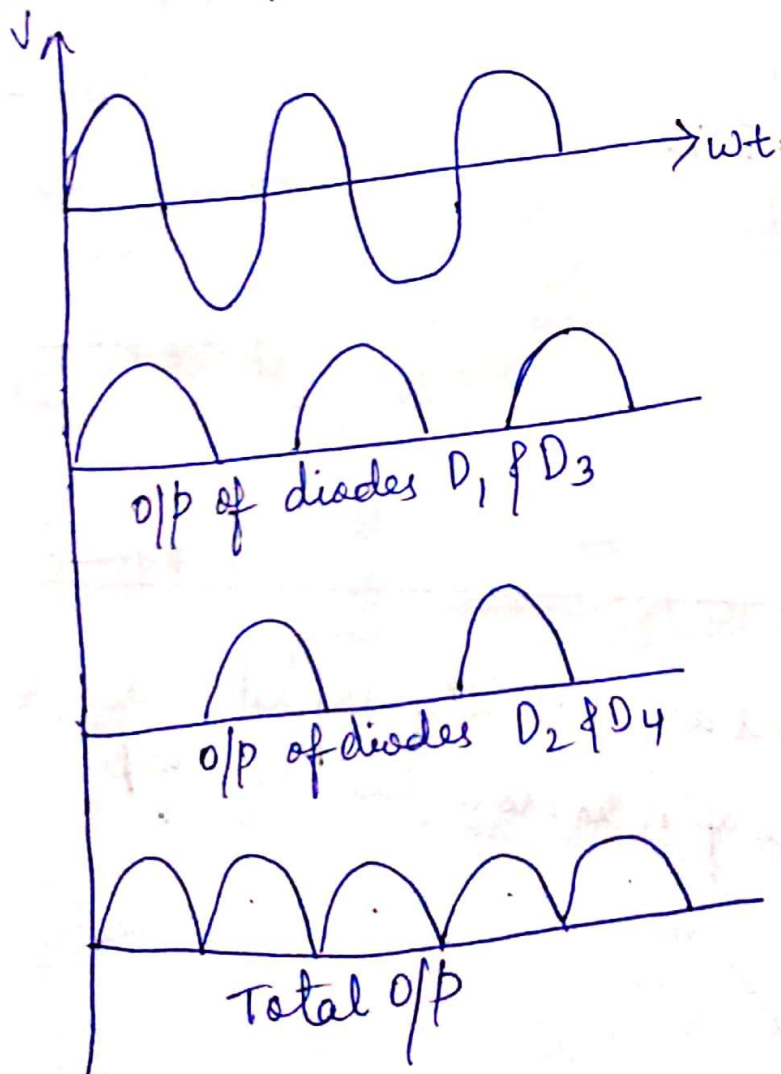\* During the -ve half cycle, terminal N of the secondary of transformer becomes +ve while the terminal M becomes -ve. Under this situation diodes  $D_2$  &  $D_4$  are forward biased (ON position) i.e they conduct whereas diodes  $D_1$  &  $D_3$  are reverse biased (OFF position) i.e they do not conduct. Now a current flows along N F B C E A M.





## Advantages

- \* No Centre-tap is required
- \* It is suitable for high voltage applications.
- \* It has less PIV rating per diode, because two diodes are present in series in each conduction path, PIV is equally shared by the two diodes.
- \* Current flows for the entire a.c cycle.

## Analysis of Bridge rectifier

$$* I_{dc} = \frac{2I_m}{\pi}$$

$$* V_{dc} = \frac{2V_m}{\pi}$$

$$* I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$* \text{Efficiency } \eta = 81.2\%$$

$$* r = 0.48$$

(Ripple factor)

$$* PIV = V_m$$

$$* TUF = 0.812$$




## Filters

\* It is a device that converts the pulsating output of a ~~rect~~ rectifier into a steady d.c level.


OR

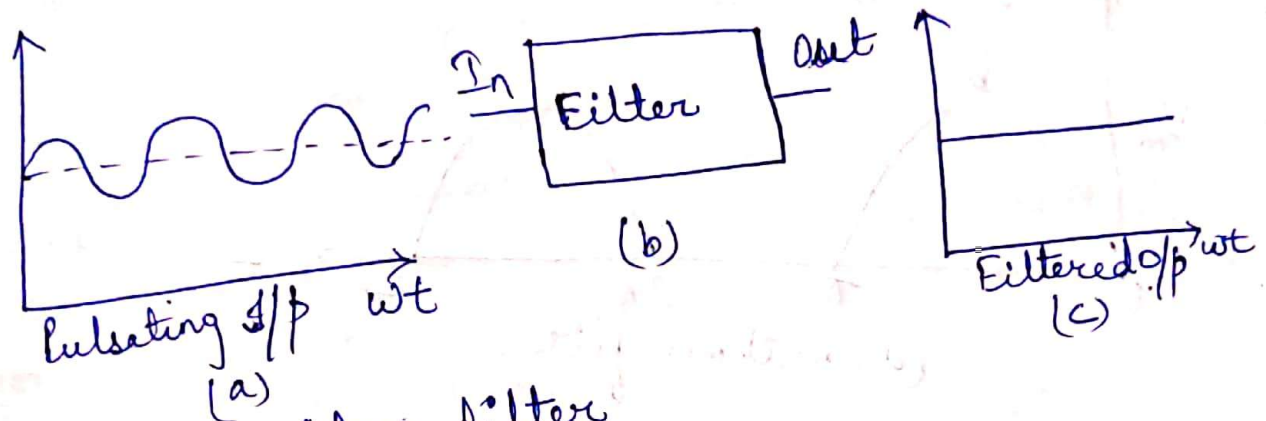\* It is a device which removes the a.c component of rectifier o/p but allows the d.c component to reach the load.



## Shunt Capacitor filter
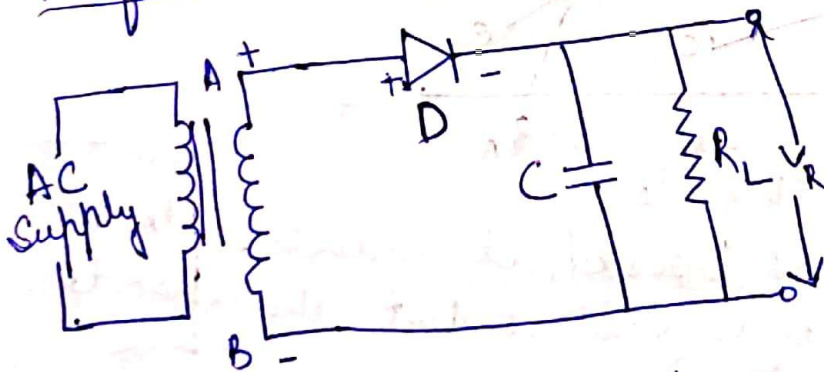
### Half wave rectifier with Capacitor filter



\* During +ve half cycle of a.c input, the diode D is forward biased and hence it conducts.

\* This quickly charges the condenser C to a voltage  $V_m$  because there is no resistance in the charging path except diode forward resistance which is negligible.


\* When the condenser is fully charged, it holds the charge till the input a.c supply to the rectifier goes negative.

\* During the -ve half cycle, the diode D is reverse biased, i.e. it does not conduct,  
 \* So, the capacitor C discharges through  $R_L$

\* During the next +ve half cycle, the capacitor voltage increases from point ~~from point~~. The process is then repeated.



(a) without filter

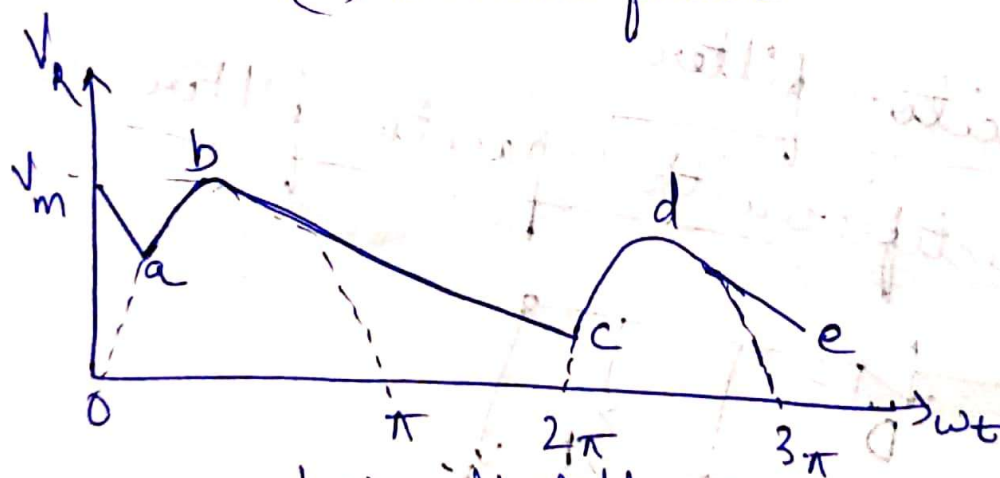


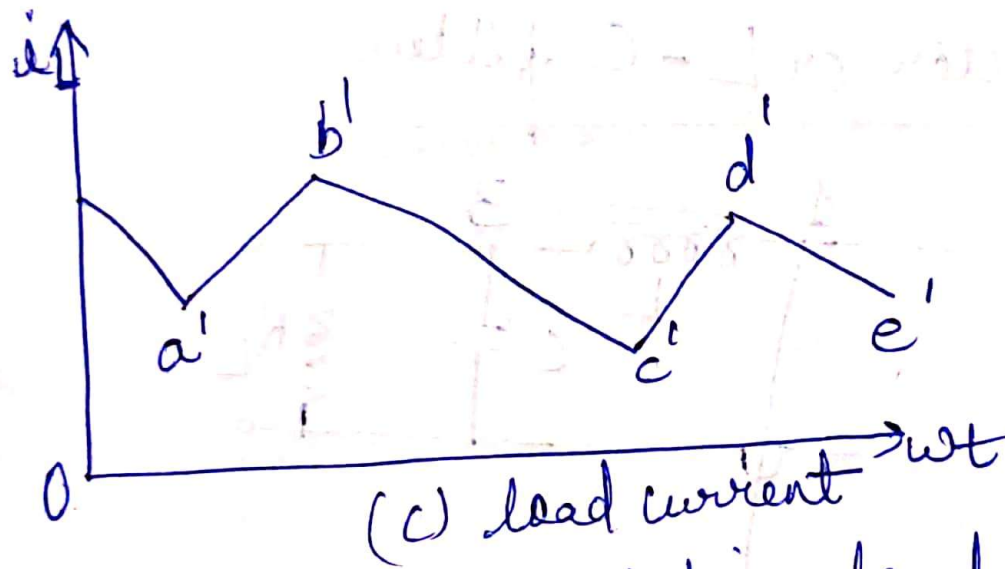(b) with filter.

\* when diode is forward biased, it conducts upto a point b and when it does not conduct, the capacitor starts discharging (b to c)

\* Again during next cycle the diode conducts (c to d) and during -ve cycle it does not conduct, the capacitor starts discharging (d to e)






\* In case of a purely resistive load, the wave shape is same as that of  $V_R$ .

\* During periods  $a'b'$  &  $c'd'$  the current is supplied by diode and during periods  $b'c'$  &  $d'e'$  the current is supplied by capacitor.

\* The instant at which conduction starts is called the cut-in point and the instant at which conduction stops is called the cut-out point.




## Choke Input filter or L-C filter

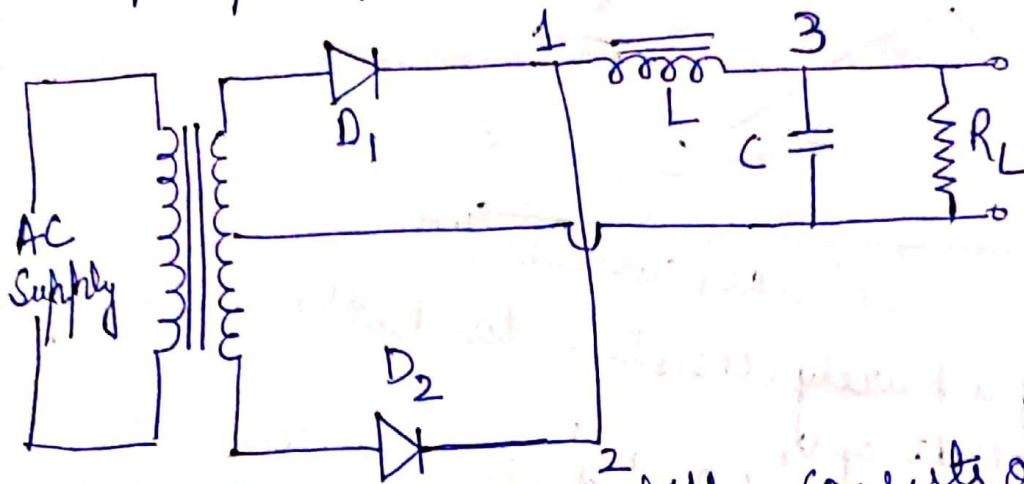


- \* Typical Choke input filter consists of a choke  $L$  connected in series with the rectifier output and a filter capacitor  $C$  across the load.
- \* The pulsating o/p of the rectifier is applied across terminals 1 & 2 of the filter circuit.
- \* The pulsating o/p of rectifier contains a.c & d.c components.
- \* The choke offers high opposition to the passage of a.c component but negligible opposition to the d.c component.
- \* The result is that most of the a.c component appears across the choke while whole of d.c component passes through the choke. This results in the reduced pulsations at terminal 3.
- \* At terminal 3, the rectifier o/p contains d.c component and the remaining part of a.c component which has managed to pass through the choke. The capacitor offers low reactance to a.c component and infinite reactance to d.c component. Therefore, d.c component reaches the load.



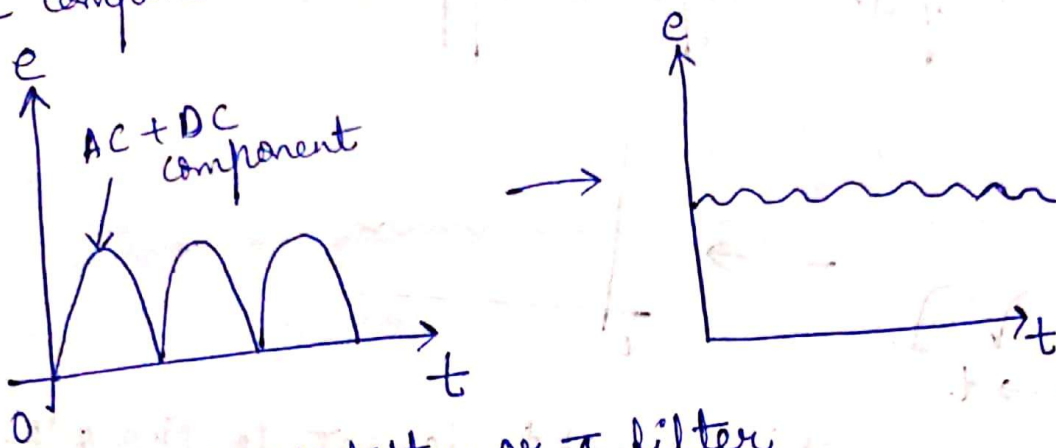\* In this way, the filter circuit has filtered out the a.c component from the rectifier o/p, allowing d.c component to reach the load.




Capacitor Input filter or  $\pi$  filter

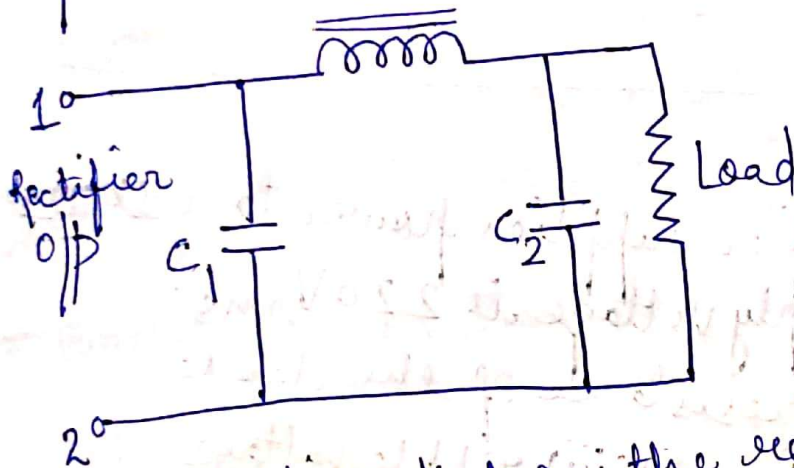

- \* The pulsating o/p from the rectifier is applied across the input terminals 1 & 2 of the filter.
- \* The filter capacitance  $C_1$  offers low reactance to a.c component of rectifier o/p while it offers infinite reactance to the d.c component. Therefore, capacitor  $C_1$  bypasses a.c component while the d.c component continues its journey to choke  $L$ .
- \* The choke  $L$  offers high reactance to the a.c component but it offers almost zero reactance to the d.c component. Therefore, it allows the d.c component to flow through it, while the unbypassed a.c component is blocked.

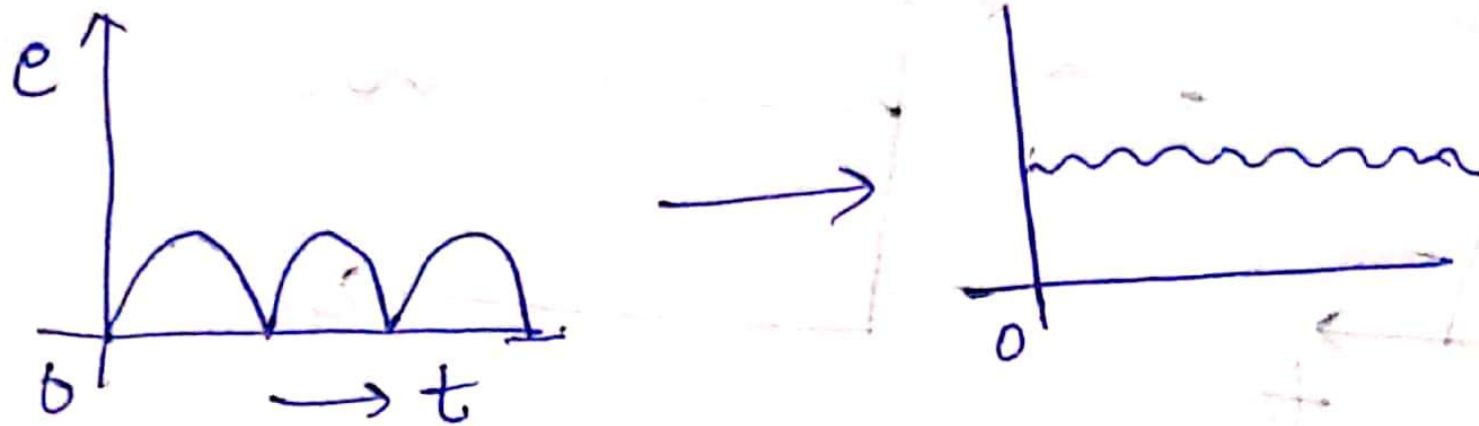\* The filter capacitor  $C_2$  bypasses the a.c component which the choke has failed to block. Therefore, only d.c component appears across the load.



Reactance  $\rightarrow$  opposition of a ckt element to the flow of current due to that element's inductance or capacitance.



## Bipolar Junction Transistor



A Transistor is commonly known Bipolar junction transistor. This is due to the fact that the current conduction in BJT is due to both types of charge carriers i.e., electrons and holes.

\* Bipolar junction transistor is a three terminal, two junction device.

\* A junction transistor is simply a sandwich of one type of semiconductor material between two layers of the other type. Accordingly, there are two types of transistors:

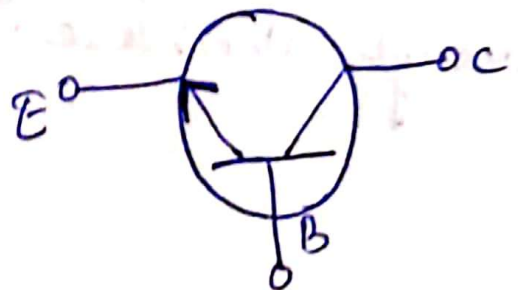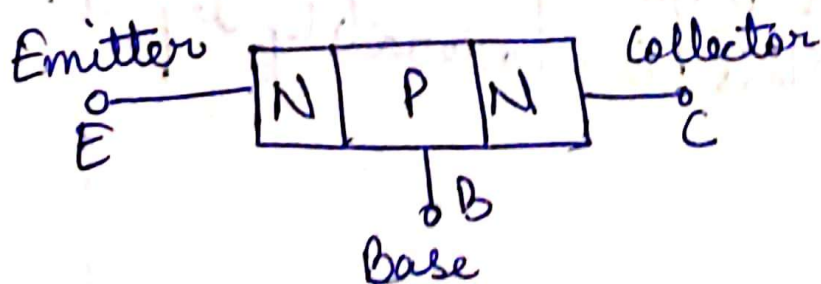
(1) N-P-N transistor and (2) P-N-P transistor.

\* When a layer of P-type material is sandwiched between two layers of N-type material, the transistor is known as N-P-N transistor.





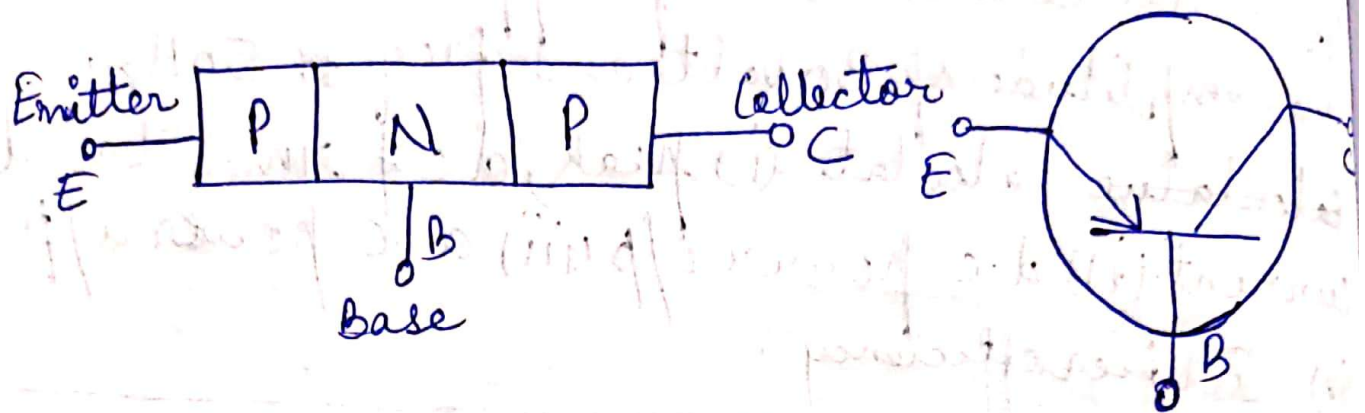\* When a layer of N-type material is sandwiched between two layers of P-type material, the transistor is known as P-N-P transistor.



A transistor has the following sections :-

- (i) Emitter → This forms the left hand section or region of the transistor. The main function of this region is to supply majority charge carriers (either holes or electrons) to the base and hence it is more heavily doped in comparison to other regions.
- (ii) Base → The middle section of the transistor is known as base. This is very lightly doped and is very thin as compared to either emitter or collector so that it may pass most of the injected charge carriers to the collector.
- (iii) Collector → The right hand section of the transistor is called as collector. The main function of the collector is to collect majority charge carriers through the base. This is moderately doped.



### Important points



\* The arrowhead is always at the emitter. The direction indicates the conventional direction of current flow i.e. in case of N-P-N transistor it is from base to emitter (base is positive with respect to emitter) while in case of P-N-P transistor it is from emitter to base (emitter is positive with respect to base).

\* The emitter is heavily doped because it has to supply the majority carriers. The collector is less heavily doped. The base is lightly doped.

\* In most of the transistors, the collector region is made physically larger than the emitter region. This is due to the fact that collector has to dissipate much greater power. Due to this difference collector and emitter are not interchangeable.
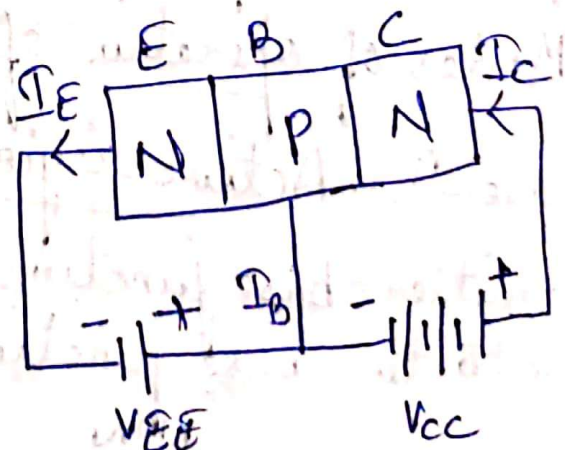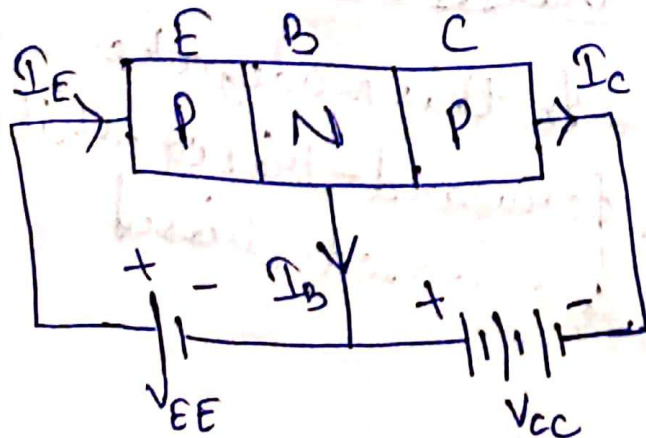
### Transistor biasing

\* The emitter-base junction is always forward-biased while the collector-base junction is always reverse-biased.





\* The emitter base junction of P-N-P transistor is forward-biased by connecting the positive terminal of  $V_{EE}$  to emitter and -ve terminal to base.

\* The emitter base junction of N-P-N transistor is forward biased by connecting the -ve terminal of  $V_{EE}$  to emitter and +ve terminal to base.


\* The collector-base junction of a P-N-P transistor is reverse-biased by connecting the -ve terminal of  $V_{CC}$  to collector while +ve terminal to base.

\* The collector-base junction of N-P-N transistor is reverse biased by connecting the +ve terminal of  $V_{CC}$  to emitter while -ve terminal to base.

\* In a transistor, a weak signal is introduced in low resistance circuit and the output is taken from the high resistance circuit.
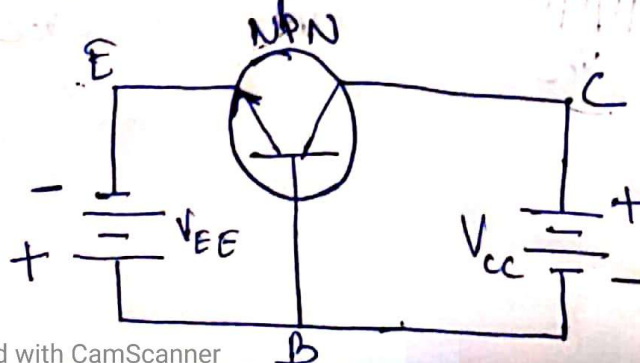
### Modes of operation of a transistor

Case-I → Active region → In this mode, the emitter-base junction is forward-biased while collector-base junction is reverse-biased.





\* In the emitter base circuit, a battery  $V_{EE}$  is connected such that -ve of the battery is connected to emitter while +ve is connected to base.


\* A battery  $V_{CC}$  is connected to collector-base circuit. +ve terminal of battery is connected to collector while -ve is connected to base.

\* In this region transistor is used for amplification.

Case - II → Saturation region → In this mode, emitter-base junction as well as collector base junction both are forward-biased.


\* The -ve of battery  $V_{EE}$  is connected to emitter and similarly the -ve of battery  $V_{CC}$  is connected to collector. The +ve terminals of both the batteries are connected to base.

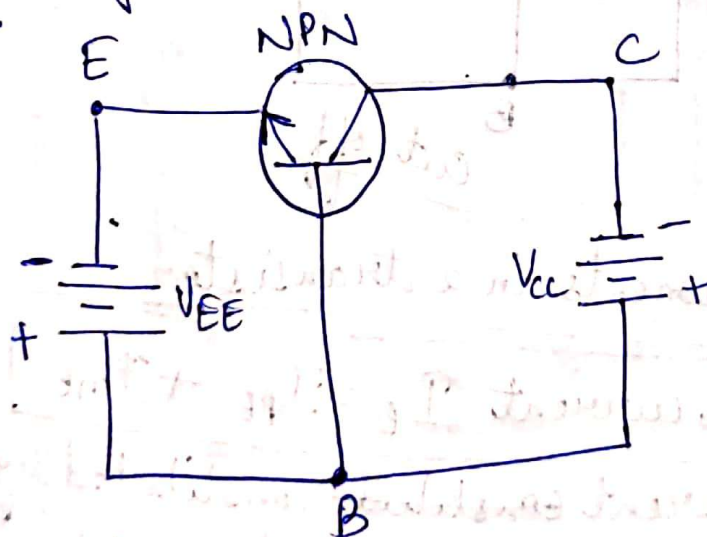\* In this region the transistor acts like a closed switch.




Case - III → Cut-off region → In this mode, both the junctions are reverse biased.

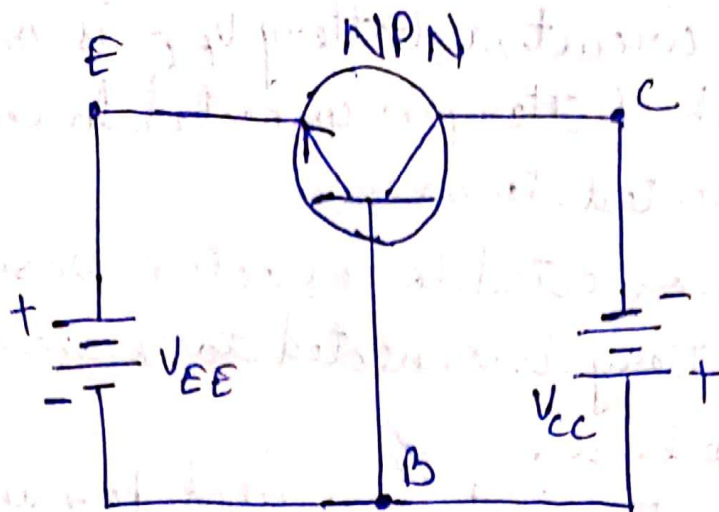\* In this region, the transistor has practically zero current because the emitter does not emit charge carriers to the base. In this situation, the transistor acts as open switch.



Case - IV - Inverted region → In this region, emitter-base junction is reverse-biased <sup>while</sup> ~~which~~ collector-base junction is forward-biased.

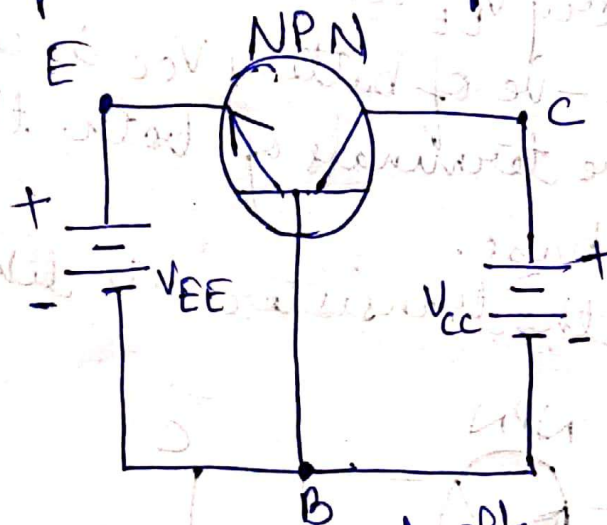\* In this region, the action of transistor is very poor.



cut-off

### Current components in a transistor

$$\boxed{\text{Total emitter current } I_E = I_{PE} + I_{NE}}$$

$I_{PE}$  = Hole current ~~constituted~~ constituted by holes (holes crossing from emitter into base)

$I_{NE}$  = Electron current constituted by electrons (electrons crossing from base into the emitter)



$$I_C = I_{PC} + I_{CO}$$


$I_{PC}$  → current caused by holes moving across collector junction  $I_C$  from N-region to P-region.

$I_{CO}$  → Reverse saturation current

Thus, for a PNP transistor

$$I_E = I_B + I_C$$

Transistor as an amplifier

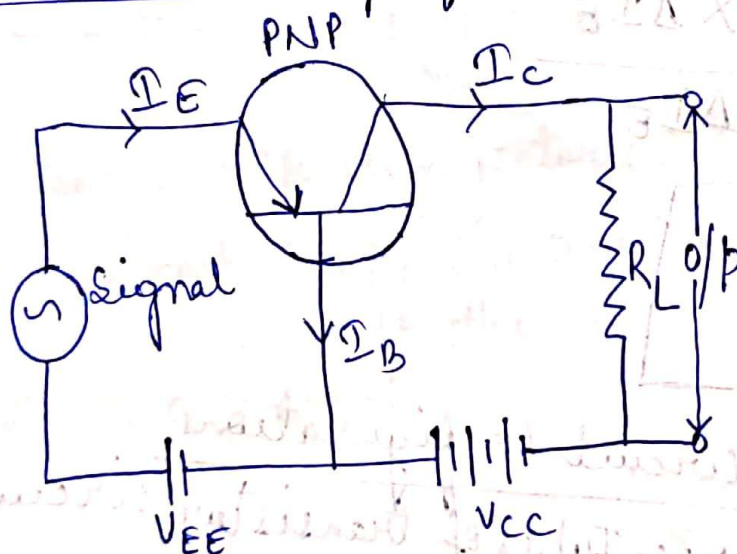

Let a small voltage change  $\Delta V_i$  between emitter and base causes a relatively large emitter-current change  $\Delta I_E$ .

\* We define by the symbol  $\alpha$  that fraction of this current change which is collected and passes through  $R_L$ . Thus

$$\alpha = \frac{\Delta I_C}{\Delta I_E} \quad \text{i.e.} \quad \Delta I_C = \alpha \cdot \Delta I_E$$

\* The Change in output voltage across the load resistor

$$\Delta V_o = R_L \times \Delta I_C$$

$$= R_L \times \alpha \times \Delta I_E$$

Under these circumstances, the voltage amplification

$$A = \frac{\Delta V_o}{\Delta V_i}$$


$$\Delta V_i = r_e \cdot \Delta I_E$$

$r_e$  = dynamic resistance of the emitter junction

$$A = \frac{R_L \times \alpha \times \Delta I_E}{r_e \cdot \Delta I_E}$$

$$r_e \cdot \Delta I_E$$

$$A = \frac{\alpha R_L}{r_e}$$

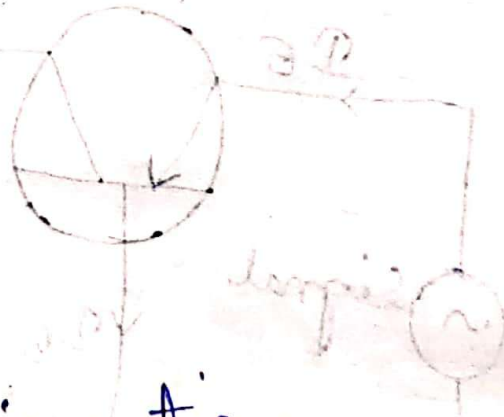

Transistor circuit configurations

There are three types of transistor circuit configurations:


- 1) Common base (CB)
- 2) Common emitter (CE)
- 3) Common collector (CC)


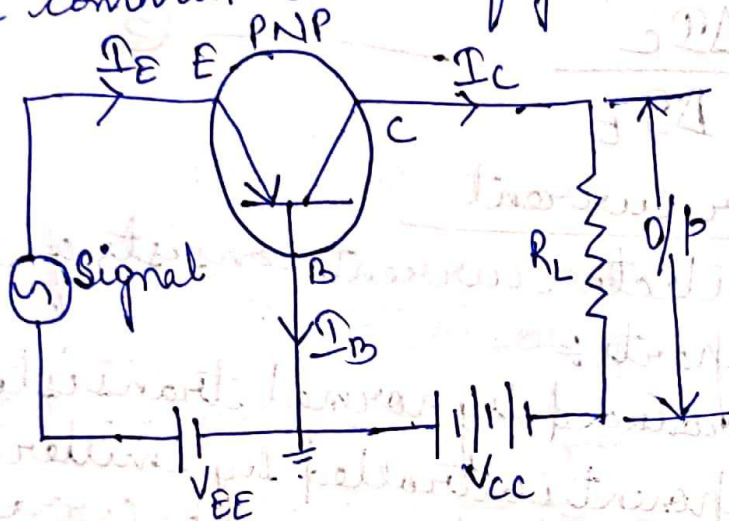
## Common-Base Configuration

\* In this configuration, the input signal is applied between emitter and base while the o/p is taken from collector and base.

\* As base is common to input and output circuits, hence common-base configurations



D.C current amplification factor ( $\alpha$ ) or d.c gain

→ When no signal is applied, then the ratio of the collector current to the emitter current is called  $\alpha_{dc}$  of a transistor

$$\alpha_{dc} = \frac{-I_C}{I_E}, \quad (-ve \text{ sign signifies that } I_E \text{ flows into transistor while } I_C \text{ flows out of it}).$$

$$\Rightarrow \boxed{\alpha = \frac{-I_C}{I_E}} \quad \text{--- ①}$$

From eq<sup>n</sup> ①

$$I_C = \alpha \cdot I_E$$

$$\Rightarrow I_B = I_E - I_C \Rightarrow I_B = I_E - \alpha I_E$$



$$\Rightarrow I_B = I_E (1 - \alpha) \quad \text{--- (2)}$$

### \*AC current gain

→ when signal is applied, the ratio of change in collector current to the change in emitter current at constant collector base voltage is defined as current amplification factor.

$$\alpha_{ac} = \frac{-\Delta I_C}{\Delta I_E} \quad \text{--- (3)}$$

### Total collector current

→ The total collector current consists of the following two parts:

- The current produced by normal transistor action i.e component controlled by emitter current. This is due to the majority carrier and its value is  $\alpha I_E$

- The leakage current. This current is due to the motion of minority carriers across base-collector junction on account of it being reverse-biased. The leakage current is abbreviated as  $I_{CBO}$  i.e collector-base current with emitter open.

### Total collector current

$$I_C = \underset{\text{Majority}}{\alpha I_E} + \underset{\text{minority}}{I_{CBO}} \quad \text{--- (4)}$$



$$I_C = \alpha(I_C + I_B) + I_{CBO}$$

$$I_C(1 - \alpha) = \alpha I_B + I_{CBO}$$


$$I_C = \left( \frac{\alpha}{1 - \alpha} \right) I_B + \left( \frac{1}{1 - \alpha} \right) I_{CBO} \quad \text{--- (5)}$$

The relation between  $\alpha$  &  $\beta$  is given by

$$\alpha = \frac{\beta}{1 + \beta}, \quad \beta = \frac{\alpha}{1 - \alpha}$$

$$I_C = \beta I_B + (1 + \beta) I_{CBO} \quad \text{--- (6)}$$

Common emitter configuration

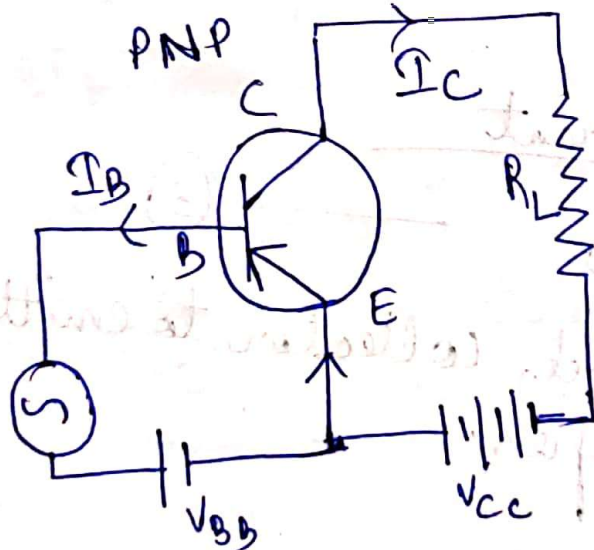

\* In this configuration, the input signal is applied between base and emitter and the output is taken from collector and emitter.

\* As emitter is common to input and o/p circuits hence the name common emitter.

## Base current amplification factor ( $\beta$ ) or d.c. current gain

\* When no signal is applied, then the ratio of collector current to base current is called ~~dc gain~~  $\beta_{dc}$  of a transistor.

$$\beta_{dc} = \beta = \frac{I_c}{I_B} \quad \text{--- (1)}$$

## A.C. current gain

\* When signal is applied, the ratio of change in collector current to the change in base current is defined as base current amplification factor.

$$\beta_{ac} = \beta_o = \frac{\Delta I_c}{\Delta I_B} \quad \text{--- (2)}$$

$$\Rightarrow I_c = \beta I_B$$

## Total collector current

$$I_c = \beta I_B + I_{CEO} \quad \text{--- (3)}$$

$I_{CEO}$  - leakage current, collector to emitter current with base open.

$$I_E = I_B + I_c$$

$$I_c = \alpha I_E + I_{CBO}$$

$$I_c = \alpha (I_B + I_c) + I_{CBO}$$

$$I_c (1 - \alpha) = \alpha I_B + I_{CBO}$$



$$I_C = \left( \frac{\alpha}{1-\alpha} \right) I_B + \frac{1}{1-\alpha} I_{CBO} \quad \text{--- (4)}$$

comparing eq<sup>n</sup> (3) & (4) we get

$$\beta = \frac{\alpha}{1-\alpha}, \quad I_{CEO} = \left( \frac{1}{1-\alpha} \right) I_{CBO} \quad \text{--- (5)}$$

substituting the value of  $I_{CEO}$  in eq<sup>n</sup> (3)

$$I_C = \beta I_B + \left( \frac{1}{1-\alpha} \right) I_{CBO}$$

$$I_C = \beta I_B + (\beta + 1) I_{CBO} \quad \text{--- (6)}$$

Relation between  $\alpha$  &  $\beta$

$$\alpha = \frac{I_C}{I_E}, \quad \beta = \frac{I_C}{I_B}$$

$$I_E = I_B + I_C \quad \text{or} \quad I_B = I_E - I_C$$

$$\beta = \frac{I_C}{I_E - I_C} = \frac{I_C / I_E}{1 - (I_C / I_E)}$$

$$\beta = \frac{\alpha}{1-\alpha} \quad \text{--- (7)}$$

~~cross~~ multiplying eq<sup>n</sup> (7), we get


$$\Rightarrow \beta(1-\alpha) = \alpha$$

$$\Rightarrow \beta - \beta\alpha = \alpha$$

$$\Rightarrow \beta = \alpha(1 + \beta)$$

$$\Rightarrow \alpha = \frac{\beta}{1 + \beta} \quad \text{--- (8)}$$

## Common Collector Configuration

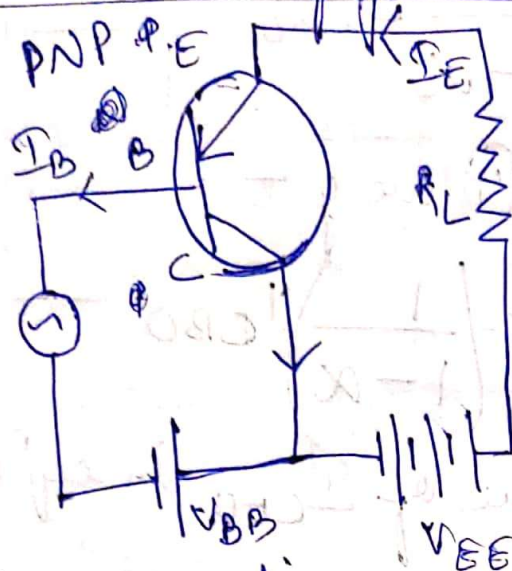

\* In this configuration, the input signal is applied between base & collector and the o/p is taken from emitter.

\* As collector is common to input and o/p circuits, hence, the name common collector configuration.

\* Current amplification factor ( $\gamma$ ) or d.c. current gain

\* When no signal is applied, then the ratio of emitter current to base current is called as  $\gamma_{dc}$  of the transistor

$$\gamma_{dc} = \gamma = \frac{I_E}{I_B} \quad \text{--- (1)}$$

### AC current gain

\* When signal is applied then the ratio of change in emitter current to the change in base current is known as current amplification factor

$$\gamma = \frac{\Delta I_E}{\Delta I_B} \quad \text{--- (2)}$$



### Total emitter current

$$I_E = I_B + I_C$$

$$\Rightarrow I_C = \alpha I_E + I_{CBO}$$

$$\Rightarrow I_E = I_B + (\alpha I_E + I_{CBO})$$

$$\Rightarrow I_E (1 - \alpha) = I_B + I_{CBO}$$

$$\Rightarrow I_E = \frac{I_B}{(1 - \alpha)} + \frac{I_{CBO}}{(1 - \alpha)}$$

$$\therefore \frac{1}{1 - \alpha} = (1 + \beta)$$

$$\Rightarrow \boxed{I_E = (1 + \beta) I_B + (1 + \beta) I_{CBO}} \quad \text{--- (3)}$$

### Relation between $\gamma$ and $\alpha$

$$\gamma = \frac{I_E}{I_B}, \quad \alpha = \frac{I_C}{I_E}$$

$$I_B = I_E - I_C$$

$$\gamma = \frac{I_E}{I_E - I_C} = \frac{1}{1 - (I_C / I_E)} = \frac{1}{1 - \alpha} \quad \text{--- (4)}$$

### Relation between $\gamma$ and $\beta$

$$\boxed{(1 - \alpha) = \frac{1}{(1 + \beta)}}$$

substituting this value in eq<sup>n</sup> (4)

$$\boxed{\gamma = \frac{1}{1 - \alpha} = (1 + \beta)} \quad \text{--- (5)}$$

# Transistor circuits

## \* Transistor Biasing

→ Among the basic functions of a transistor is amplification.

→ For faithful amplification, the following three conditions must be satisfied:-

(i) the emitter-base junction should be forward biased.

(ii) the collector-base junction should be reverse biased.

(iii) there should be proper zero signal collector current.

→ The proper flow of zero signal collector current and the maintenance of proper collector-emitter voltage during the passage of signal is known as transistor biasing.

→ A transistor is biased either with the help of battery or associating a circuit with the transistor.

→ The circuit used with the transistor is known as biasing circuit.

## \* Stabilisation

→ The maintenance of the stable operating point is known as stabilisation.

→ Stabilisation of the operating point is necessary due to the following reasons:-



(1) Temperature dependence of  $I_C$

(2) Individual variations

(3) Thermal runaway.

\* Temperature dependence of  $I_C$

→ The instability of  $I_C$  is principally caused by the following three sources :-

- The collector leakage current  $I_{CO}$  is greatly influenced by temperature changes. The  $I_{CO}$  doubles for every  $10^\circ\text{C}$  rise in temperature.

- Increase of  $\beta$  with increase of temperature.

- Variation of  $V_{BE}$  (base to emitter voltage) with temperature. Here it should be remembered that  $V_{CE}$  also changes with temperature but the change is very small. Hence  $I_C$  is almost independent of  $V_{CE}$ .

\* Individual Variations → when a transistor is replaced by another transistor of the same type the value of  $\beta$  and  $V_{BE}$  are not exactly the same. Hence, the operating point is changed. So, it is necessary to stabilise the operating point ~~irrespective~~ irrespective of individual variations in transistor parameters.

\* Thermal runaway → Depending upon the construct<sup>n</sup> of a transistor, the collector junction can withstand a max<sup>m</sup> temperature.


→ The increase in the collector junction temperature is due to thermal runaway.

→ When a collector current flows in a transistor it is heated i.e its temperature increases.

→ If no stabilization is done, the collector leakage current also increases. This further increases the transistor temperature. Consequently there is a further increase in collector leakage current.


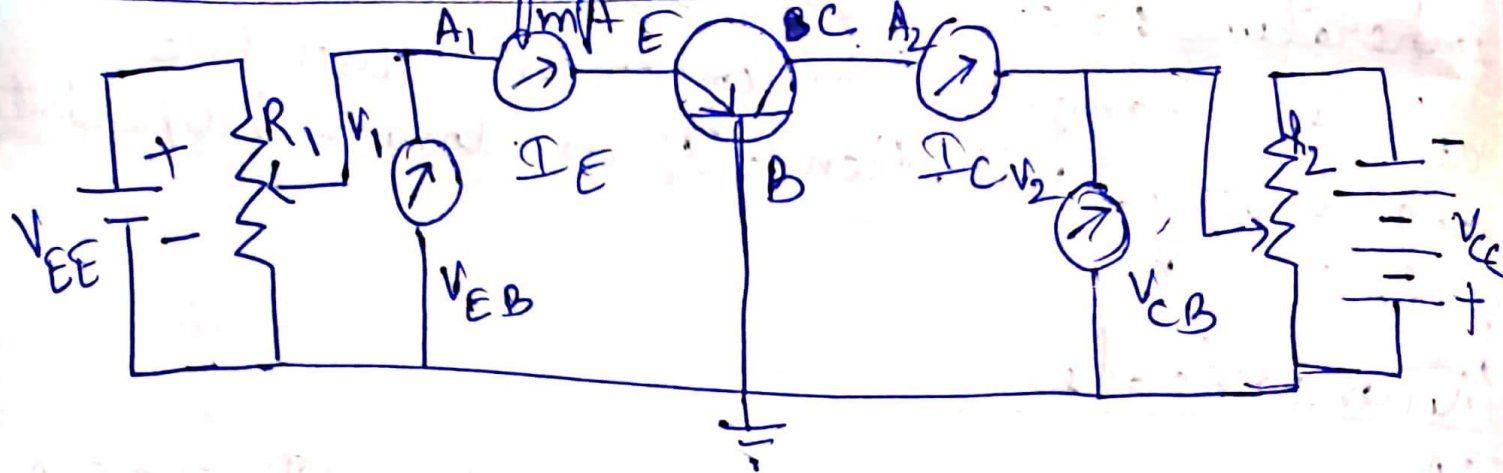
## Common Base Configuration Characteristics



\* The battery  $V_{EE}$  supplies forward bias to the emitter base junction through potential divider  $R_1$ .

\* Similarly, the battery  $V_{CC}$  supplies reverse bias to the collector base junction through potential divider  $R_2$ .

\* In the circuit, milliammeters are connected in series with emitter and collector to measure emitter current  $I_E$  and  $I_C$  respectively.

\* Similarly, voltmeters are connected in parallel across  $E$  &  $B$  to measure the voltage  $V_{EB}$  and across  $C$  &  $B$  to measure the voltage  $V_{CB}$  respectively.

\* Here, the quantities emitter to base voltage  $V_{EB}$  & emitter current  $I_E$  correspond to input circuit and collector to base voltage  $V_{CB}$  and collector current  $I_C$  to the o/p ckt.

### Input Characteristics


\* The curve between  $I_E$  &  $V_{EB}$  at constant  $V_{CB}$  represents i/p characteristics.

\* For plotting the i/p characteristics, the  $V_{CB}$  is kept fixed,  $V_{EB}$  is varied with the help of potential divider  $R_1$  and the emitter current is noted for each value of  $V_{EB}$ .

\* The following points are noted from the characteristics:-

→ There exists a cut in, offset or threshold voltage  $V_{EB}$  below which the emitter current is very small.

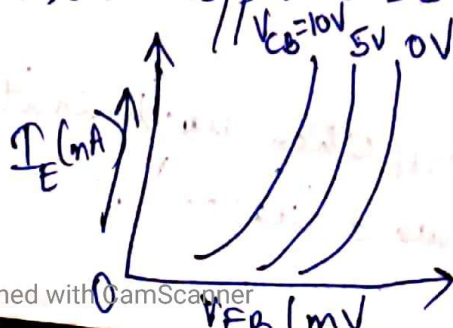→ The emitter current  $I_E$  increases rapidly with small increase in emitter-base voltage  $V_{EB}$ . This shows that i/p resistance is very small.





## Output Characteristics

\* The curve between collector current  $I_C$  and collector base voltage  $V_{CB}$  at constant emitter current  $I_E$  represents o/p characteristics.

\* For plotting o/p characteristics, the emitter current  $I_E$  is kept fixed. With the help of potential divider  $R_2$ , the value of  $V_{CB}$  is varied in steps and the collector current  $I_C$  is noted for each value of  $V_{CB}$ .

\* Following points are noted from the characteristics

(i) In the active region (when the collector junction is reverse biased and emitter junction is forward biased), the collector current is essentially independent of collector voltage and depends only upon the emitter current. Because  $\alpha$  is less than, but almost equal to unity, the magnitude of collector current is slightly less than that of the emitter current.


(ii) Although  $I_C$  is practically independent of  $V_{CB}$  over the work.

(ii) In the cut off region (when emitter & collector junction both are reverse-biased), a small amount of collector current flows ~~also~~ even when emitter current  $I_E = 0$ . This is the collector leakage current  $I_{CBO}$ .

(iii) In the saturation region (when both emitter & collector junctions are forward biased), the



## Common emitter Configuration

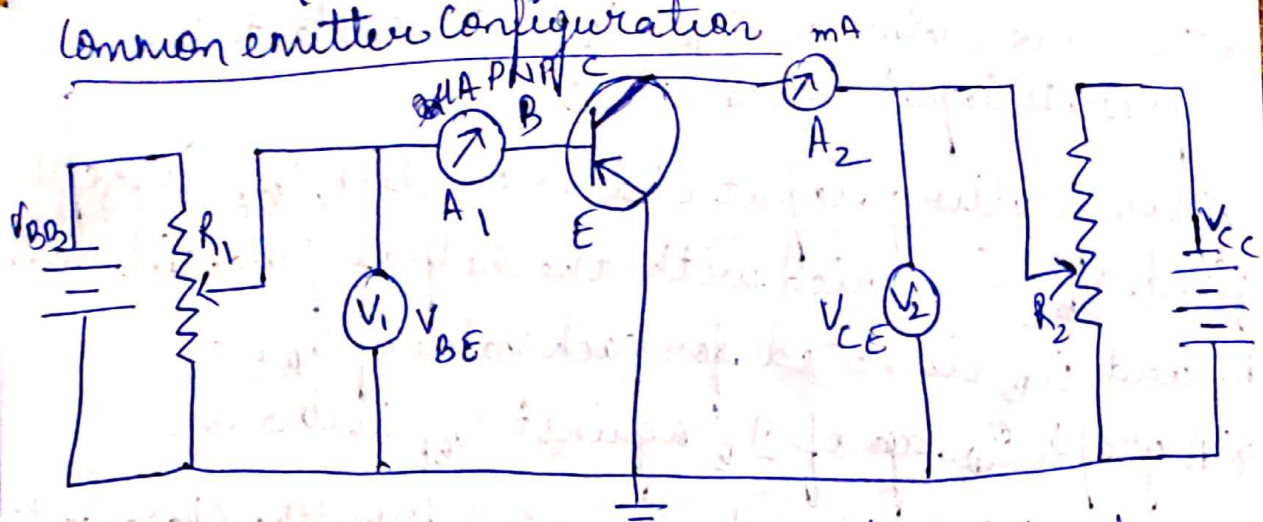

\* In the circuit, the battery  $V_{BB}$  provides forward bias to emitter-base junction with the help of potential divider  $R_1$ .

\* The voltmeter  $V_1$  measures the base-emitter voltage  $V_{BE}$ .


\* The microammeter  $A_1$  measures the base current  $I_B$ .

\* A battery  $V_{CC}$  is connected between collector and emitter through potential divider  $R_2$ .

\* The +ve terminal of the battery is connected to emitter while -ve terminal is connected to the collector so that the collector is reverse biased.

\* The voltmeter  $V_2$  measures the collector-emitter voltage  $V_{CE}$  and the milliammeter  $A_2$  measures the collector current.

## Input Characteristics

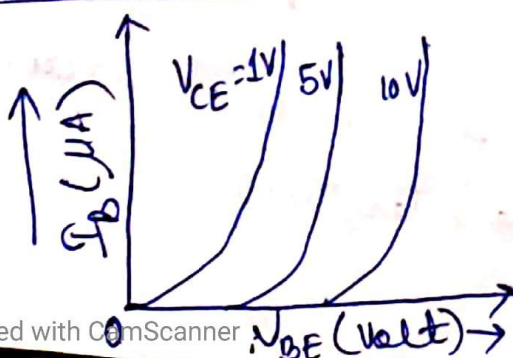



\* The curve between  $I_B$  &  $V_{BE}$  at constant  $V_{CE}$  represents input characteristics.

\* For plotting input characteristics,  $V_{CE}$  is kept fixed.  $V_{BE}$  is varied with the help of potential divider  $R_1$  and  $I_B$  is noted for each value of  $V_{BE}$ .

\* A graph ~~of~~ of  $I_B$  against  $V_{BE}$  is drawn.

\* The following points are noted from the characteristics  
→ The characteristics resembles that of a forward biased diode curve.

→ In this case,  $I_B$  increases less rapidly with  $V_{BE}$  as compared to common base configuration.

This shows that the i/p resistance of common-emitter circuit is higher than that of common-base circuit.

Input Resistance  $r_{i1}$  → The ratio of change in ~~base current~~  $V_{BE}$  to the resulting change in  $I_B$  at constant  $V_{CE}$ .

$$r_{i1} = \left. \frac{\Delta V_{BE}}{\Delta I_B} \right|_{V_{CE} = \text{constant}}$$

Output Characteristics → \* The curve between  $I_C$  and  $V_{CE}$  at constant  $I_B$  represents o/p characteristics.

\* For plotting o/p characteristics,  $I_B$  is kept fixed. With the help of potential divider  $R_2$ , the value of  $V_{CE}$  is varied and the  $I_C$  is noted for each value of

$V_{CE}$ .

\* A graph of  $I_C$  against  $V_{CE}$  is drawn. The curve obtained is known as o/p characteristics.



\* Following points are noted :-

→ In the active region, for small values of  $I_B$ , the effect of collector voltage over  $I_C$  is small while for large base current values this effect increases. The shape of characteristics is same as in common base configuration but with the difference that collector current is larger than  $I_B$ .

→ When  $V_{CE}$  has very low value, the transistor is said to be saturated and it operates in the saturation region. In the saturated region, the change in  $I_B$  does not produce a corresponding change in  $I_C$ .

→ When  $V_{CE}$  is allowed to increase too far, collector-base junction completely breaks down and due to this avalanche breakdown, collector current increases rapidly. In this case, transistor is damaged.

→ In the cut off region, a small amount of collector current flows even when base current  $I_B = 0$ . This is called  $I_{CEO}$ .

o/p resistance -  $r_o = \left. \frac{\Delta V_{CE}}{\Delta I_C} \right|_{I_B = \text{constant}}$

CB configuration

$r_i = \left. \frac{\Delta V_{EB}}{\Delta I_E} \right|_{V_{CB} = \text{constant}}$

$r_o = \left. \frac{\Delta V_{CB}}{\Delta I_C} \right|_{I_E = \text{constant}}$



## \*Stability Factor

→ The stability factor  $S$  is defined as the rate of change of  $I_C$  with respect to the reverse saturation current  $I_{CO}$ , keeping  $\beta$  &  $V_{BE}$  constant

$$S = \frac{\Delta I_C}{\Delta I_{CO}}$$

### Stability factor for common base configuration

$$I_C = \alpha I_E + I_{CO} \quad \text{--- (1)}$$

Differentiating eq<sup>n</sup> (1) we get

$$\frac{dI_C}{dI_{CO}} = 0 + 1$$

$$\frac{dI_C}{dI_{CO}} = 1$$

$$\frac{dI_C}{dI_{CO}} = 1$$

$$\Rightarrow \boxed{S = 1}$$

### Stability factor for common emitter configuration


$$I_C = \beta I_B + (1 + \beta) I_{CO}$$

$$\frac{dI_C}{dI_B} \frac{dI_B}{dI_{CO}} = (1 + \beta)$$

$$\boxed{S = 1 + \beta}$$

# \* Different methods for transistor biasing

## → Base resistor method / Fixed bias

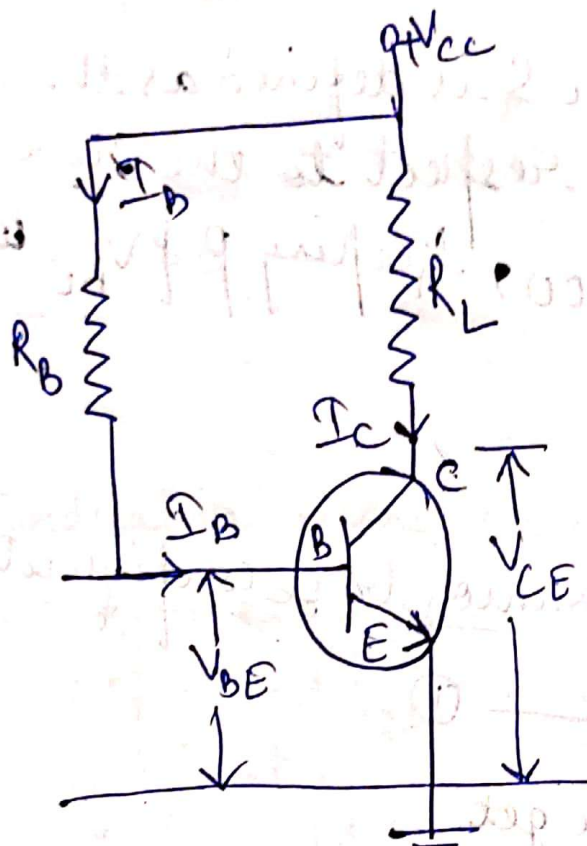

Acc to Kirchhoff's voltage law

$$V_{CC} = I_B R_B + V_{BE}$$

$$R_B = \frac{V_{CC} - V_{BE}}{I_B}$$


$$\Rightarrow I_B = \frac{I_C}{\beta}$$

$$\Rightarrow R_B = \frac{(V_{CC} - V_{BE}) \beta}{I_C}$$

Stability factor  $S = 1 + \beta$



## Collector to base bias

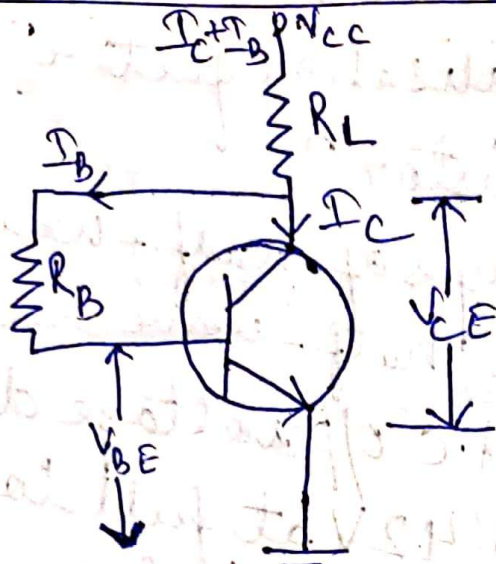

\* This circuit is same as base bias ~~ex~~ except that base resistor  $R_B$  is returned to collector rather than to  $V_{CC}$ .

### Circuit analysis

$$\text{Voltage drop across } R_L = (I_C + I_B) R_L \approx I_C R_L$$

$$V_{CC} = I_C R_L + I_B R_B + V_{BE}$$

$$\Rightarrow R_B = \frac{V_{CC} - I_C R_L - V_{BE}}{I_B}$$


$$\frac{I_B}{I_C} = \frac{1}{\beta}$$

$$R_B = \frac{(V_{CC} - I_C R_L - V_{BE}) \beta}{I_C}$$

## Stability factor

$$S = \frac{1 + \beta}{1 + \beta \left( \frac{R_L}{R_L + R_B} \right)}$$

## Voltage divider bias

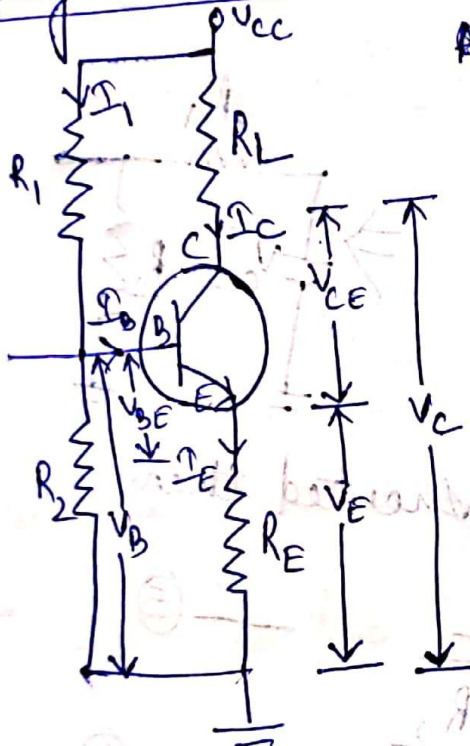

## Circuit analysis

Let us assume  $I_1$  flows through  $R_1$ . As the base current  $I_B$  is very small the current flowing through  $R_2$  can also be taken as  $I_1$ .

The calculation of  $I_C$  is as follows:-

$$I_1 = \frac{V_{CC}}{R_1 + R_2} \quad \text{--- (1)}$$

The voltage  $V_2$  developed across  $R_2$  is given by

$$V_2 = \left( \frac{V_{CC}}{R_1 + R_2} \right) R_2 \quad \text{--- (2)}$$

Applying KVL to the base circuit

$$V_2 = V_{BE} + I_E R_E$$

$$V_2 = V_{BE} + I_C R_E$$

$$I_C = \frac{V_2 - V_{BE}}{R_E} \quad \text{--- (3)}$$




Collector emitter voltage can be calculated as;  
Applying KVL to the collector side

$$V_{CC} = I_C R_L + V_{CE} + I_E R_E$$

$$= I_C R_L + V_{CE} + I_C R_E$$

$$\Rightarrow V_{CE} = V_{CC} - I_C (R_L + R_E) \quad \text{--- (4)}$$


circuit analysis using thevenin theorem

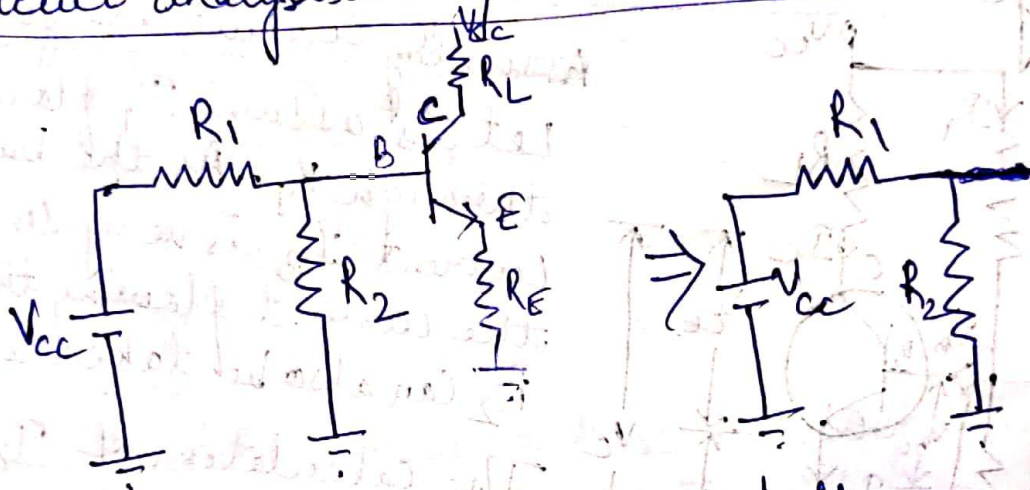

If voltage source is shorted then

$$R_{th} = (R_1 \parallel R_2) = \frac{R_1 R_2}{R_1 + R_2} \quad \text{--- (5)}$$
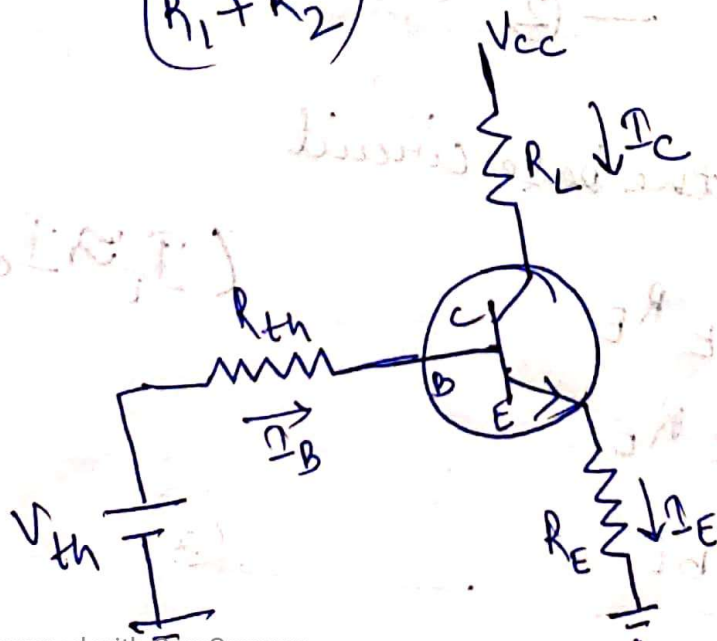
$$V_{th} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} \quad \text{--- (6)}$$



Applying KVL to the base emitter circuit

$$V_{th} = I_B R_{th} + V_{BE} + I_E R_E$$
$$= I_B R_{th} + V_{BE} + (I_B + I_C) R_E \quad \text{--- (7)}$$

Applying KVL to emitter-collector circuit

$$V_{CC} = I_C R_L + V_{CE} + (I_B + I_C) R_E$$

$$V_{CE} = V_{CC} - I_C (R_L + R_E) \quad \text{--- (8)}$$

From eq<sup>n</sup> (8)

$$I_C = \frac{V_{CC} - V_{CE}}{R_L + R_E}$$

substituting value of  $I_C$  in eq<sup>n</sup> (7) we have

$$V_{th} = I_B R_{th} + V_{BE} + \left( I_B + \frac{V_{CC} - V_{CE}}{R_L + R_E} \right) R_E$$

$$V_{th} = I_B R_{th} + V_{BE} + I_B R_E + \frac{V_{CC} R_E}{R_L + R_E} - \frac{V_{CE} R_E}{R_L + R_E} \quad \text{--- (9)}$$

Stability factor

$$\frac{R_B}{R_E} = \frac{(S-1)(1+\beta)}{(1+\beta-S)}$$




# Advantages and disadvantages of RC coupled amplifier

## Advantages

- Excellent frequency response
- Very Compact circuit
- Cheaper in Cost
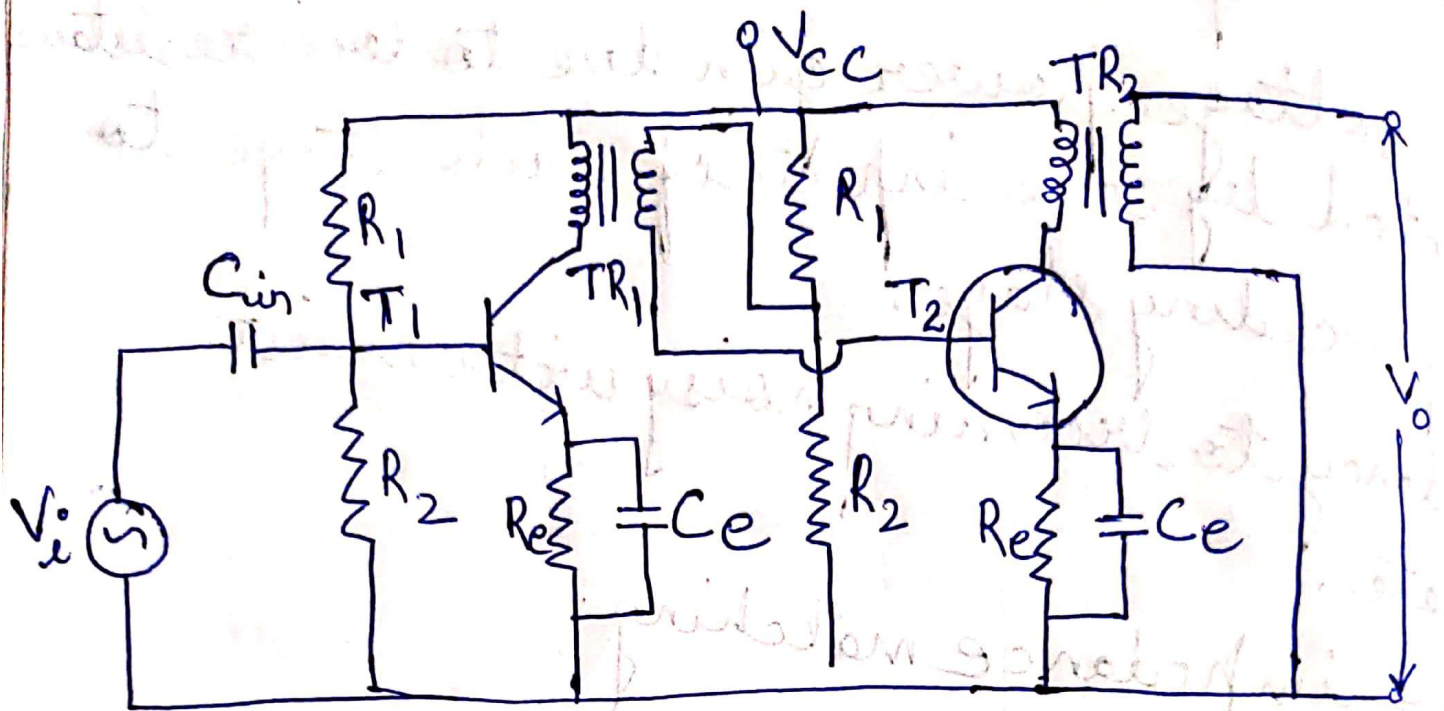
## Disadvantages

- Low voltage power gain due to low resistance presented by the input of each stage to the preceding stage.
- Tendency to becoming noisy with moist climate.
- Poor impedance matching.



\* A Coupling transformer  $TR_1$  is used to feed the output of first stage to the input of next stage.

\* The collector load is replaced by primary winding of the transformer.

\* The secondary is connected between base of the second stage and voltage divider i.e., the secondary of transformer gives input to the next stage.



- \* The transformer  $TR_2$  is the output transformer. The other components are same as in R-C coupled amplifier.
- \* There is no coupling capacitor. The d.c isolation between the two stages is provided by the transformer itself.
- \* When the input is applied to the base of transistor  $T_1$ , it is amplified and appears across the primary of transformer  $TR_1$ .
- \* By magnetic induction, it is passed to the secondary of the transformer.
- \* Now, the output is applied to the base of transistor  $T_2$ . The amplified output appears across the primary of the transformer  $TR_2$ .

### Advantages

- \* The absence of resistor  $R_L$  in the collector circuit eliminates the unnecessary power loss in the resistor.
- \* The operation of a transformer coupled system is more efficient because of low d.c.
- \* Due to excellent impedance matching, the transformer coupling provides higher gain.




## Disadvantages

- \* It has poor frequency response
- \* The coupling transformer is bulky and costly.

## Feedback Amplifiers

Feedback - The process of combining a fraction of output energy back to the input is known as feedback.

### General theory of feedback

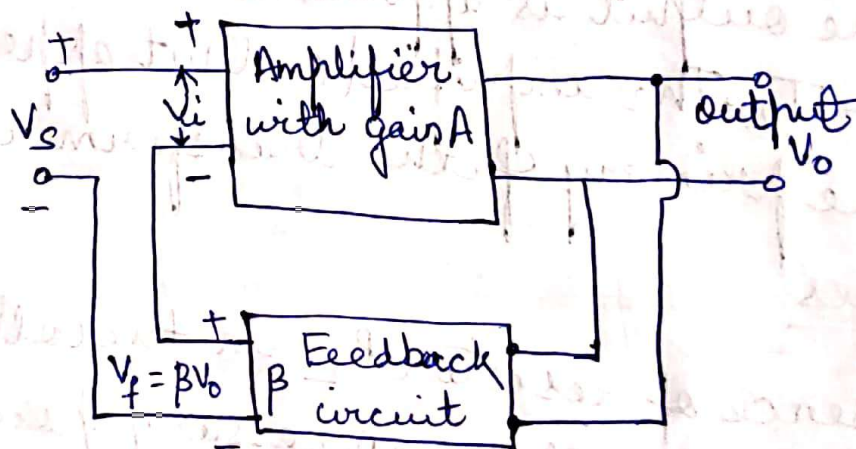

- \* The feedback amplifier has two parts i.e. amplifier and feedback circuit.
- \* The feedback circuit usually consists of resistors.
- \* This returns a fraction (say  $\beta$ ) of the output voltage back to the input.



\* Let  $A$  be the gain of the amplifier i.e. the ratio of output voltage  $V_o$  to the input voltage  $V_i$ . This is the gain of the amplifier without feedback.

\* The feedback network extracts a voltage  $V_f = \beta V_o$  from the output  $V_o$  of the amplifier.

\*  $V_i = V_s + V_f = V_s + \beta V_o$  (Positive feedback)

\*  $V_i = V_s - V_f = V_s - \beta V_o$  (Negative feedback)

\* The quantity  $\beta = V_f / V_o$  is called as feedback ratio or feedback fraction.

\* Consider the case of negative feedback. The output  $V_o$  must be equal to the input voltage  $(V_s - \beta V_o)$  multiplied by the gain  $A$ .

$$*(V_s - \beta V_o)A = V_o$$

$$\Rightarrow AV_s - A\beta V_o = V_o$$

$$\Rightarrow AV_s = V_o (1 + A\beta)$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{A}{1 + A\beta}$$

\* Let  $A_f$  be the overall gain of the amplifier. This is defined as the ratio of output voltage  $V_o$  to the applied signal voltage  $V_s$ .

$$A_f = \frac{\text{output voltage}}{\text{Input voltage}} = \frac{V_o}{V_s}$$


$$* A_f = \frac{A}{1 + A\beta} \quad (\text{For negative feedback})$$

$$* A_f = \frac{A}{1 - A\beta} \quad (\text{For positive feedback})$$

\* Consider the following three cases

- For negative feedback  $A_f < A$
- For positive feedback  $A_f > A$

Negative feedback circuit

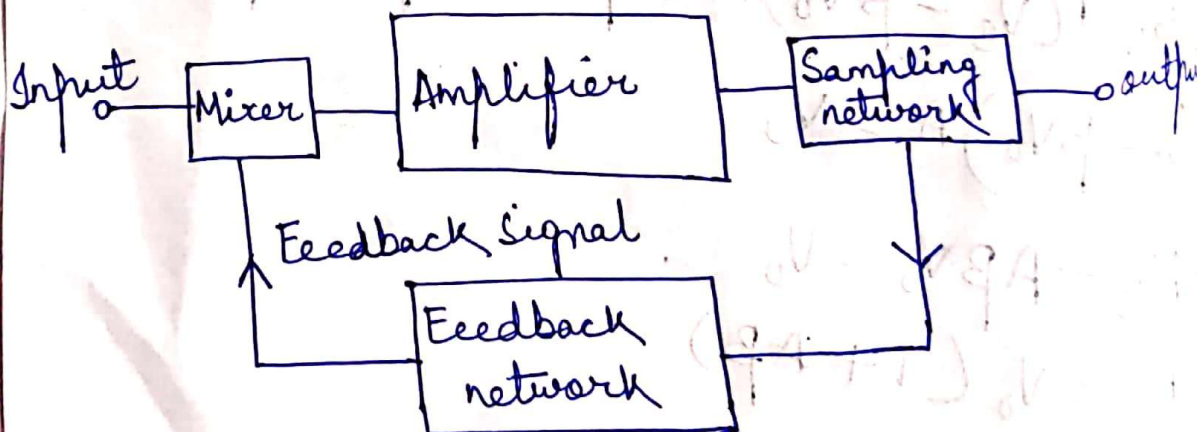

\* When the feedback signal is out of phase with the input signal and thus opposes it then the feedback is called negative feedback



\* The negative feedback amplifier introduces a phase shift of  $180^\circ$  in the input while the feedback network introduces no phase shift.

\* There are two types of negative feedback circuits i.e

(a) Negative voltage feedback - In this method, the voltage feedback to the input of amplifier is proportion to the output voltage. This is further classified into following two categories:

- (i) Voltage-series feedback
- (ii) Voltage-shunt feedback

(b) Negative current feedback - In this method, the voltage feedback to the input of the amplifier is proportional to output current. This is further classified into following two categories:

- (i) Current-series feedback
- (ii) Current-shunt feedback



## Advantages of negative feedback

- (i) Stabilization of gain
- (ii) Reduction in distortion
- (iii) Reduction in noise
- (iv) Change in input impedance
- (v) Change in output impedance
- (vi) Increase in bandwidth.

## Power amplifier

\* The power amplifiers are large signal amplifiers which raise the power level of the signals. It is a device which converts d.c power to a.c power and whose action is controlled by the input signal.

\* On the basis of the mode of operation, the power amplifiers may be classified as


- (i) Class A power amplifier
- (ii) Class B power amplifier
- (iii) Class C power amplifier



## Difference between voltage amplifier and power amplifier

| Characteristic    | Voltage amplifier    | Power amplifier                         |
|-------------------|----------------------|---|
| $\beta$           | high                 | low                                     |
| $R_C$             | high                 | low                                     |
| Input voltage     | low                  | high                                    |
| Power output      | low                  | high                                    |
| Collector current | low                  | high                                    |
| output impedance  | high                 | low                                     |
| Coupling          | usually R-C coupling | invariably transformer or tuned circuit |

# Transformer coupled class A amplifier

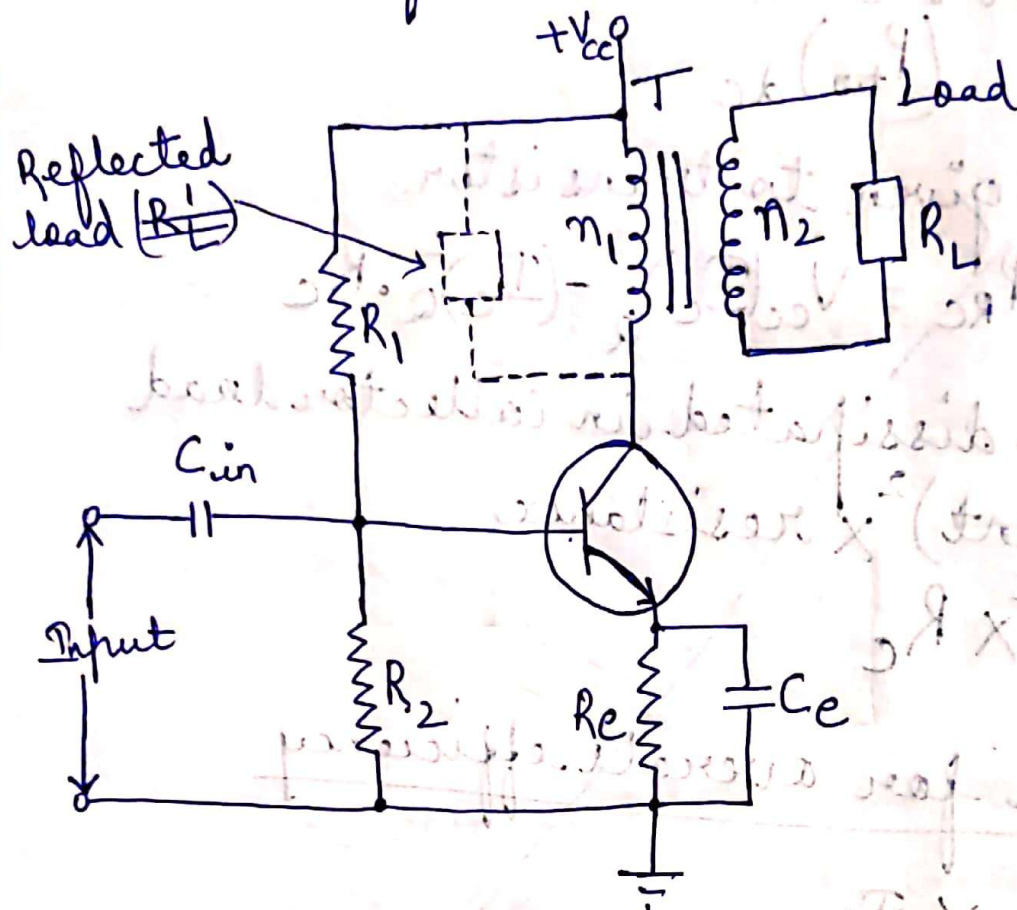

$R_L' =$  effective input resistance

$$= \frac{V_1}{I_1}$$

$R_L =$  effective output resistance

$$= \frac{V_2}{I_2}$$

$$R_L' = \left( \frac{n_1}{n_2} \right)^2 R_L = n^2 R_L$$

$$n = \frac{\text{number of turns in primary}}{\text{number of turns in secondary}} = \frac{n_1}{n_2}$$



$$(\eta)_{\text{collector}} = \frac{(P_o)_{ac}}{(P_{tr})_{dc}} \quad , \quad (P_{tr})_{dc} = V_{cc} \times (I_c)_Q$$

$$(P_o)_{ac} = V_{rms} \times I_{rms} = \frac{V_{cc}}{\sqrt{2}} \times \frac{(I_c)_Q}{\sqrt{2}}$$

$$V_{rms} = \frac{1}{\sqrt{2}} \left[ \frac{(V_{ce})_{\max} - (V_{ce})_{\min}}{2} \right] = \frac{1}{\sqrt{2}} \left[ \frac{(V_{ce})_{\max}}{2} \right]$$


$$= \frac{2V_{cc}}{2\sqrt{2}} = \frac{V_{cc}}{\sqrt{2}}$$

$$I_{rms} = \frac{1}{\sqrt{2}} \left[ \frac{(I_c)_{\max} - (I_c)_{\min}}{2} \right] = \frac{1}{\sqrt{2}} \left[ \frac{(I_c)_{\max}}{2} \right]$$

$$= \frac{2(I_c)_Q}{2\sqrt{2}} = \frac{(I_c)_Q}{\sqrt{2}}$$

$$(\eta)_{\text{collector}} = \frac{V_{cc} \times (I_c)_Q}{2 \times V_{cc} \times (I_c)_Q} = \frac{1}{2} = 50\%$$

# Class-A push pull amplifier

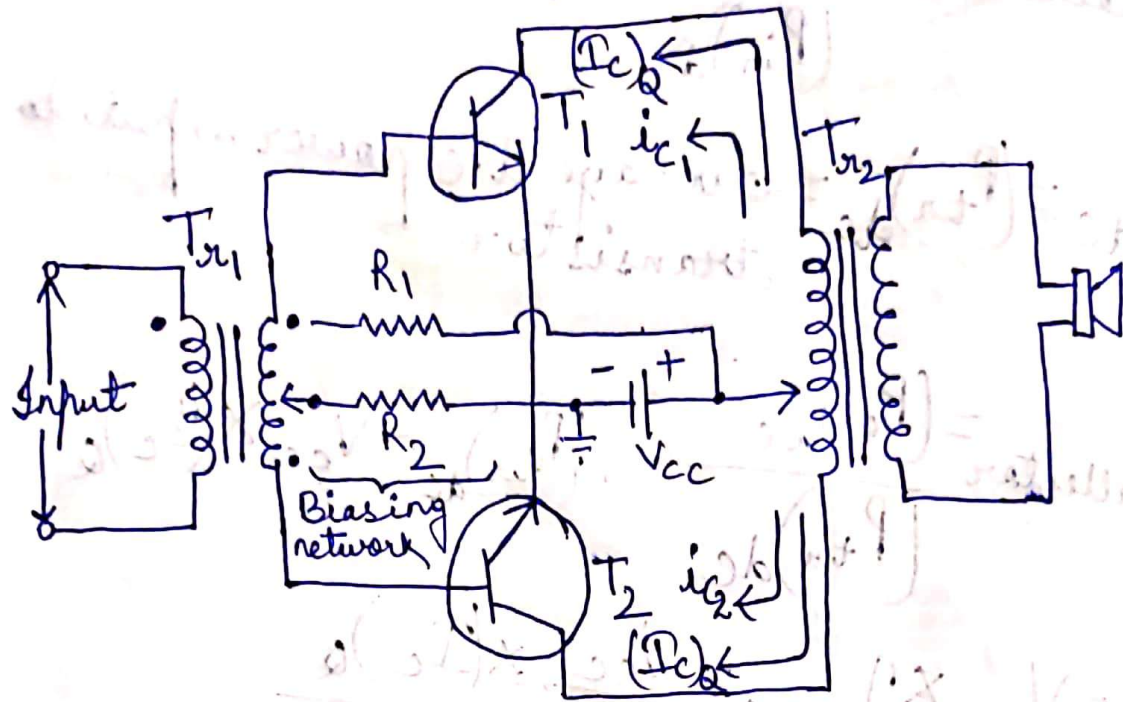

## Circuit arrangement

\* Two identical transistors  $T_1$  and  $T_2$  are used. The emitter terminals of the two transistors are connected together.

\* The input signal is applied to the inputs of two transistors through centre tapped transformer,  $T_{r1}$ . This transformer provides opposite polarity signals to the two transistor inputs.

\* The collectors of both the transistors are connected to the primary of output transformer  $T_{r2}$ .

\* The collector terminals of the two transistors are connected to the supply  $V_{cc}$  through the primary of output transformer.



\* Resistors  $R_1$  &  $R_2$  provide biasing arrangement  
circuit operation

\* The two transistors  $T_1$  &  $T_2$  carry d.c components of collector currents  $(I_C)_Q$ . These currents are equal in magnitude and flow in opposite directions through the primary of transformer  $T_2$ .

\* When the input signal voltage is positive, the base of transistor  $T_1$  is more positive while the base of transistor  $T_2$  is less positive.  
\* Hence the collector current  $i_{C1}$  of transistor  $T_1$  increases while the collector current  $i_{C2}$  of transistor  $T_2$  decreases.

\* These currents flow in opposite directions in two halves of the primary of output transformer.

\* Similarly, for the negative input signal, the collector current  $i_{C2}$  will be more than  $i_{C1}$ .

\* The voltage developed across the load will again be due to the difference  $(i_{C2} - i_{C1})$ .

\* The difference of two collector currents is


$$i_{C1} - i_{C2} = i_{C1} + (-i_{C2})$$

\* It is obvious that during any given half cycle of input signal, one transistor is



being driven (or pushed) into conduction while the other being non-conducting (pulls out). Hence, the name push-pull amplifier.

### Class B push-pull amplifier

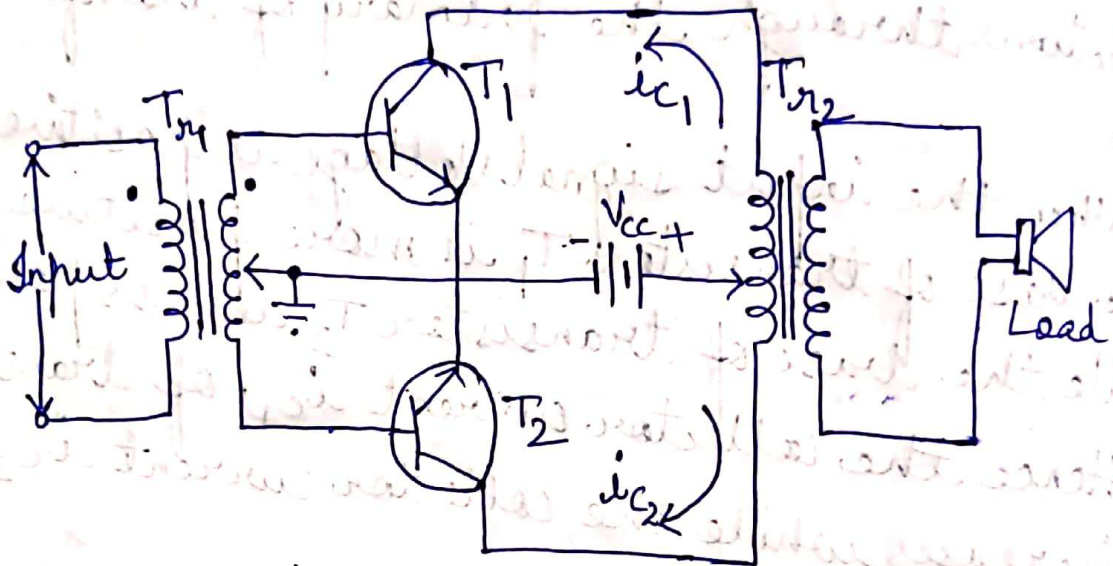

### Circuit operation

\* When no signal is applied, both the transistors are cut-off. Hence, no current is drawn from supply source  $V_{cc}$ .

\* When the input signal is applied, the transformer  $T_1$  produces two signals which are  $180^\circ$  out of phase with each other.

\* The transistors  $T_1$  and  $T_2$  are driven by these two signals.

\* During positive half cycle of the signal, transistor  $T_1$  conducts because its base is driven positive. Now, collector current  $i_{c1}$  flows.



\* Transistor  $T_2$  does not conduct because its base is negative. Thus,  $i_{C2}$  is zero.

\* During negative half of the input signal, transistor  $T_2$  conducts and allows a current  $i_{C2}$  to flow, while transistor  $T_1$  becomes non-conducting.

### Oscillators

\* An Oscillator is a device which generates an alternating voltage. It may also be defined as a circuit which generates an a.c. output signal without requiring any externally applied input signal.

#### Types of oscillators

\* According to the nature of generated waveform:-

(i) Sinusoidal or harmonic oscillator - The oscillators which produce sinusoidal or nearly a sinusoidal waveform of a definite frequency are known as sinusoidal oscillators.

(ii) Relaxation or non-sinusoidal oscillator → The oscillators which produce square waves, triangular waves, pulses or sawtooth waves are known as relaxation oscillators.



\* According to the frequency of generated signals

(i) Audio frequency oscillators → The oscillators which generate signals in the audio frequency range are known as audio frequency oscillators.

(ii) Radio frequency oscillator → The oscillators which generate signals in the radio frequency range are called radio frequency oscillators.

\* Sinusoidal oscillators may be further subdivided into following categories:-

(i) Tuned circuits or LC feedback oscillators -  
Oscillators using tuned circuits are known as LC feedback oscillators. Ex - Tuned collector, Harley, Colpitts etc.


(ii) RC phase shift oscillators → Oscillators using RC network are known as RC phase shift oscillators. Ex - phase shift oscillator and Wein-bridge oscillator.



(iii) Negative resistance oscillator  $\rightarrow$  The oscillators which use an active device that possesses a current voltage characteristic curve of negative slope within some range of operation are known as negative resistance oscillators. Ex - tunnel diode oscillator.

(iv) Crystal oscillators  $\rightarrow$  When piezoelectric crystals are used in place of LC circuit for higher frequency stability, the oscillators are called as crystal oscillators.

\* Essentials of transistor oscillator

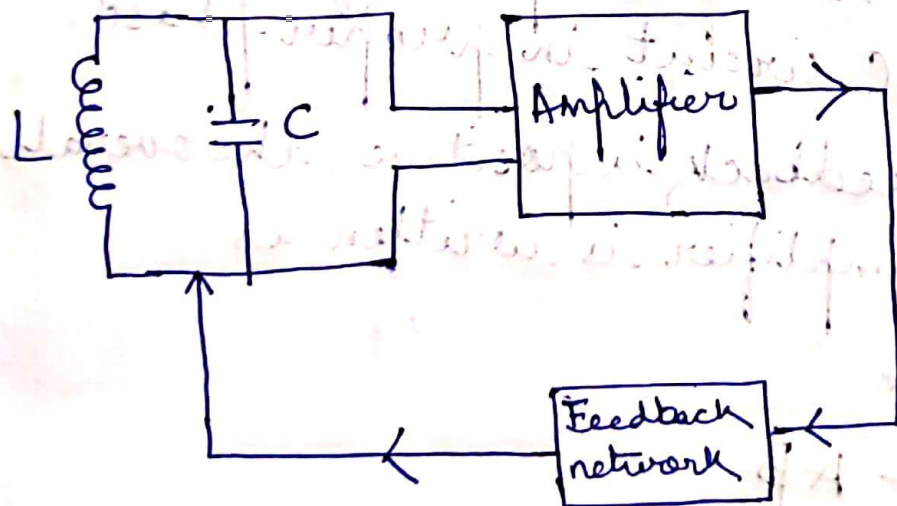

(i) Tank circuit  $\rightarrow$  The tank circuit consists of an inductance L connected in parallel with capacitor C. It is known as frequency determining network. The frequency of



Oscillations in the circuit depends upon the values of inductance and capacitance.

(ii) Transistor amplifier → The function of the amplifier is to amplify the oscillations produced by LC circuits. The amplifier receives d.c power from battery and converts it into a.c power for supplying to the tank circuit. The oscillations produced in tank circuit are applied to the input of the transistor. The transistor increases the output of these oscillations.

(iii) Feedback circuit → The function of feedback circuit is to transfer a part of the output energy to LC circuit in proper phase.

When the feedback is positive, the overall gain of the amplifier is written as

$$A_f = \frac{A}{1 - AB}$$

$AB$  = feedback factor or loop gain.

\* If  $AB = 1$ ,  $A_f = \infty$ . Thus the gain becomes infinity i.e. there is output without any




input. The condition  $AB = 1$  is known as Barkhausen criterion of oscillation.

### Barkhausen criterion of oscillation

It states that:-

- 1) The total phase shift around the loop, as the signal proceeds from input through amplifier, feedback network and back to input again, is precisely  $0^\circ$  or  $360^\circ$ .
- 2) The magnitude of the product of the open loop gain of amplifier  $A$  and feedback factor  $\beta$  is unity i.e.  $AB = 1$ .

### Tuned collector oscillator

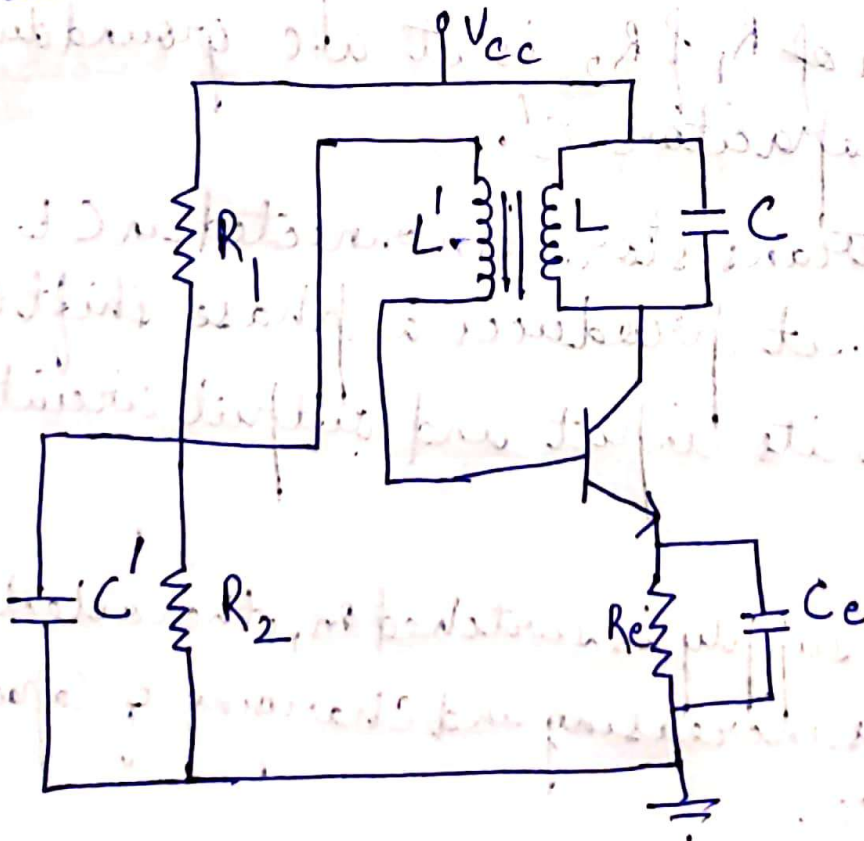

\* The Capacitance  $C$  and  $L$  form the tank circuit. As the tank circuit is connected in the collector circuit, the oscillator is known as tuned collector oscillator.

\* The resistors  $R_1$ ,  $R_2$  and  $R_e$  are used to d.c bias of the transistor.

\* Capacitors  $C_e$  &  $C'$  are bypass capacitors. They bypass resistances  $R_e$  and  $R_2$  respectively so that they have no effect on the a.c operation of the circuit.

\* The secondary of the transformer provides a.c feedback voltage. The feedback voltage appears across base-emitter junction because the junction of  $R_1$  &  $R_2$  is at a.c ground due to bypass capacitor  $C'$ .

\* As the transistor is connected in CE configuration, it produces a phase shift of  $180^\circ$  between its input and output circuits.

### Working

\* When the supply is switched on, the collector current starts increasing and charging of capacitor  $C$  takes place.




\* When the capacitor is fully charged, it discharges through inductance  $L$ . Now, oscillations are produced.

\* These oscillations induce some voltage in inductance  $L'$  by mutual induction. The frequency of voltage in  $L'$  is the same as that of tank circuit and its magnitude depends upon the number of turns in  $L'$  and coupling between  $L$  and  $L'$ .

\* The voltage induced causes corresponding variations in base current. These variations in  $I_B$  are amplified  $\beta$  times and appear in collector circuit.

\* A part of the amplified energy is used to overcome the losses of tank circuit and rest is radiated in the form of electromagnetic waves.

## Hartley oscillator

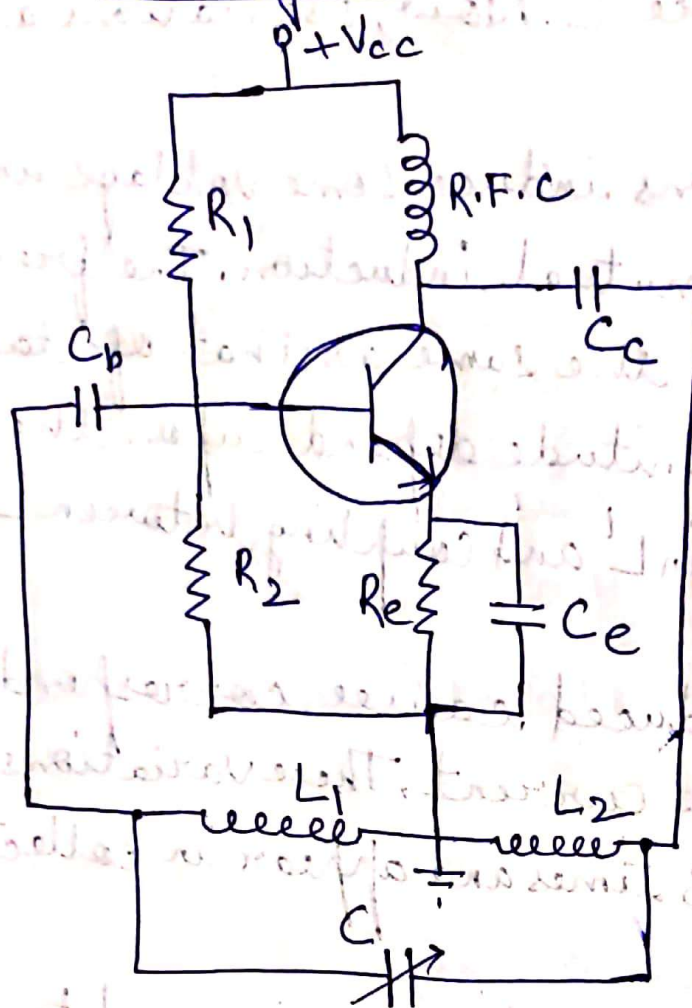

\* Hartley oscillator is very popular and is commonly used as a local oscillator in radio receivers.

\* The resistors  $R_1$ ,  $R_2$  and  $R_e$  provide necessary bias conditions for the circuit.

\* Capacitor  $C_e$  provides a.c ground thereby preventing any signal degeneration.

\* The Radio Frequency Choke (R.F.C.) offers very high impedance to high frequency currents i.e. acts like a d.c. short and a.c. open. Thus, it provides d.c. load for collector and keeps a.c. currents out of d.c. supply source.



\* The function of  $C_c$  and  $C_b$  to block d.c. and to provide an a.c. path.

\* The frequency determining network is a parallel resonant circuit consisting of inductors  $L_1$  &  $L_2$  and variable capacitor  $C$ .

### Working

\* When the collector supply voltage is switched on, a transient current is produced in the tank circuit. The oscillatory current in the tank circuit produces a.c. voltage across  $L_1$ .

\* In this way a feedback between output and input circuits is accomplished.


\* So, there is a phase reversal of  $180^\circ$  between output and input.

\* The common-emitter amplifier also produces a further  $180^\circ$  phase shift between input and output voltages.

\* Thus, total phase shift becomes  $360^\circ$ . This makes the feedback positive which is the essential condition for oscillations.



## Colpitt's oscillator

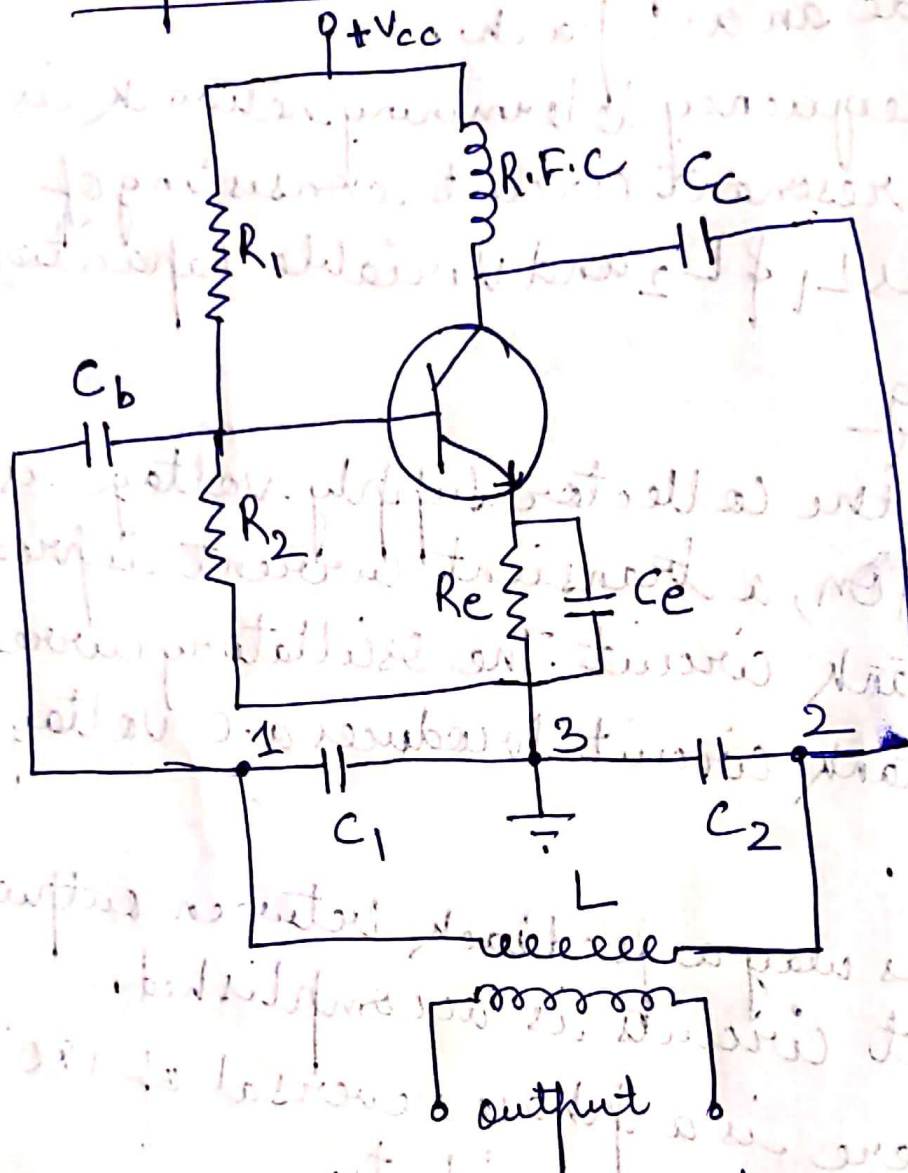

\* The frequency determining network is a parallel resonant circuit consisting of capacitors  $C_1$  and  $C_2$  and the inductor  $L$ .

### Working

\* When the collector supply voltage is switched on, a transient current is produced in the tank circuit.

\* The oscillations across  $C_1$  are applied to the base emitter junction and appear in the amplified form in the collector circuit and



supply losses to the tank circuit.


\* If terminal 1 is at positive potential with respect to terminal 3 at any instant, then terminal 2 will be at negative potential with respect to 3 at that instant because terminal 3 is grounded.

\* Therefore, points 1 and 2 are  $180^\circ$  out of phase. A further phase shift of  $180^\circ$  is produced by the transistor.

\* In this way, feedback is properly phased to produce continuous undamped oscillations.

\* In other words, energy is supplied to the tank circuit in phase with the oscillations and if  $A\beta$  is greater than one, oscillations are sustained in the circuit.

### Phase-shift oscillator

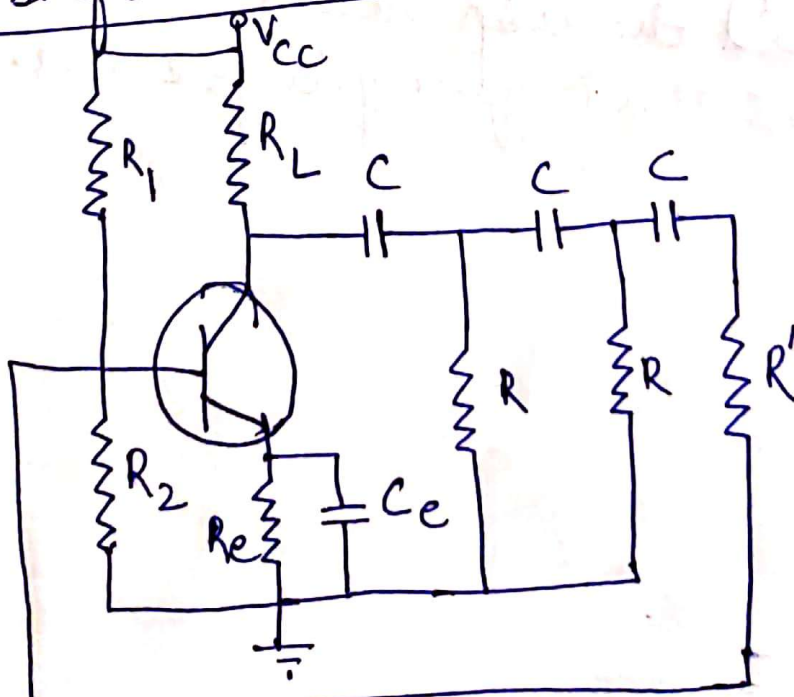



\*  $R_1 - R_2$  provides DC emitter base bias.  $R_L$  is the load which controls the collector voltage.

\*  $R_e - C_e$  combination provides temperature stability and prevents AC signal degeneration.

\* The output of the amplifier goes to a feedback network which consists of three identical R-C sections.

### Working


\* Here R-C network produces a phase shift of  $180^\circ$  between input and output voltages. Since CE amplifier produces a phase of  $180^\circ$ , the total phase change becomes  $360^\circ$  or  $0^\circ$  which is the essential requirement of sustained oscillations.

\* The RC phase shift networks serve as frequency determining circuit.

\* Since, Only at a single frequency the net phase shift around the loop will be  $360^\circ$ , a sinusoidal waveform at this frequency is generated.



# Wien - Bridge Oscillator

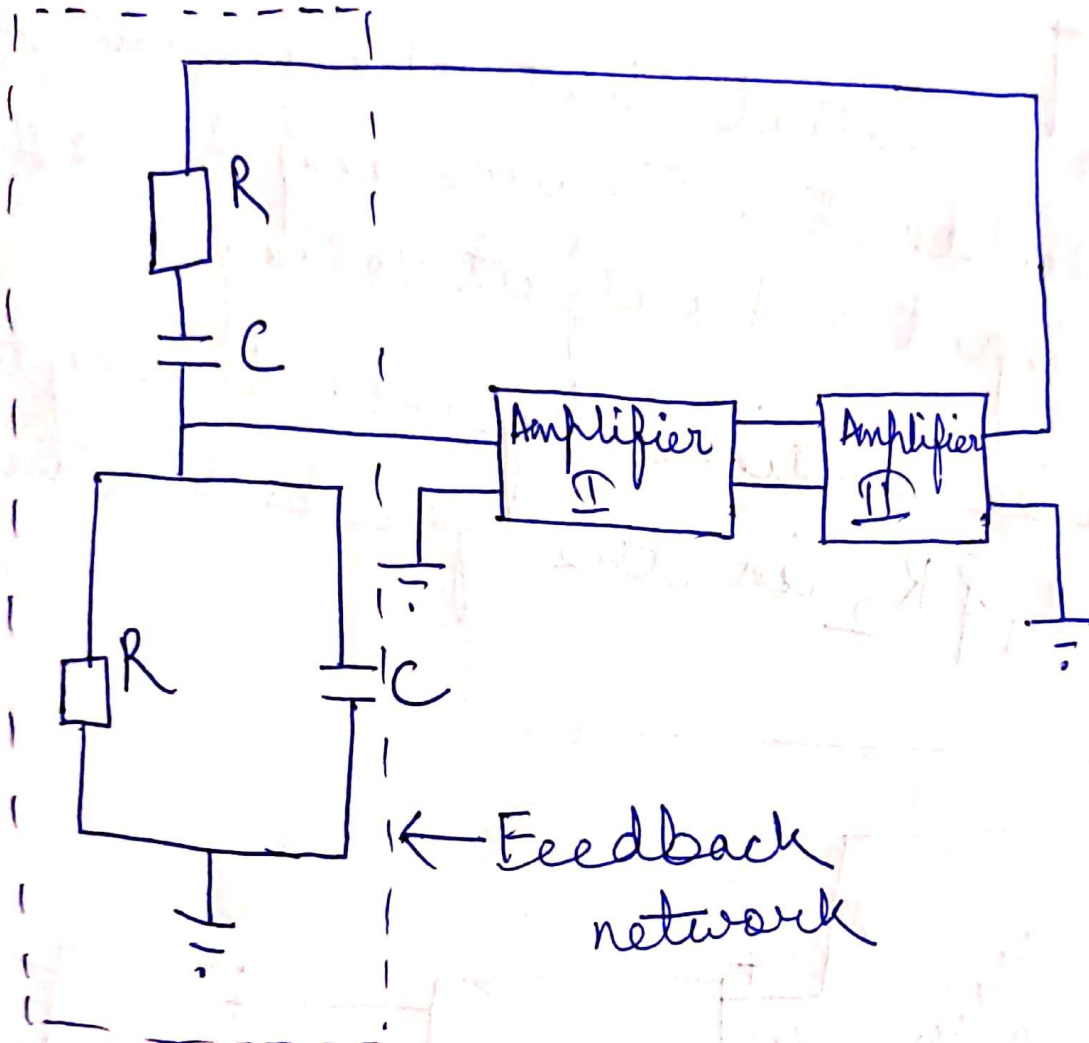

(fig-1)

\* The oscillator consists of two stages of R-C coupled amplifier and a feedback network.


\* The voltage across the parallel combination of R and C is fed to the input of amplifier I.

\* The output of amplifier II is not fed to amplifier I because amplifier I will amplify signals over a wide range of frequencies and hence the direct coupling would result in poor frequency stability!

~~\* By adding~~

\* It is now essential that the feedback network should not introduce any phase shift between its input and output voltages.

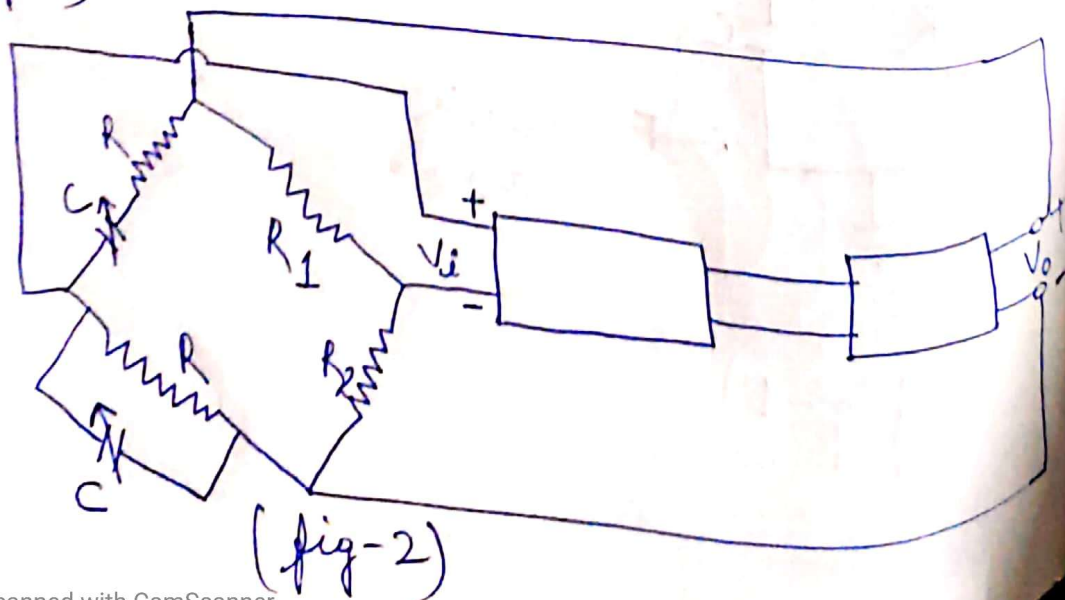\* This can be obtained by introducing two resistances  $R_1$  &  $R_2$  in the feedback network (fig-2)






- \* We can vary the frequency of this oscillator by varying the two capacitors simultaneously.
- \* The range of the frequency of the oscillator can be changed by using different values of resistors  $R$ .

# Field effect transistors

\* FET is a ~~unipolar~~ three terminal unipolar semiconductor device in which current is controlled by an electric field.



\* Classification of FET

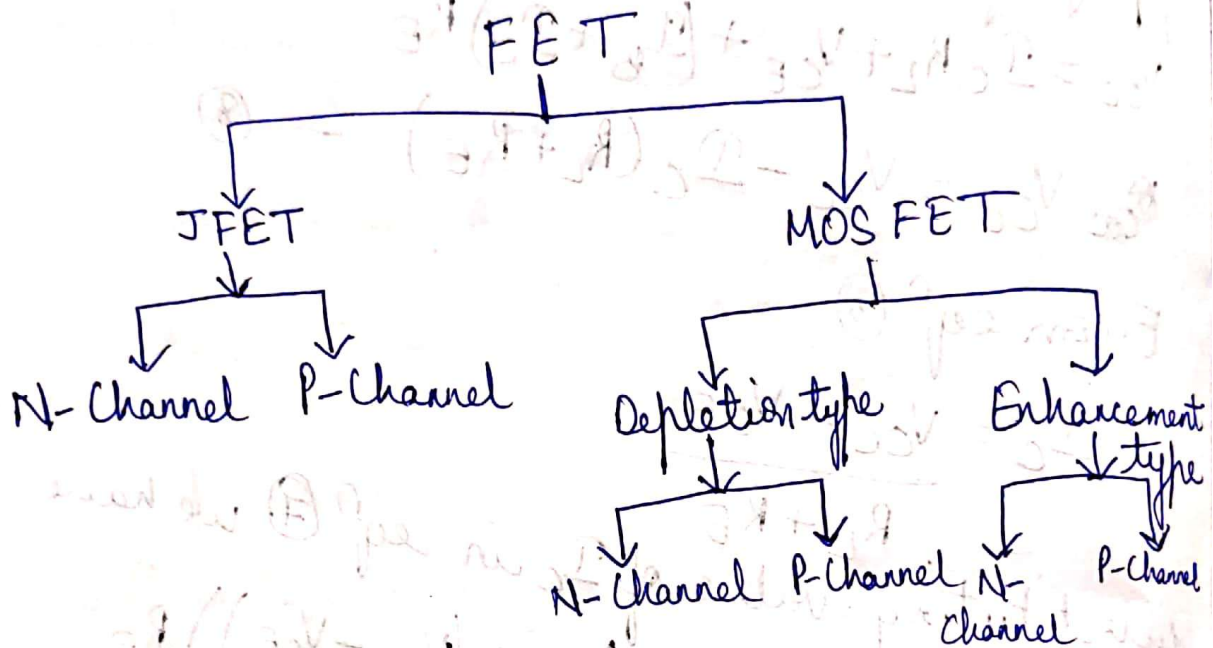

## Advantages of JFET over BJT.

| JFET  | BJT  |
|---|--|
| 1) Unipolar device (current conduction is only due to one type of carrier either electron or hole). | 1) Bipolar device (current conduction by both types of carriers i.e. electron & hole). |
| 2) Voltage driven device  | 2) Current driven device   |
| 3) Low noise level  | 3) High noise level  |
| 4) High input impedance   | 4) Low input impedance   |
| 5) Gain is characterised by transconductance  | 5) Gain is characterised by voltage gain.  |
| 6) Better thermal stability   | 6) Less thermal stability.   |



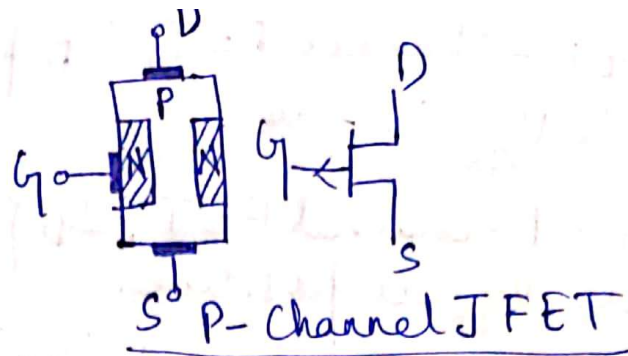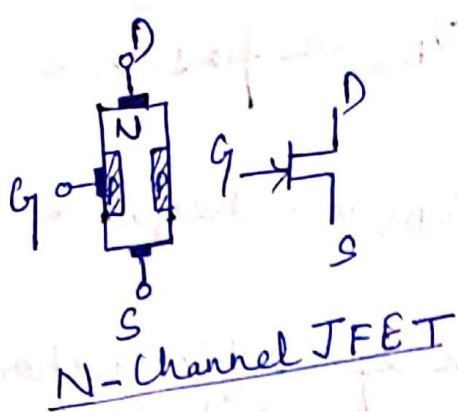


Source - The Source S is a terminal through which the majority carriers enter the bar.


Drain - The drain D is a terminal through which the majority carriers leave the bar.

Gate - These are two internally connected heavily doped impurity regions which form two P-N junctions.

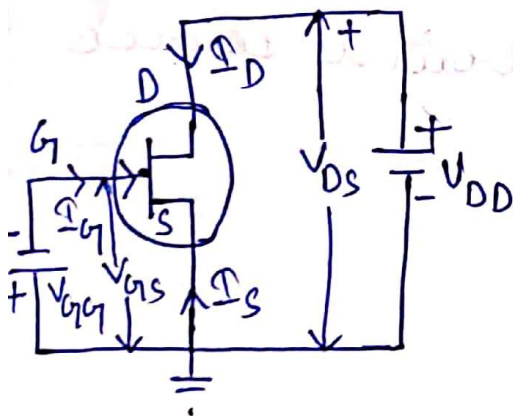Channel - The space between two gates through which majority carriers pass.



N-Channel

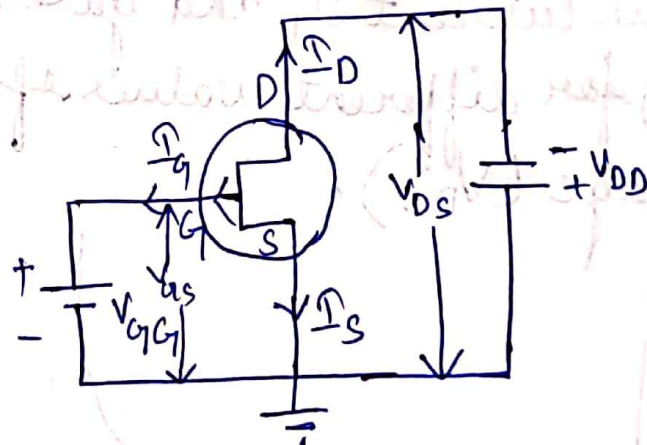

\* Assumed positive directions of  $I_S$ ,  $I_G$  &  $I_D$  are into the FET

\* The direction of arrow at the gate indicates the direction in which the gate current flows when gate junction is forward biased.

\* For N-Channel FET,  $I_D$  &  $V_{DS}$  are positive while  $V_{GS}$  is -ve.


\* For P-Channel FET,  $I_D$  &  $V_{DS}$  are negative while  $V_{GS}$  is positive.

\* The source, gate and drain of FET correspond to emitter, base and collector of a bipolar transistor.
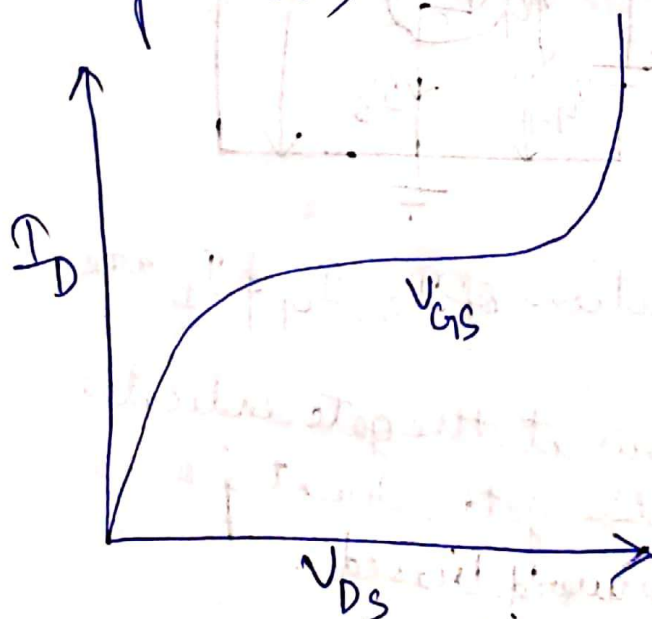
### Characteristics of JFET


\* Drain Characteristics → The curves between drain current ( $I_D$ ) and drain to source voltage ( $V_{DS}$ ) for different values of gate to source voltage ( $V_{GS}$ ).

\* Transfer Characteristics → The curve between drain current  $I_D$  and gate to source voltage ( $V_{GS}$ ) for different values of drain to source voltage ( $V_{DS}$ ).



Drain Characteristic



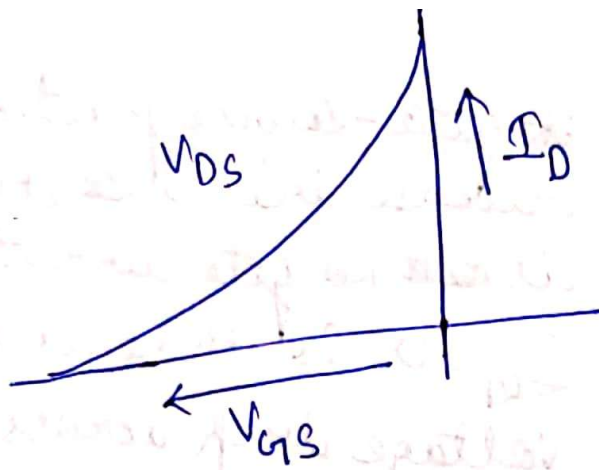

## FET parameters

\* D.C drain resistance ( $R_{DS}$ )

$$R_{DS} = \frac{V_{DS}}{I_D}$$

\* A.C drain resistance ( $r_d$ )

$$r_d = \left( \frac{\Delta V_{DS}}{\Delta I_D} \right)_{V_{GS} = \text{constant}}$$


\* Transconductance

$$g_{fs} = \left( \frac{\Delta I_D}{\Delta V_{GS}} \right)_{V_{DS} = \text{constant}}$$

## Biasing of FET circuits

- 1) Fixed-bias
- 2) Self bias
- 3) Current-source
- 4) Voltage-divider

## Fixed bias

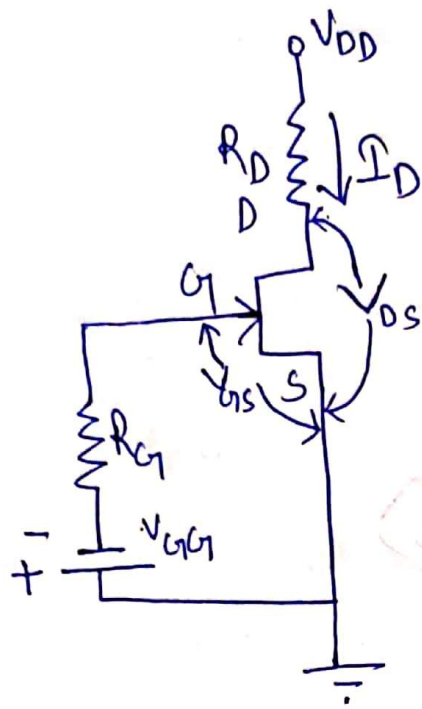

\* gate-source junction is reverse biased so there is ~~no~~ no gate current  $I_G$ .  $I_G = 0$ . So, there is no voltage drop across  $R_G$ .

Applying KVL to the i/p circuit we have

$$V_{GG} + V_{GS} = 0$$

$$V_{GS} = -V_{GG}$$

The drain current is given by

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_p} \right)^2$$

$I_{DSS}$  - Drain current when gate is shorted to source.

$V_p$  = Pinch-off voltage.


Applying KVL to o/p ckt

$$V_{DD} = I_D R_D + V_{DS}$$

$$\Rightarrow V_{DS} = V_{DD} - I_D R_D$$



## Self bias

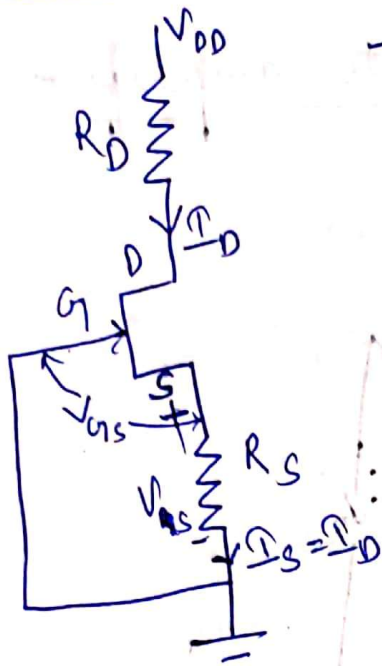

$$-V_{GS} = V_{DS} = 0 \quad V_S = I_D R_S$$

$$V_{GS} = -V_{DS}$$

$$V_{GS} = -I_D R_S$$


$$V_G = I_{G1} R_{G1} = 0$$

$$V_{GS} = V_G - V_S = 0 - I_D R_S$$

$$V_S = V_G - V_{GS} = 0 - (-I_D R_S)$$

$$V_{GS} = V_G - V_S = 0 - I_D R_S$$

## Voltage divider bias

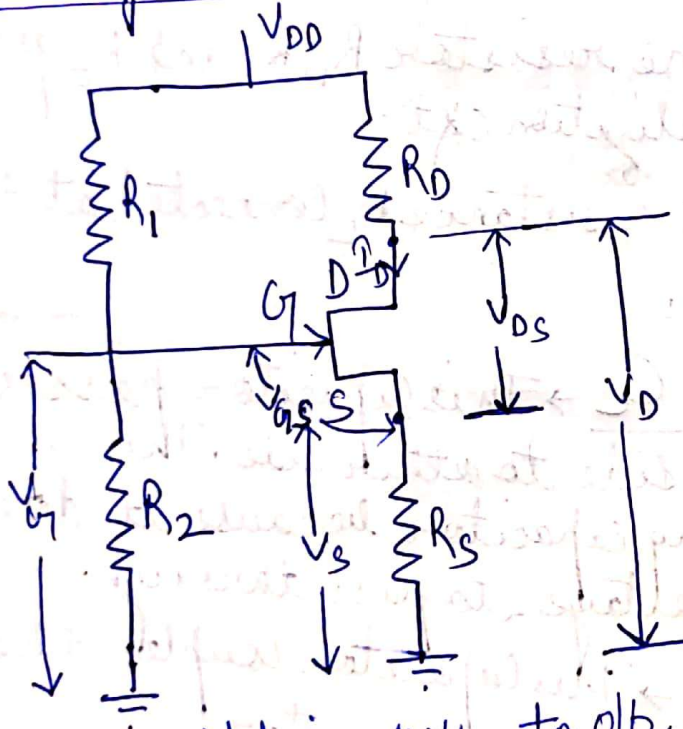

$$V_G = \left( \frac{V_{DD}}{R_1 + R_2} \right) R_2 \quad \text{--- ①}$$

$$V_S = V_G - V_{GS}$$

$$I_D R_S = V_G - V_{GS}$$

$$V_{GS} = V_G - I_D R_S \quad \text{--- ②}$$

$$\boxed{I_D = \frac{V_S}{R_S} = \frac{V_G - V_{GS}}{R_S}}$$

Applying KVL to o/p side

$$V_{DD} = I_D R_D + V_{DS} + I_D R_S$$

$$V_{DD} = I_D R_D + V_{DS} + I_D R_S$$


$$\boxed{V_{DS} = V_{DD} - I_D (R_D + R_S)}$$

# Operational Amplifiers

①

\* The operational amplifier is a direct-coupled, high gain, negative feedback amplifier.

## Circuit symbol of an op-amp

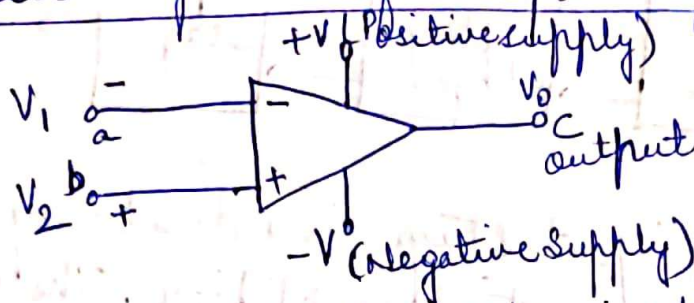


\* OP-Amp has two input terminals and a single output terminal.

\* Terminal a is the inverting terminal which indicates that a signal applied at the terminal a will appear amplified but phase inverted at terminal c.

\* Terminal b is called as non-inverting terminal which indicates that a signal applied at the terminal b will appear amplified but in phase at terminal c.

\* The two d.c sources, named as  $+V$  &  $-V$  are required for biasing of op-amp. These voltages are equal in magnitude with opposite polarities.

## Equivalent circuit of op-amp

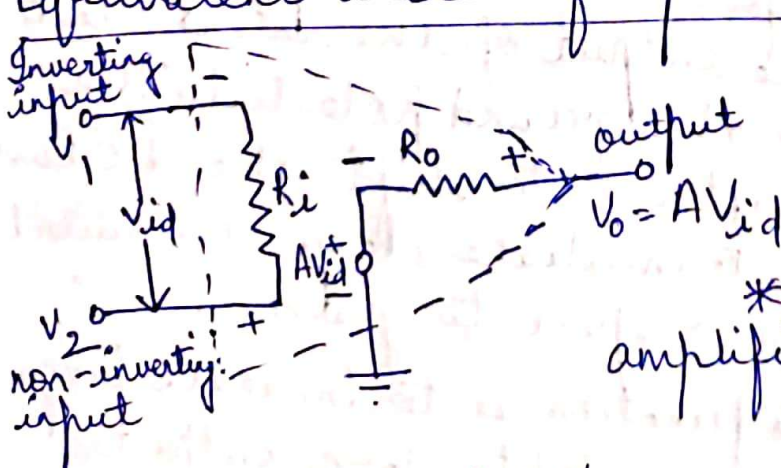

\* The difference i/p voltage

$$V_{id} = V_2 - V_1$$

\* The gain of the amplifier  $A = \frac{\text{output}}{\text{difference between two i/p signals}}$


$$\Rightarrow A = \frac{V_0}{V_2 - V_1}$$



$$\Rightarrow A = \frac{V_o}{V_{id}} \Rightarrow \boxed{V_o = A V_{id}}$$

(2)

## \* OP-AMP stages

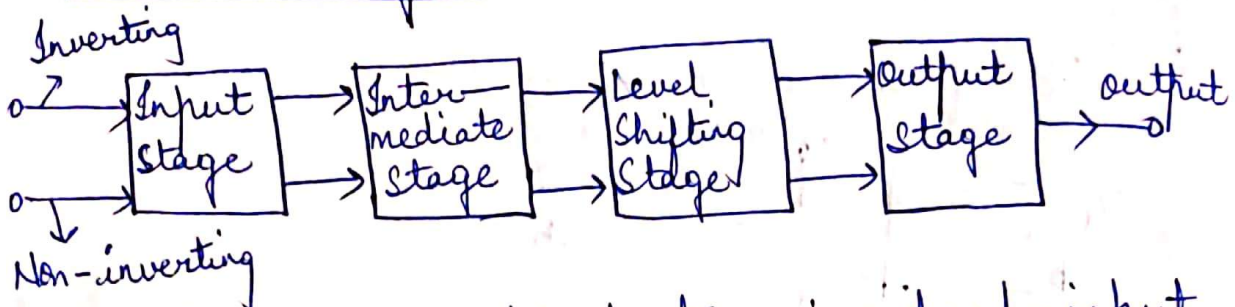

→ Input stage → The input stage is a dual-input, balanced output differential amplifier. The function of differential amplifier is to provide most of the voltage gain to OP-AMP. The differential amplifier in the input stage rejects the common noise signals present at the input terminals and amplifies only the difference between the input signals.

→ Intermediate stage → It is a dual input, unbalanced output differential amplifier. This is driven by output of first stage and is used to provide some additional gain. There is a direct coupling between the first two stages.

→ Level shifting stage → As direct coupling is used, the d.c at the output of the intermediate stage is well above the ground potential. The function of level shifter is to shift the d.c level at the output of intermediate stage downwards to zero volt with respect to ground.

output stage → Its function is to increase large output voltage swing capability, large output

current swing capability of the amplifier and to provide low output resistance.

(3)

### \* Open-loop OP-AMP configurations


→ when there exists no connection between the output and input terminals of OP-AMP, then it is known as open loop OP-AMP.

There are 3 open-loop configurations

- a) Differential amplifier
- b) Inverting amplifier
- c) Non-inverting amplifier.

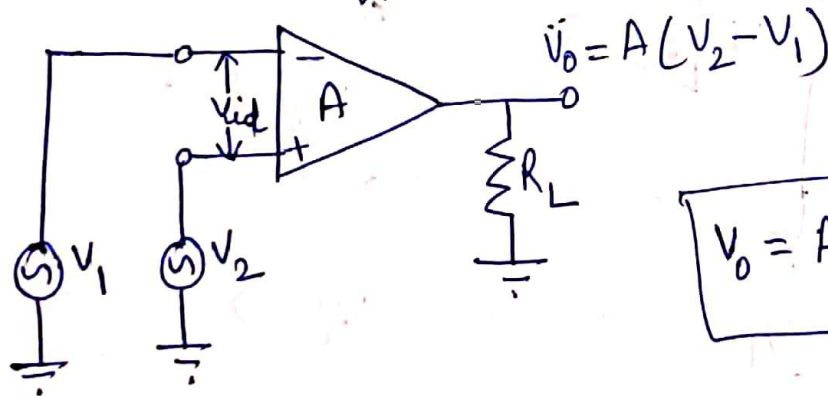
### \* Differential amplifier

→ As the OP-AMP amplifies the difference between two input signals and hence this configuration is called as differential amplifier.



$$V_o = AV_{id} = A(V_2 - V_1)$$

### \* Inverting amplifier

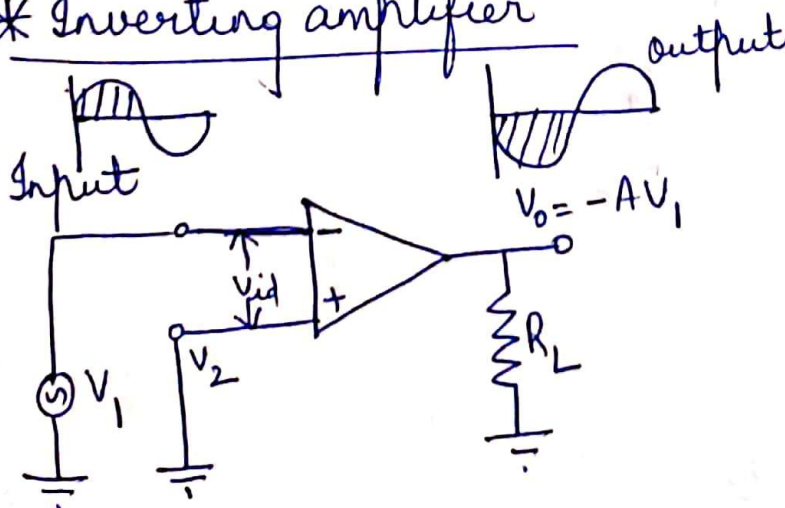


$$\begin{aligned} V_2 &= 0 \\ V_o &= AV_{id} = A(V_2 - V_1) \\ \Rightarrow V_o &= -AV_1 \end{aligned}$$



\* Non-inverting

(4)

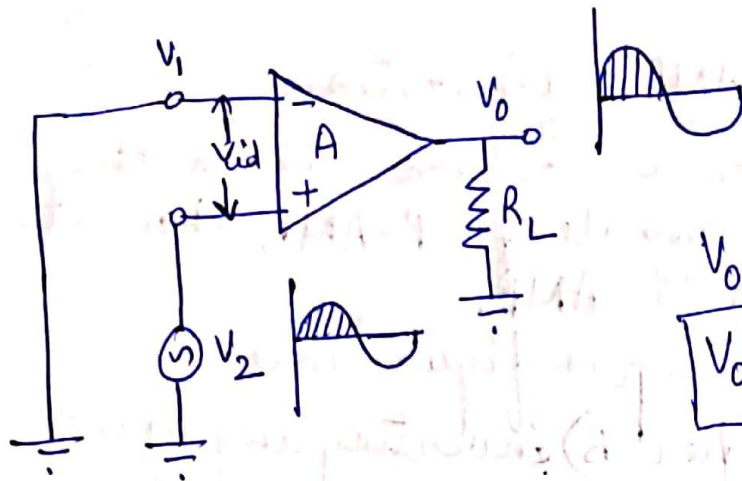


$$V_1 = 0$$

$$V_0 = AV_{id} = A(V_2 - V_1)$$

$$V_0 = AV_2$$

\* Inverting OP-AMP with feedback

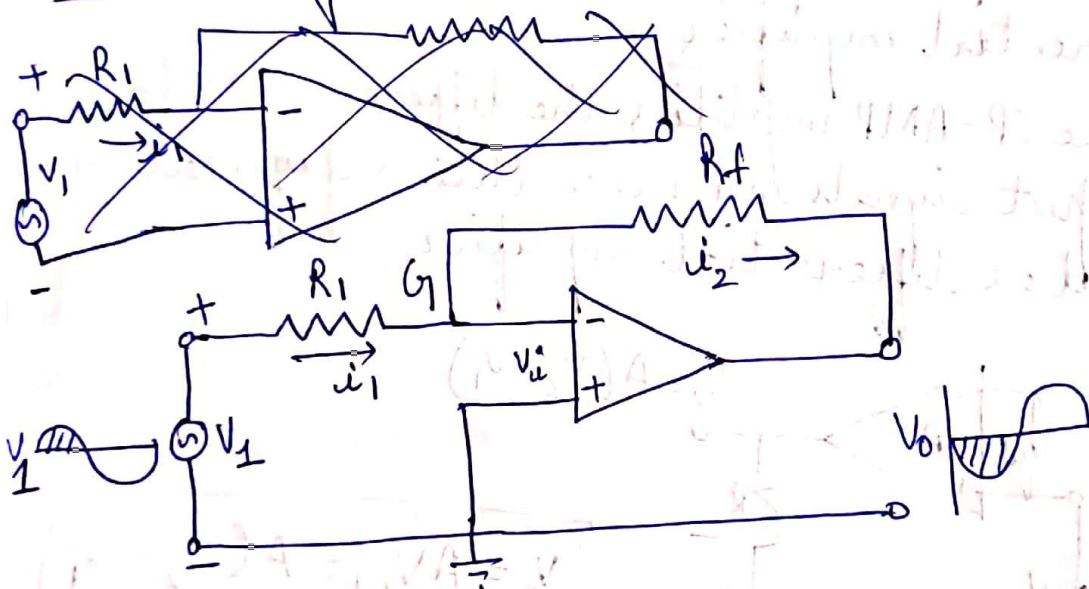

$$i_1 = \frac{V_1 - V_i}{R_1} = \frac{V_1}{R_1}$$

$$V_i = 0$$


$$i_2 = \frac{V_i - V_0}{R_f} = \frac{-V_0}{R_f}$$

$$\frac{V_1}{R_1} = -\frac{V_0}{R_f}$$

Voltage gain  $A_V = \frac{V_0}{V_1} = -\frac{R_f}{R_1}$


## Non-inverting OP-AMP with feedback

(5)

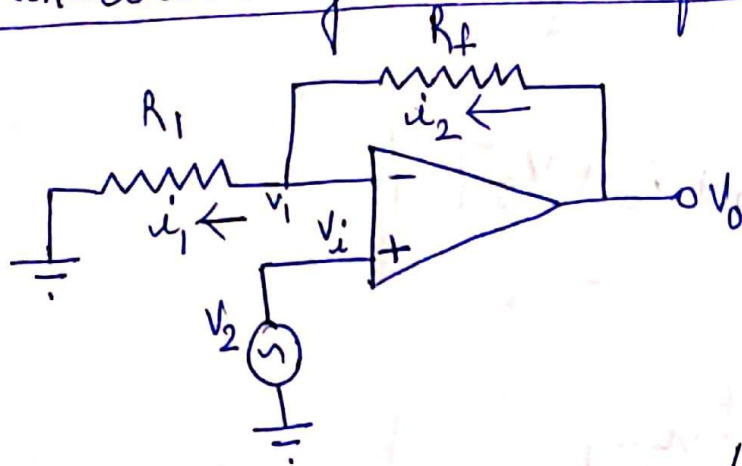

$$i_1 = \frac{V_2}{R_1}, i_2 = \frac{V_0 - V_2}{R_f}, A_V = \left(1 + \frac{R_f}{R_1}\right)$$

## Voltage follower/Buffer

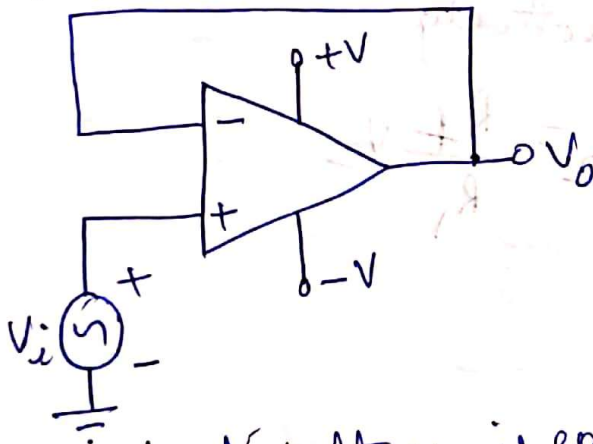


$$A_V = 1$$

$$V_0 = V_2 = V_i$$

\* The output voltage is equal and in-phase with the input i.e OP-AMP circuit acts as a voltage follower

## Adder or summing amplifier

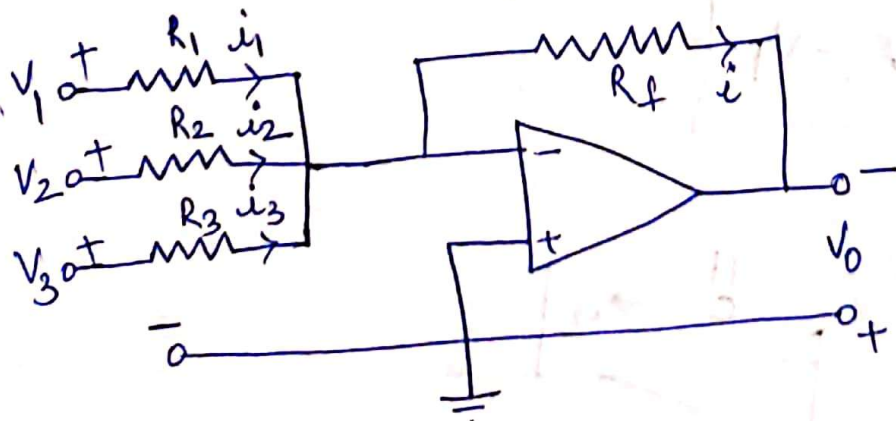

$$i_1 = \frac{V_1}{R_1}, i_2 = \frac{V_2}{R_2}, i_3 = \frac{V_3}{R_3}, i = \frac{V_0}{R_f}$$




$$V_0 = -[V_1 + V_2 + V_3]$$

6

if  $R_f = R/3$  then

$$V_0 = -1/3 [V_1 + V_2 + V_3]$$

### Subtractor

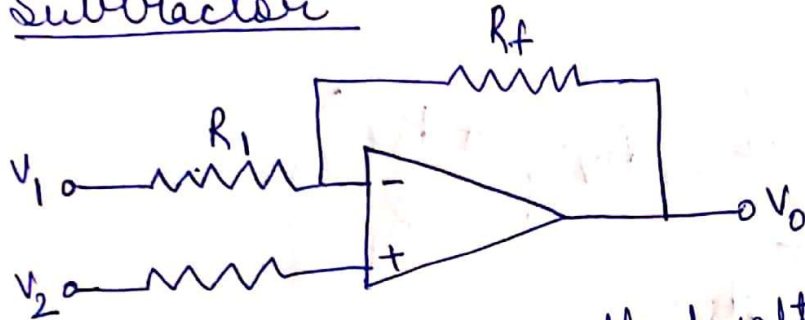

Let  $(V_0)_1$  &  $(V_0)_2$  be the output voltages produced by input voltages  $V_1$  &  $V_2$  respectively

$$(V_0)_1 = -\frac{R_f}{R_1} V_1, (V_0)_2 = \frac{R_f}{R_1} V_2$$

$$V_0 = (V_0)_1 + (V_0)_2$$


$$V_0 = -\frac{R_f}{R_1} V_1 + \frac{R_f}{R_1} V_2$$

$$V_0 = \frac{R_f}{R_1} (V_2 - V_1) = k(V_2 - V_1)$$

if  $R_f = R_1$

$$V_0 = V_2 - V_1$$

### Integrator

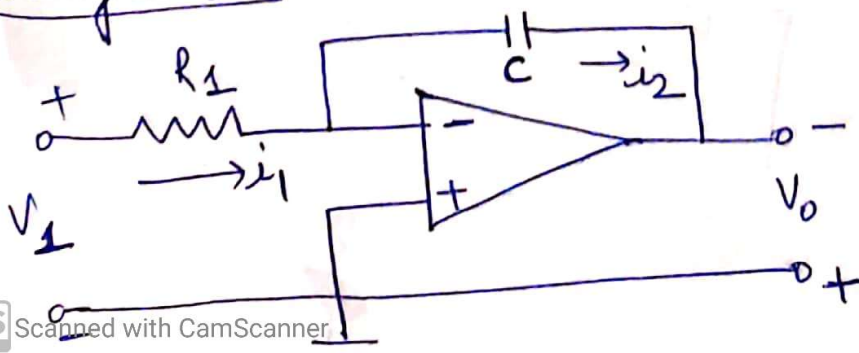

The capacitive impedance  $X_C$  can be expressed as

$$X_C = \frac{1}{j\omega C} = \frac{1}{sC}$$

$$s = j\omega$$

(7)


$$i_1 = \frac{V_1}{R_1} ; i_2 = -\frac{V_o}{X_C} = -sC V_o$$

$$\Rightarrow \frac{V_1}{R_1} = -sC V_o \Rightarrow \frac{V_o}{V_1} = -\frac{1}{sCR_1} \quad \text{--- (1)}$$

eq<sup>n</sup> (1) can be rewritten in time domain as

$$V_o(t) = -\frac{1}{R_1 C} \int V_1(t) dt$$

Differentiator

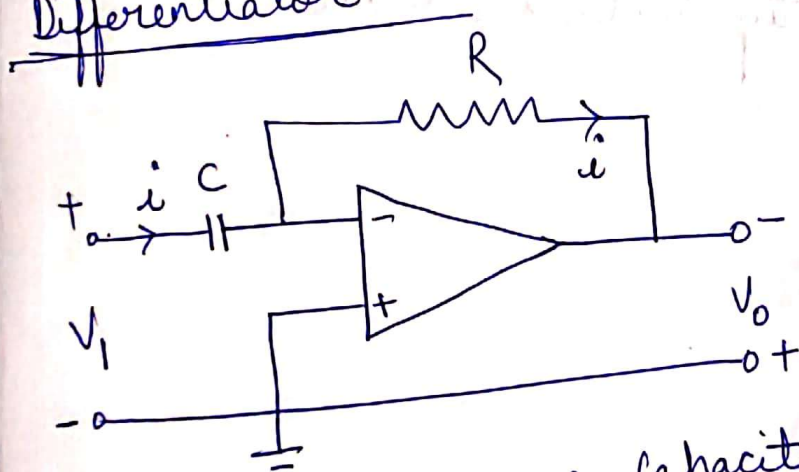

$$V_1 = \frac{q}{C}, \quad q = \text{charge on capacitor} \quad \text{--- (1)}$$

$$\frac{dV_1}{dt} = \frac{1}{C} \frac{dq}{dt} = \frac{i}{C}, \quad \text{where } \frac{dq}{dt} = i \quad \text{--- (2)}$$


$$V_o = -iR \quad \text{--- (3)}$$

substituting the value of  $i$  from eq<sup>n</sup> (2) in eq<sup>n</sup> (3)

$$V_o = -CR \frac{dV_1}{dt}$$



# Comparator

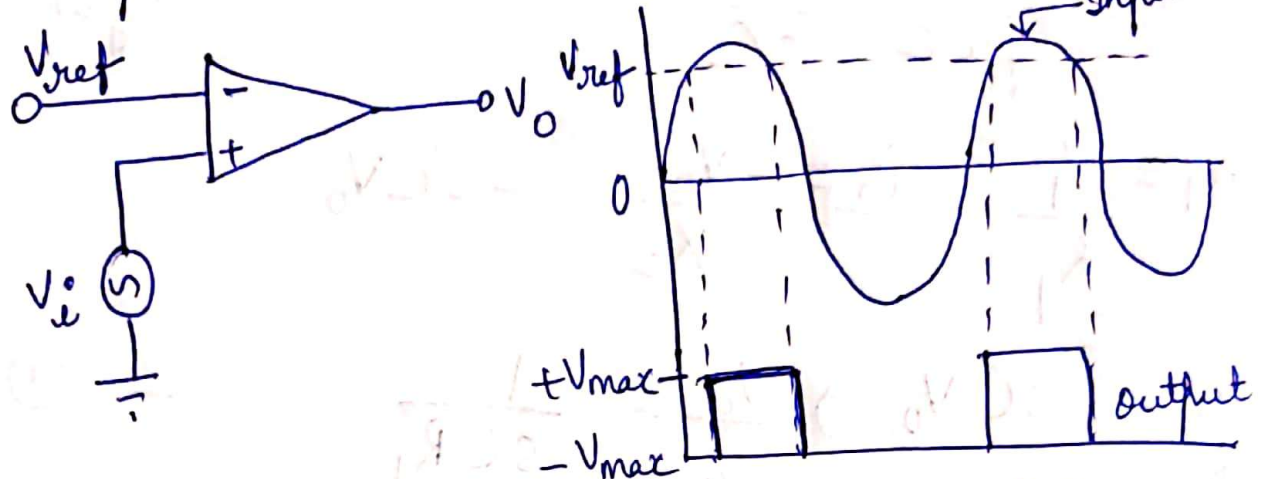

\* Comparator is a circuit which compares two voltages and provides an output that indicates the relationship between them.

Hence, comparator may be used to compare :-

- two changing voltages like two sine waves
- a changing voltage with a set d.c reference voltage.

# Chapter - I :: MEASURING INSTRUMENTS :-

Instrument :- An instrument is a device for determining indicating, measuring & recording physical quantities the value or magnitude of a quantity known as instrument (device - A tool or equipment made for a particular purpose).

Measurement :- It is the process of comparison b/w an unknown quantity with a predefined quantity. (known) (value in cm)

→ It is a process by which we convert physical parameters into numerical values.

→ Measurement is done by connecting a measuring instrument into a system under consideration & observing the response on the instrument.

Application :- For recording or observing the o/p of a process.

- To control a process of operation
- For analysis purpose.

## Methods of measurement

It can be broadly classified into two categories

### (I) Direct method

→ It includes comparison with standard fundamental quantities finding the unknown magnitude.

→ mass, length, time etc.  
Elect current, Temp., Amt of Substance (mole), Luminous intensity

### (II) Indirect method

→ In this method the unknown quantity is indirectly compared against a standard & the result is expressed as numerical.

→ most preferred method.

→ Power, Area

## Some Important Terminologies

(1) Accuracy :- The degree of closeness of an instrument reading b/w the true value & measured value.

→ In other words accuracy means the rightness.



Precision - It is defined as the measure of consistency or repeatability of a measurement.  
i.e. For a given i/p, how many times the o/p of the instrument remains same.

→ Precision means exactness, ~~word~~ term precision comes from 'precise' which means 'clearly or sharply defined.'

E.g. An ammeter doesn't give 100% accurate value of current, but whenever the same ~~test~~ current is measured it gives the same reading. The ammeter is said to be precision ammeter though it is <sup>not</sup> perfectly accurate.

Resolution or Discrimination -

→ The smallest change in the measured quantity to which the measurement will respond.

Sensitivity - The ratio of change in o/p to the change in i/p of the instrument.

$$\text{Sensitivity} = \frac{\text{change in o/p}}{\text{change in i/p}} \quad \left( S = \frac{\text{Torque ratio}}{\text{weight in PMM}} \right)$$

Error - measurement is done to check whether the measured quantity is equal to the true value or the predefined standard. Whenever the measured value is not equal to true value an error is produced.

→ Error is defined as the deviation or difference of true value from measured value.

Mathematically  $e = Y_n - X_n$

where  $e = \text{absolute error}$

$Y_n = \text{true value}$

$X_n = \text{measured value}$

$$\% \text{ Error} = \frac{\text{Absolute value}}{\text{True value}} \times 100$$

$$\Rightarrow \% E = \frac{e}{Y_n} \times 100$$

$$\Rightarrow \% E = \frac{Y_n - X_n}{Y_n} \times 100$$

### Types of Error

① Gross Error ② Systematic Error ③ Random Error

#### ① Gross Error

→ Gross error occurs largely due to human mistakes i.e. misreading of instrument ~~errors~~ at the time of calculating the measurement results, incorrect adjustment, improper application of instrument, mishandling, computational mistake etc.

→ The gross error can't be eliminated completely but can only be minimized.

→ One of the frequently occurred gross error is due to improper use of an instrument, it can be minimized by taking proper care in reading



& reloading measurement availability.

## ② Systematic errors

→ Systematic error occurs due to divided into 3 categories (I) Instrumental error

(II) Environmental error

(III) Observational error.

→ Systematic error occurs due to shortcomings <sup>(defect/fault)</sup> of the instruments; such as due to defective parts of the instrument, effect of environment on the instrument or due to user.

→ (I) Instrumental error are due to the mechanical structure of the instruments. ~~cases~~ covers such as mechanical error, constructional error, error due to damage etc.


(II) Environmental error are due to external weather condition of the instrument & the observer. The factors include temp, pressure, humidity, magnetic or electrostatic field etc.

(III) Observational error due to observer or person taking reading. These error such as parallax error or vision error, faulty reading of meter scale etc.

### ⑧ Random errors

→ All other known or unknown causes of errors are called Random errors. These errors include lack of knowledge, poor design, poor maintenance etc.
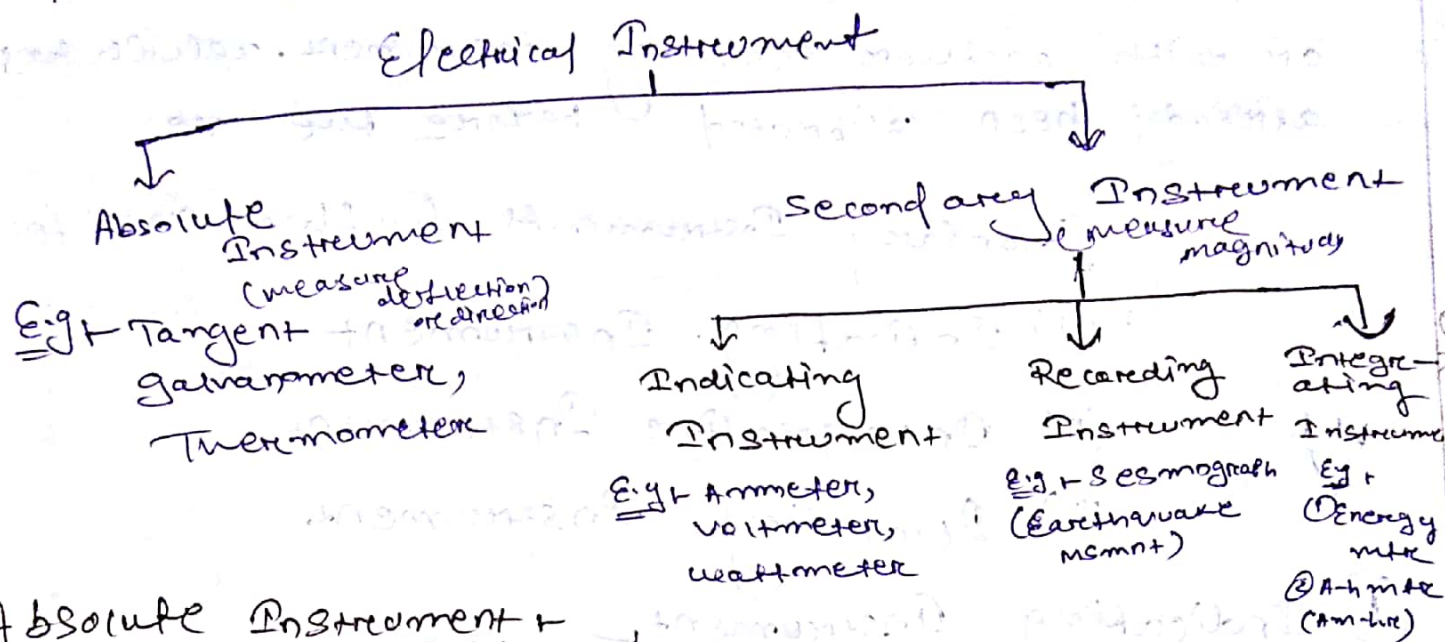
## Classification of measuring Instruments



### Absolute Instrument

→ These instruments give the measured value in terms of instrument constant & its deflection.

→ This type of instrument doesn't give direct readings

→ Such types of instruments don't require comparison with any other standard.

E.g. - Tangent galvanometer

Let meter constant = 3

reading =  $2 \times 3 = 6$



→ Tangent galvanometer which gives the value of the current to be measured in

terms of tangent of the angle of deflection produced.

→ These types of instruments are rarely used in laboratories for standardisation purpose.



## Secondary Instruments

- These instruments gives direct reading.
- These instruments are so constructed that the deflection of such instruments gives the magnitude of the electrical quantity to be measured directly.
- These instruments are required to be calibrated by comparison with either an absolute instrument or with another secondary instrument, which has already been calibrated before the use.

Secondary Instruments further classified as;

- (I) Indicating Instrument
- (II) Integrating Instrument
- (III) Recording Instrument

### ① Indicating Instrument

- These instrument are gives the value of the quantity to be measured by the deflection of the pointer.
- These instruments indicates the magnitude of an electrical quantity at the time when it is being measured. The indication are given by a pointer moving over a calibrated scale.
- It has scale & pointer mechanism.
- E.g → Ammeter, Voltmeter, Wattmeter, Frequency meter, Power factor meter etc.

## (i) Integrating Instrument

→ These instruments integrate or summarise an event over a specific period of time & gives the of result.

→ The summation given by such an instrument is the product of time & an electrical quantity under measurement

Eg: Energy meter, Ampere hour meter.  $1 \times 1000$   
 $1000 \text{ Wh} = 1 \text{ unit}$

## (ii) Recording Instrument

→ These instruments keeps a continuous record of the variation of the magnitude of an ~~ea~~ electrical quantity to be observed <sup>by an observer</sup> over a definite period of time

→ In such instrument moving system carries a light weight pen which touches lightly over a sheet of graph paper for recording purpose.

Eg: Recording voltmeter, Recording wattmeter,  
(use in power house)

Seismograph etc., EEG M/C.  
(Electrocardiogram M/C)

## Types of forces required for the indicating instrument

→ There are 3-types of forces are required for the satisfy operation of any indicating instrument.

They are:-

- (1) Deflecting Force.
- (2) Controlling Force.
- (3) Damping Force.



## (1) Deflecting Force

→ Deflecting force is also called as operating force.

→ This force helps in rotating the instrument movement from zero position.

→ The system producing the deflecting force is called as deflecting system or moving system.

→ So the deflecting system converts the electrical quantity i.e. current or voltage into mechanical force.

→ The torque produced by the deflecting force is called as deflecting torque.

→  $T_d$ 's value depend upon the electrical signal to be measured. ( $T_d$ )

## (2) Controlling Force

→ The act of this force is opposite to the deflecting force.

→ The force opposes the deflecting force & increase with the deflecting force of a moving system is called as controlling force.

→ The torque produce by the controlling force is known as controlling torque ( $T_c$ ).

→ This torque opposes the deflecting torque & increases with the deflection of the moving system.

→ The pointer is brought to rest at a position when the deflecting torque & controlling torque are equal in magnitude.  
i.e.  $T_d = T_c$  is known as definite position/  
final steady state position/equilibrium/  
rest.

→ The system which produce controlling torque is called controlling system.

The func<sup>n</sup> of controlling system are;


→ To produce a torque equal & opposite to the deflecting torque at the final steady position of the pointer in order to make the deflection of the pointer definite for a particular magnitude of current.

→ To bring back moving system to it's zero position when the force causing the instrument moving system to deflect is remove.

→ The controlling or balancing torque in indicating instrument is obtained by  
(i) Spring control (ii) Gravity control.



# ① Spring Control :-

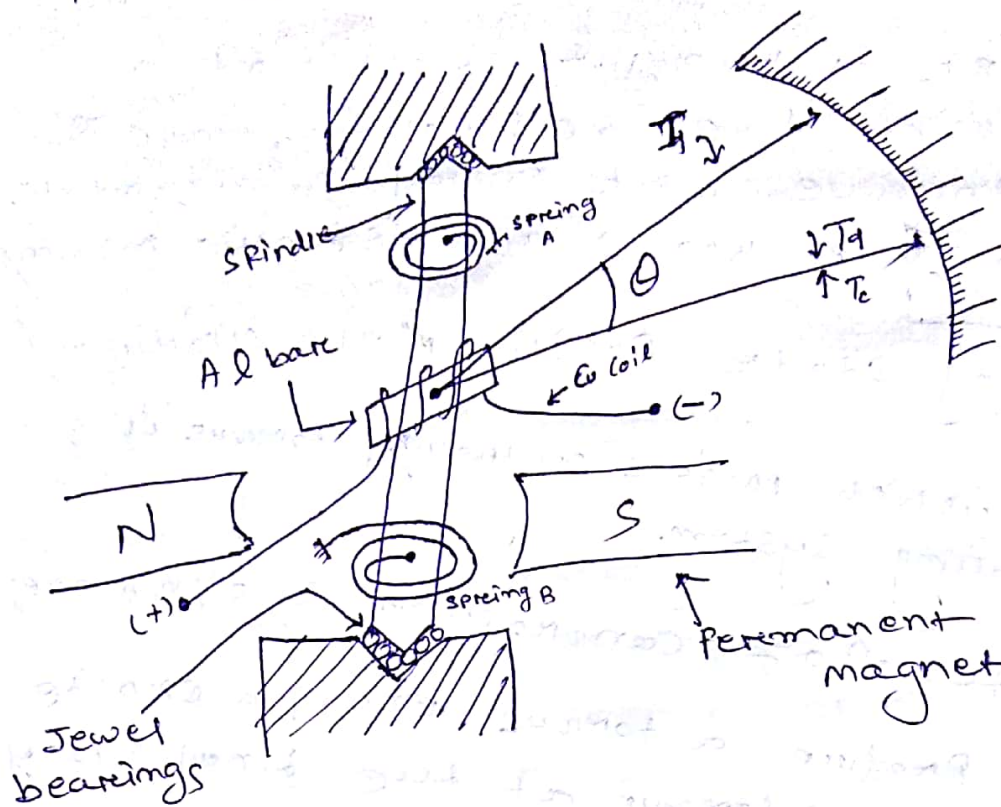

→ Two spiral spring usually of phosphor-bronze are wound in opposite direction on the spindle or moving system, which is used in indicating instruments for controlling purpose.

→ When moving system deflects, one of the spring is open & another close in opposite direction. i.e. the spring get twisted in opposite direction which produce controlling torque ( $T_c$ )

→ Here,  $T_c \propto \text{angle of deflection of the pointer } (\Theta)$

$$\text{i.e. } T_c \propto \Theta$$

$$\Rightarrow \boxed{T_c = K_s \Theta}$$

where  $K_s = \text{spring const.}$

8  $T_d \propto$  Current flowing through the instrument (I)

i.e.  $T_d \propto I$

$$T_d = K I$$

So at final steady state position:-

$$T_d = T_c$$

$$\Rightarrow K I = K_s \theta$$

$$\Rightarrow \theta = \left( \frac{K}{K_s} \right) I$$

$$\therefore \theta \propto I$$

$$\text{or } \theta = K I$$

i.e. The scale is uniform or linear

### Advantages

- Linear or uniform scale
- It can be mounted for both horizontal as well as vertically.


### Disadvantages

- Complex construction than gravity control.
- Accidental stress may damage the spring.
- change in temp. effect the spring length & hence  $T_c$ .
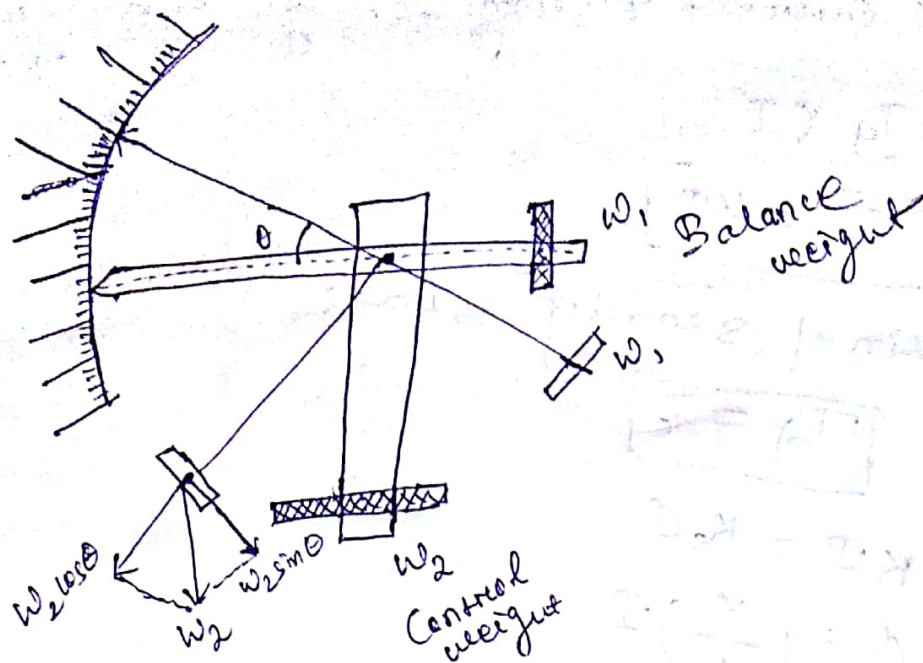
### (ii) Gravity control method

- In gravity control instrument, a small weight is attached to the moving system in such a way that it produces a restoring or controlling torque when the system is deflected.





- Here two weights  $w_1$  &  $w_2$  are attached to the pointer.
- The func<sup>n</sup> of  $w_1$  is to balance the weight of the pointer &  $w_2$  provides the controlling torque.
- When the pointer is at zero,  $w_2$  hangs vertically downwards.
- Here the deflected position of  $w_2$  can be converted into two components when pointer is deflected through angle  $\theta$ . i.e.  $w_2 \sin \theta$  &  $w_2 \cos \theta$ .
- Only  $w_2 \sin \theta$  will provide controlling torque ( $T_c$ )

$$T_c \propto w_2 \sin \theta$$

$$\& \quad T_d \propto I$$

→ At initial steady state position  $T_d = T_c$

$$\Rightarrow I = w_2 \sin \theta$$

$$\Rightarrow \boxed{I \propto \sin \theta}$$

→ therefore gravity control instrument have non-uniform scale.

## Advantages

- No temperature effect
- Cheaper than the spring controlled instrument

## Disadvantages

- Non-uniform scale.
- Instrument has to keep in vertical position.
- Because of gravity the pointer will take while coming to steady state.

Note - Spring control instrument can be placed in any direction & gives linear scales, hence it is used in all instruments.

## Comparison b/w gravity control & spring control

### Gravity Control

- Independent of temperature.
- It has non-uniform scale
- It can be used only in vertical position
- It is cheaper than spring control

### Spring Control

- Variation of temp. causes an error in the instrument.
- ~~It~~ It has uniform scale.
- It can be used ~~any~~ in any position (i.e. either vertical or horizontal).
- It is costlier than gravity control.

## Damping Force

→ Damping force is the force by which the moving system comes to its equilibrium position rapidly & smoothly without any oscillation.

→ The Torque produced by the damping force is called as damping torque.



→ Damping torque enable to prevent oscillation of the moving system & makes the pointer to reach to its final position quickly & smoothly.

→ Due to inertia of the moving system subjected to deflecting & restoring torques a no. of vibration will be produced before coming finally to rest.


→ To avoid this, a damping torque is required which opposes the motion & makes the pointer comes to rest.

→ The  $D.T$  is necessary to bring the pointer to rest position quickly, otherwise due to inertia of the moving system the pointer will oscillates about its final steady state position.


The damping torque can be produced by 3 ways:

- (a) Air friction damping.
- (b) Fluid friction damping.
- (c) Eddy current ~~and~~ damping.
- (d) Electromagnetic damping.

### (a) Air friction damping

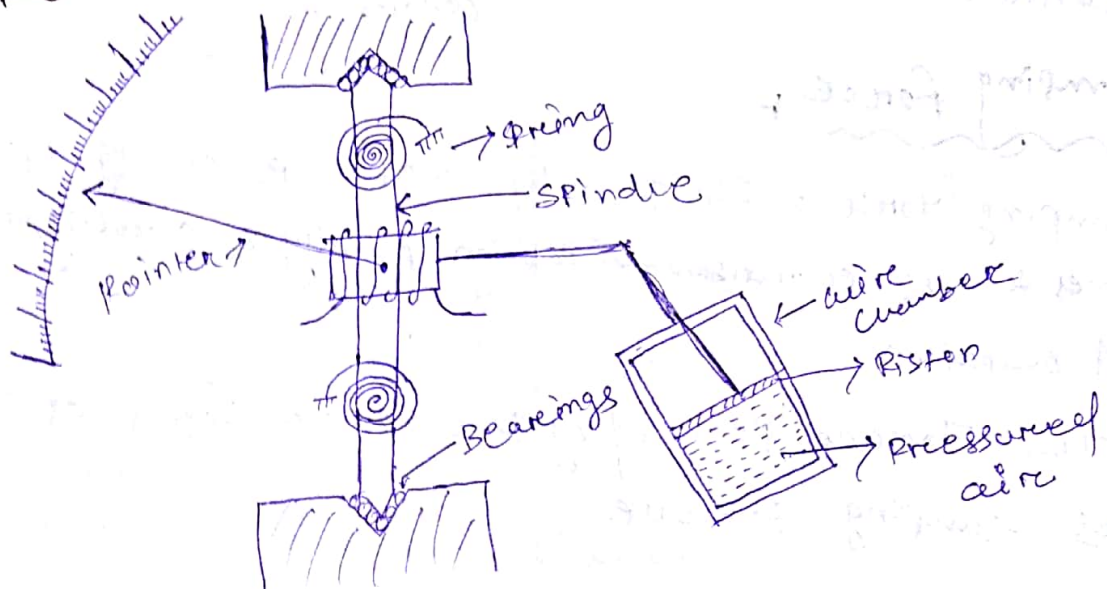

of 1/2 1/2 1/2

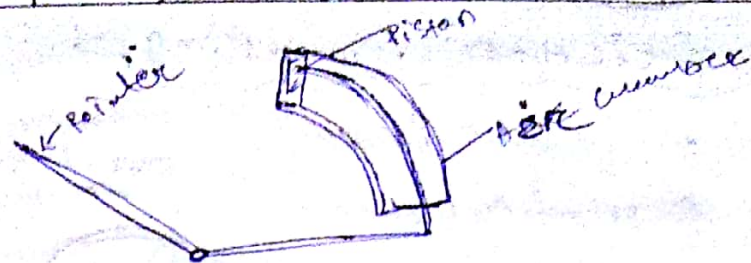

- It works on the principle of air pressure & friction.
- It consists of a light aluminium piston which is attached to the moving system.
- The piston is placed inside an air chamber.
- When there is an oscillation on the piston pointer, then the piston will move upwards & downwards in the air chamber.
- The oscillation of moving system is damped by the action of air in the chamber.
- When the pointer moves upward or downward in the air pressure inside the chamber in either direction created & damps the moving part.
- When piston moves downward, the pressurized air gets compressed, which opposes the movement of pointer & hence oscillation of the system is reduced.

### Advantages -

- Very simple & cheap method of damping.
- It doesn't require any permanent magnet.
- Low maintenance.
- Can be mounted horizontally & vertically.


Note \* This method is suitable for the instrument having weak magnetic field.

Ex - MI instrument, Electrodynamometer, wattmeter


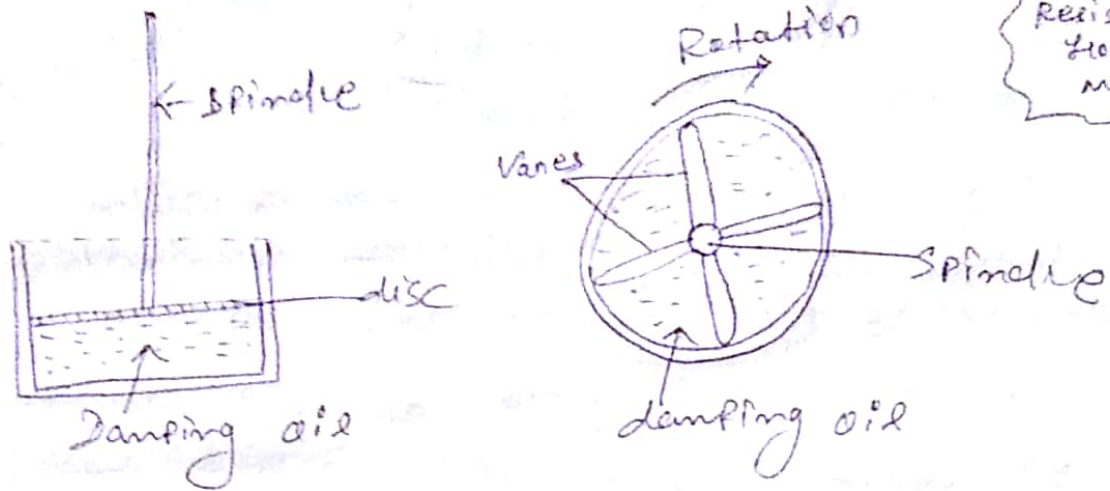
# Fluid Friction Damping

viscosity - physical property of fluid. Resistance to flow. how much sticky



→ In this type of damping, oil is used in place of air & as the viscosity of oil is greater the damping force is also corresponding greater.

→ Here the damping force is produced due to fluid substances.

→ Here the vanes are attached to the spindle of the moving system, which are submerged in oil.

→ The vanes are dipped into a pot of damping oil & are completely submerged by the oil.

→ The motion of the moving system is also opposed by the friction of the damping oil on the vanes.

→ The damping force, thus created always increases with the increase in velocity of vanes.

→ Due to friction of the fluid a force is produced so that oscillations are reduced accordingly.

→ There is no damping force when the vanes are stationary.

→ The damping oil must have following properties

(i) must be a good insulator.

(ii) should be non-evaporating.

(iii) should not have corrosive action upon the metal.

(iv) The viscosity of the oil should not change with the temperature

### Disadvantages

→ These instruments must be placed in vertically only.

→ more maintenance is required.

Note - This method is suitable for ~~low~~ instruments having low deflecting torque.

E.g. Electrostatic Voltmeter



### (c) Eddy current damping

→ This method of damping is based on the principle that <sup>but non-magnetic material</sup> ~~conducting material~~ moved in a magnetic field, an emf is induced in it which causes a current called eddy current.

→ Due to this eddy current a force exists b/w them & the field.

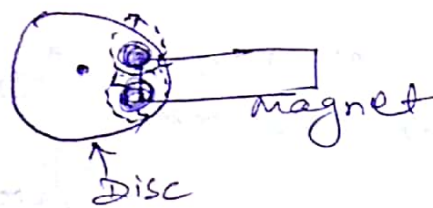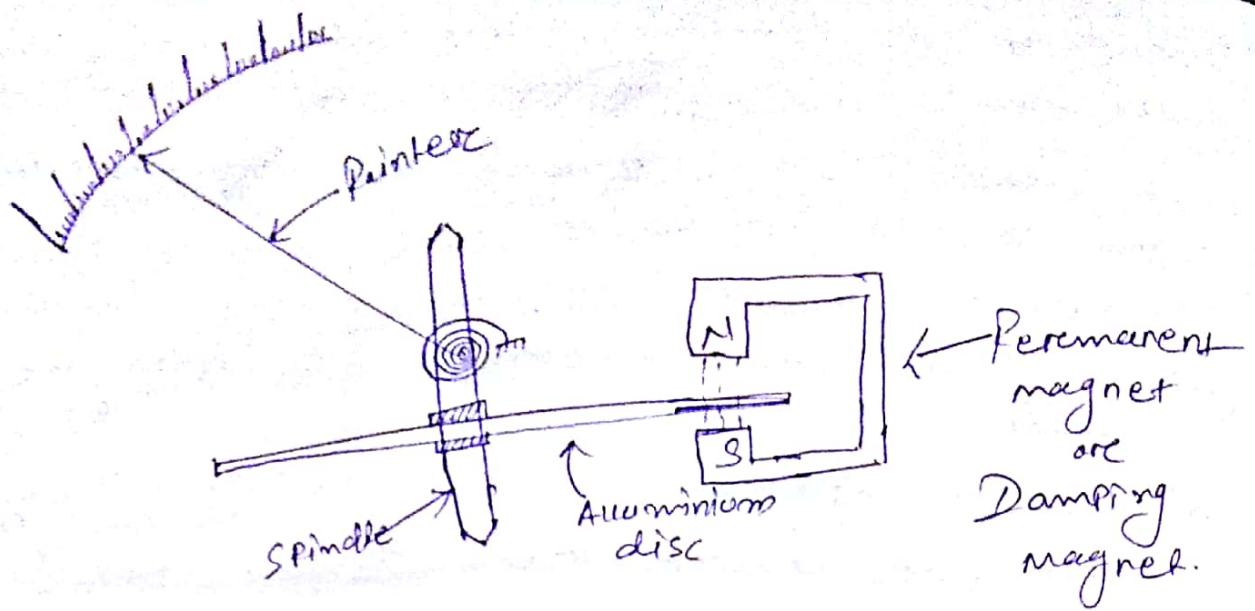→ According to Lenz's law this force is always in opposition to the force causing rotation of the conducting material, thus it provides the necessary eddy damping.





→ Here a Cu or Al disc carried by spindle is moved b/w the poles of a permanent magnet

→ If the disc moves clockwise, the emf induced in the disc & circulate eddy current as shown in dotted lines.

→ It follows from Lenz's law that this current exerts a force opposing the motion producing friction & hence provides damping.

## Calibration of Instrument

→ Calibration is a comparison b/w the known measurement & the measurement using measuring instrument.

→ The calibration of measuring instrument has ~~two~~ <sup>two</sup> objects;

1) ~~to~~ <sup>to</sup> check the accuracy of the instrument


2) It determines the history of locations & applications of the instrument

\* Why calibration is important?


→ The accuracy of our measuring instrument degrades over time, so the calibration of the instrument is important because it gives the opportunity to check the error & accuracy.

## (Chapter - 2) - Analog Ammeters & Voltmeters
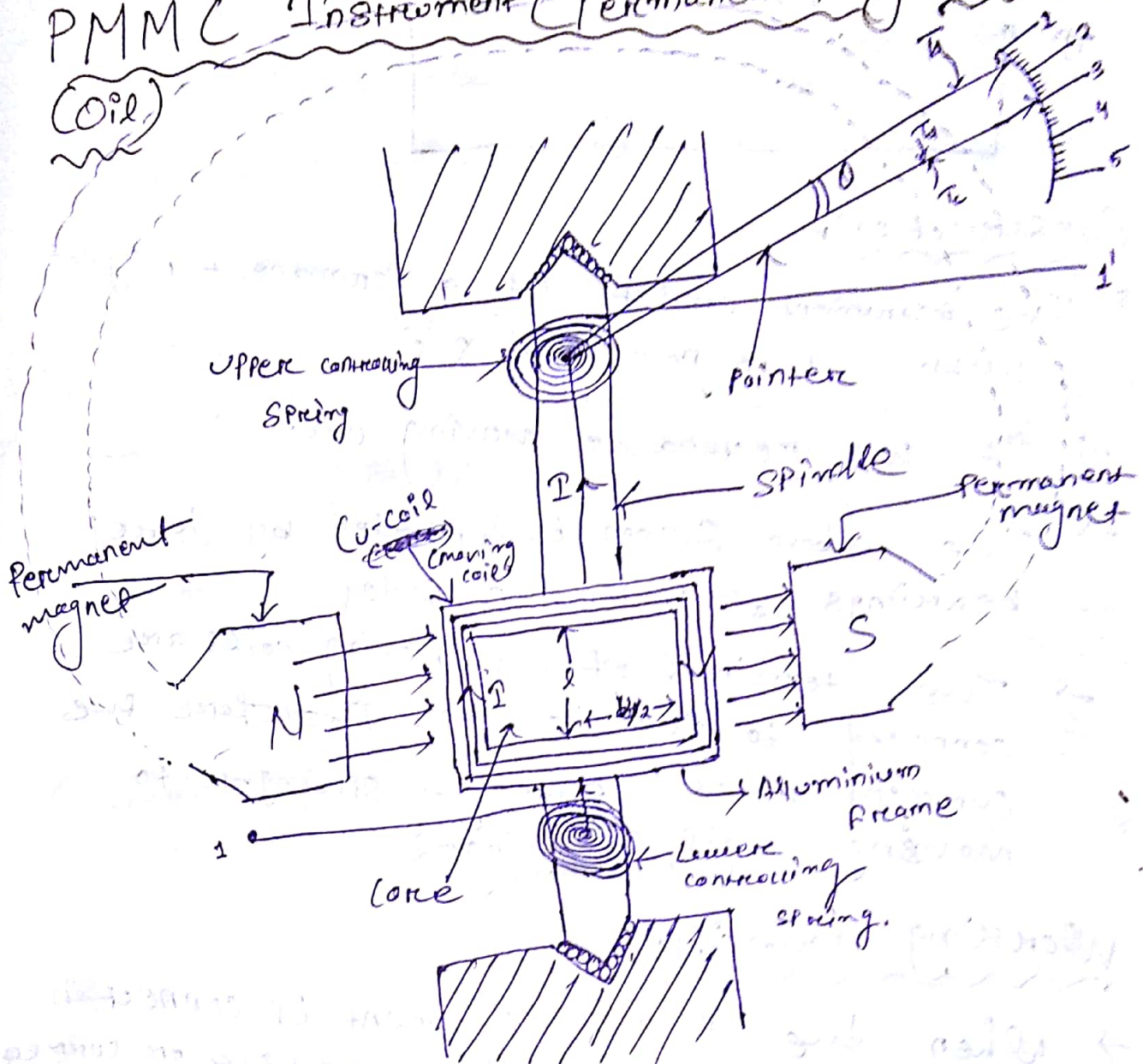
### PMMC Instrument (Permanent Magnet Moving Coil)





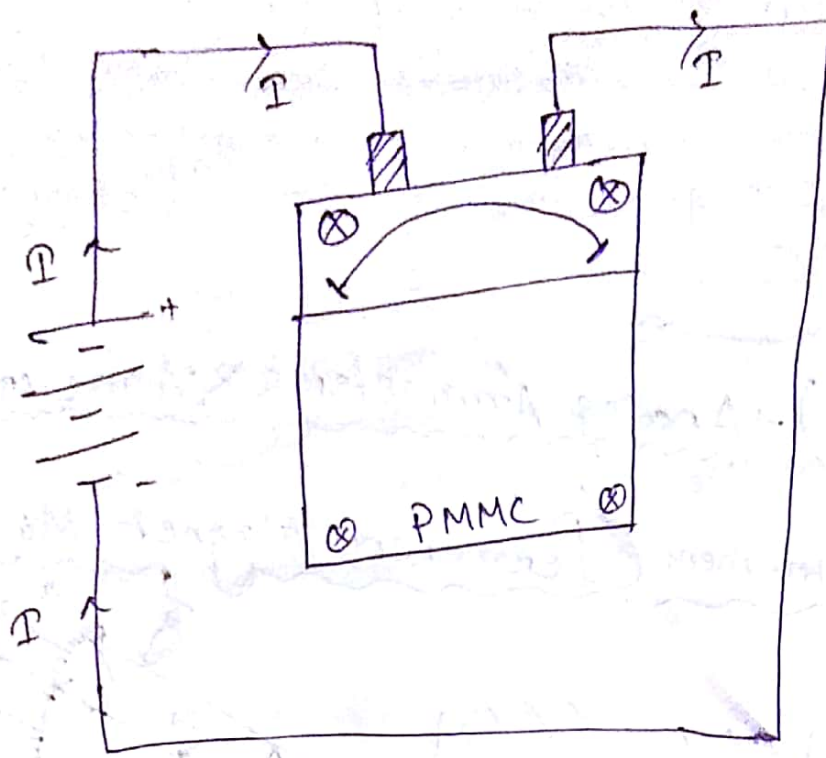

### Construction

- The instrument consists of a permanent magnet with two poles 'N' & 'S'.
- It has rectangular moving coil.
- The above system is supported by jewel bearings at both the sides.
- The terminals of the moving coils are connected to the springs. Therefore the current flows through Spring-1 to moving coil & Spring-2.

### Working Principle

- When the PMMC instrument is connected in the circuit to measure the voltage or current, then the current carrying coil is placed in a magnetic field of the permanent magnet.

→ Acc<sup>o</sup> to the Lorentz's force a mechanical force is developed in the Aluminium bar.

As a result a mechanical torque acts on it. so that the pointer attached to the moving system moves in the clock-wise direction over the scale to indicate the value of current or voltage to be measured.

### → Deflecting Torque ( $T_d$ )

If a current  $I$  amp is flows in the coil then the force acting on each side of the coil is;

$$F = BIL \text{ (Newton)} \quad F = BIL \sin \theta \quad (\because \theta = 90^\circ)$$

$$T_d = \text{Force} \times \perp^{\text{r}} \text{ distance}$$

where

$B$  = flux density (web/m<sup>2</sup>)

$I$  = current (A)

$l$  = length of the coil

$b$  = breadth of the coil.

$N$  = No. of turns of the coil.

for n no. of turns

$$= BIL \times b$$

$$= B \cancel{I} (l \times b)$$

$$= B \cancel{I} (A) \quad (\because A = l \times b)$$

$$T_d = B \cancel{I} A \quad \text{or} \quad T_d = N B I A$$

$$T_d \propto I$$

$$\text{or} \quad T_d = n B I A$$



### Controlling Torque

Due to Spring control  $T_c = K_c \theta$

At final steady state position or at equilibrium point

$$T_c = T_d$$

$$K_c \theta = N B I A \Rightarrow \theta = \frac{N B I A}{K_c}$$



→  $\theta \propto I$  → The scale is uniform or linear

$I > 0 \Rightarrow \theta > 0$

$I < 0 \Rightarrow \theta < 0$

### Advantages of PMMC

1. Uniform scale
2. Eddy current damping is effective
3. High efficiency.
4. Requires less power for operation.
5. No hysteresis as magnetic field is const.
6. Very reliable & accurate.

$$T_{avg} \approx T_{net} \approx 0$$

### Disadvantages

- It can't be used for AC measurement.
- More expensive, than the moving Iron Instrument.
- Errors occur due to control spring i.e. due to ageing effect.

### Errors in PMMC Instruments

#### ① Due to magnetic field density

- magnetic field density decreases with weakening of permanent magnet due to ageing effect, which tends to decrease the deflection of needle of instrument.

#### ② Due to spring control

- The value of spring const decreases with weakening of spring due to ageing &

temp effect, which will increase the deflection of the pointer & magnetic flux density.


### ③ Error due to moving coil

When the increase in resistance of moving coil is increases with temp, then the current flowing through the coil ~~increase~~ decreases accordingly.

### Extension of Range of PMMC Instrument
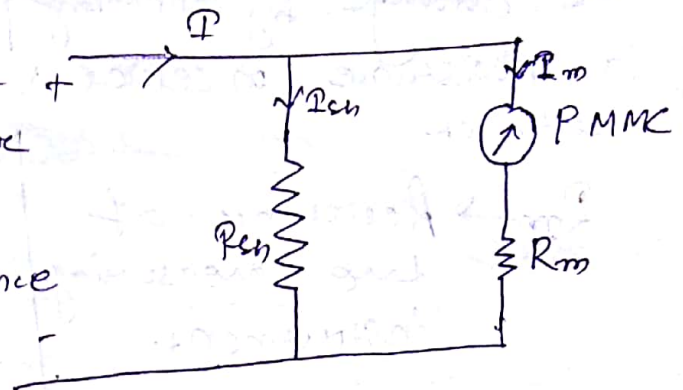
#### ① As an Ammeter

→ Since the shunt resistance is in parallel with the meter then the voltage drop across the shunt resistance & voltage drop across the meter must be same.



⇒  $R_m$  = Internal Resistance of the meter

$R_{sh}$  = Shunt Resistance in  $\Omega$ .

$I_{sh}$  = Shunt Current

$I$  = Current to be measured.

$I_m = I_{fs}$  = full scale deflection current.

from the above ckt

$$\boxed{V_{sh} = V_m}$$

$$\Rightarrow I_{sh} R_{sh} = I_m R_m$$

$$\Rightarrow (I - I_m) R_{sh} = I_m R_m \quad \left[ \because I_{sh} = I - I_m \right]$$

$$\Rightarrow R_{sh} = \frac{I_m R_m}{I - I_m}$$

$$\Rightarrow R_{sh} = \frac{R_m}{\left( \frac{I}{I_m} - 1 \right)}$$



Let  $\frac{I}{I_m} = m$  i.e. multiplying factor

$I$  = New range

$I_m$  = old range


$$R_{sh} = \frac{R_m}{m-1}$$

$R_{sh} \ll R_m$  as we need more current

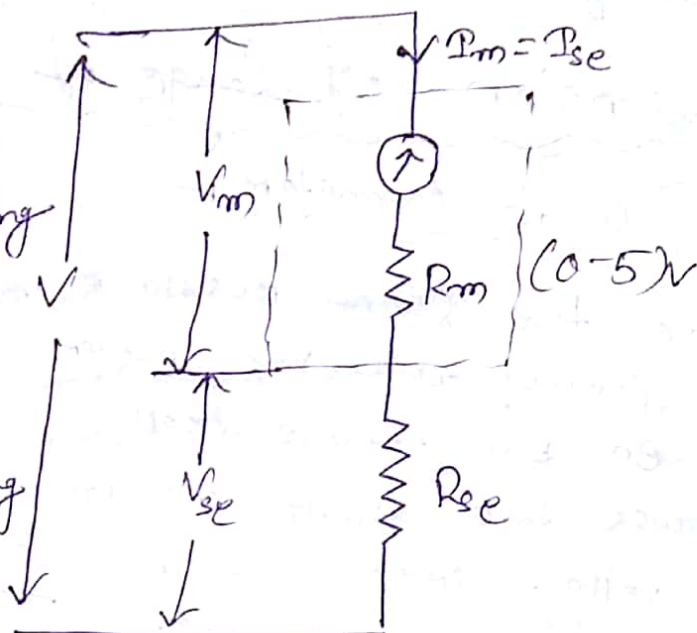(b) PMMC instr. as a voltmeter

The range of the PMMC instrument can be changed by connecting a resistance in series with it.

$R_m$  → Resistance of the measuring instrument



$R_{se}$  → multiplier series resistance

$V_m$  → Voltage across the meter

$V_{se}$  → Voltage across the series resistance

From the above CKT  
 $I_m = I_{se}$

$$\frac{V_m}{R_m} = \frac{V_{se}}{R_{se}} = \frac{V - V_m}{R_{se}}$$

$$\Rightarrow R_{se} = \left( \frac{V - V_m}{V_m} \right) R_m$$

$$\Rightarrow R_{se} = \left( \frac{V - V_m}{V_m} \right) R_m$$

$$\Rightarrow R_{se} = R_m \left( \frac{V}{V_m} - 1 \right)$$

$$\Rightarrow R_{se} = R_m (m - 1)$$



$\because \frac{V}{V_m} = m = \text{multiplier factor}$   
new range  
old range

# Moving Iron Instrument (MI Instrument)

mainly two type! they are  
① Attraction type
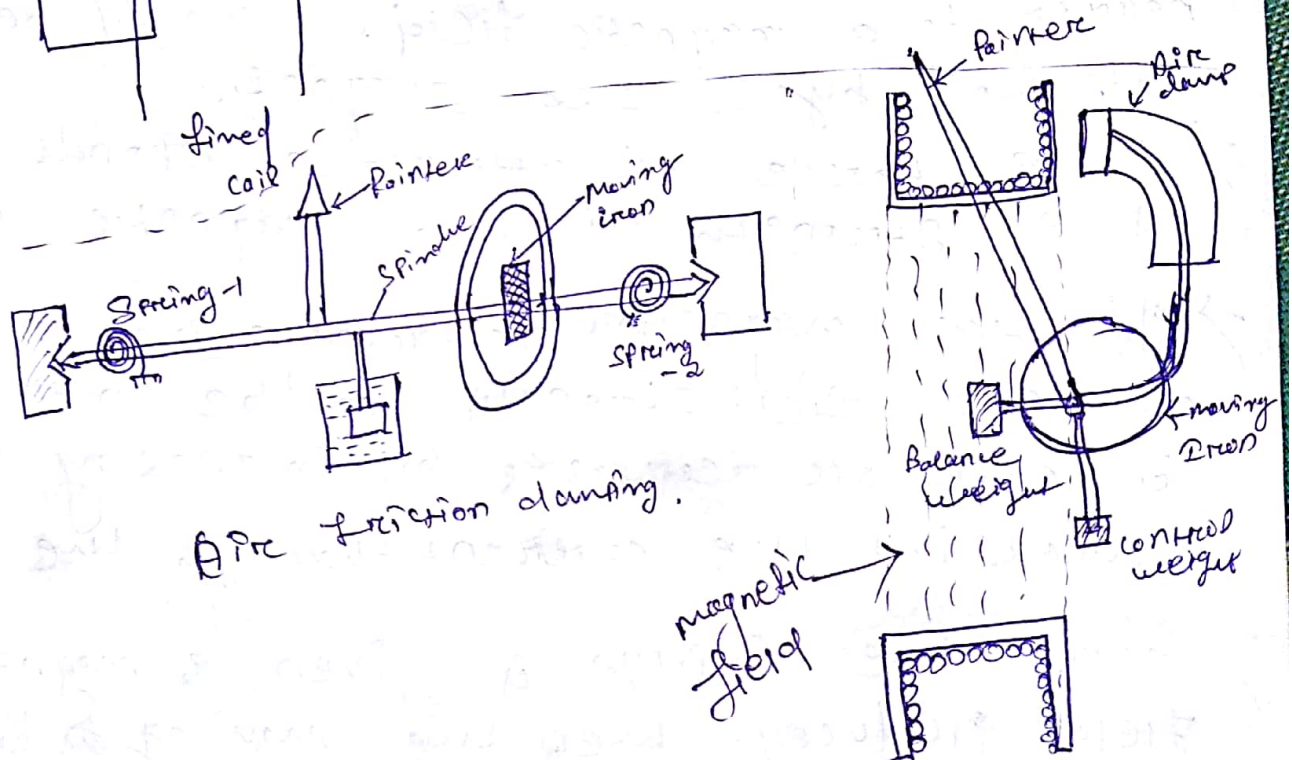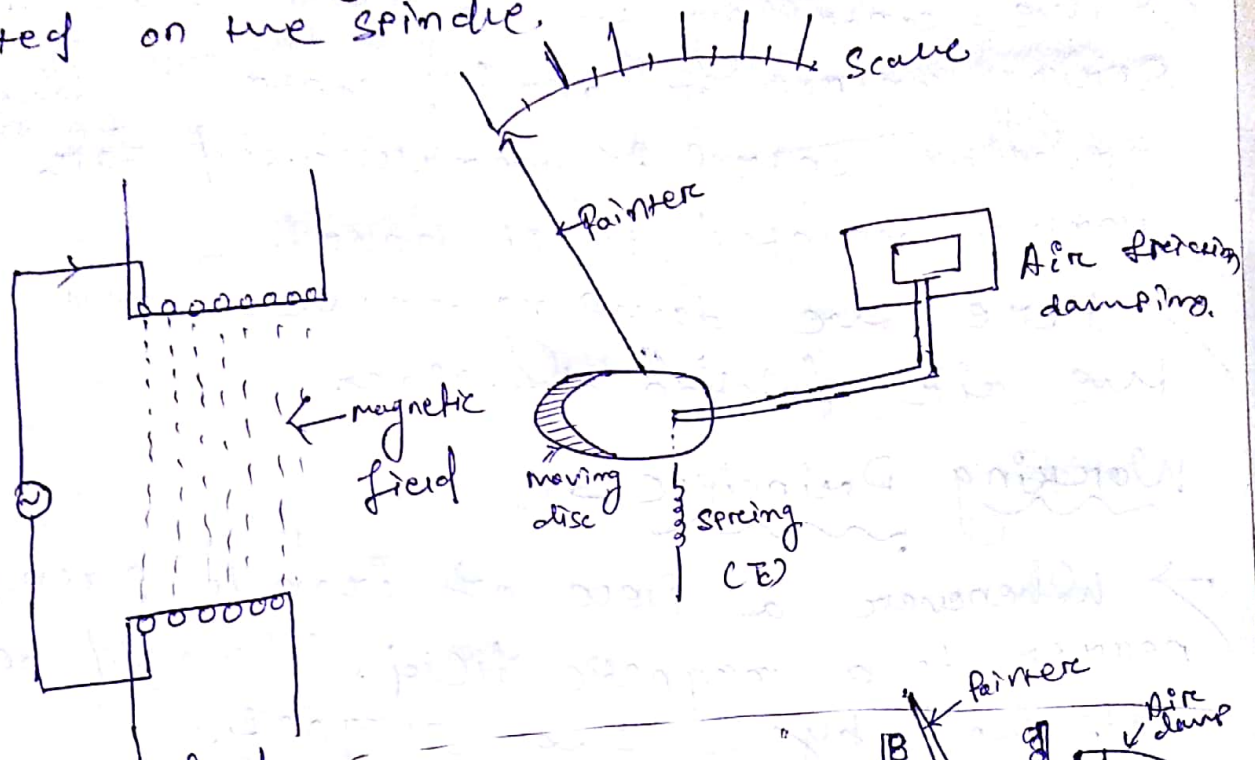
## Construction

It consists of a fixed coil & moving ~~coil~~ iron piece. The moving iron is a flat disc which is mounted on the spindle.





## Construction


- It consists of a fixed coil & moving iron piece. The moving iron is a flat disc which is mounted on spindle. A pointer is moves over a graduated scale.
- The no. of turns of the fixed coil depends upon the range of the instrument.
- The controlling torque is provided by either spring control or gravity control. & the gravity control is generally used for the vertical mounted panel board.
- Here the damping torque is provided by the air friction damping.

## Working Principle

- Whenever a piece of iron is placed nearer to a magnetic field, it would be attracted by the magnet.
- The force of attraction depends upon the strength of the magnetic field.
- If the magnetic electromagnet then the magnetic field strength can be ~~increased~~ increased or decreased by increasing or decreasing the current through the coil.
- When the supply is given & magnetic field produced then the moving iron moves from weak field to strong magnetic field & the pointer moves

from one position to other position.

## ② Repulsion Type MI Instrument

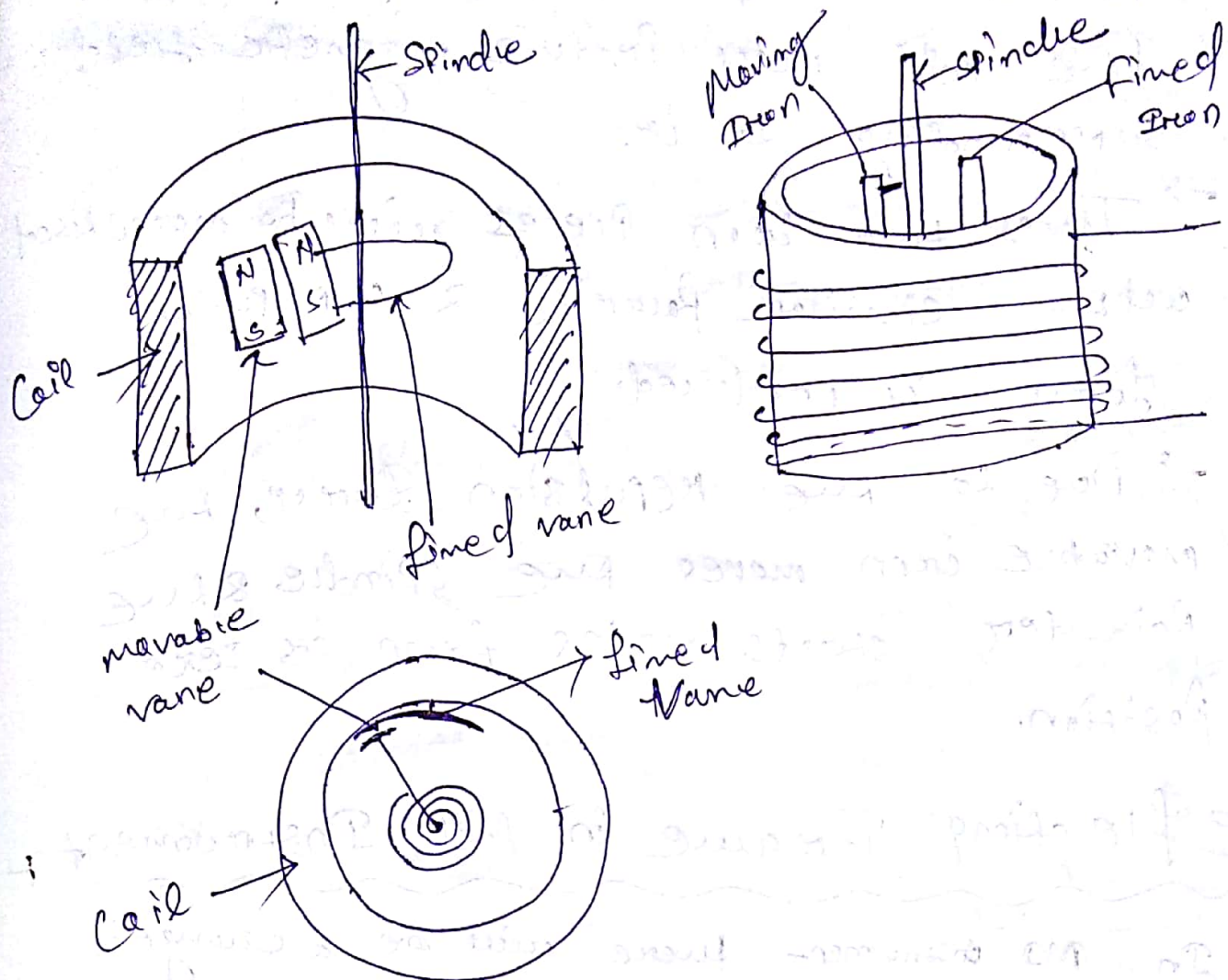

### Construction

- It consists of a hollow cylinder which will carry the operating current.
- The core consists of two iron pieces
  - (i) ~~one~~ one is fixed iron piece which is attached to the hollow cylinder.
  - (ii) Other is movable iron piece which is attached to the spindle.



## Working Principle

- When the instrument is connected to the supply current will flow in the fixed coil & the coil will produce magnetic field surrounding to it.
- Thus two iron pieces will be magnetised with similar polarity & a repulsion force is produced.
- Due to the repulsion force, the movable iron moves the spindle & the pointer starts moving from its zero position.

## Deflecting Torque in MI Instrument


- In MI instrument there will be a change in energy stored in the magnetic field due to change in inductance of the fixed coil.
  - This is because the Iron disc always try to occupies the position of minimum reluctance ( $\because$  Inductance is inversely proportional to the reluctance  $L \propto \frac{1}{S}$ )
- Let EMF Induce on the coil

$$V = \frac{d}{dt} LI$$

→ The medium of magnetic field & coil is air & relative  $\mu = \mu_0$   
 → when the disc enter to the magnetic field  
 $\mu$  changes to  $\mu_0 \mu_r$  because the medium  $\mu$  of m-field is  
 not completely air means  $\mu_r > 1$ .  
 where  $\mu_0 = \text{Relative Permeability of free space or air}$   
 $= 4\pi \times 10^{-7}$

$\mu_r = \frac{\text{change in relative permeability}}{\mu_0}$

(1 in free space or vacuum)

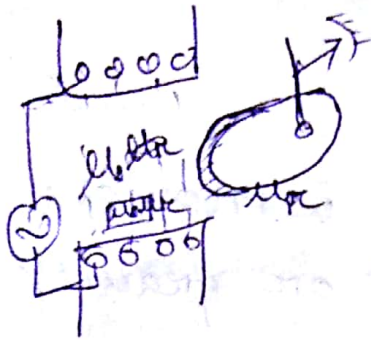

when Relative permeability changes Inductance  
 of coil changes because Inductance  
 depend upon  
 relative permeability.

$$L \propto \mu_0 \mu_r$$

$$L = \frac{\mu_0 \mu_r N^2 A}{l}$$

→ Inductance of a coil  
 $N = \text{no. of turns.}$

Inductance changes when position of moving  
 Iron changes, i.e. when  $\theta$  changes  
 then  $L$  changes.

$$L \propto \theta$$

so the Torque  
 is given by

$$T = \frac{dU}{d\theta}$$

→ Potential/Storage  
 Energy.

We know

Energy stored in an Inductor is

$$\frac{1}{2} LI^2 = U = \text{Potential energy}$$

We know Torque changes due to

Change in  $\theta$  &  $L$ .

$$T = \frac{1}{2} LI^2$$

$$T = U = \frac{1}{2} LI^2$$

Differentiating  $U$  w.r.t  $\theta$



$$T_d = \left( \frac{dD}{d\theta} = \frac{1}{2} I^2 \frac{dL}{d\theta} \right)$$

$$\Rightarrow \boxed{T_d = \frac{1}{2} I^2 \frac{dL}{d\theta}}$$

$$\text{So } \boxed{T_d \propto I^2} \quad \text{AC \& DC} \quad \boxed{T_d \propto V^2}$$

Controlling torque

Here controlling torque is provided by either spring control or gravity control

$$\boxed{T_c \propto \theta}$$


$$\Rightarrow \boxed{T_c = k_c \theta} \quad k_c = \text{Spring const.}$$

For steady state  $T_d = T_c$

$$\Rightarrow \frac{1}{2} I^2 \frac{dL}{d\theta} = k_c \theta \Rightarrow \theta = \frac{1}{2k_c} I^2 \frac{dL}{d\theta}$$


$$\Rightarrow \boxed{\theta \propto I^2}$$

(Non-linear <sup>Scale</sup> relation)

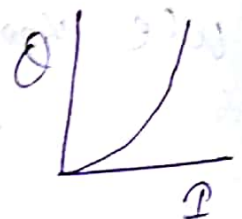

\* All indicating inst. works for AC as well as DC  
concept PMMC

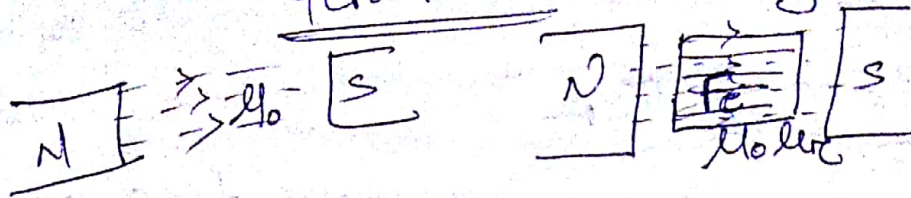Permeability - Adding to permit flow magnetic flux



$B$  = m. field density

$H$  = m. field strength




$$\mu = \frac{B}{H} = \text{Absolute } (\text{H/m}) \text{ Permeability}$$

$\mu$  = permeability is the relative increase or decrease in the resultant magnetic field inside a material compared with magnetizing field in which the given material is located.


$$B_0 = \mu_0 H$$
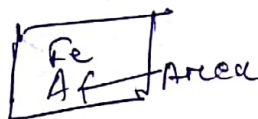
$$(\mu_0 = \text{P. of space} = 4\pi \times 10^{-7} \text{ Tm/A})$$



$$B_i = \frac{N}{A}$$

Induced  
field  
density

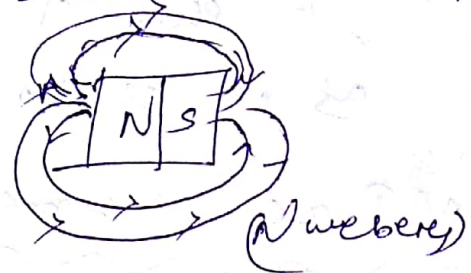

$$B = B_0 + B_i$$

$$= \mu_0 H + \frac{N}{A}$$

$$= \mu_r \cdot \mu_0 H = \mu_r B_0$$

$$\mu_r = \frac{B}{B_0} = \frac{B (\text{material})}{B_0 (\text{vacuum})}$$

$\mu_r$  = not const., changes with

$\mu_r = \frac{1}{5} \text{ (air)}$   
 $\frac{1}{5} \text{ (water)}$

→ position of material  
with re. to magnetic  
field

→ frequency of the field

→ temp.

→ any other factors.

$\mu_r$  = Relative Permeability of a material is the ratio b/w the flux density produced in the material & the flux density produced in a vacuum by the same magnetising force.



## Advantages MP as ammeter

→ Instrument used to measure the current in the ckt <sup>should be</sup> always connected in series with the ckt & carries the current to be measured.

→ The current flowing through the coil produces the desired deflecting torque.

→ It should have low resistance coil as it is to be connected in series.

## MP as Voltmeter

→ When MP inst. used to measure voltage ~~across~~ b/w two points in a ckt it should be always connected in parallel

→ Current flowing through the operating coil of the meter produces deflecting torque.

→ It should have high resistance <sup>coil</sup> ~~with~~ a high resistance of order of kilo-ohms is connected in series with the coil of the instrument

# Extension Range of Ammeter & Voltmeter

## M.I. type Instrument

- For a given M.I. instrument the Amp-torques necessary to produce full scale deflection are const
- One can ~~extend~~ <sup>extend</sup> the range of ammeter by providing a shunt coil with the moving iron or moving coil.
- Voltmeter range can be extended by connecting a resistance in series with the coil, hence the same coil winding specification may be employed for a no. of ranges.

### Advantages

- used for both AC & DC.
- No current carrying path in moving system hence inst reliable.
- good accuracy




### Disadvantages





- Non-uniform scale
- Error due to free magnetic field, hysteresis - error etc
- High power consumption



# DYNAMOMETER TYPE INSTRUMENT
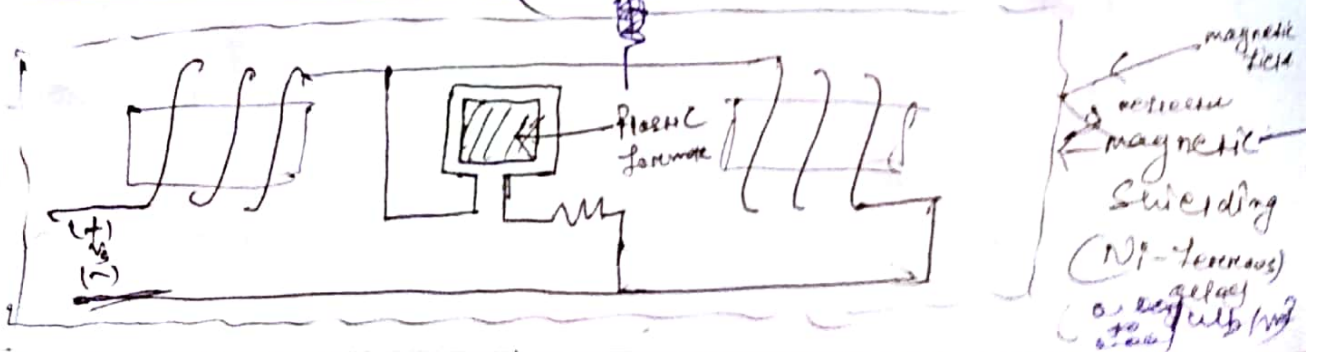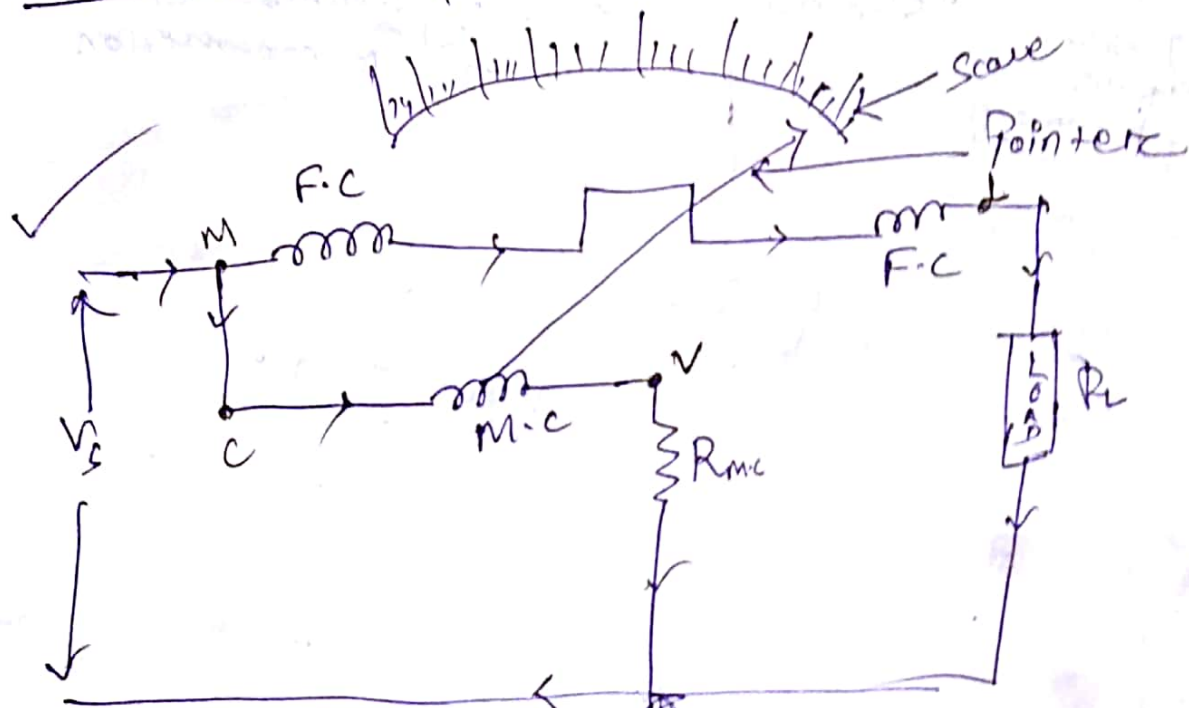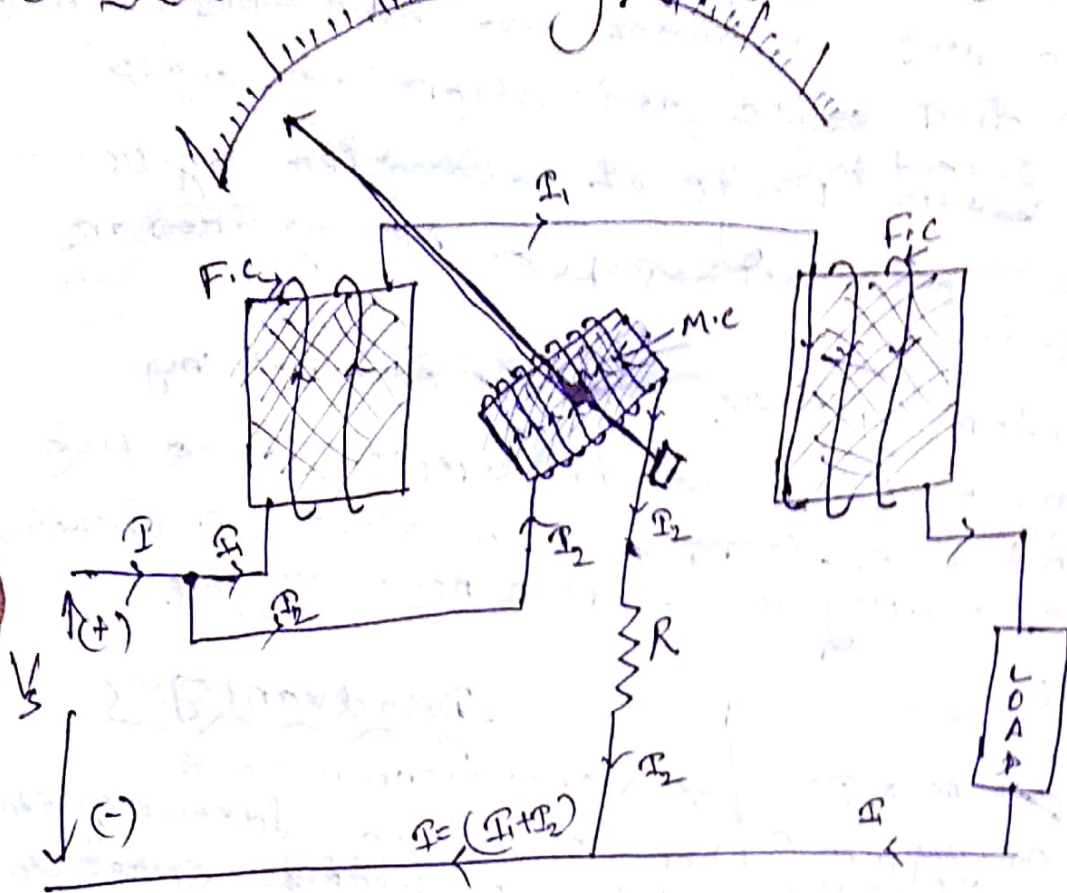
## ① Dynamometer Type Wattmeter Instrument



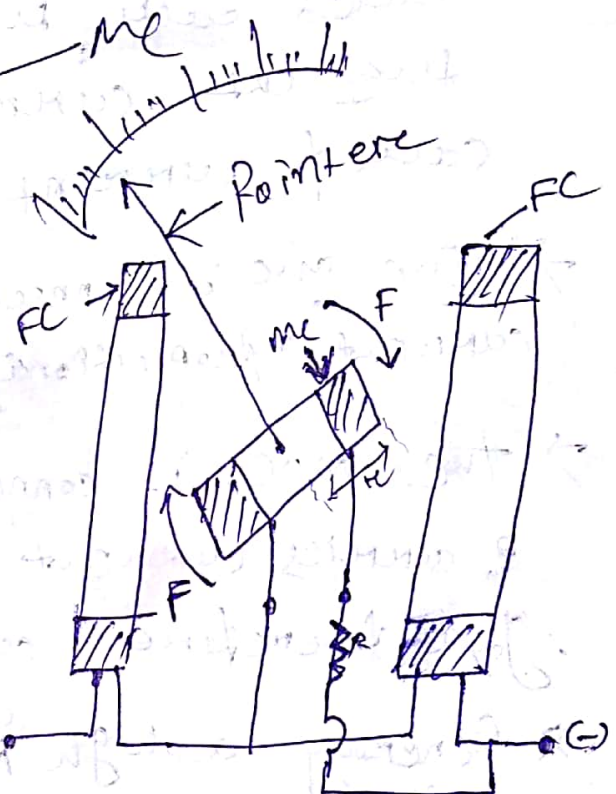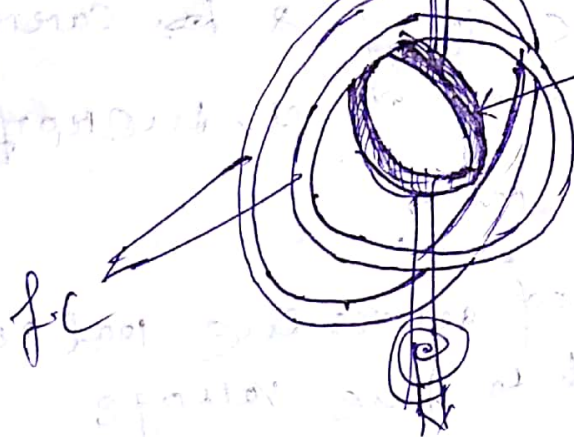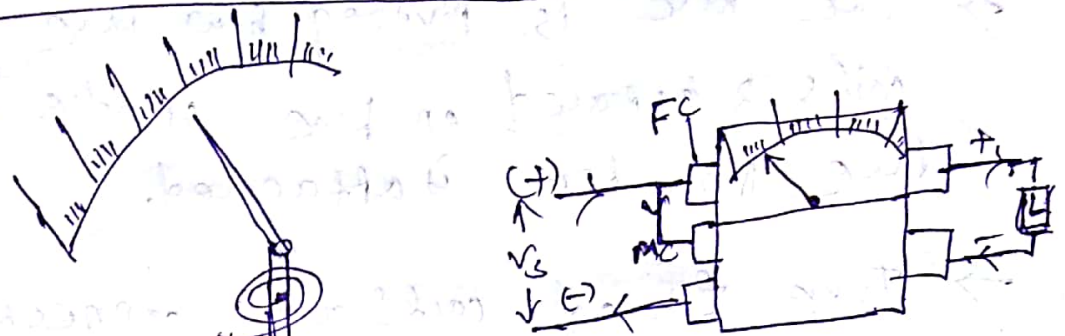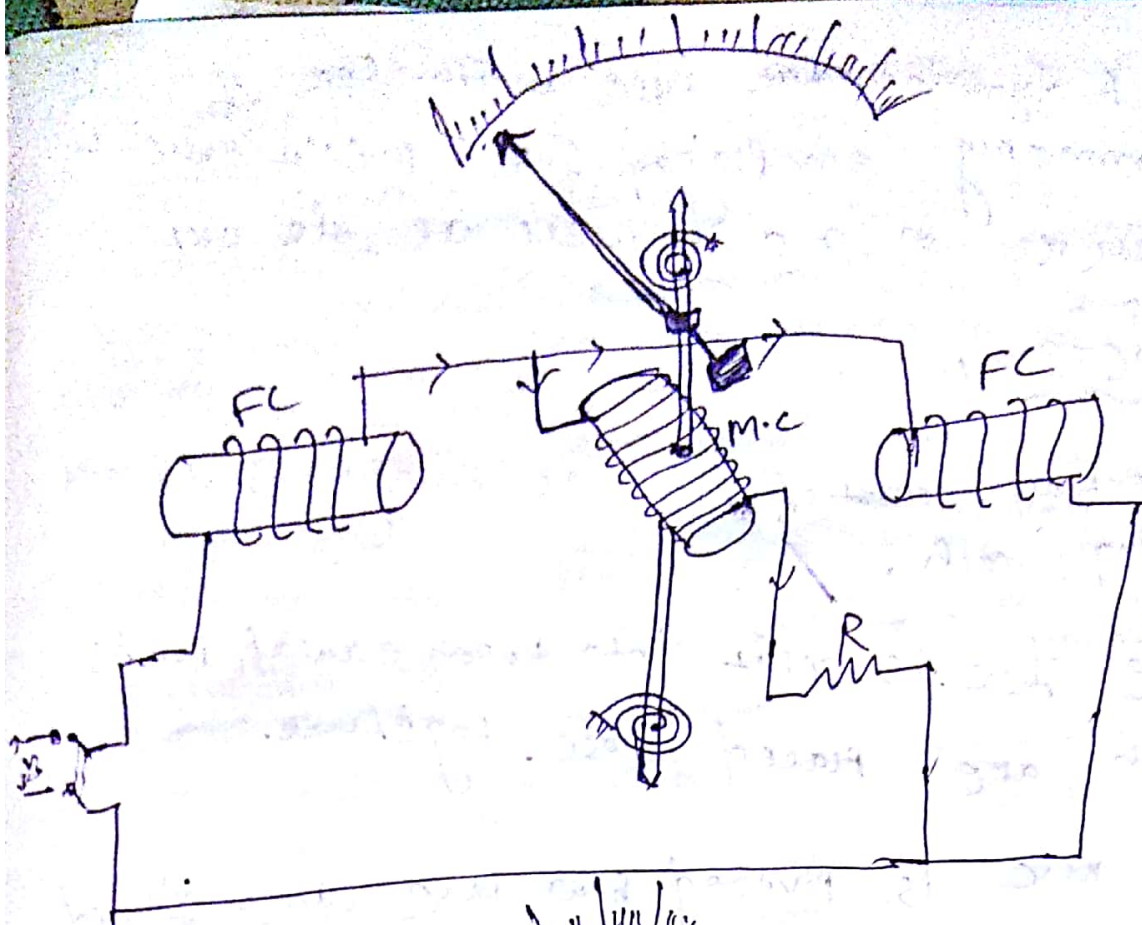

→ to neglect the effect of stray magnet.



Defn A dynamometer type wattmeter is most commonly employed for measurement of power in a.c as well as d.c.

### CONSTRUCTION

→ It essentially consist of two coils, namely fixed coil & moving coil.

→ The f.c is split into two equal parts which are placed close together.

→ The m.c is pivoted b/w the two fixed coils & is placed on the spindle to which the pointer is attached.

→ The fixed coils are connected in series with the load & carry the ckt current. It is, therefore called current coil.

→ The m.c is connected across the load & carries current proportional to the voltage.

→ The m.c is connected across the load & carries current proportional to the voltage. It is, therefore called potential coil.

→ Generally a high  $R$  is connected in series with potential coil to limit the current.


through it.

→ The controlling torque is provided by spring (which also serve the additional purpose of reading current into out of the moving coil).

→ In  $\phi$  type inst. plastic frame is used instead of Al frame to reduce Eddy current.

→ Air friction damping is employed in such inst. instruments.

## WORKING PRINCIPLE

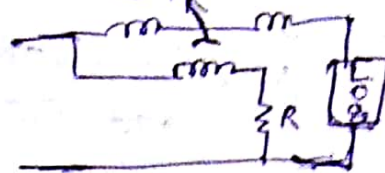

→ The C.C. is connected in series with load so that it carries the net current

→ The P.C./V.C. is connected across the load so that it carries current proportional to the voltage


→ Due to the current in the coils, mechanical force exists b/w them. The result is that the moving coil, moves the pointer over the scale.

→ The pointer comes to rest at a position where deflecting torque is equal to the controlling torque.  $C.T = T_c$

## TORQUE IN DYNAMOMETER TYPE W-METER
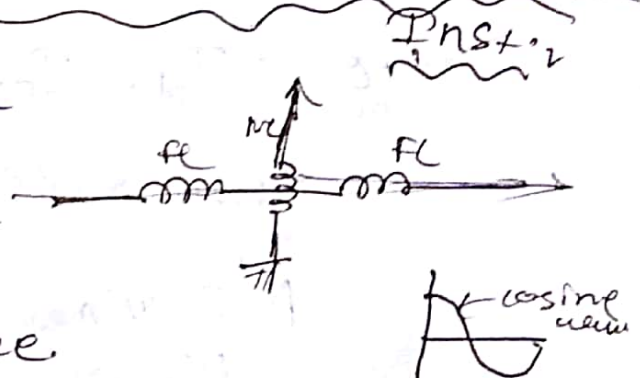
### Deflecting Torque

→ When m.c. moving ~~far~~ far from f.c. then magnetic field starts to reduce.






Then the deflecting torque produced in m.c. is directly proportional to current through F.C & current through m.c.

i.e.  $T_d \propto I_{mc} I_{fc}$

$T_d = I_{FC} I_{mc} \frac{dm}{d\theta}$

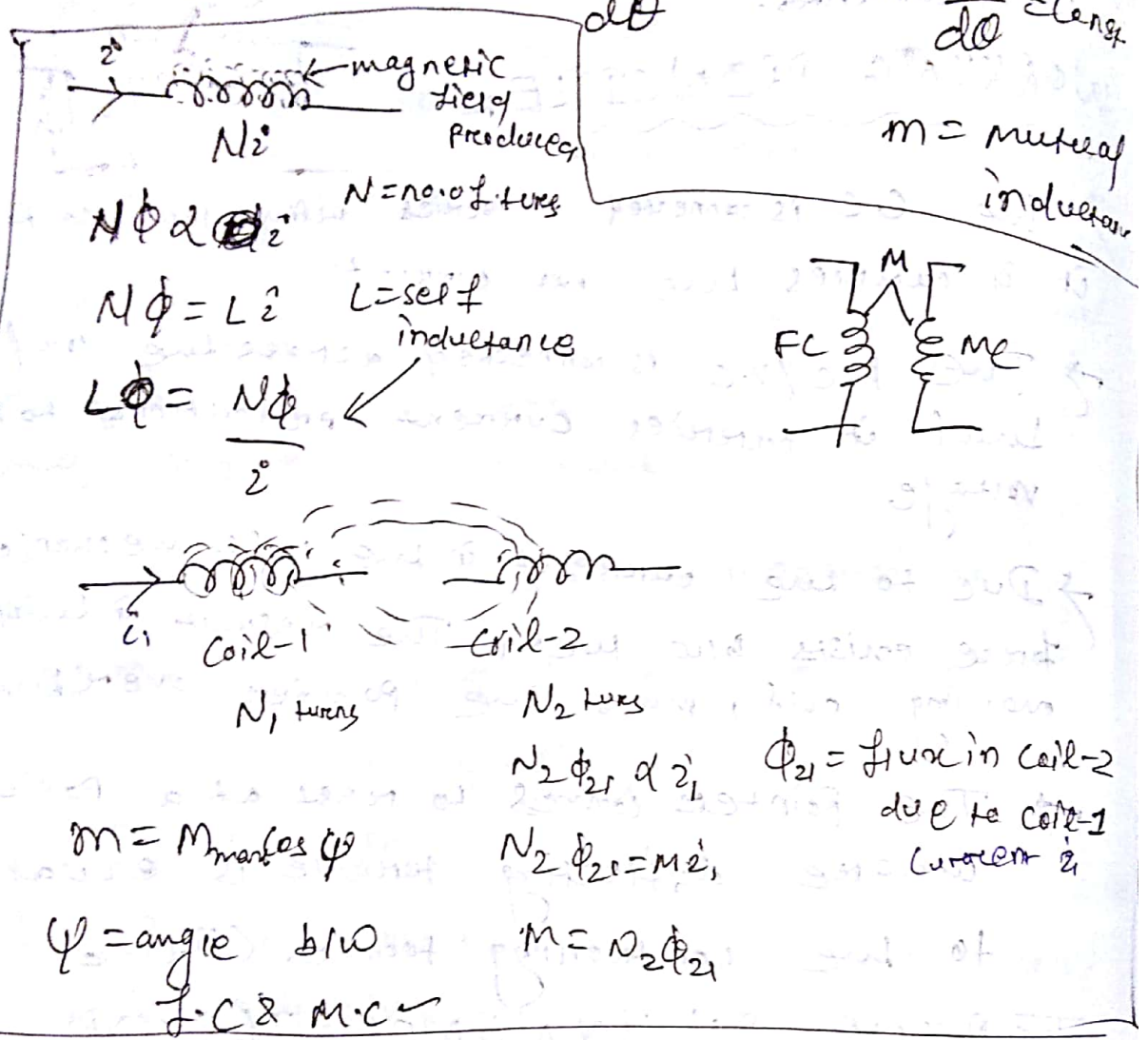where  $\frac{dm}{d\theta} = \text{const.}$




i.e.  $T_d = I_{FC} I_{mc} \frac{dm}{d\theta}$

Now make  $\frac{dm}{d\theta}$  const.

$M = m_{\max} \cos \phi$

$\phi = \theta$

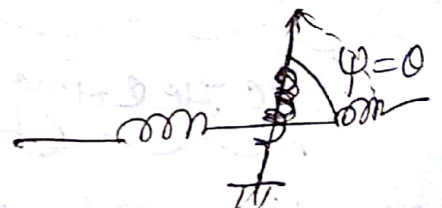


$\phi = \text{angle b/w P.M. \& F.C}$

$\phi = \text{angle b/w M.C \& F.C}$

$$m = m_m \cos \theta$$

$$\frac{dm}{d\theta} = m_m \sin \theta \neq \text{const.}$$

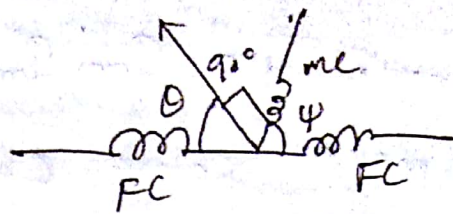✓ If pointer placed  $90^\circ$  from moving coil.



$$\theta + 90^\circ + \psi = 180^\circ$$

$$\psi = 90^\circ - \theta$$

$$m = m_m \cos \psi$$

$$= m_m \cos (90^\circ - \theta)$$

$$\Rightarrow m = m_m \sin \theta$$

$$\frac{dm}{d\theta} = m_m = \text{const.}$$

we know

$$\sin \theta \approx \theta$$

$$\sin \frac{\pi}{6} = 0.5$$

$$\Rightarrow \frac{\pi}{6} = 0.52 \approx \sin \frac{\pi}{6}$$

→ In ED type Inst. pointer is placed  $90^\circ$  from the moving coil.

$$T_d = I_{fc} \neq I_{mc} \frac{dm}{d\theta}$$

→ ED works on ac as well as dc

✓ in case of dc,  $I_{mc} = I_1$

$$T_d = I_1 I_2 \frac{dm}{d\theta}$$

$$I_{fc} = I_2$$

arg. name are const. var

In case of AC

$$I_{mc} = I_m \sin \omega t$$

$$I_{fc} = I_m \sin (\omega t - \phi)$$



$$T_{\text{instantaneous}} T_d = I_{m1} I_{m2} \sin \omega t \sin(\omega t - \phi) \frac{dm}{d\omega}$$

To make same calibration for AC as well as DC take average value

$$T_{\text{avg}} = \frac{1}{2\pi} \int_0^{2\pi} T_{\text{inst.}} d\omega t$$

$$\Rightarrow T_{\text{avg}} = \frac{I_{m1} I_{m2}}{2\pi} \int_0^{2\pi} (\cos(2\omega t - \phi) \cos \phi) d\omega t$$

$$= \frac{I_{m1} I_{m2}}{4\pi} \left[ \frac{\sin(2\omega t - \phi)}{2} \right]_0^{2\pi} + \cos \phi \cdot [\omega t]_0^{2\pi}$$

$$= \frac{I_{m1} I_{m2}}{4\pi} \left[ \frac{\sin(2\pi - \phi)}{2} - \frac{\sin(-\phi)}{2} \right] + (\cos \phi) [2\pi - 0]$$

$$= \frac{I_{m1} I_{m2}}{4\pi} \left[ \frac{-\sin \phi}{2} + \frac{\sin \phi}{2} \right] + (\cos \phi) [2\pi - 0]$$

$$= \frac{I_{m1} I_{m2}}{4\pi} \times (\cos \phi) (2\pi)$$

$$T_{\text{avg}} = \frac{I_{m1}}{\sqrt{2}} \times \frac{I_{m2}}{\sqrt{2}} \cos \phi \frac{dm}{d\omega}$$

$$T_{\text{avg}} = (I_{\text{fe}})_{\text{rms}} \times (I_{\text{me}})_{\text{rms}} \cos \phi \frac{dm}{d\omega}$$

$$\begin{aligned} \sin A \cos B &= \cos(A+B) \\ &\quad - \cos(A-B) \end{aligned}$$

$$\begin{aligned} \sin \omega t \sin(\omega t - \phi) &= \cos(2\omega t - \phi) \\ &\quad - \cos \phi \end{aligned}$$

$$T_d = I_{\text{fe}} I_{\text{me}} \cos \phi \frac{dm}{d\omega}$$

$\phi = \text{angle between } I_{\text{fe}} \text{ \& } I_{\text{me}}$

→ ED type inst. always read RMS value

In case

$$B = \mu_0 \mu_r \frac{NI}{l}$$


$$F = B I_2 \cdot l \cdot N$$

$$F = \mu_0 \mu_r \frac{N^2 I_1 I_2}{2l}$$

$$T_d = F \cdot 2r$$

$$\Rightarrow T_d = \mu_0 \mu_r \frac{N^2 I_1 I_2}{2l} \cdot 2r$$

$$T_d \propto I_1 I_2$$

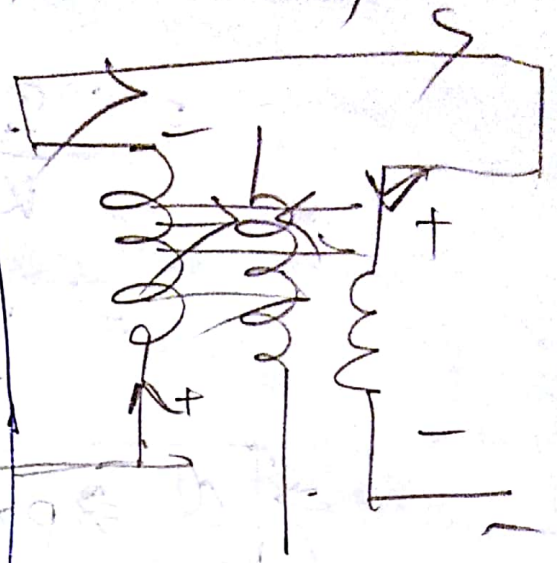

$T_d$

② Controlling Torque

→ The controlling torque is produced due to spring.

$$T_c \propto \theta$$

$$T_c = K_c \theta$$

At equilibrium

$$T_d = T_c$$

For DC

$$\Rightarrow I_1 I_2 \frac{dM}{d\theta} = K_c \theta$$

$$\Rightarrow \theta = \frac{I_1 I_2}{K_c} \frac{dM}{d\theta}$$

$$\theta \propto I_1 I_2$$

$K_c = \text{Spring const.}$

$\theta = \text{angle of deflection.}$

For AC

$$T_d = T_c$$

$$\Rightarrow I_{fc} I_{mc} \cos \phi \frac{dM}{d\theta}$$

$$= K_c \theta$$

$$\Rightarrow \theta = \frac{I_{fc} I_{mc} \cos \phi}{K_c} \frac{dM}{d\theta}$$



We know that  $P_{mc} = \frac{V}{R_{mc}}$

$$\Rightarrow 0 = \cancel{P_{mc}} \frac{I_{fe} \cdot V}{K_c \cdot R_{mc}} \cos \phi \frac{dm}{d\theta}$$

$$= \frac{I_{fe} \cdot V}{K_c \cdot R_{mc}} \cos \phi \frac{dm}{d\theta}$$

$$= \frac{V I_{fe} \cos \phi}{K_c \cdot R_{mc}} \frac{dm}{d\theta}$$

$$\Rightarrow \boxed{Q \approx P \left( \frac{1}{K_c \cdot R_{mc}} \frac{dm}{d\theta} \right)}$$

where  $P = \text{avg. power being measured}$

### Advantages


- Used for both AC & DC operation
- Uniform scale
- Light weight due to air core.
- Less power consumption.
- Range of the instrument can be easily change.
- Can be measured in vertical & horizontal position.
- Accuracy is more.

### Disadvantages

- Readings can be affected by stray magnetic field, therefore entire magnetic surrounding is received.

→ Error occurs due to the inductance of the M.C or P.C or pressure coil at low power factor is vary.

Dynamometer type Instrument as ammeter

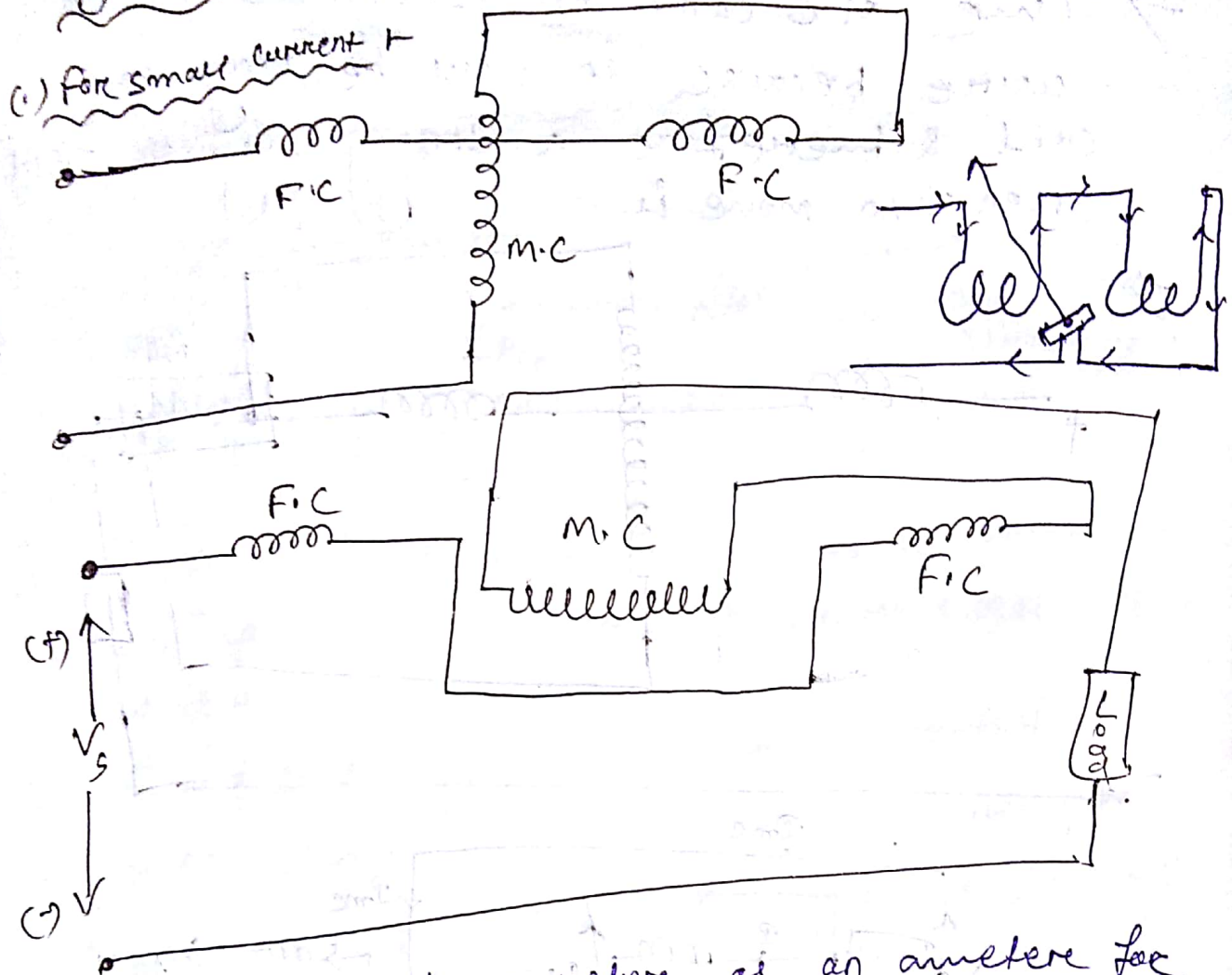

→ To use the dynamometer as an ammeter for a measurement of small current the moving coil & fixed coil are connected in series. ~~at this~~ In this case current in fixed coil equal to the current in moving coil.

$$I_{fc} = I_{mc}$$

when  $T_d = T_c$




$$\theta \propto I_{fc} I_{mc}$$

$$\theta \propto I^2$$



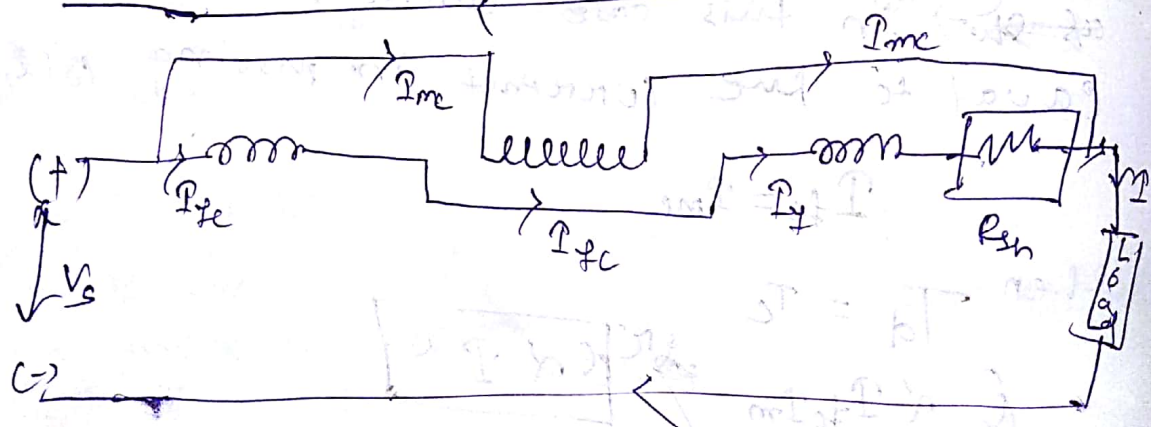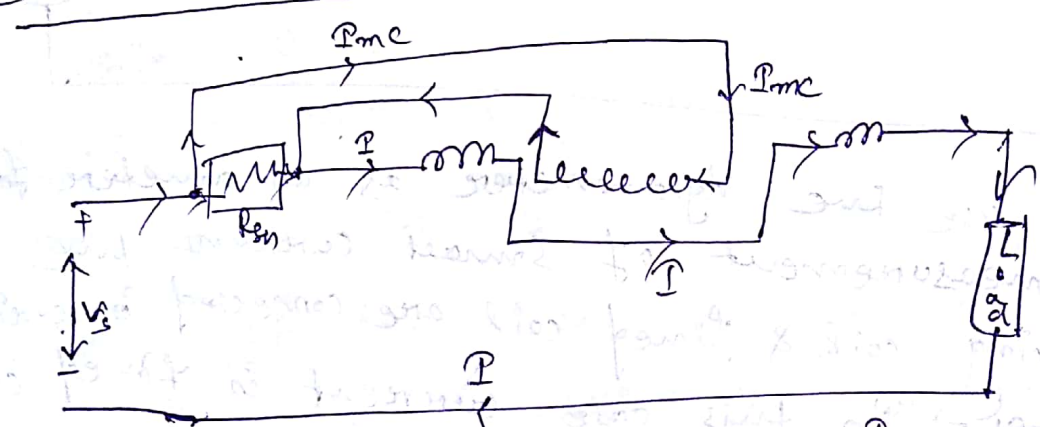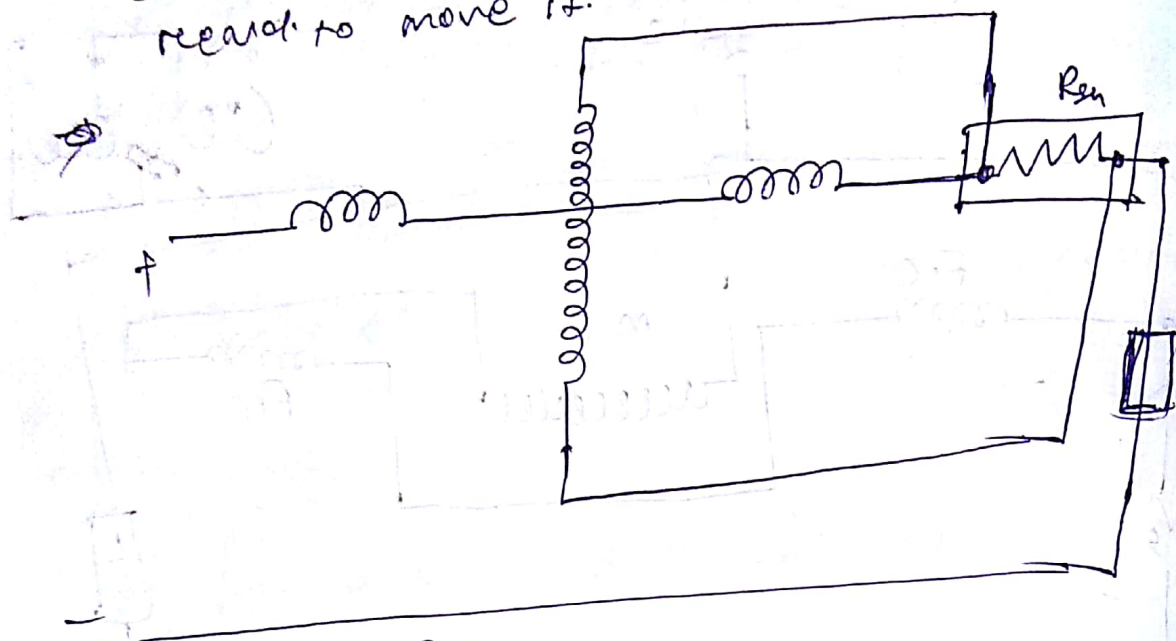
(ii) For high current, when the DM is ~~used~~ to be used for measurement of higher currents, the F.C are wound with wire.

→ The m.c can't be wound with such wire because it will ~~be~~ <sup>become</sup> very heavy coil & therefore hard to move it. a strong magnetic field



→ The difficulty is overcome by connecting the moving coil terminals of a short resistance  $R_{sh}$  or one terminal of M.C & one terminal of  $R_{sh}$  can be connected <sup>across</sup> the short resistance. For measurement of higher current.

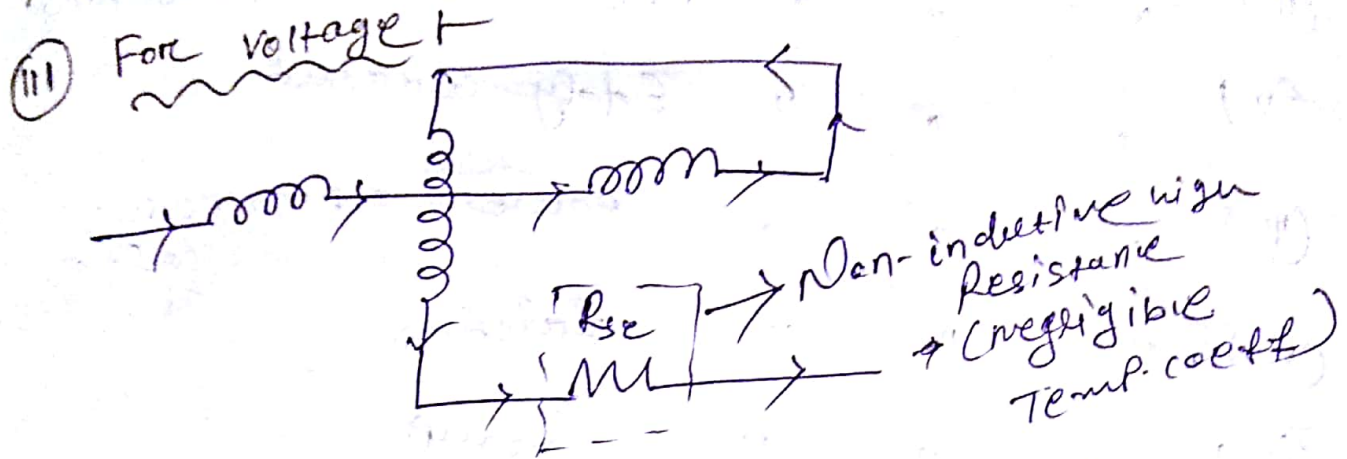→ ~~Thus the  $R_{sh}$  limits the current in M.C.~~



→ When DM is to be used as a voltmeter the coils are wound with high resistance

→ Fixed & moving coils are connected in series along with a high Non-inductive, ~~low~~ resistance  $R_{se}$  which have negligible Temp. coeff.

→ In this case same current flows through both of the fixed & moving coils.

$$T_d \propto V^2$$

$$T_d = T_c$$

$$\propto V^2$$




## Error in dynamometer type Instruments


→ The various types of errors in DM-type instruments are

- (i) Error due to M.C or Pressure coil Inductance
- (ii) " " " " M.C or P.C Capacitance
- (iii) " " " " Eddy current
- (iv) " " " " power loss in pressure coils or M.C
- (v) " " " " friction
- (vi) " " " " temp.
- (vii) " " " " stray magnetic field


# Induction type Instrument

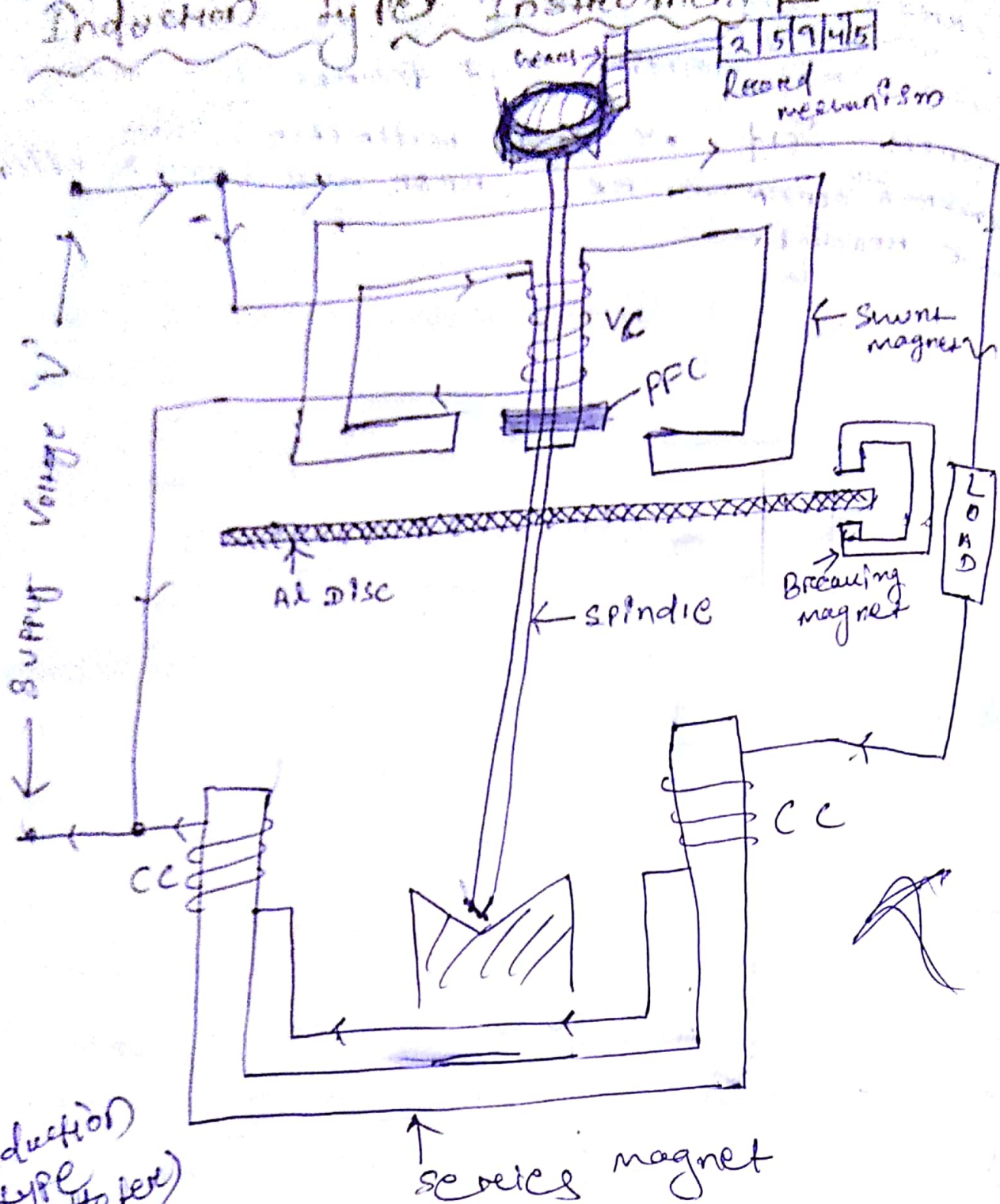

Induction type wattmeter

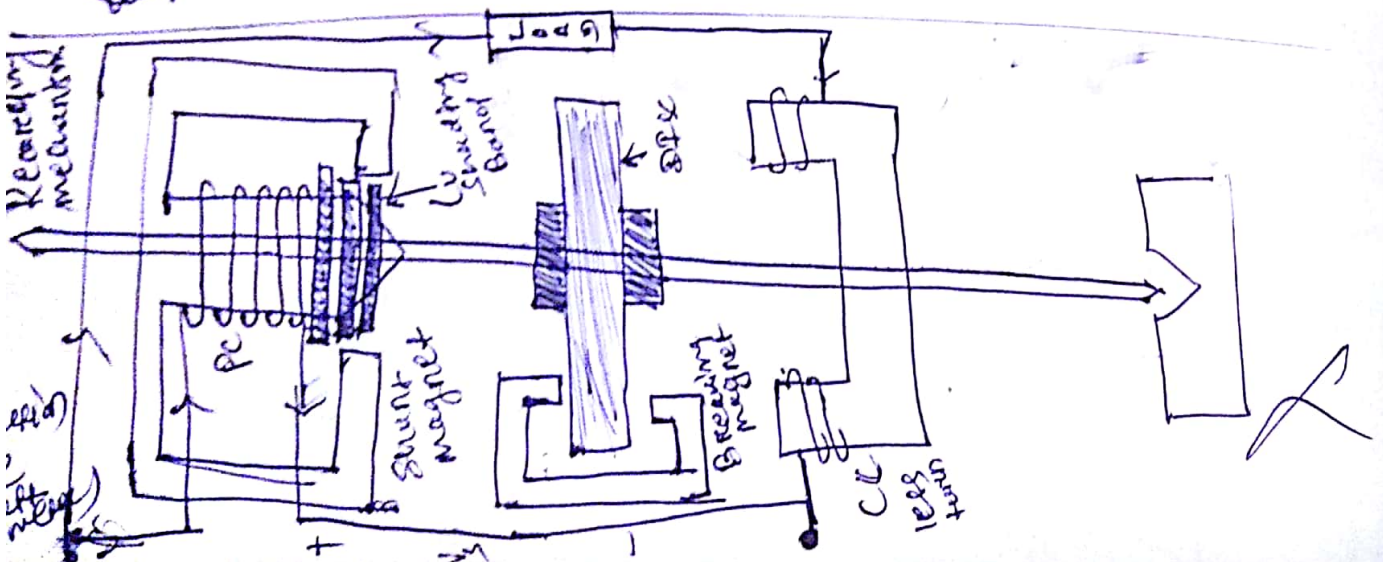



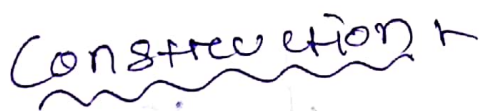

- Scanned with CamScanner


→ A Pointere is attached to the  
 spindle.  
 The springs controlling fore and  
 the provided by two strings.  
Working principle

→ When current flowing  
 through the coil flux  
 lines coming from one  
 pole to another pole  
 of electromagnet through  
 the air gap

→ The disc cuts the  
 flux lines.

→ Let flux is  $\phi$   
 current is  $I$

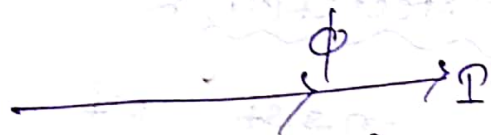→ Due to current  $I$  flux  $\phi$  is created  
 so there is no phase difference  
 b/w  $I$  &  $\phi$




→ When A.C. disc cuts the flux lines  
 there will be a circulating eddy  
 current induced in the disc.

→ The eddy current  $I$  induced due  
 to  $\text{cmf}$  which has been  
 induced due to induction  
 of the flux at that disc



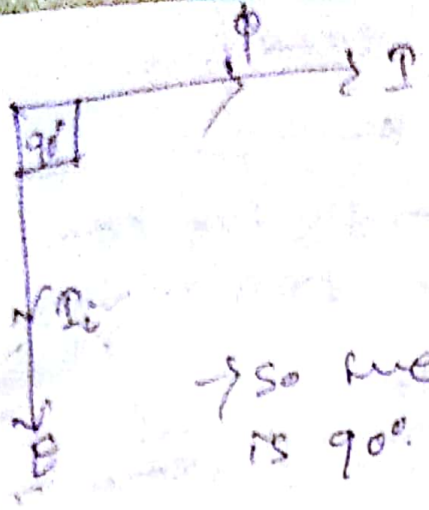→ The  $\text{emf}$  lags the flux  $\phi$  by  
 $90^\circ$  ~~due to~~ because the disc  
 is very resistive.





→ The eddy current  $I_2$  has no phase diff. with induced emf 'E'.

→ So the phase diff. b/w  $\phi$  &  $I_2$  is  $90^\circ$ .

→ ~~Therefore~~ Torque will be produced due to the  $\phi$  of the electromagnet & the eddy current ' $I_2$ '.



→ Therefore the Torque is directly proportional to the value of  $\phi \& I_2$  & as well as cosine angle  $\phi$  b/w  $\phi \& I_2$ .


$$\therefore T = K \phi I_2 \cos 90^\circ$$

$T$  = value of torque acting on the disc. ( $K$  = Proportionality const.)

$$\therefore T = 0$$

There is no torque acting on the this neither rotation.

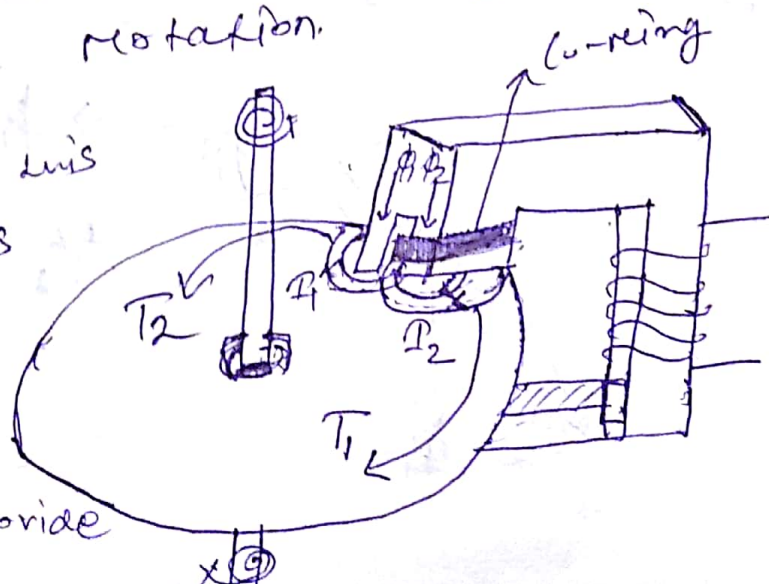→ To overcome this a groove piece is cut from one pole face of the electromagnet & a Cu ring is provide



to a ~~rough~~ grooved pole face.

→ Now there will be two flux induce of, one through the copper winding  $\phi_1$  & another flux through the electromagnet  $\phi_2$


→ Due to main flux ( $\phi$ ) ~~due to~~ <sup>of</sup>  $\phi$  in 'C' ring one current will induce in 'C' ring & that current will produce another flux which will ~~produce another~~ <sup>of</sup> the main flux.

→ Because of the opposition of new flux & main flux a resultant flux  $\phi_2$  is produce.

→  $\phi_1$  is in phase with main flux  $\phi$

→ Due to opposition of main flux  $\phi_2$  is induced there is some phase diff b/w ~~main flux~~  $\phi_1$  &  $\phi_2$  is  $\beta$ .

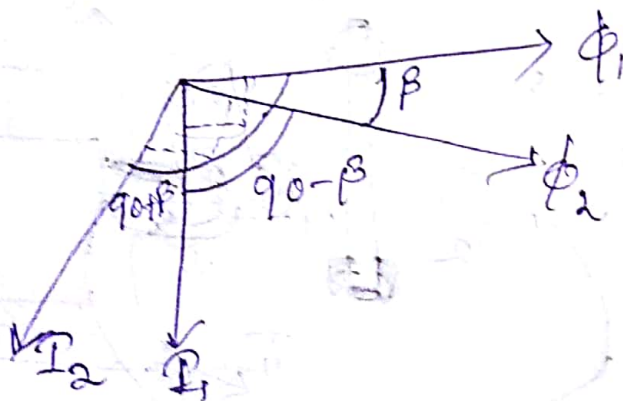→  $I_1$  eddy current induced due to  $\phi_1$   
Similarly  $I_2$  due to  $\phi_2$





→ Now there will be a torque acting on disc due to interaction of  $\phi_2$  &  $I_1$

(No torque due to interaction of  $\phi_1$  &  $I_2$  & also  $\phi_2$  &  $I_2$ .)

Let the torque be  $T_1$

$$\therefore T_1 = k_1 I_1 \phi_2 \cos(90^\circ - \beta)$$

$k_1 \equiv \text{prop. const.}$

$$\text{But } I_1 \propto \phi_1 \Rightarrow I_1 = k_0 \phi_1$$

$$\cancel{I_1} \propto \phi_2 \text{ & } \cos(90^\circ - \beta) = \sin \beta$$

So we can write

$$\boxed{T_1 = k \phi_1 \phi_2 \sin \beta}$$

where  $k = \text{prop. const. of } \phi_1 \text{ & } I_1 \text{ & } k_1$

$$\boxed{k = k_1 k_0}$$

Similarly due to interaction of  $\phi_1$  &  $I_2$  another torque acting.

$$\therefore T_2 = k_2 I_2 \phi_1 \cos(90^\circ + \beta)$$

$$\cancel{I_2} \propto \phi_2 = k_0 \phi_2$$

$$\cos(90^\circ + \beta) = -\sin \beta$$

$$\therefore \boxed{T_2 = -k \phi_1 \phi_2 \sin \beta}$$

→ Because of two torques  $T_1$  &  $T_2$  there will be a resultant torque that will deflect the disc & hence we can write

$$T_d = T_1 - T_2$$

$$= k_1 \phi_1 \phi_2 \sin \beta - (-k \phi_1 \phi_2 \sin \beta)$$

$$= k \phi_1 \phi_2 \sin \beta + k \phi_1 \phi_2 \sin \beta$$

$$\boxed{T_d = 2k \phi_1 \phi_2 \sin \beta}$$

$$\therefore \boxed{T_d \propto \phi_1 \phi_2}$$

The actual cause of  $\phi_1$  &  $\phi_2$  is main current  $I$  entering through the coil

$$\text{So } \phi_1 \propto I \checkmark$$

$$\phi_2 \propto I \checkmark$$

$$\therefore \boxed{T_d \propto I^2}$$

→ The controlling torque provided by the spring

$$T_c \propto \theta$$

At steady state

$$T_d = T_c$$



$$\Rightarrow 2k\phi_1\phi_2 \sin\theta = k_c \theta$$

$$\Rightarrow \theta = \frac{2k\phi_1\phi_2 \sin\theta}{k_c}$$

$$\boxed{\theta \propto \phi_1\phi_2} \checkmark$$

### Advantages ✓

- Less expensive as compared to MD instrument
- It has high torque to weight ratio as compared to other instruments.
- Accuracy is good.

### Disadvantages ✓

- Can use for AC measurements only.
- Non linear scale
- consume more power as comp. to other instruments.
- Errors are caused due to temp., waveform & frequency changes.

# Rectifier Type Instrument

Rectifier  $\rightarrow$  AC signal to DC signal

$\rightarrow$  For diff. signals we use diff instr.

For AC signal  $\rightarrow$  RMS value should measure


DC signal  $\rightarrow$  Avg. value should measure

$\rightarrow$  ~~Some~~ AC signals can't be measured by AC-instr.  
~~like~~ communication signals i.e. wireless signal.

$\rightarrow$  communication signals are low volt. & high freq. signal

$\rightarrow$  MI, dynamometer, & Induction type meters are the instr. can measure

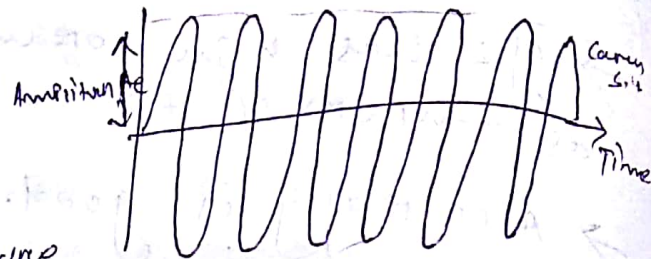AC-signal but can't measure this type of signal



$\rightarrow$  This instr. can only measure those AC-signal which have <sup>only</sup> power frequency (i.e. 50 to 60 Hz)   
 i.e. which freq. we can generate & transmit.

$\rightarrow$  ~~It~~ only PMMC type indicating instrument can measure communication signal (AC)

$\rightarrow$  PMMC instr. <sup>can</sup> only measure DC, so it need some extra arrangement to measure high freq. signal.

$\rightarrow$  A rectifier circuit arrangement with the PMMC instr. so that it can measure ~~the average~~ <sup>this type</sup> value of signal.




AC  $\rightarrow$  Rectifier  $\rightarrow$  DC  $\rightarrow$  Avg value  $\times$  Form Factor

$$\Rightarrow \text{Avg. value} \times \frac{\text{RMS}}{\text{Avg. value}}$$

$$= \text{RMS} = \text{AC value.}$$

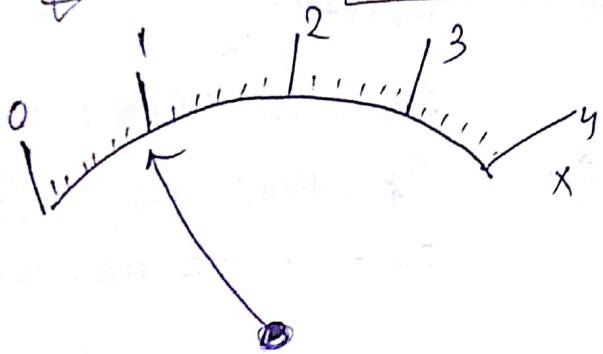$\rightarrow$  i.e. Reading of Rectifier type inst = PMMC meter reading  $\times$  Form Factor



$\times$  F.F. = Reading of Rectifier type inst.

$\rightarrow$  After rectification of signal PMMC instrument measure the Avg. value of DC component & then the Avg. value multiply with form factor so that user get RMS value which is AC quantity value.

$\rightarrow$  Instead of multiplying repeatedly with form factor the measured value with the scale is replaced by another calibrated scale which is already multiplied with F.F. So calibrated that it is already multiply with F.F.

$\rightarrow$  There is a limitation of rect. type instrument :-


(1) while measuring a signal the nature of the signal shouldn't be changed i.e. if it's sinusoidal then only sinusoidal calibrated inst. used otherwise it will give error at o/p.

→ Basically rectifier type inst. are two types.

(1) Half wave Rectifier,

(2) Full wave Rectifier.

① Half wave Rectifier type

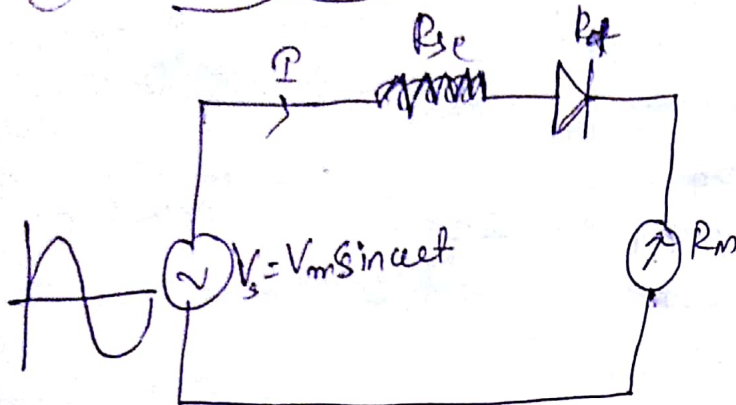

where

$R_{se}$  = series resistance

$R_d$  = diode resistance

$R_m$  = meter resistance

Ideal diode =  $R = 0 \rightarrow F.B$   
 $R = \infty \rightarrow R.B$

practical "  $R = R_d \rightarrow F.B$

$R = \infty \rightarrow R.B.$

→ In this circuit a rectifying element is connected in series with the sinusoidal volt. source, PMMC inst. & a series multiplier resistance ( $R_{se}$ )

→ The func<sup>n</sup> of the resistance is to limit the current drawn by PMMC instrument

→ The given circuit is a voltmeter, so

$$R_{ew} \text{ or } R_v = R_{se} + R_d + R_m$$

$$V_s = V_m \sin \omega t$$

$$I_{avg} = \frac{I_m}{\pi} \quad \& \quad I_m = \frac{V_m}{R_{ew}}, \quad \begin{cases} V_m = \sqrt{2} V_{rms} \\ V_{rms} = \frac{V_m}{\sqrt{2}} \\ V_{avg} = \frac{V_m}{\pi} \end{cases}$$

$I_m$  = meter current



$$I_{avg} = \frac{V_m}{\pi (R_{ew})} = \frac{V_m}{\pi (R_{se} + R_d + R_m)} = \frac{\sqrt{2} \times V_{rms}}{\pi (R_s + R_d + R_m)}$$

$$= \frac{V_{avg}}{R_{ew}}$$

$$I_{avg} = 0.45 \frac{V_{rms}}{R_{ew}}$$

$$V_{avg} = 0.45 V_{rms}$$

$$I_{avg} = \frac{V_{avg}}{R_{ew}}$$

$$\therefore V_{avg} = 0.45 V_{rms}$$

$$FF = \frac{V_{rms}}{V_{avg}}$$

$$V_{rms} = FF \cdot V_{avg}$$

$$V_{avg} = \frac{V_{max}}{\pi}$$

$$V_{rms} = \frac{V_{max}}{\sqrt{2}}$$

$$V_{rms} = 1.11 \times V_{avg}$$

$$V_{rms} = 1.11 V_{avg}$$

$$\% \text{ Error} = \left( \frac{V_{rms} - V_{true}}{V_{true}} \right) \times 100$$

$$= \left( \frac{1.11 V_{avg} - FF \cdot V_{avg}}{FF \cdot V_{avg}} \right) \times 100$$

→ Hence sensitivity of half wave rectifier instrument with ac is 0.45 times its sensitivity with dc.



$$V_{FSD} = 1.11 R_{ew} I_{mFSD}$$

$$R_v = \frac{1}{1.11} \times \left( \frac{1}{I_{mFSD}} \right) \times V_{FSD}$$

$$\frac{R_v}{V_{FSD}} = 0.90 S_{ac} = S_{ac}$$

$$S_{ac} = 0.45 S_{dc}$$

## ② Full wave Rectifier type

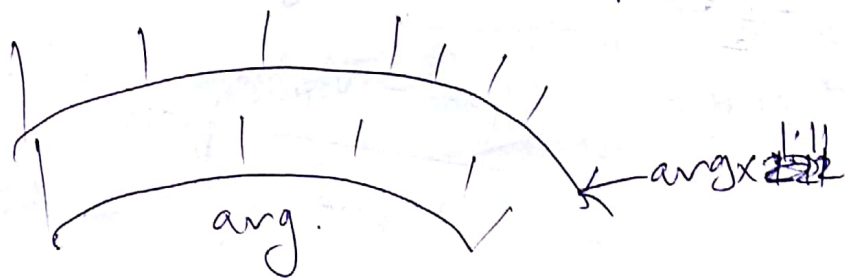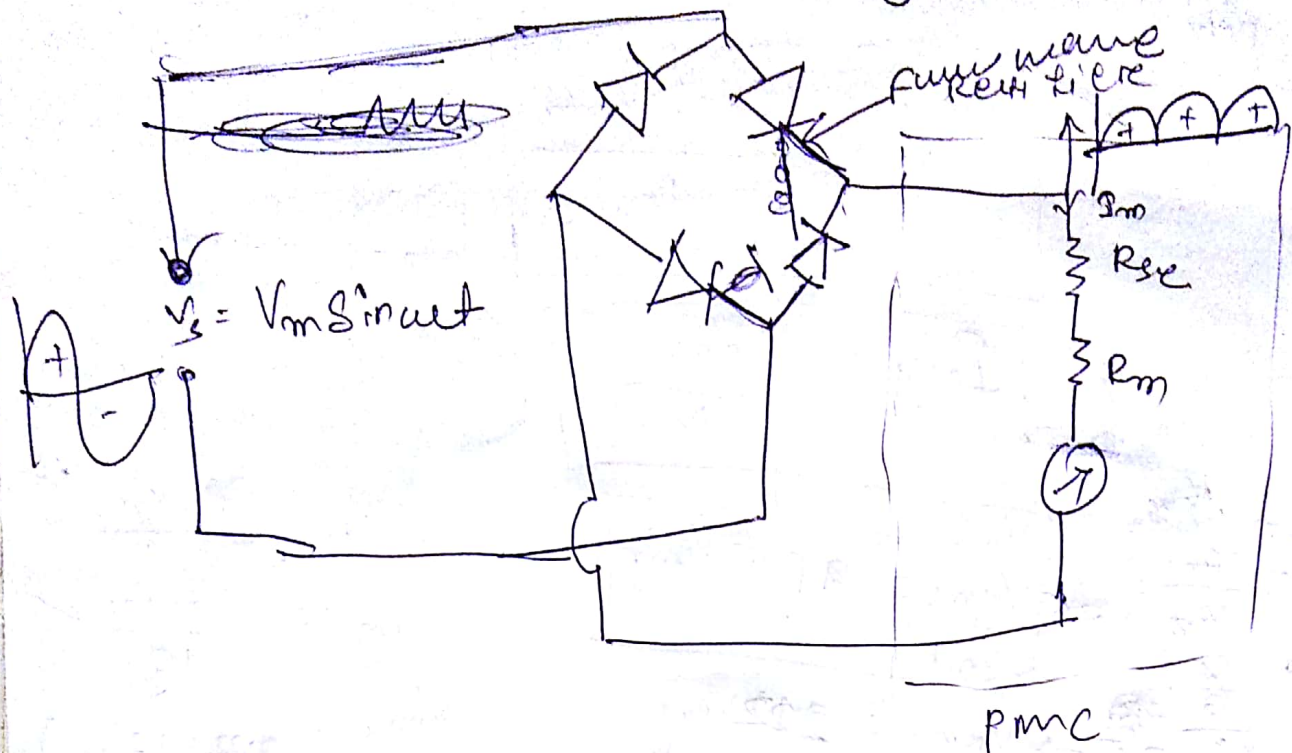

→ In this case a full wave bridge rectifier is connected ~~in series~~ across a PMMC instrument & a series multiplier resistance & a voltage source.

$$R_{eq} \text{ or } R_v = R_s + R_m + 2R_d$$

( $2R_d \rightarrow$  because <sup>only</sup> two diodes ~~only~~ conduct at a time)

$$I_{avg} = \frac{2 I_m}{\pi}$$

$$V_s = V_m \sin \omega t$$

$$V_m = \sqrt{2} V_{rms}$$

$$V_m = \frac{\pi}{2} V_{avg}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$V_{avg} = \frac{2 V_m}{\pi}$$



$$\frac{2}{\pi} \left( \frac{V_m}{R_s + R_m + 2R_d} \right) = \frac{2}{\pi} \left( \frac{\sqrt{2} V_{rms}}{R_s + R_m + 2R_d} \right)$$

$$I_{avg} = \frac{0.9 V_{rms}}{R_v}$$

$$\frac{2.22}{\pi}$$

$$I_{avg} = \frac{2.22}{\pi} V_{rms}$$

$$V_{avg} = \frac{2}{\pi} V_m$$

$$V_{rms} = 1.11 V_{avg}$$

In dc case

$$I_m = \frac{V_s}{R_{ew} \text{ or } R_v} = \frac{V_s}{R_v} \quad (V_s \Leftrightarrow V_{rms})$$

$$(I_m)_{ac} = \frac{0.9 V_{rms}}{R_v} = 0.9 (I_m)_{dc}$$

$$(I_m)_{ac} = 0.9 (I_m)_{dc}$$

$$V_{FSD} = 1.11 \times R_v \times I_{mFSD}$$

$$\theta \propto I \rightarrow \theta_{ac} = (0.9) \times \theta_{dc}$$

$\theta$  = angle of deflection.

Sensitivity

$$S = \frac{\theta}{V} \quad S \propto \theta \propto \frac{1}{V}$$

$$S_{ac} = 0.9 S_{dc} \quad \checkmark$$

$$V_{FSD} =$$

Form factor =  $\frac{RMS}{Avg}$

$\frac{V_{rms}}{V_{avg}}$

$V_{avg} = \frac{FWR}{2} \frac{V_m}{\pi}$

$V_{rms} = \frac{V_m}{\sqrt{2}}$

FWR FF =  $\frac{\frac{V_m}{\sqrt{2}}}{\frac{2 V_m}{\pi}} = \frac{\pi}{2\sqrt{2}} = 1.11$

~~HWR F.F. =  $\frac{V_m}{\pi}$~~

HWR F.F. =  $\frac{\frac{V_m}{\sqrt{2}}}{\frac{V_m}{\pi}} = 2.22$

HWR


$V_{avg} = \frac{V_m}{\pi} \cdot \frac{\pi}{2}$

$V_{rms} = \frac{V_m}{\sqrt{2}}$


Extend the range of instruments by shunts & multipliers

SHUNT - A shunt is a low-value resistance having minimum temp. coeff. & is connected parallel with the measuring instrument to extend the range.

→ shunts are used of ammeters.

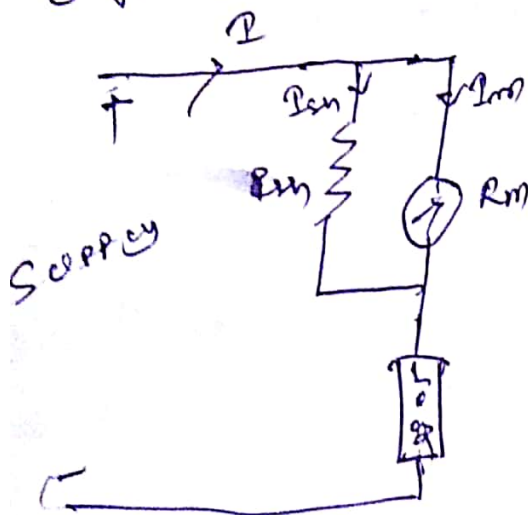

For the range extends

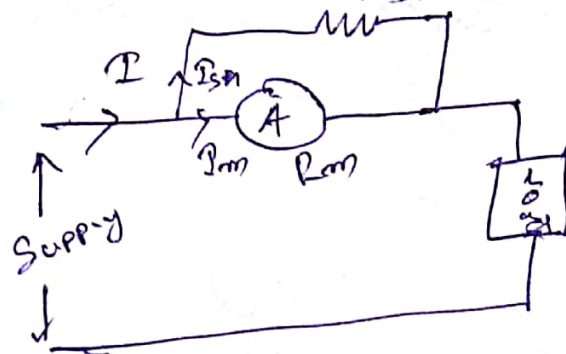



Let  $I$  = current of the cut to be measured

$I_m =$  " Passing through the instrument or ammeter

$I_{sh}$  = current passing through the shunt.

$R_{sh}$  = Resistance of the shunt.

$R_m$  = Resistance of the meter/ammeter.

Thus,  $I = I_m + I_{sh}$  (1)

Also since the voltage drop across the shunt & the instrument is same.

$$\therefore P_{Sn} R_{Sn} = I_m R_m \quad \text{or} \quad R_{Sn} = \frac{I_m}{P_{Sn}} R_m$$

Substituting,  $I_{sn} = I - I_m$  from eqn-①, we get

$$R_{sh} = \frac{I_m}{(I - I_m)} \cdot R_m$$

or  $R_{su} = \frac{R_m}{\left(\frac{P}{P_m} - 1\right)}$  ————— (11)



→ The ratio of  $\frac{P}{P_m}$  is known as "multiplying factor of the shunt". The ratio  $\frac{P}{P_m}$  denoting by  $N$ , we have

$$R_{sn} = \frac{R_m}{N-1}$$

→ The swansts are made of a material such as;  $\text{manganin (Cu, Mn, \& Ni)}$ , which has a negligible temp. coeff. of resistance.

Multipplier  $g_t$  is a highly non-inductive resistance connected in series with the instrument to extend the range of the meter.

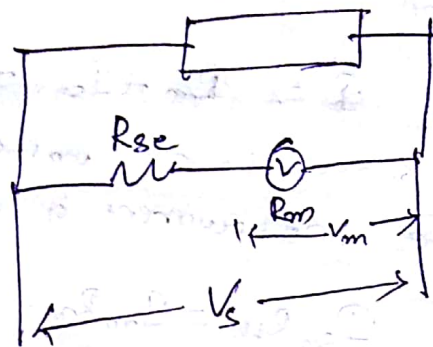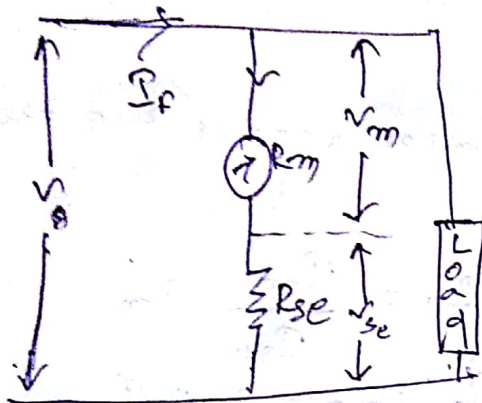→ multipliers are used for the <sup>range</sup> extension of voltmeters.



Let  $I_f$  = Full scale deflection current of voltmeter

$R_m$  = Internal resistance of the instrument or voltmeter

$V_s$  = Voltage of the vt to be measured

$V_m$  = Voltage drop across  $R_m$

$V_{se}$  = " " " "  $R_{se}$

The V-drop across the internal resistance ~~at the~~ <sup>series</sup> & external resistance ~~on~~  $R_{se}$  are directly proportional to their resistance values, since the same current ( $I_f$ ) passing through them, i.e.,

$$V_{se} = I_f R_{se} \quad \& \quad V_m = I_f R_m$$



$$\text{or } \frac{V_{se}}{V_m} = \frac{I R_{se}}{I R_m} = \frac{R_{se}}{R_m}$$

$$\text{or } \frac{V_{se}}{V_m} + 1 = \frac{R_s}{R_m} + 1$$

$$\Rightarrow \frac{V_{se} + V_m}{V_m} = \frac{R_{se} + R_m}{R_m}$$

$$\Rightarrow \boxed{\frac{V}{V_m} = \frac{R_s + R_m}{R_m}} \quad (\because V = V_{se} + V_m)$$

The ratio of the voltage across the entire ckt to the voltage across the instrument

$\left(\frac{V}{V_m}\right)$  is called the multiplying power or multiplication factor or multiplier (m).

$$\therefore \boxed{m = \frac{R_{se} + R_m}{R_m}} \quad (m = \frac{V}{V_m})$$

$$\Rightarrow \boxed{R_{se} = R_m(m-1)}$$


i.e. - for measuring  $m$  times the voltage, range of the instrument, the resistance of series multiplier resistance is equal  $(m-1)$  times the internal resistance of the instrument

## Numericals

- ① A PMMC inst. gives full scale deflection with 5mA & has a resistance of  $5\Omega$ . calculate the resistance of the necessary components in order that instruments may be used as:
- ② (i) 2A & 5A ammeters (ii) 10V & 100V voltmeters

Sol<sup>n</sup>

(i) For  $I = 2A$ .

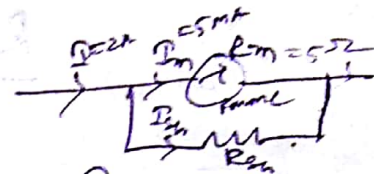


multiplication factor  $N = \frac{I}{I_m} = \frac{2A}{5 \times 10^{-3}A} = 400$

Thus  $R_{sh} = \frac{R_m}{N-1} = \frac{5}{400-1} = 0.0125\Omega$

For  $I = 5A$ .

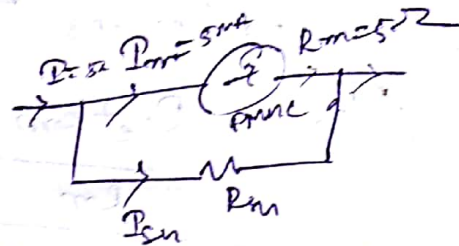$N = \frac{I}{I_m} = \frac{5}{5 \times 10^{-3}} = 1000$




$R_{sh} = \frac{R_m}{N-1} = \frac{5}{1000-1} = \frac{5}{999} \approx 5 \times 10^{-3}\Omega$

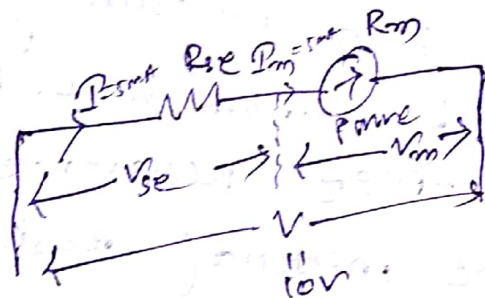(ii) For  $V = 10V$

meter volt. drop?

$V_m = I_m R_m$   
 $= 5 \times 10^{-3} \times 5$   
 $= 25mV$



Multiplication factor:  $m = \frac{V}{V_m} = \frac{10}{25 \times 10^{-3}} = 400$




$$R_{se} = R_m(m-1) = 5(400-1) = 1995$$

For  $V=100V$

$$V_m = 25mV$$
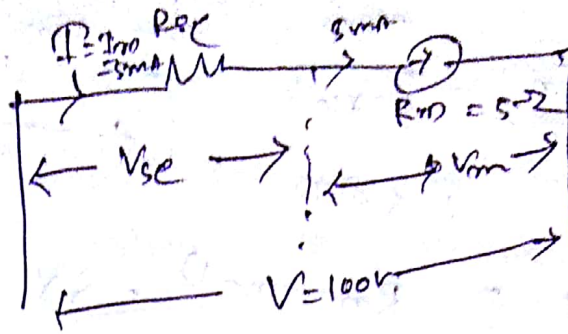
$$m = \frac{V}{V_m} = \frac{100}{25 \times 10^{-3}} = 4000$$




$$R_{se} = R_m(m-1) = 5(4000-1) = 19995 \Omega$$

② How will you use a PMMC inst. which gives FSD at 50mV p.d. & 10mA current as,

(i) Ammeter 0-10A (ii) Voltmeter 0-250V range.

Given  $V$ -drop across meter  $V_m = 50mV$

$$FSD: I_m = 10mA$$

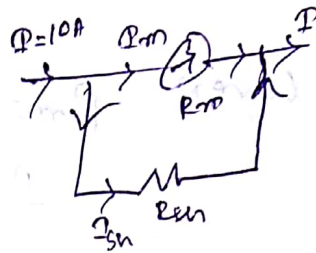

(i) As ammeter 0-10A range

$$\text{Meter resistance: } R_m = \frac{V_m}{I_m} = \frac{50 \times 10^{-3}}{10 \times 10^{-3}} = 5 \Omega$$


$$R_m = 5 \Omega$$

$$m = \frac{I}{I_m} = \frac{10}{10 \times 10^{-3}} = 1000$$

$$R_{sh} = \frac{R_m}{(m-1)} = \frac{5}{(1000-1)} = 5.005 \times 10^{-3} \Omega$$

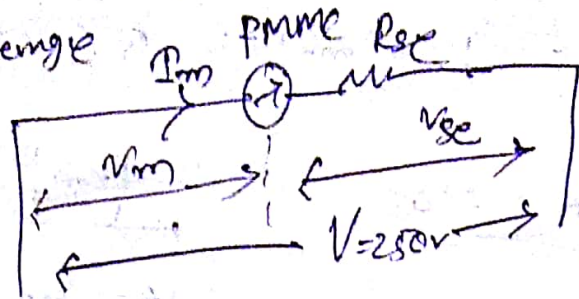(ii) Voltmeter 0-250V range

$$m = \frac{V}{V_m} = \frac{250}{50 \times 10^{-3}} = 5000$$



$$R_{se} = R_m(m-1) = 50(5000-1) = 249950 \Omega$$

- (3) A moving coil inst. having a resistance of  $50 \Omega$  has a FSD of  $1 \text{ mA}$ , calculate
- $R_{sh}$  to convert in Ammeter of  $2 \text{ A}$  range
  - Net resistance of meter.

Sol<sup>n</sup>

Given  $R_m = 50 \Omega$ ,  $I_m = I_{mA} = 1 \times 10^{-3} \text{ A}$

$$I = 2 \text{ A}$$


$$m = \frac{I}{I_m} = \frac{2}{1 \times 10^{-3}} = 2000$$

$$\begin{aligned} (i) R_{sh} &= \frac{50}{m-1} \\ &= \frac{50}{2000-1} = \frac{50}{1999} = 0.025 \Omega \end{aligned}$$

$$(ii) R_{net} = R_m \parallel R_{sh}$$

$$= 50 \parallel 0.025$$

$$= \frac{50 \times 0.025}{50 + 0.025}$$

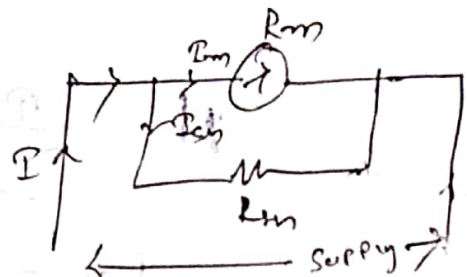

$$= 0.02498 \Omega$$



1) A moving coil inst. has a 'R' of  $2\Omega$ , it reads upto  $250V$  when a 'R' of  $5000\Omega$  is connected in series with it. Find the current range of Inst. when it is used as an ammeter with the coil connected across a shunt resistance of  $2m\Omega$ .

sol<sup>n</sup>

$$R_m = 2\Omega$$

$$V_m = ?$$

$$I_{se} = ?$$

$$V = 250$$

$$I_m = ?$$

$$R_{se} = 5000\Omega$$

$$I = ?$$

$$R_{se} = \frac{R_m}{\frac{I}{I_m} - 1}$$

$$R_{sh} = \frac{V - V_m}{I_m}$$

$$V = I_m (R + R_m) \Rightarrow 250 = I_m (5000 + 2)$$

$$\Rightarrow I_m = 49.98mA$$

$$V_m = \frac{I_m}{R_m} = \frac{49.98 \times 10^{-3}}{2} =$$

$$R_{sh} = 2m\Omega = 2 \times 10^{-3}\Omega$$

$$I_{sh} = \frac{I_m R_m}{R_{sh}} = \frac{49.98 \times 10^{-3} \times 2}{2 \times 10^{-3}}$$


$$= 49.98A$$

$$I_{\text{range}} = I_m + I_{sh} = 49.98 \times 10^{-3} + 49.98$$

$$= 50.02A$$
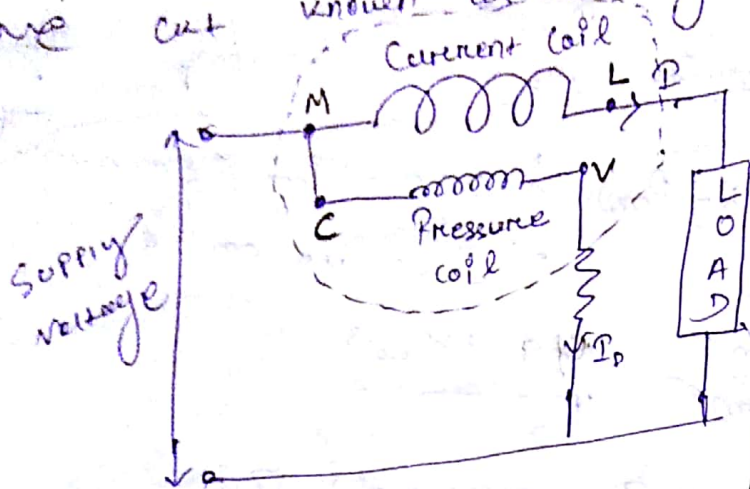
# CHAPTER-3: WATTMETERS & MEASUREMENT {OF POWER}


WATTMETER - The wattmeter is an instr. for measuring the electric power in watts of any given ckt.  
 → The ~~power~~ instr. consist of two coils, one coil is in series with the ckt. known as current coil & the <sup>other</sup> coil connected in parallel with the ckt. known as voltage coil.



M = main supply  
 L = Load  
 C = common  
 V = voltage.

→ The given ckt diagram is basic construction of any wattmeter.

## ELECTRODYNAMOMETER TYPE WATTMETER

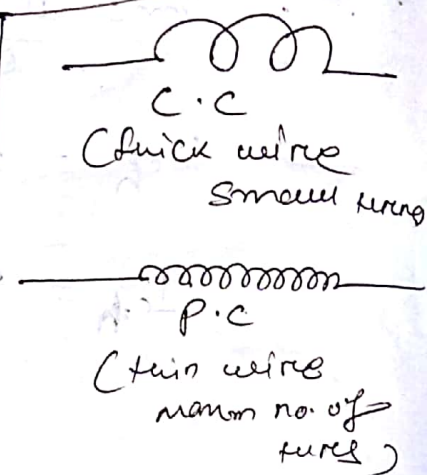

- These instr. are similar in design & construction to electro-dynamometer type ammeter & voltmeters.
- It consist of two coils are connected in diff. ckt arrangement to measure the power.
- The fixed coils or field coils are connected in series with the load & so carry the current in the ckt, therefore the fixed coils form current coil. are CC in wattmeter.
- The moving coil is connected in parallel with the load & carries a current proportional to



stage & it is called the pressure coil or voltage coil or P.C. of the wattmeter.

### Construction

→ It consists of two coils, one is fixed coil & other one is moving coil.

→ The FCs carries the current in the circuit & they are divided into two halves FC<sub>1</sub> & FC<sub>2</sub>

→ The fixed coils ~~can be made~~ can be made to carry considerable current so that there is no problem in carrying the current.

→ The fixed coils are wound with heavy wires & less no. of turns.

→ The moving coil is mounted on a pivoted spindle & is embraced by the fixed current coils.


→ A high non-inductive ~~or a high resistive~~ resistance is connected in series with the moving coil to limit the current to a small value, since the MC carries a current proportional to the voltage.

→ Both FC & MC are air cored in electrodynamic type instrument.

→ Spring control is used for the instrument.



→ Air friction damping is used in ~~for~~ for damping force to come.

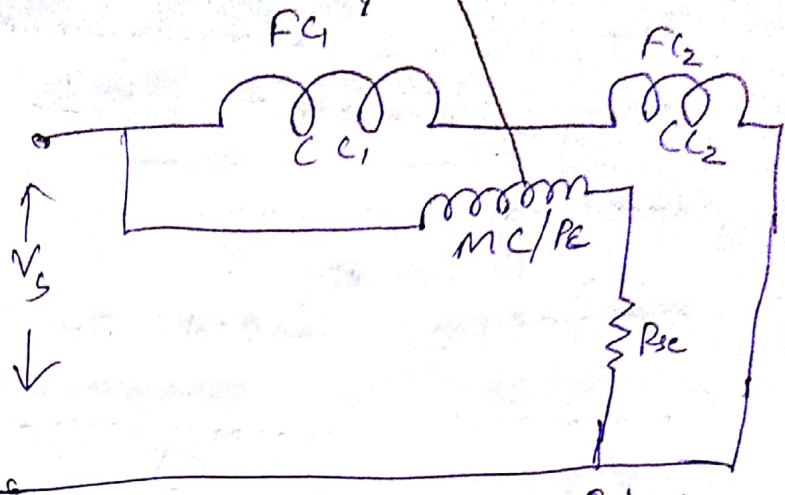→ It is equipped with mirror type scales & knife edge pointers to remove reading errors due to Parallax.


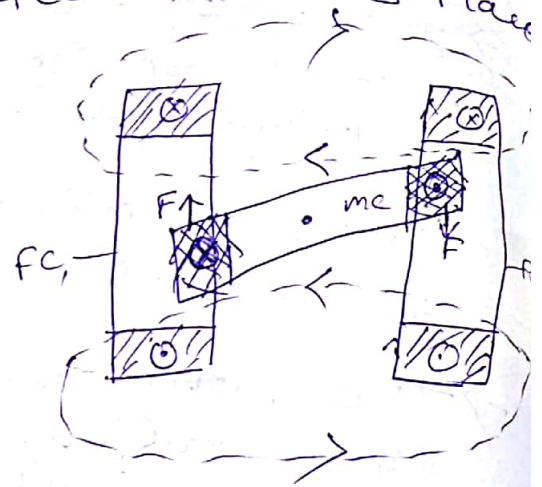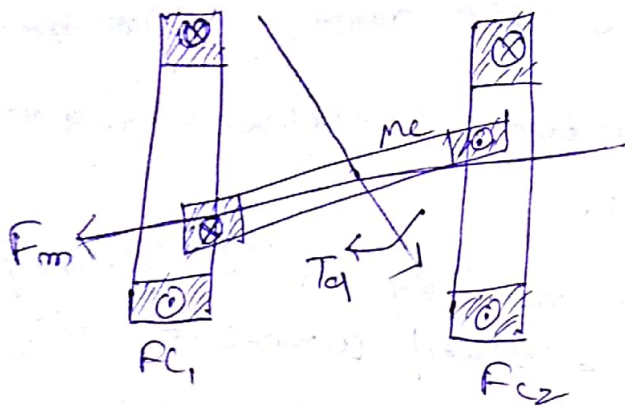
## Working Principle:-

→ The basic dynamometer type w-meter working principle is that when a current carrying moving coil is placed in the magnetic field produced by the current carrying fixed coil, a force is exerted on the coil sides of the mc & deflection takes place.



→ In other words when the field produced by the current carrying moving coil tries to come in line with the field produced by the current carrying fixed coil, a deflecting torque is exerted on the moving system & deflection takes place.



→ when power is to be measured in a ckt, the wattmeter is connected in the ckt.

The C.C. is connected in series with the load, carries the load current & the P.C. is connected in parallel with the load carries the current proportional to the voltage across the load.


→ The FC produces a main field  
 flux & MC " a rotating field  
 flux. produced by MC (i.e. rotating

→ The flux produced by mc (i.e. rotating field flux) tries to come in line with the main field flux, which produces a deflecting torque on moving coil.

→ Thus, the pointer attached to the spindle of the MC deflects. The deflection is controlled by controlling force, produced by the springs.

TORQUE EXPRESSIONS IN DYNAMO  
METER TYPE WATTMETER →

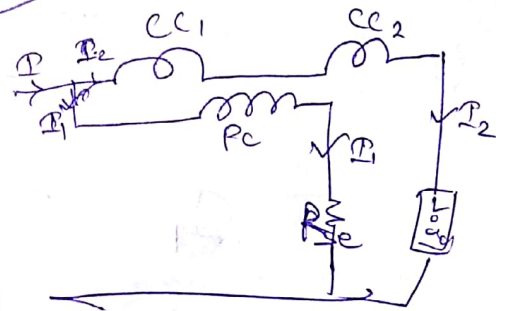→ We know that instantaneous  
torque in ED type inst.  
is directly proportional to  
the product of instantaneous  
values of current flowing  
the coil & the rate of  
change with the ckt.



through book  
- Charge of Sun

Let  $i_1$  &  $i_2$  be the instantaneous values of current in PC & CC.

$$\therefore T_{inst} = i_1 i_2 \frac{dM}{d\theta}$$

where  $\theta$  is the angle

Now let the applied value of voltage across a PC be

$$V_{inst} = V_{max} \sin \omega t$$

Assuming the P.C. ckt. has a very high resistance, so it can be treated as purely resistive

Therefore current in PC is in phase with the voltage & its instantaneous value can be written as

$$I_P = \frac{V_{inst}}{R_{sc} + R_m} = \frac{V_{inst}}{R_p}$$

where  $R_p$  is the resistance of P.C. ckt.

$$I_1 = \frac{V_m \sin \omega t}{R_p} = I_{m0} \sin \omega t$$

~~Ans~~



of the voltage by an angle  $\phi$  then instantaneous value of current in C.C is

$$I_2 = I_{m2}(\sin(\omega t - \phi))$$

$$\therefore T_{inst} = \frac{I_{m1} \sin \omega t \cdot I_{m2}(\sin \omega t - \phi) \cdot d\omega}{V_m \sin \omega t \cdot I_m (\sin \omega t - \phi) d\omega}$$

$$T_{inst} = \frac{V_m I_m \sin \omega t \cdot \sin(\omega t - \phi) d\omega}{R_p}$$

$$T_{inst} = \frac{V_m I_m}{R_p} \sin \omega t \cdot \sin(\omega t - \phi) d\omega$$

$$= \frac{V_m I_m}{R_p} (\cos(\omega t - \omega t + \phi) - \cos(\omega t + \omega t - \phi))$$

$$= \frac{V_m I_m}{R_p} \cos \phi = \frac{V_m \frac{I_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}}}{R_p} \cos \phi$$

$$= \frac{P}{R_p} \cos \phi$$

$$= \frac{V_{rms} I_{rms} \cos \phi}{R_p}$$

$$T_{inst} = \frac{P}{R_p}$$

$$T_{inst} = \frac{V_m I_m}{R_p} (\cos \phi - \cos(2\omega t - \phi)) d\omega$$

Average deflecting torque can be obtained by integrating ~~inst~~ <sup>Time</sup> from time 0 to T, where T is the time period of cycle

$$T_d = \frac{1}{T} \int_0^T T_{inst.} dt$$

$$= \frac{1}{T} \int_0^T \left[ \frac{V_m I_m}{R_p} (\sin \omega t) \left( \sin \omega t - \phi \right) \right] dt$$

$$T_d = \frac{1}{T} \frac{V_m I_m}{R_p} \frac{dM}{d\phi} \int_0^T [\cos \phi - \cos(2\omega t - \phi)] dt$$

$$= \frac{1}{2} \frac{V_m I_m}{R_p} \frac{dM}{d\phi} \cos \phi$$

$$= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \times \frac{1}{R_p} \cos \phi \frac{dM}{d\phi}$$

$$= V_{rms} I_{rms} \times \frac{1}{R_p} \cos \phi \frac{dM}{d\phi} = VI \cos \phi \frac{dM}{d\phi}$$

$$T_{avg} = \frac{P}{R_p} \frac{dM}{d\phi} = \frac{VI \cos \phi}{R_p} \frac{dM}{d\phi}$$

controlling torque is given by  $T_c = k_c \theta$   
 $\theta$  = angle of deflection.



At steady state condition

$$T_d = T_c$$

$$\Rightarrow \frac{V I \cos \phi}{R_p} \frac{dM}{d\theta} = K_c \theta$$

$$\Rightarrow \boxed{\theta = \frac{P}{R_p K_c} \frac{dM}{d\theta}}$$

$$\Rightarrow \boxed{\theta = K P \frac{dM}{d\theta}}$$

where  $P$  = Power being measured

$$K = \frac{1}{R_p K_c}$$

Errors in Dynamometer type wattmeter  
Methods of their Correction:-

→ The various types of errors in DM type wattmeter are-

(i) Error due to pressure coil inductance

(ii) " " " " capacitance

(iii) " " " Eddy current

(iv) " " " Power loss in P.C.

(v) " " " Friction.


(vi) " " " Temperature

(vii) " " " Stray magnetic field
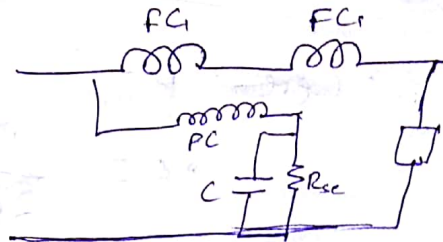
## (i) Error due to PC Inductance

→ In ideal DM-type w-meter the current is in phase with supply voltage. But practically when the PC inductance the current will lag behind the applied voltage.

→ Inductance of the PC will be reduced by means of capacitors connected in parallel with the portion of resistor.



## (ii) Error due to PC Capacitance

→ The PC ~~may~~ circuit may have capacitance as well as inductance, so due to high value of capacitance the effect of capacitor tends to lead the current by the applied voltage.

→ If the capacitive reactance is equal to the inductive reactance then there will be no error.

## (iii) Error due to Eddy current

→ Eddy current errors are induced in the solid metal parts, by the alternating magnetic field produced by the current coil. It alters the magnitude & phase of this field & so produce an error.

→ The EC induces in the coil creates its own magnetic field, this field affects the main current flows through the coil & error occurs.

## (iv) Error due to parallel loss in PC coil


→ These errors are due to alternative wattmeter connection.



→ In general the wattmeter having M-C short cut  
 of L-C points are short then the C.C. carry  
 more current so more turn produced.

→ So to eliminating the error, a compensating coil  
 is used with the current coil.
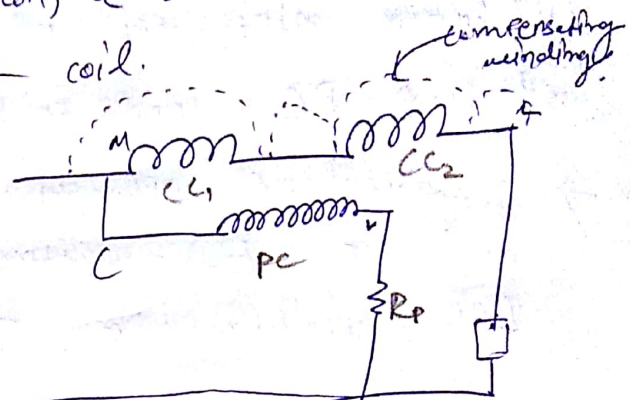
$$\phi = (\phi_L + \phi_p - \phi_p) = \phi_L$$



(v) Errors due to friction =

→ Friction error occurs due to the weight of the M.C.  
 → So to reduce the frictional error, it becomes  
 necessary that the weight of the moving  
 system should be reduced to minimum possible  
 value.

## Wattmeter Types -

→ Generally there are two types of wattmeter  
 (i.e. a) L.P.F (Low P.F wattmeter)  
 (b) U.P.F (Unit P.F wattmeter)

(1) L.P.F Electro-dynamometer type wattmeter

→ The instrument that measures the power  
 of the circuit having low value of power factor  
 is known as Low power factor wattmeter.

→ Measurement of power in the circuits having  
 low power factor (< 0.5) by ordinary e-dynamometer  
 wattmeter is difficult & inaccurate, because:-

(i) The deflecting torque on the moving sys. is small even when the CC & PC are fully excited.


(ii) Error introduced because of the inductance of the PC tends to be large at LPF.

→ Therefore, special modifications are carried out in ED-wattmeter to convert it into LPF wattmeter, These are:

(i) Pressure coil current

The PC ckt is designed for having a low value of resistance so that the high value of current passes through it. This current produces the deflecting torque on the MC.

(ii) Compensation of inductance of PC

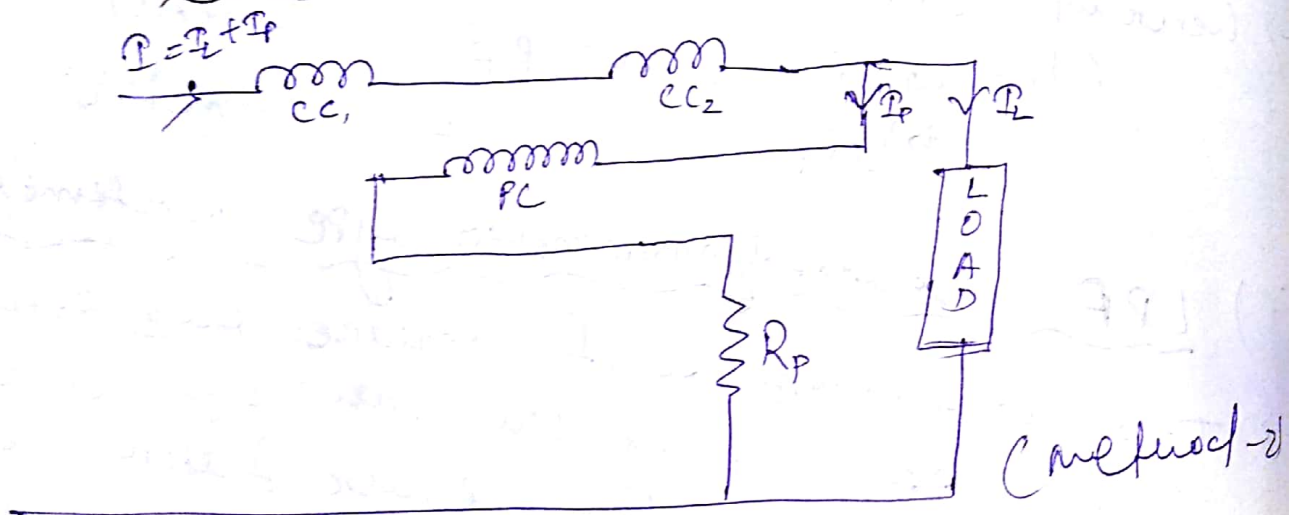


→ In this method the ckt arrangement is different

$$P = VI \cos \phi$$

$$P_{avg} = \frac{VI}{2}$$



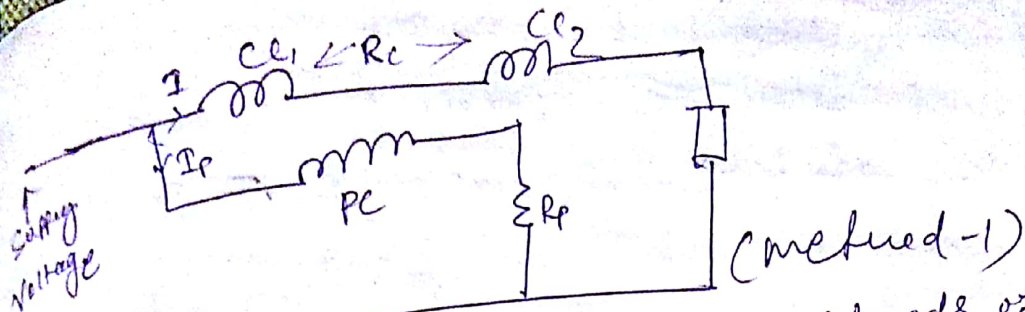

There are two alternate methods of connecting the wattmeter in the ckt.

method-1 → The PC is parallel connected to supply voltage & the CC is connected in series with the supply voltage.

→ The magnitude of supply voltage across the PC is equal to the supplied voltage, i.e.  $V = V_{PC}$

→ The total power measured by the PC is equal to the sum of the power loss in the load & the power loss in the CC.

Let DC supply given in this method

Current coil reading =  $I$

$R_c$  = internal resistance of CC

Potential coil " =  $I R_c + V$

Wattmeter reading =  $V I + I^2 R_c$


True value =  $V I$

Error = measure value - TV

$$= V I + I^2 R_c - V I = I^2 R_c$$


(If  $P \propto \frac{1}{\cos \phi}$ ) →  $I \propto \frac{1}{\cos \phi}$ , Low current high P-f

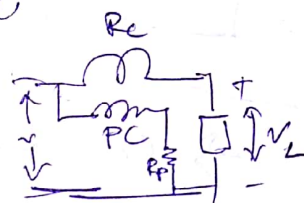→ So this method is used for low P-f or low power factor & low current



Method - 2: The PC is not connected in parallel with the load. So the magnitude of the PC voltage  $\neq$  supplied voltage.

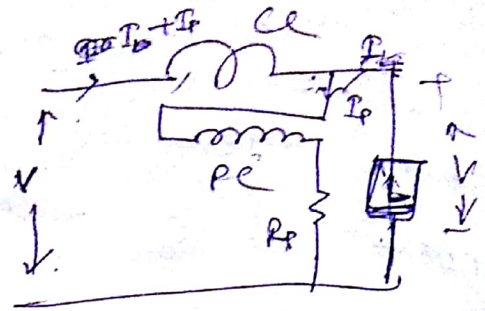→ The o/p power obtained from the ckt is equal to the sum of the load power loss & the power loss of the PC.




Reading of CC =  $I_o + I_P$

" " PC =  $V$

Wattmeter reading =  $V I_o + V I_P$

(where  $I_P = \frac{V}{R_P}$ ) =  $V I_o + \frac{V^2}{R_P}$

True value of power =  $V I_o$

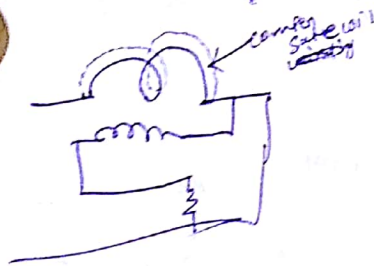

Error =  $V I_o + \frac{V^2}{R_P} - V I_o$

Error =  $\frac{V^2}{R_P}$

→ So this is used for High current & Low power factor.

→ The high value of current causes the error in the wattmeter reading. For reducing the error, the compensating coil is used in the ckt.

→ The compensating coil compensates the error in the ckt when induced because of Low p.f.



### (iii) Compensation for Inductance of P.C.

→ The small amount of inductance is present in the P.C. This inductance cause the error in reading.

→ The error caused by the P.C. inductance is given by :-  $V I \sin \phi \tan \beta$


where  $\phi$  = angle b/w voltage & current of the C.C.

$\beta$  = angle b/w voltage & current of the

→ With low p.f. the value of  $\phi$  is large & therefore the error is corresponding large.

→ Hence in L.P.F. wattmeter ~~error must have to be compensated~~ induced in it.

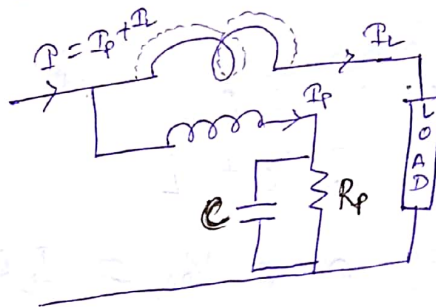→ This is done by connecting a capacitor across a part of series resistance in the P.C.




### (iv) Small controlling torque

→ L.P.F. wattmeters are designed with a small controlling torque so that they give FSD for low power factor.

## ⑤ UPF Type wattmeter

- The instrument that measures the power of the circuit having ~~low~~ high value of power factor ( $\cos \phi$ ) or close to unity value of P.F. known as UPF type wattmeter.
- The circuit arrangement connection is same as an ordinary wattmeter connection.
- The PC is connected to supply voltage & the CC is connected in series with the supply voltage, so  $|V_s| = |V_{pc}|$
- ~~where~~  $V_s =$  supply voltage  
 $V_{pc} =$  voltage across PC

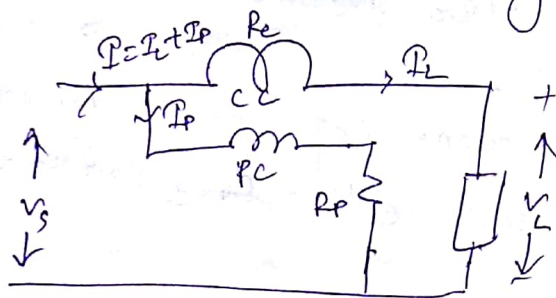

$R_c =$  internal resistance of CC

$I_L =$  current flowing through CC to load

$I_p =$  current flowing through PC.

Voltage drop across CC &  
 $= I_L R_c + V_L$

" " across PC  $= V_{pc} = I_L R_c + V_L$

i.e.  $V_{cc} = V_{pc}$

~~wattmeter reading~~  
 Current across CC  $= I_L$

" voltage " PC  $= V_{pc} = I_L R_c + V_L$




Wattmeter reading  $= VI \cos \phi$   
 $= VI + I^2 R_e$

~~True value~~ True value  $= VI$   
 Error  $= I^2 R_e$

of  $P$  &  $V$  const  $I \propto \frac{1}{\cos \phi}$   
 So this arrangement is used for low current & high p.f.

## INDUCTION TYPE WATTMETER

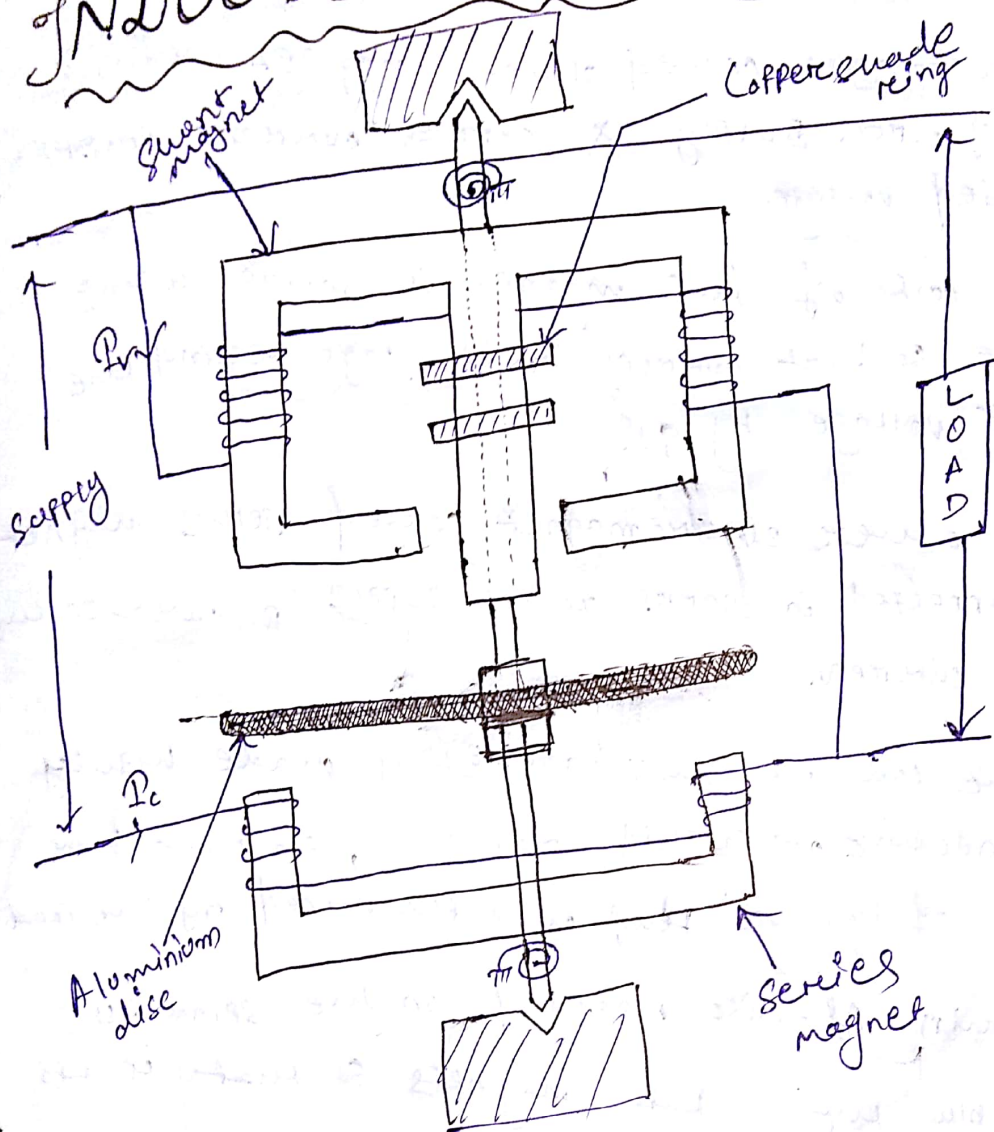

→ Induction type wattmeter belongs to the family of induction type measuring instrument.

→ These types of watt-meters operate on the same working principle on which the induction type ammeter & voltmeter operates.

→ The Induct type wattmeter is used to measure ac power supply only. Due to phase difference it can't be used for dc supply.

### Construction

→ It consists of two laminated electromagnets.

→ One electromagnet called shunt magnet which is connected across supply & carries current proportional to applied voltage.

→ The coil of this magnet is made highly inductive so that current in it lags behind the supply voltage by  $90^\circ$ .

→ The other electromagnet called series magnet is connected in series with supply & carries the load current.

→ The coil of this magnet is made highly non-inductive or highly resistive, so that the angle of lag or lead is determined by the load.

→ A thin Al-disc mounted on the spindle is placed b/w the two magnets so that it cuts the fluxes of both the magnets.

→ The controlling torque is provided by two spiral springs.



→ Two or more adjustable copper ~~and~~ shading rings are provided on the central limb of the shunt magnet to make the phase angle displacement b/w magnetic field set up by shunt magnet & ~~series magnet~~ supply voltage is approx.  $90^\circ$ .

→ The damping torque in induction type instruments is provided by the eddy current produced in the rotating disc.

### Working Principle

→ The principle of operation of an Induc<sup>n</sup> wattmeter is same as that of induc<sup>n</sup> ammeters & voltmeters, i.e. induc<sup>n</sup> principle.

→ But Induc<sup>n</sup> type wattmeter <sup>having</sup> is different arrangement from Induc<sup>n</sup> type voltmeter & ammeter.

→ In this type of instrument two separate coils are used to produce rotating flux, in place of one coil ~~one electromagnet~~ with split phase arrange as in Induc<sup>n</sup> type voltmeter & ammeter.

→ when the wattmeter is connected in the ckt to measure a.c power, the shunt magnet carries current proportional to the supply voltage & the series magnet carries the load current.

→ The two fluxes produces two eddy currents in the aluminium disc.

→ ~~Due~~ Due to the interaction b/w the two fluxes & two eddy currents, the deflecting torque is produced in the aluminium disc, which causes

The pointer connected to the moving system to move over the scale.

## Torque Expression In Induc<sup>n</sup> wattmeter

Let  $V$  = Applied voltage

$I_c$  = Load current carried by the series magnet or current magnet

$I_v$  = current carries by the shunt magnet or voltage magnet



$\cos \phi$  = Power factor of the load.

$\phi_c$  = Flux produced ~~on the disc~~ due to current  $I_c$

$\phi_v$  = Flux produced ~~on the disc~~ due to current  $I_v$ .

$i_{c1}$  = Eddy current ~~produced~~ induced on the disc due to  $\phi_c$

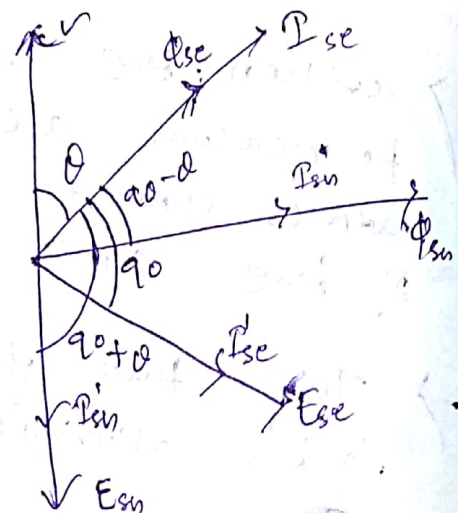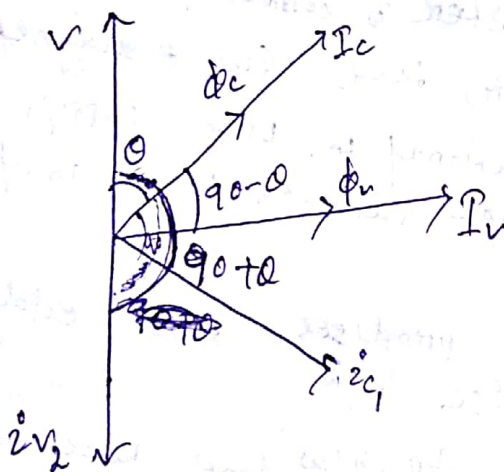$i_{c2}$  = Eddy current induced on the disc due to  $\phi_v$ .





→ The current  $I_v$  in the shunt magnet lags the applied voltage  $V$  by  $90^\circ$  & ~~so~~ <sup>due to this</sup> flux  $\phi_v$  is produced by it.

→ The current  $I_c$  in the series magnet is the load current & hence lags behind the applied voltage  $V$  by an angle ' $\phi$ '.

→ The flux  $\phi_c$  produced by current  $I_c$  is in phase with it.

→ Therefore  $I_v$  &  $I_c$  having a phase diff. of  $(90^\circ - \phi)$  apart from each other & as well as the fluxes  $\phi_v$  &  $\phi_c$  also apart ~~from~~  $(90^\circ - \phi)$  from each other.

→ Due to flux  $\phi_v$  the eddy current  $i_v$  induces in the Al-disc.

→ Similarly due to flux  $\phi_c$  eddy current  $i_c$  induces in the disc.

→  ~~$i_c$~~   $i_c$  lags behind the flux  $\phi_c$  by an angle  $90^\circ$  & also  $i_v$  lags  $\phi_v$  by angle  $90^\circ$ .

→ Therefore two torques developed on the disc,  $T_1$  due to interaction of  $\phi_c$  &  $i_v$  &  $T_2$  due to " of  $\phi_v$  &  $i_c$ .

Resultant deflecting Torque

$$T_d = T_1 - T_2$$

$$T_d \propto \phi_c \phi_v \sin(90^\circ - \phi)$$

$$\therefore T_d \propto \phi_c \phi_v \sin(90^\circ - \phi)$$

$$T_d \propto VI \cos \phi \quad \left( \because \phi_v \propto V \right)$$

$$\phi_c \propto I$$

$T_d \propto \text{AC Power}$

$$T_d = K V I \cos \phi$$

Here in this instrument it has uniform scale  
Since controlling torque provided by fine  
springs

$$T_c \propto \theta$$

$$T_c = K_c \theta$$

At final steady state condition

$$T_d = T_c$$

$$\Rightarrow K V I \cos \phi = K_c \theta$$

$$\Rightarrow \boxed{\theta = K_1 V I \cos \phi} \quad \left( \because K_1 = \frac{K}{K_c} \right)$$

$$\theta \propto V I$$

Measurement of power in 3- $\phi$  system

$\rightarrow$  There are 3 methods are used for measurement  
of power in 3- $\phi$  ckt.

- (i) 3-wattmeter method.
- (ii) 2-wattmeter method.
- (iii) Single wattmeter m/d.

\* Generally 2-wattmeter methods are  
used for measurement of power  
both balanced & unbalanced load.




## (ii) 2-wattmeter method

Let,  $I_R, I_Y$  &  $I_B$  be the RMS value of phase current, i.e.  $I_R = I_Y = I_B = I_L = I_{ph}$

$V_R, V_Y$  &  $V_B$  be the RMS value of phase voltage, i.e.  $V_{RN} = V_{YN} = V_{BN} = V_{ph}$   
 $V_{RY} = V_{YB} = V_{RB} = V_L$

$$V_L = \sqrt{3} V_{ph}$$

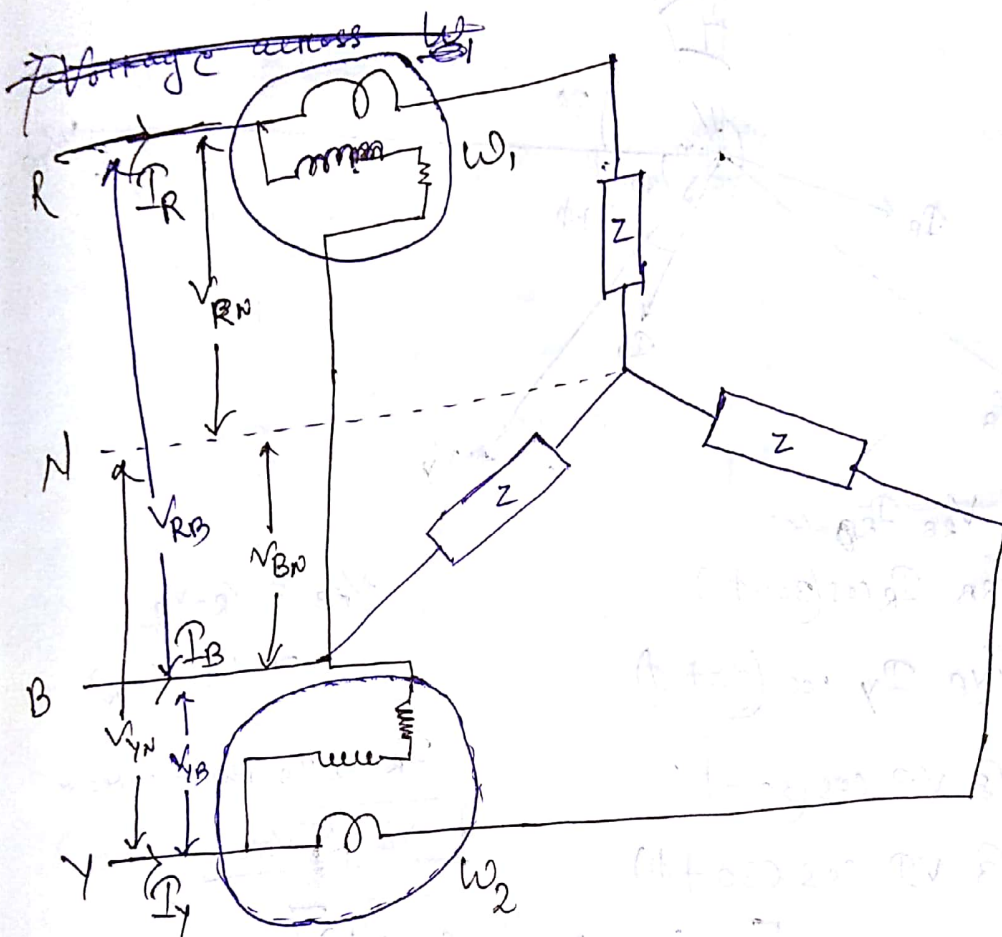

For unbalanced load

$$W_1 = V_{RB} I_R$$

$$W_2 = V_{YB} I_Y$$

$$I_R + I_Y + I_B = 0 \Rightarrow (I_R + I_Y = -I_B)$$

$$W_1 + W_2 = V_{RB} I_R + V_{YB} I_Y$$

$$= (V_R - V_B) I_R + (V_Y - V_B) I_Y$$

$$= I_R V_R + I_Y V_Y - V_B (-I_B)$$

$$W_1 + W_2 = I_R V_R + I_Y V_Y + I_B V_B \quad \checkmark$$

For balance

~~$\omega = V_R V_{RB} \cos$~~


$$V_R = V_m \sin \omega t$$

$$V_Y = V_m \sin(\omega t - 120^\circ)$$

$$V_B = V_m \sin(\omega t - 240^\circ)$$

$$\omega_1 = I_R V_{RB} \cos \theta$$

$$\omega_2 = I_Y V_{YB} \cos \theta$$

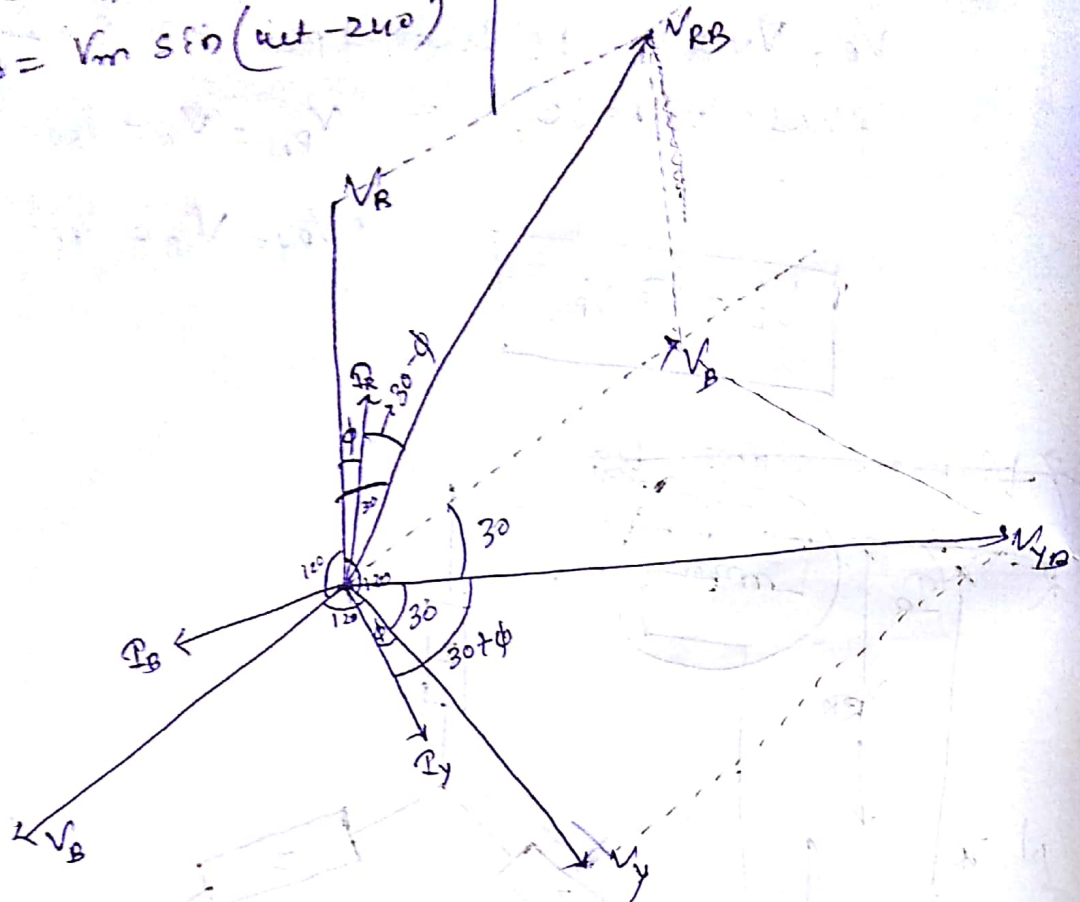

~~$\omega_1 = V_{RB} I_R \cos$~~

$$\omega_1 = V_{RB} I_R \cos(30 - \phi)$$

$$\omega_2 = V_{YB} I_Y \cos(30 + \phi)$$

or  $\omega_1 = \sqrt{3} V_L I \cos(30 - \phi)$

$$\omega_2 = \sqrt{3} V_L I \cos(30 + \phi)$$

$$\omega_1 + \omega_2 = \sqrt{3} V_L I [\cos(30 - \phi) + \cos(30 + \phi)]$$

$$= \sqrt{3} V_L I [\cos 30 \cos \phi + \sin 30 \sin \phi$$

$$+ \cos 30 \cos \phi - \sin 30 \sin \phi]$$

$$= \sqrt{3} V_L I (2 \cos 30 \cos \phi)$$

$$= \sqrt{3} V_L I \times \frac{\sqrt{3}}{2} \cos \phi$$

$$V_{RB} = V_R - V_B$$

$$\text{or } V_R + (-V_B)$$

$I_R, I_Y, I_B$  Phase current

$$V_L = \sqrt{3} V_{ph}$$



$$\Rightarrow \boxed{W_1 + W_2 = 3 VI \cos \phi} \rightarrow 3\phi \text{ Active Power} \quad (1)$$

for reactive power

$$W_1 - W_2 = \sqrt{3} VI [\cos(30^\circ - \phi) - \cos(30^\circ + \phi)]$$

$$\boxed{W_1 - W_2 = \sqrt{3} VI \sin \phi} \quad (2)$$

$$\text{or } \boxed{\sqrt{3}(W_1 - W_2) = 3 VI \sin \phi} \rightarrow 3\phi \text{ Reactive Power}$$

for power factor

$$\frac{\text{eqn (2)}}{\text{eqn (1)}}$$

$$\frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} = \frac{\sqrt{3} VI \sin \phi}{3 VI \cos \phi} = \tan \phi$$

$$\Rightarrow \frac{\sqrt{3} W_1 - W_2}{W_1 + W_2} = \tan \phi$$

$$\Rightarrow \phi = \tan^{-1} \left( \frac{(W_1 - W_2) \sqrt{3}}{W_1 + W_2} \right)$$

$$\cos \phi = \cos \left[ \tan^{-1} \left\{ \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} \right\} \right]$$

special case

case-I If P.F. is unity

$$\cos \phi = 1$$

$$\phi = 0$$

$$W_1 = \sqrt{3} VI \cos(30^\circ - \phi) = \frac{3 VI}{2}$$

$$W_2 = \sqrt{3} VI \cos(30^\circ + \phi) = \frac{3 VI}{2}$$

$$\boxed{W_1 = W_2}$$

$\therefore$  At UPF both w-mtr read same

Q) I asked in exam both w-mtr read same then what is the P.f?

$$\phi = \tan^{-1} \left( \frac{\sqrt{3} (\omega_1 - \omega_2)}{\omega_1 + \omega_2} \right)$$

$$\omega_1 = \omega_2 = \omega$$

$$\therefore \phi = \tan^{-1} \left( \frac{\sqrt{3} (\omega - \omega)}{2\omega} \right) = 0$$

$$\boxed{\phi = 0, \cos \phi = 1}$$

Case-II If P.f is 0.866

$$\cos \phi = 0.866 \text{ then}$$

$$\phi = 30^\circ$$

$$\boxed{\omega_1 = \frac{\omega_2}{2}}$$

$$\begin{aligned} \omega_1 &= \sqrt{3} V \Phi \\ \omega_2 &= \sqrt{3} \frac{V \Phi}{2} \end{aligned}$$

∴ If P.f is 0.866 one of the w-mtr reads half of the other.

$$\phi = \tan^{-1} \left[ \frac{\sqrt{3} \left( \frac{\omega_2}{2} - \omega_2 \right)}{\frac{\omega_2}{2} + \omega_2} \right] = \tan^{-1} \left( \frac{1}{\sqrt{3}} \right) = -30^\circ \text{ (lagging)}$$

Case-III If P.f is 0.5

$$\cos \phi = 0.5 \text{ then}$$

$$\phi = 60^\circ$$

$$\begin{aligned} \omega_1 &= \frac{3V\Phi}{2} \\ \omega_2 &= 0 \end{aligned}$$

∴ At 0.5 P.f one of the w-mtr reads 0.

$$\text{Let } \omega_2 = 0$$

$$\phi = \tan^{-1} \left( \frac{\sqrt{3} (\omega_1 - 0)}{(\omega_1 + 0)} \right) = \tan^{-1} \sqrt{3} = 60^\circ$$

$$\cos \phi = 0.5$$



Case - IV

If  $P.F. < 0.5$

$\cos \phi < 0.5$  so  $\phi > 60^\circ$

~~$\phi > 60^\circ$~~

Let  ~~$\phi > 60^\circ$~~   $\phi = 70^\circ$

$$\begin{aligned} W_1 &= \sqrt{3} V_L \cos 40^\circ = +ve \text{ value} \\ W_2 &= \sqrt{3} V_L \cos(100^\circ) = -ve \text{ value} \end{aligned}$$

[  $P.F. < 0.5$  one of the wattmeter reads -ve value ]

Q) A 3- $\phi$ , 440V motor load has a p.f. of 0.6. Two wattmeters connected to measure the power, i.e. 25 kW. Find the reading of each watt.

Sol<sup>n</sup> Given  $W_1 + W_2 = 25 \text{ kW}$

$$V_L = 440 \text{ V}$$

$$\cos \phi = 0.6$$

$$\phi = \cos^{-1} 0.6 = 53.13^\circ$$

We know that

$$\tan \phi = \frac{\sqrt{3} (W_1 - W_2)}{W_1 + W_2}$$

$$\Rightarrow \tan(53.13^\circ) = \frac{\sqrt{3} (W_1 - W_2)}{25}$$

$$\Rightarrow \frac{1.33 \times 25}{\sqrt{3}} = W_1 - W_2$$

$$\Rightarrow W_1 - W_2 = 19.42 \text{ kW}$$

$$W_1 = ?$$

$$W_2 = ?$$

$$W_1 - W_2 = 19.42$$

$$W_1 + W_2 = 25$$

$$\frac{2W_1 = 19.42 + 25}{2}$$

$$\Rightarrow W_1 = \frac{19.42 + 25}{2}$$

$$= 22.21 \text{ kW}$$

$$W_2 = 2.88 \text{ kW (Ans)}$$

# Chapter-4

## ENERGY METERS

### MEASUREMENT OF ENERGY

Energy is the total power delivered or consumed over a time interval, i.e.

$$\text{Energy} = \text{Power} \times \text{Time}$$

$$E = \int (\text{power}) \times dt$$


Kwh meter - AC Supp  
Amph meter - DC Supp

It is integrating type meter

$$\text{Acronym} = \frac{\text{Power}}{P} \times \frac{\text{hour}}{h} = \frac{\text{Energy}}{E}$$

It works only on AC-supply

Induced type Energy meter

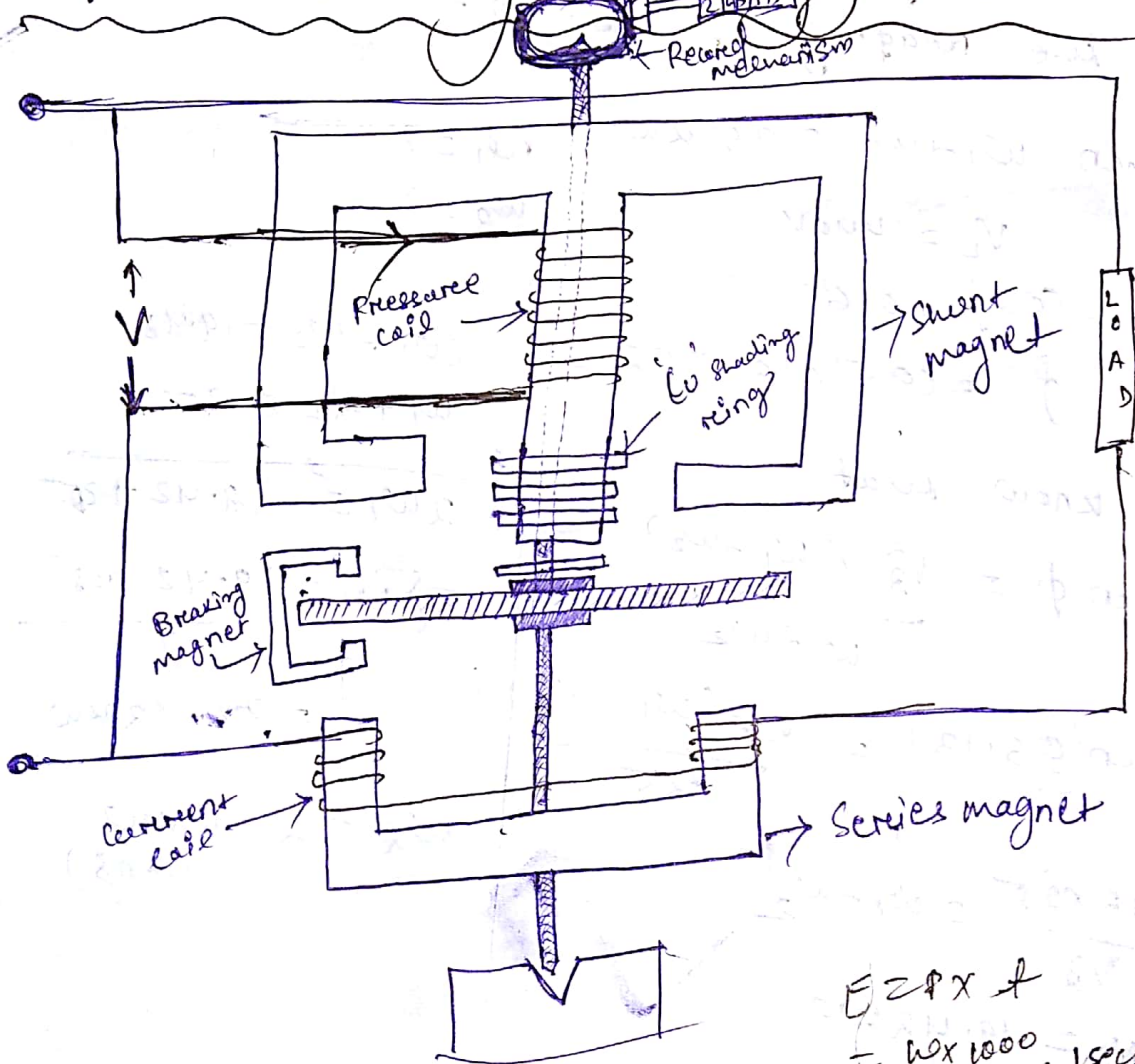

$$E = P \times t$$

$$= \frac{W \times 1000}{1000} \times \frac{1800 \times 3600}{3600}$$

$$E = \frac{KW}{1000} \times \frac{t}{3600} \times 3600$$

2600 Kwh.



It operates on induction principle. (Which = 1 unit)  
 It is integrating type instrument which consume power commutatively over period of time.

Construction →

There are 4 main part of the operating mechanism

- (i) Driving System
- (ii) Moving System
- (iii) Braking System
- (iv) Registering or Recording system.

(i) Driving System →

- The driving system consist of shunt magnet & series magnet which is M-shaped
- The shunt magnet carries the current proportional to the supply voltage, which is having many no. of turns of thin wire.
- The series magnet which is U-shaped carries the current proportional to the load current, which is having less no. of turns of thick wire.

(ii) Moving System →

- A thin Al-disc is placed b/w two magnet.
- A deflecting torque produced in the disc due to the interaction of the two eddy current.
- Due to the interaction b/w the two fluxes & two eddy currents the deflecting torque is produced in the aluminium disc, which cause the pointer to move over the scale.

(iii) Braking System →

- A permanent magnet is placed near the Al-disc which is also known as braking magnet.
- The eddy current induced in the aluminium disc produces a braking torque, which opposes the rotation of disc.

$$T_b \propto N$$



## (iv) Registering and Recording mechanism

- ~~This system is used to record or register the~~  
~~no. of~~
- This system used a record mechanism which is used to register or recording no. of rotation of the Al-disc, which is proportional to the energy consumed in kWh.

## Working Principle

- The working principle of 1- $\phi$  Induction type energy meter is same as Induction type ammeter, voltmeter & wattmeter.
- In Induction type energy meter is an extra recording mechanism.
- When the energy meter is connected in at the CC carries the load current & PC carries the current proportional to the supply voltage.
- The ~~flux~~ magnetic field produced by ~~short magnet~~ series magnet in phase with the line current.
- The magnetic field produced by short magnet is in quadrature (to the power) with the applied voltage, ~~thus a phase diff. exists.~~ ( $\phi = \frac{1}{2} \pi$ )
- Thus, a phase diff. exists b/w the fluxes produced by the two coils.
- Therefore a rotating magnetic field is setup which interacts with disc & a deflecting torque ( $T_d$ ) is produced.



→ Due to deflecting torque the disc starts to rotating the no. of revolution made by the disc depend upon the energy passing through the meter.

→ The spindle attached to a recording mechanism so that energy consumed in the unit is directly recorded in kWh.

→ The speed of the disc is adjusted by adjusting the position of braking magnet.

### Compensation of Error

#### ① Friction or No Load compensation


→ The friction error are serious at light load condition. So it is necessary to overcome the friction at the bearings & recording mechanism.

→ This is usually done by placing a small shading loop in the air gap of the shunt magnet. (w/ shading)
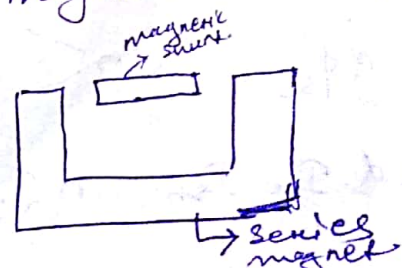
#### ② Overload compensation

→ Through the majority of braking action is provided by the braking magnet, the shunt magnet & series magnet also exert some amount of braking torque. Since the fluxes are cut by the rotating disc.

→ So, to compensate this error, a magnetic shunt is provided in the series magnet.



### ③ Compensation for Creeping

→ In some meters a slow but a continuous rotation of disc is obtained even at no load when the potential coil is excited. This is known as creeping.

→ This may be due to the overcompensation of friction, stray magnetic field or excess of supply voltage than normal.

→ Such creeping is prevented by cutting two holes or slots in the disc on opposite sides of the spindle.



### ④ Temperature Error Compensation

→ By changing the temperature, the parameter of the coils change slightly which introduce a small error in meters. However, this error is negligible small & there is no need to prevent any means to eliminate the error.

### ⑤ Frequency Error Compensation

→ Since the energy meters are used normally at fixed frequency, therefore, they are designed & adjusted to have minimum error at rated supply frequency which is normally 50 Hz in India.

Torque expression

$$T_d \propto \phi_{se} \phi_{sh} \sin \delta$$

$$T_d \propto I_{se} I_{sh} \sin \delta$$

$$T_b \propto N$$

$$T_d = T_c$$


$$P \propto N$$

pure consumed by load

$$T_d \propto \frac{VI}{Z} \sin(\delta - \phi)$$

$$\delta \neq \Delta = 90^\circ$$

$$T_d \propto \frac{VI}{Z} \cos \phi$$

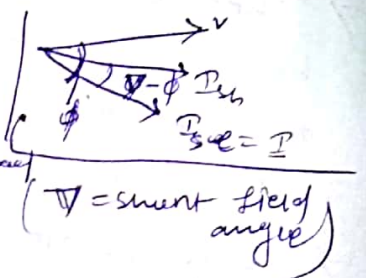

$T_d \propto P$  (if P.c of EM is highly inductive)



## Energy meter Testing

→ The testing of energy meter is done by compensation with the revolution of the standard & the test meter.

→ The error of the meter under test is found by counting the no. of revolutions & comparing with the no. of revolutions of the substandard.

So the error at any load =

$$E = \frac{N_2 K_1 - N_1 K_2}{N_1 K_2} \times 100$$

Where  $N_1$  = revolution shown on substandard.  
 $N_2$  = " " " test meter

$K_1$  = Constant of the substandard in revolution per kWh

$K_2$  = constant of test meter in revolution per kWh

meter const

$$E = N \times K$$

$$K = \frac{N}{E} \rightarrow \text{meter const.}$$

$$\text{meter const} = \left( \frac{\text{No. of revs}}{\text{kWh}} \right)$$

Ex:  $\frac{1200}{\text{kWh}}$

Chapter 5 } + measurement of speed, frequency & power factors

## Tachometer

→ Tachometer is a speed measurement device whereas Tacho is related to speed & meter is related to measurement.

→ It converts a ~~mechanical~~ mechanical deviation to electrical signal i.e. voltage is induced & measured by the voltmeter connected to it.

→ There are 3-types of tachometers are used

- (1) AC Tachometer Generator
- (2) DC Tachometer Generator
- (3) Eddy Current Tachometer or Drag Cup Tachometer
- (2) DC Tachometer Generator

→ It is a small dc generator whose o/p is mechanical (i.e speed of the shaft) & o/p is the induced voltage at the armature terminals

→ Here emf depends upon two factors

- (1) Field Excitation
- (II) Speed of the shaft

### Construction & Working

→ Here a permanent magnet is used to provide the magnetic field.


→ The generated voltage proportional to the product of  $\Phi_m$  & speed of the shaft.

→ Since the  $\Phi_m$  of the permanent magnet is constant, the voltage generated is proportional to the speed.

→ This emf is measured with the help of a moving coil voltmeter having a uniform scale & calibrated directly in terms of speed.



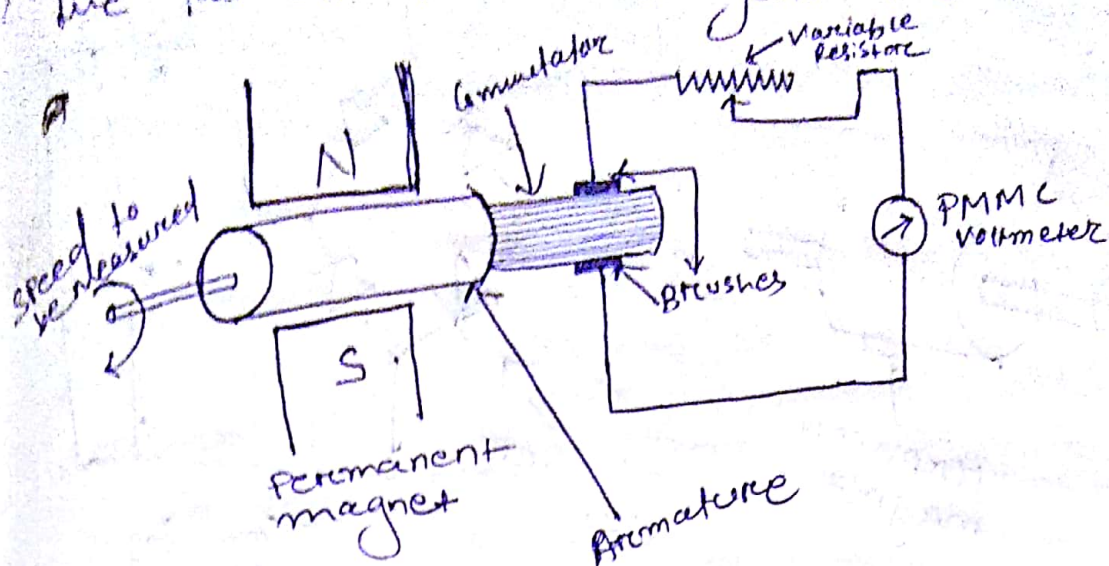→ A Series resistance is used in the ckt to limit the current from the generator.



### Advantages :-

- Direction of rotation is directly indicated by the Polarity of o/p Voltage.
- o/p Voltage is typically  $10\text{mV/rpm}$  & can be measured with conventional type dc voltmeter.


### Disadvantage -

- Commutation & brushes required periodic maintainance.
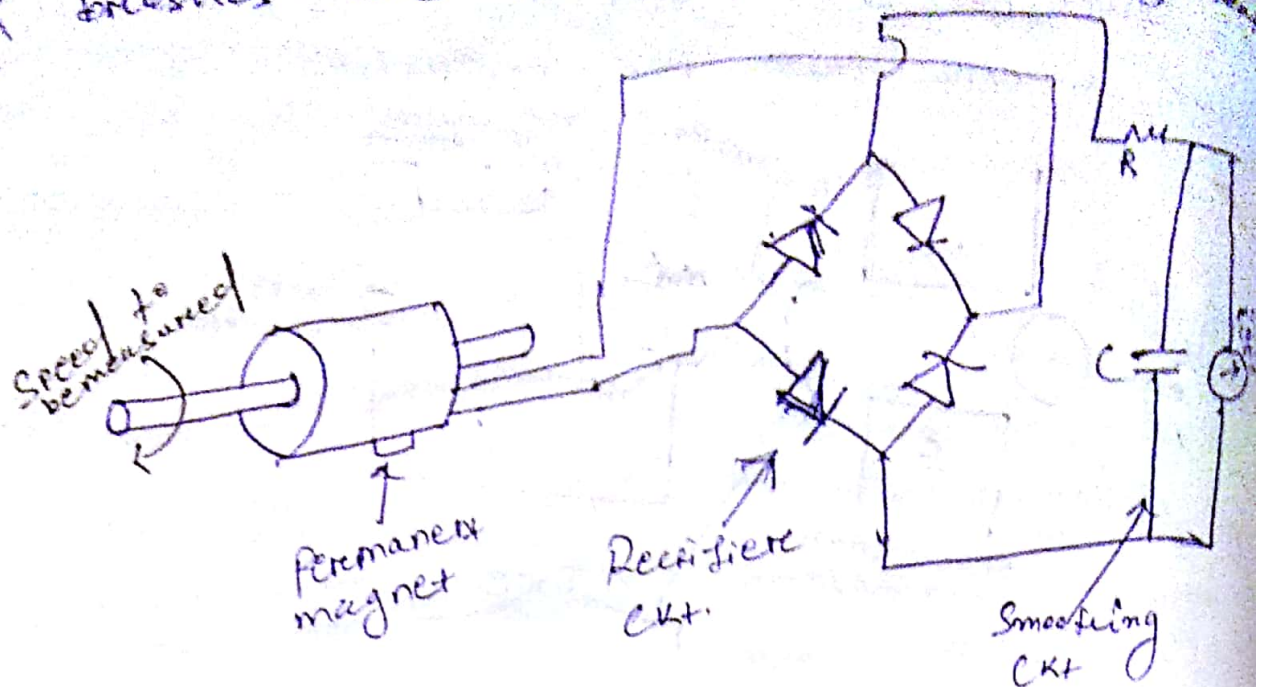
### DC Tachometer

- The DC-tachometer generator uses the commutator & brushes which have many disadvantages.
- The AC-tachometer generator designed for reducing the problem.
- The AC-tachometer has stationary armature & rotating magnetic field. Thus the commutation

Brushes are absent in AC-tachometer generator



### Construction & Working

- When the magnetic field rotates an emf will be induced in the stationary coil of the stator.
- Then the current will flow through the rectifier ckt which rectifies it.
- The Resistance 'R' will protect the device by limiting the current generated.
- A smoothing ckt is used where a filter capacitor is used to smooth the o/p.
- Then the emf can be measured with the help of the voltmeter having uniform scale & calibrated directly.



in terms of speed.

### Advantages

→ Cost of generation is less as compared to the DC generator.

### Disadvantages


→ The non-linear relationship obtains between o/p voltage & i/p voltage when the rotor rotates at high speed.

## Frequency meters

→ Frequency meters are classified into <sup>various</sup> ~~two~~ types

- (a) ~~Electrical~~ mechanical Resonance type
- (b) Electrical Resonance type
- (c) Electrodynamometer type.
- (d) Weston type.
- (e) Ratio meter type.
- (f) Saturable core type


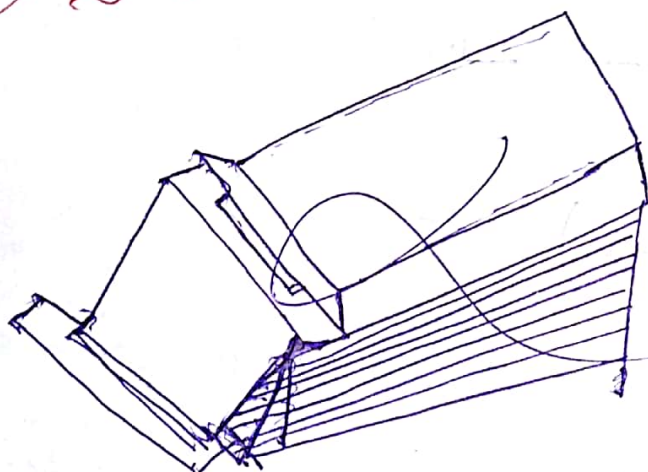
### (a) mechanical Resonance type (Vibrating Reed type)



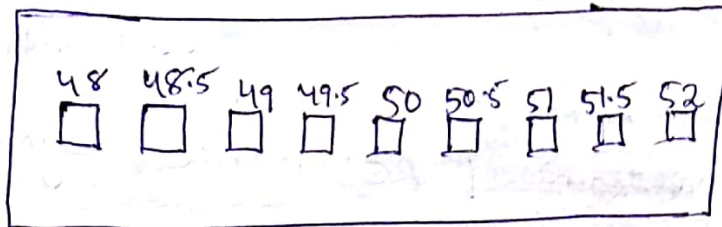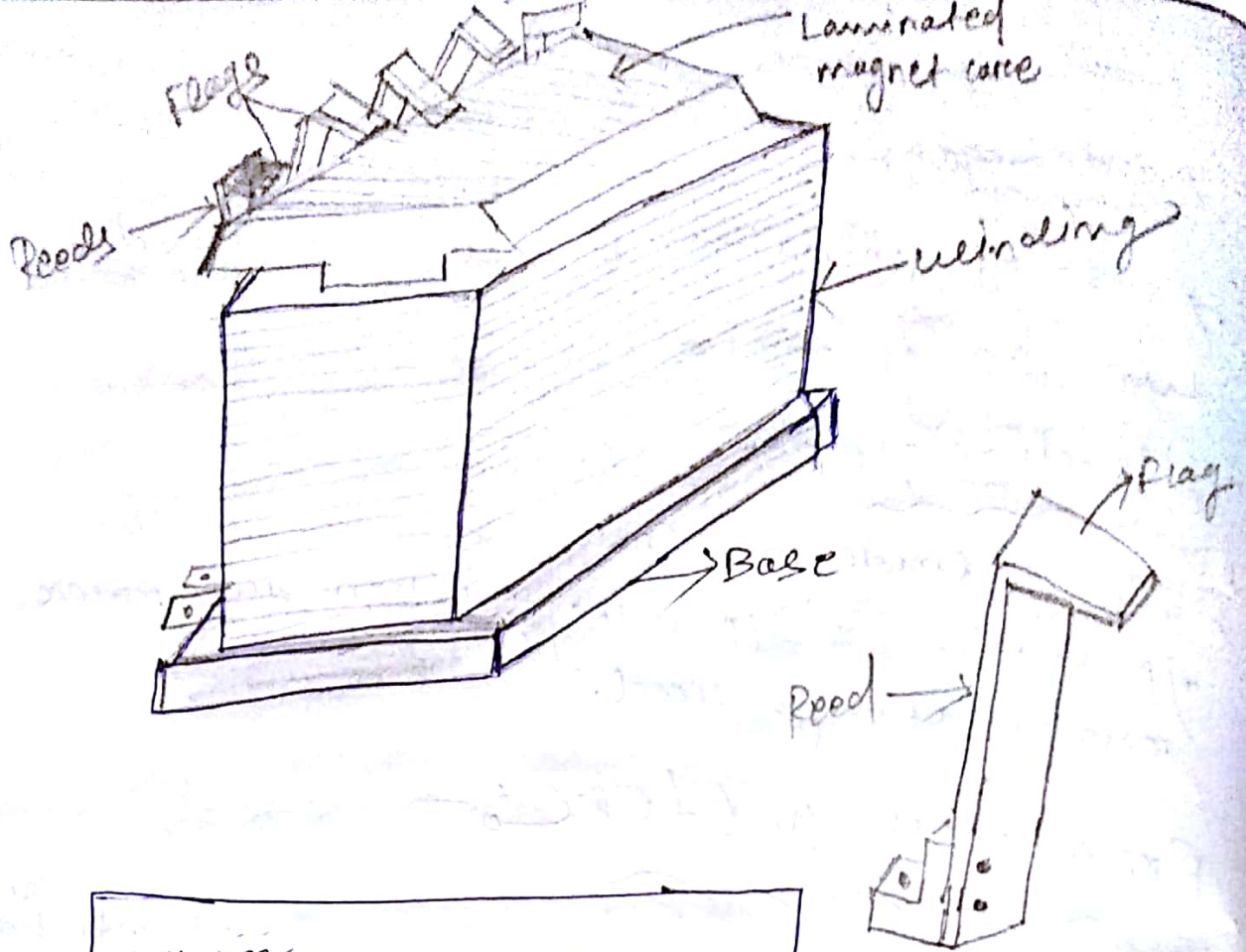
#### Construction

→ It consists of a no. of thin steel strips called reeds.


→ These reeds are placed in a row alongside & close to an electromagnet.



(a)

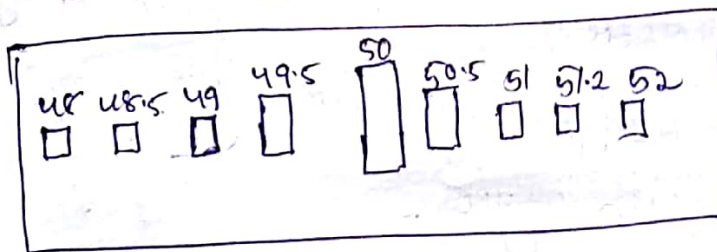


(b)

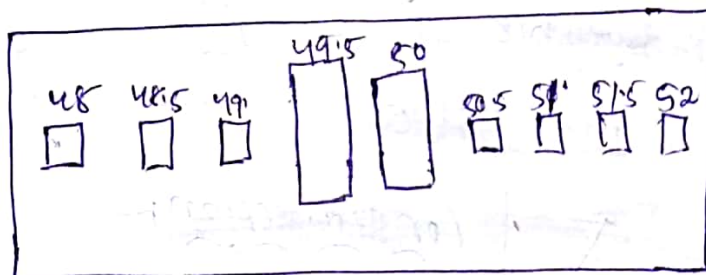

(c)

(Indications from vibrating reeds)

Amplitude of

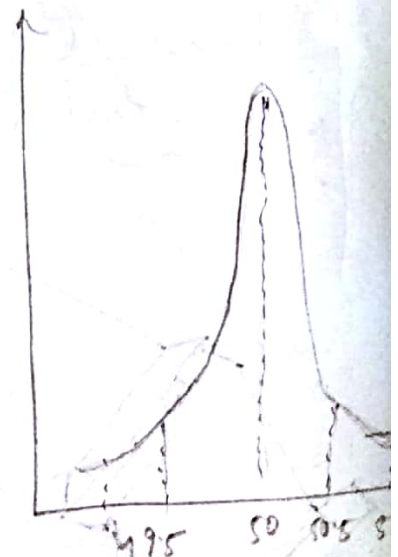

Frequency of



2091  
→ The electromagnet was a connected iron core & its coil is connected in series with a resistance across the supply whose frequency is to be measured.

→ Each reed is approximately about 4mm wide & 0.5mm thick. All the reeds are not exactly similar to each other. The reeds are not exactly similar to each other.

### Working

→ When the frequency meter is connected across the supply whose frequency is to be measured the coil of the electromagnet carries a current  $i$  which alternates at the supply frequency.

→ The force of attraction b/w the reeds & the electromagnet is proportional to  $i^2$  & therefore the force varies at twice the supply frequency.

→ This force exerted on the reeds varies every half cycle.

→ All the reeds will tend to vibrate, but the reeds whose natural frequency is equal to twice the supply frequency.

→ All the reeds will tend to vibrate, but the reeds whose natural frequency


is equal to twice the supply frequency  
~~is equal to~~ will be in resonance  
& vibrate mostley.

→ Normally the vibration of other  
need so slight as to be unobservable.

## ② Electrical Resonance type frequency meter

### a) Electrodynamic Type

Normal frequency

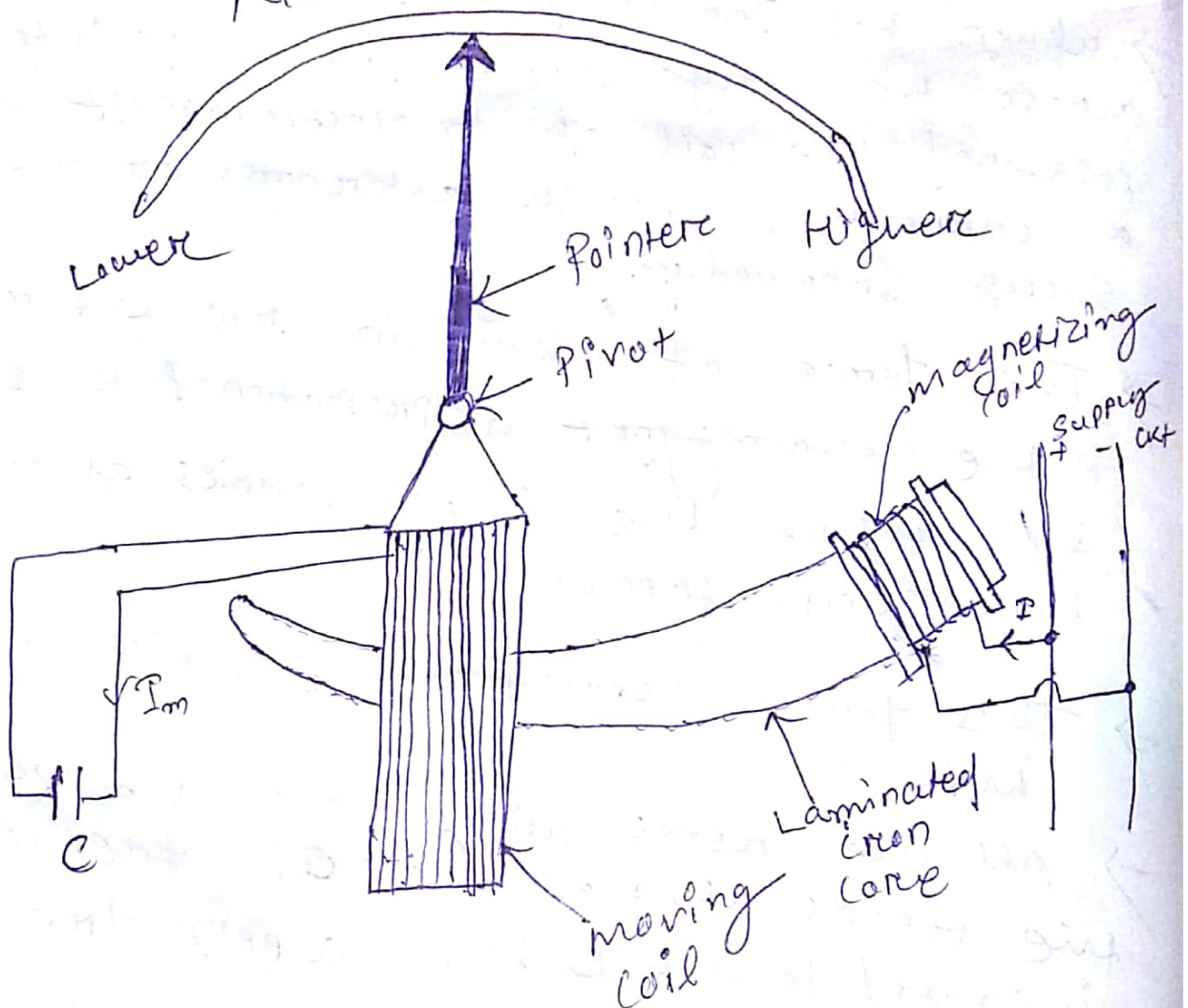



## Construction


- It consists of a lined coil which is connected across the supply whose frequency is to be measured. This coil is called magnetizing coil.
- The magnetizing coil is mounted on a laminated iron core.
- The iron core has a cross-section which varies gradually over the length being maximum near the end.
- At the <sup>near</sup> end side of iron core the magnetizing coil is mounted & minimum at the other end.
- A pointer is attached to the moving coil.
- The pointer of the moving coil are connected to a suitable capacitor  $C$ .

## Working


- The magnetizing coil carries a current  $I$  & produces a flux  $\phi$ . If we neglect resistance of the coil & the iron losses in the core, then the flux  $\phi$  is in phase with current  $I$ .

→ The flux  $\phi$  being alternating in nature induces an emf (E) in the moving coil. This emf lags the flux by an angle  $90^\circ$ .

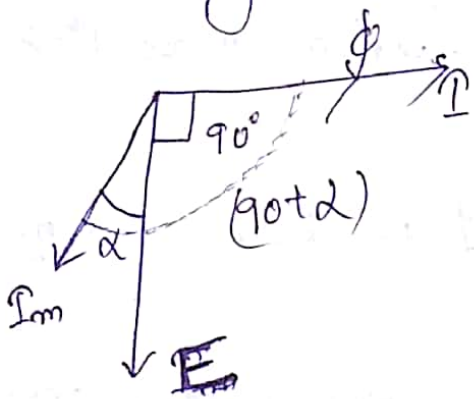
→ The emf induced circulates a current  $I_m$  in the moving coil. The phase of the  $I$  & current  $I_m$  depend upon the inductance  $L$  & capacitance  $C$  of the moving coil.



(a) (Inductive)  
( $X_L$ )

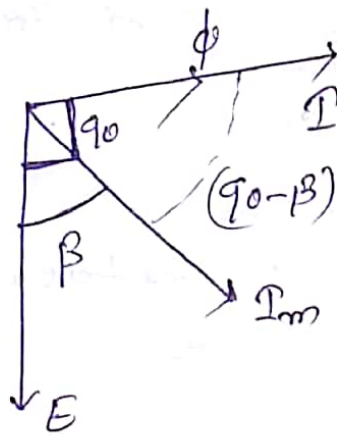

(b) ( $X_C$ )  
(capacitive)

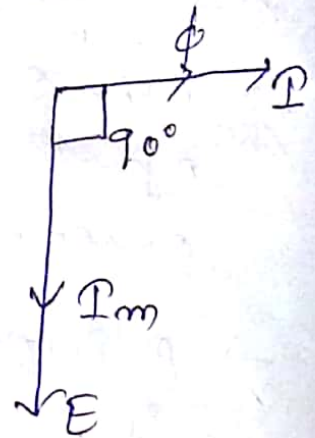

(c) (Resonance)  
( $X_L = X_C$ )

Let the moving coil is assumed to be inductive then torque acting on the moving coil is

$$T_d \propto I_m \cos(90 + \alpha) = T_d \propto I_m \cos(90 + \alpha)$$

If the moving coil is assumed to be capacitive then the torque acting on the moving coil is

$$T_d \propto I_m \cos(90 - \beta) = T_d \propto I_m \cos(90 - \beta)$$



70) If the inductive reactance is equal to the capacitive reactance then the ckt is in resonance condition. Therefore the ckt is purely resistive &  $I_m$  is in phase with 'E' & the deflecting

$$\text{torque} \propto I_d \propto I_m \cos 90^\circ$$

$$\Rightarrow T_d = K I_m \cos 90^\circ$$

$$\Rightarrow T_d = 0 \quad (\because \cos 90^\circ = 0)$$

(Rest condition of pointer)

or  
(Steady state condition)

So there is no requirement for controlling force arrangement in this type of instrument.

→ For a fixed frequency the capacitive reactance is constant but the inductive reactance for the moving coil is not constant. This is because the inductance of the moving coil depends upon the position which the moving coil occupies on the iron core.

→ If the inductive reactance is greater than the capacitive reactance ( $X_L > X_C$ ) then the torque must move the coil to a position where


$$X_L = X_C$$

→ A decreased inductive reactance is obtained if the moving coil moves away from the magnetizing coil.

→ The coil arm comes to rest when

$$X_L = X_C$$

## (b) Dynamometer type frequency meter

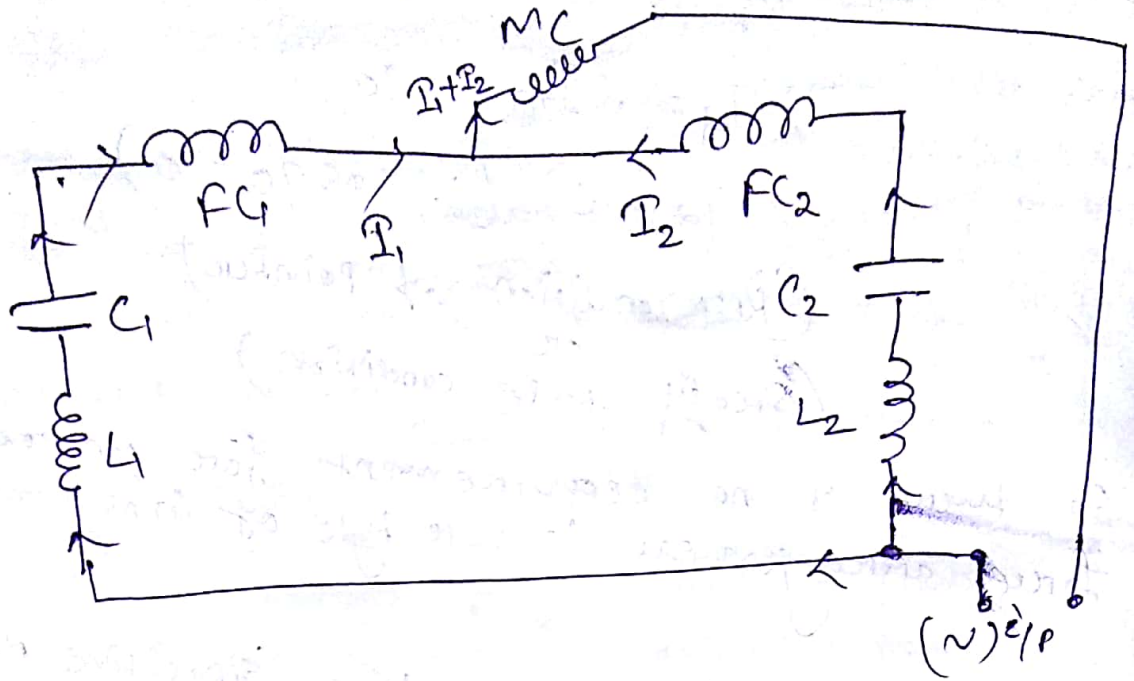

→ The f.c is divided into two parts  $FC_1$  &  $FC_2$ .  
 - The two part of the f.c form two separate resonant ~~ckt~~ ckt.

→ The torque on the m.c is proportional to the current through the ~~the~~ m.c.

→  $FC-1$  is in series with an inductance  $L_1$  & a capacitance  $C_1$  forming a resonant ckt, the frequency of this ckt  $f_1$  slightly below the lower end of the instrument scale.

→  $FC-2$  is in series with inductance  $L_2$



8 capacitance  $C_2$  forming a resonance circuit, which frequency  $f_2$  slightly ~~become~~ <sup>is</sup> lower and higher than the upper end of the instrument scale.

→ For the applied frequency (which is to be measured) the  $fC-1$  is operate above the resonant frequency ( $X_{L1} > X_{C1}$ ) with current  $i_1$  & the  $fC-2$  is operate below the resonant frequency ( $X_{C2} > X_{L2}$ ) with current  $i_2$ .

→ One fixed coil circuit is inductive & other is capacitive in nature

→ Therefore the torque produced by the two currents  $i_1$  &  $i_2$  & the torque is the resultant torque between the two torque.

→ Hence the meter scale can be calibrated in terms of frequency.

### Power Factor meters

→ The instrument which is used for the measurement of power factor is known as power factor meter.

→ There are two types of Power Factor meters:-  
(1) Electrodynamometer type  
(2) Moving iron type.




# ① Dynamometer type Power factor meter

→ Acc<sup>n</sup> to Phase distribution of <sup>electrical</sup> Power supply it is further divided into two types

i.e- (a) 1- $\phi$  Electro dynamometer type P.f meter

(b) 3- $\phi$  Electro dynamometer type P.f meter
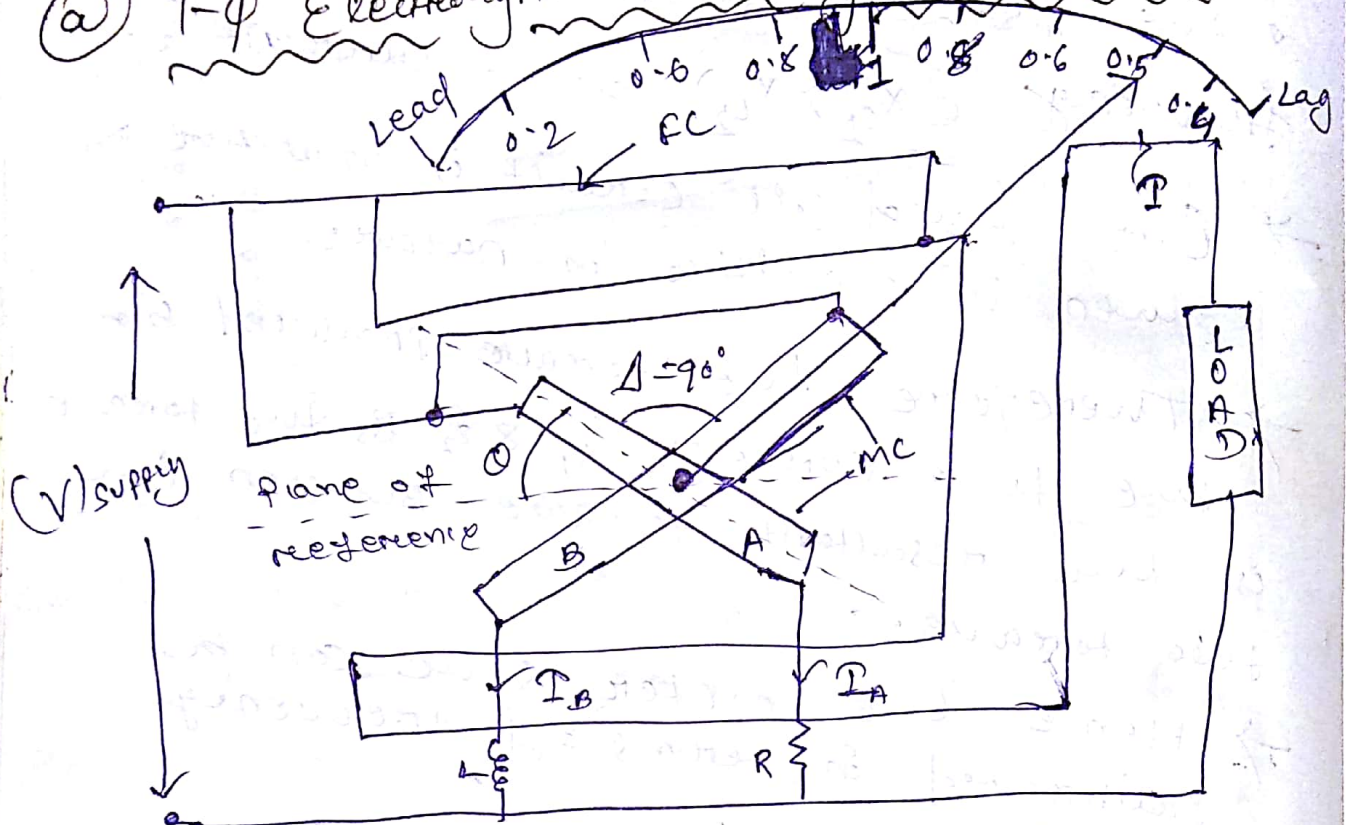
## ② 1- $\phi$ Electro dynamometer type P.f meter



→ It consists of a fixed coil which acts as a current coil. This coil is split into two

parts & carries the current of the

Ckt. Therefore magnetic field produced by the Ckt is proportional to the supply current.

→ Two identical pressure coil 'A' & 'B' pivoted on a spindle constitute the moving system.



Pressure coil 'A' has a non-inductive resistance 'R' connected in series with it & coil 'B' has a highly inductive choke coil 'L' connected in series with it.

Operation →

Let us assume that <sup>current</sup> through 'coil-B' lags the voltage by an angle  $90^\circ$  & the angle b/w two moving coil is  $90^\circ$ .

Now there will be two deflecting torques  $T_A$  &  $T_B$  acting on the moving coil.

$$T_A = KV I M_{\max} \cos \phi \sin \theta$$

$$T_B = KV I M_{\max} \cos(90^\circ - \phi) \sin(90^\circ + \theta) \\ = KV I M_{\max} \sin \phi \cos \theta$$

Here  $M_{\max}$  = maximum value of mutual inductance b/w two coil.

So at steady state position

$$T_A = T_B$$

$$\Rightarrow KV I M_{\max} \cos \phi \sin \theta = KV I M_{\max} \sin \phi \cos \theta$$


$$\Rightarrow \frac{\sin \theta}{\cos \theta} = \frac{\sin \phi}{\cos \phi}$$

$$\Rightarrow \tan \theta = \tan \phi$$

$$\Rightarrow \boxed{\theta = \phi}$$

( $\phi$  = phase angle of meter  
 $\theta$  = angle of deflection)
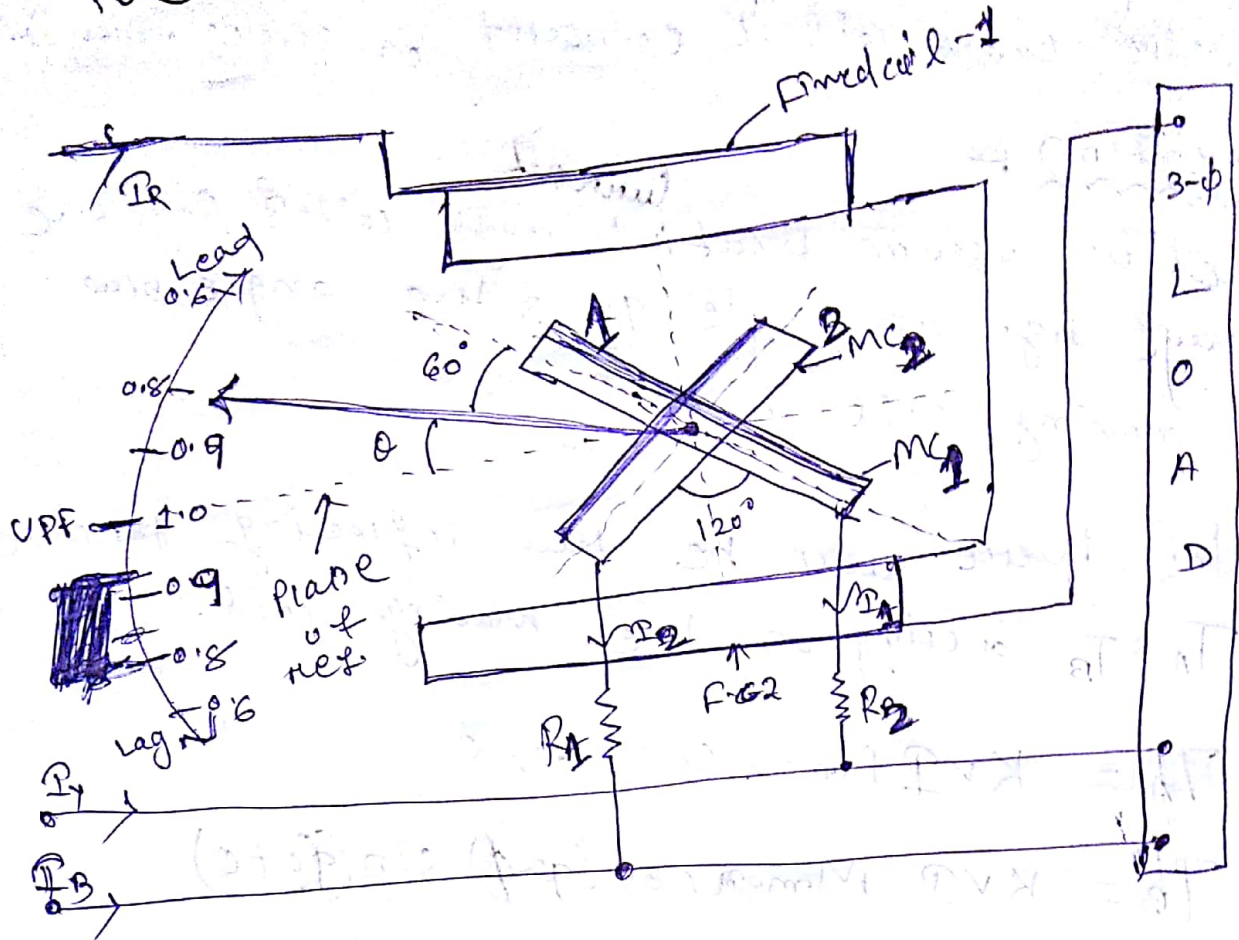
## ⑥ 3- $\phi$ Dynamometer type P.f meter



### Construction

→ It consists of two fixed coils connected in series in one of the phases & carries the line current as shown in above figure.

→ The two identical moving coils ~~MC1 & MC2~~ <sup>MC1 & MC2</sup> are fixed with their planes by an angle  $120^\circ$  apart & connected across two remaining phases, through the resistances.

### Working

→ when 3- $\phi$  P.f meter is connected in the circuit under balanced load conditions the angle through which the pointer is deflected from the unity power factor position is equal to the



→ The deflection in 3- $\phi$  power factor meter are independent of frequency & waveform, since the current in the two moving coils are both affected in the same way by any change of frequency. \*→

Torque acting on coil  $\rightarrow$

$T_A = K \sqrt{I_{\text{max}}} \cos(30 + \phi) \sin(60 + \phi)$   
 $T_B = \sqrt{3} K \sqrt{I_{\text{max}}} \cos(30 + \phi) \sin(60 + \phi)$

Torque acting on coil 2 is

$$T_2 = K V_{RB} I M_{max} \cos(30 - \phi) \sin(120 + \theta)$$

$$T = \sqrt{3} K V I M_{max} \cos(30 - \phi) \sin(120 + \theta)$$

→ Torque  $T_1$  &  $T_2$  act in the opposite directions & the moving ~~coil~~ system takes up a position where


~~$T_1 = T_2$~~

$$T_1 = T_2$$


$$\therefore \cos(30 + \phi) \sin(60 + \theta) = \cos(30 - \phi) \sin(120 + \theta)$$

$$\boxed{\theta = \phi}$$

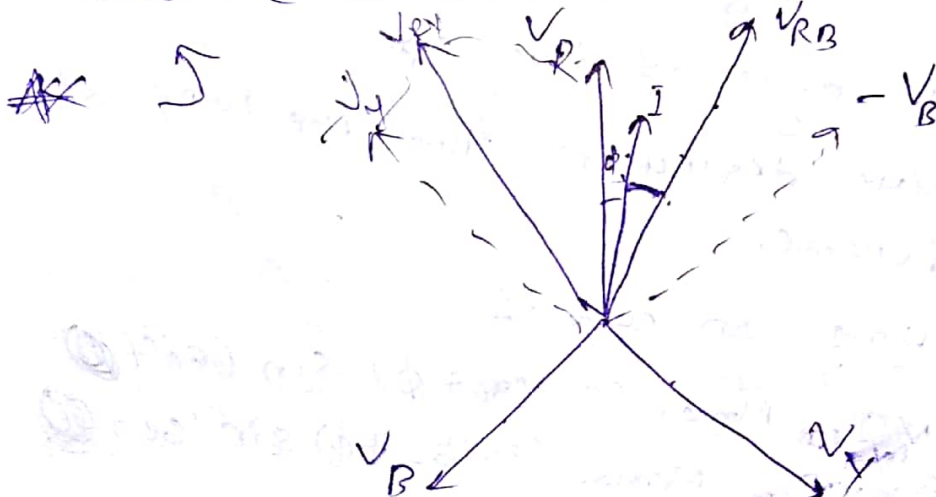Thus the angular deflection of the pointer from the plane of reference is equal to the phase angle of the ckt to which the meter is connected.





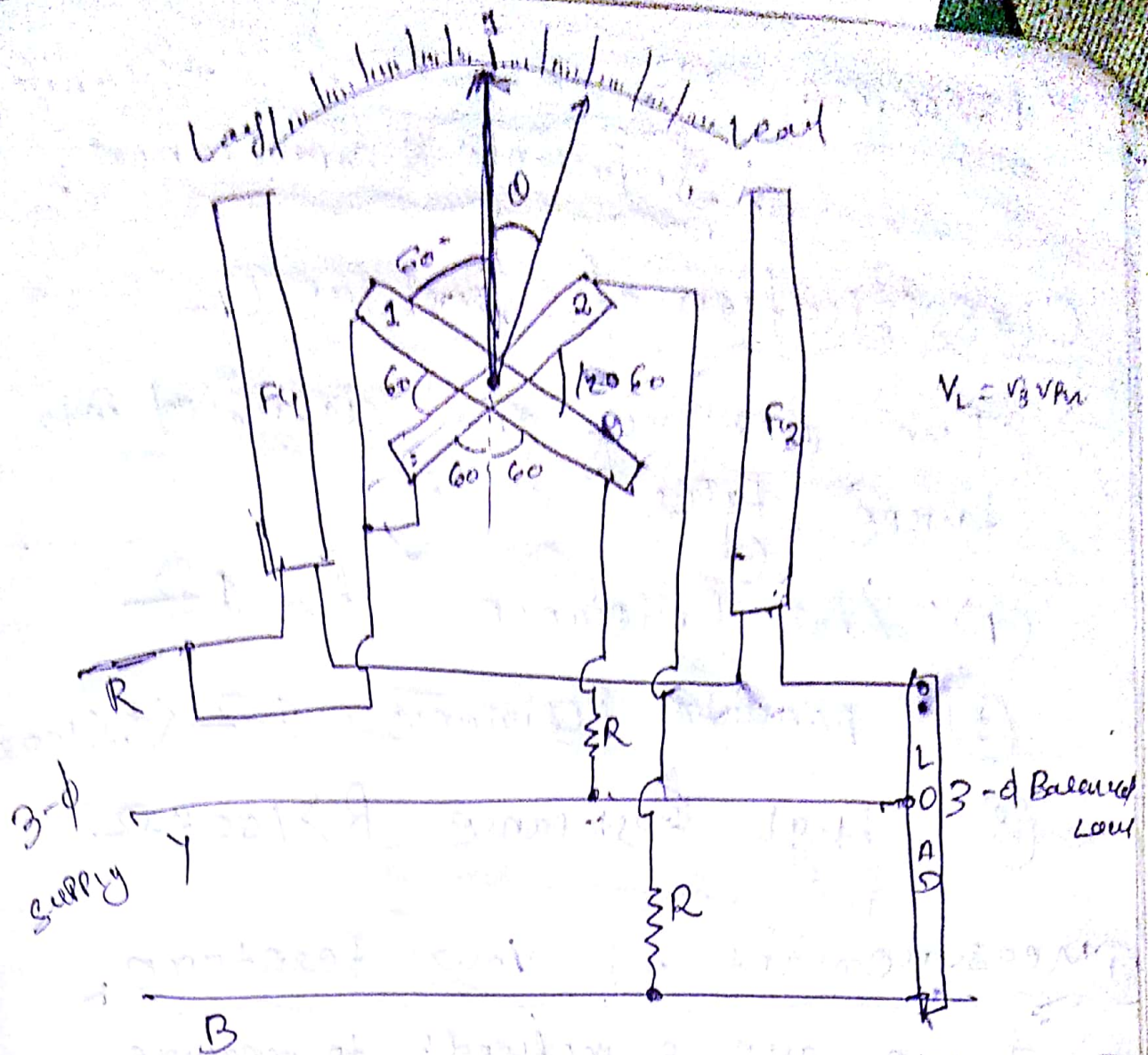

$$T_1 = \frac{K M_{max} V_{Ry} I}{\sqrt{2}} \cos(30+\phi) \cdot \sin(60+\theta)$$

$$T_2 = \frac{K M_{max} V_{Ry} I}{\sqrt{2}} \cos(30-\phi) \cdot \sin(120+\theta)$$

$$T_1 = T_2$$

$$\sqrt{3} K \cos(30+\phi) \cdot \sin(60+\theta) = \cos(30-\phi) \cdot \sin(120+\theta)$$

$$\frac{\sin(120+\theta)}{\cos(30-\phi)}$$

$$\Rightarrow \frac{\cos(30+\phi)}{\cos(30-\phi)} = \frac{\sin(120+\theta)}{\sin(60+\theta)}$$

$$\Rightarrow \frac{\frac{\sqrt{3}}{2} \cos \phi - \frac{1}{2} \sin \phi}{\frac{\sqrt{3}}{2} \cos \phi + \frac{1}{2} \sin \phi} = \frac{\sin(120+\theta)}{\sin(60+\theta)}$$

# Chapter-6 Measurement of Resistance, Inductance & Capacitance

## Classification of Resistance

→ The resistance are classified into three types.


- (1) Low Resistance  $R \leq 1 \Omega$
- (2) Medium Resistance  $1 \Omega < R \leq 100 k\Omega$
- (3) High Resistance  $R > 100 k\Omega$ .

## Measurement of Low Resistance

→ There are 3-methods to measure low resistance, i.e.-

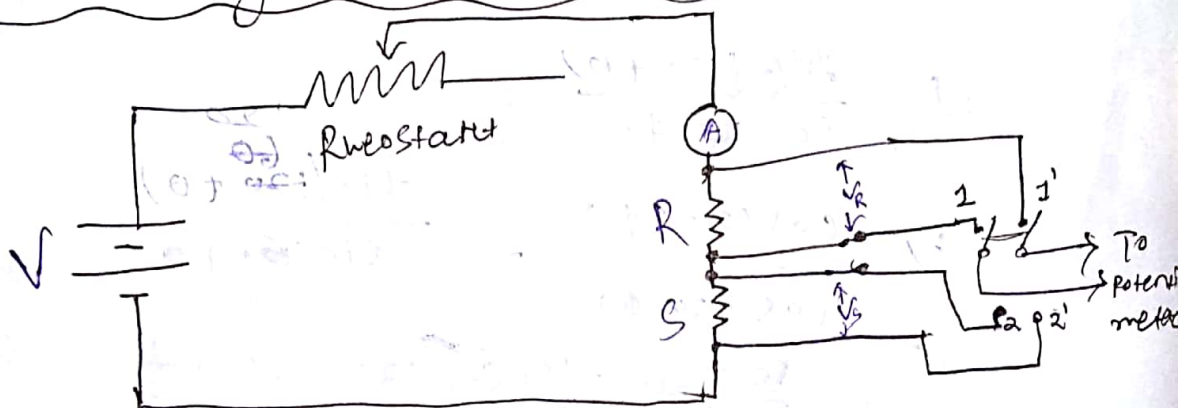- (i) Kelvin double bridge method
- (ii) Potentiometer method.
- (iii) Ammeter-voltmeter method (or voltage drop method)

Measurement of low resistance by Potentiometer method





→ The circuit of measurement of resistance with a potentiometer is shown in above fig.

→ The unknown resistor ( $R$ ) is connected in series with the standard known resistor ( $S$ ).

→ The current through the circuit is controlled with the help of a rheostat.

→ Here a two pole double throw switch is used, when the switch is in position 1 & 1', the unknown resistance  $R$  is connected to the potentiometer.

→ Let the reading of the potentiometer is  $V_R$ .

$$\boxed{V_R = I \cdot R} \quad \text{--- (1)} \quad I = \frac{V_R}{R}$$

→ Now the switch is in position 2 & 2' then the standard resistor ( $S$ ) is connected to the potentiometer.

→ Let the reading of the potentiometer is  $V_S$ .  $\boxed{V_S = I \cdot S}$  --- (2)  $\Rightarrow I = \frac{V_S}{S}$

By dividing eqn (1) & (2)


from eqn (1) & (2)

$$\frac{V_R}{V_S} = \frac{I \cdot R}{I \cdot S}$$
$$\Rightarrow \boxed{R = S \cdot \frac{V_R}{V_S}}$$

$$\frac{V_R}{R} = \frac{V_S}{S}$$
$$\Rightarrow \boxed{R = \frac{V_R}{V_S} \times S}$$

∴ since the value of the standard resistor (S) is accurately known then the value of the 'R' can also be known accurately.
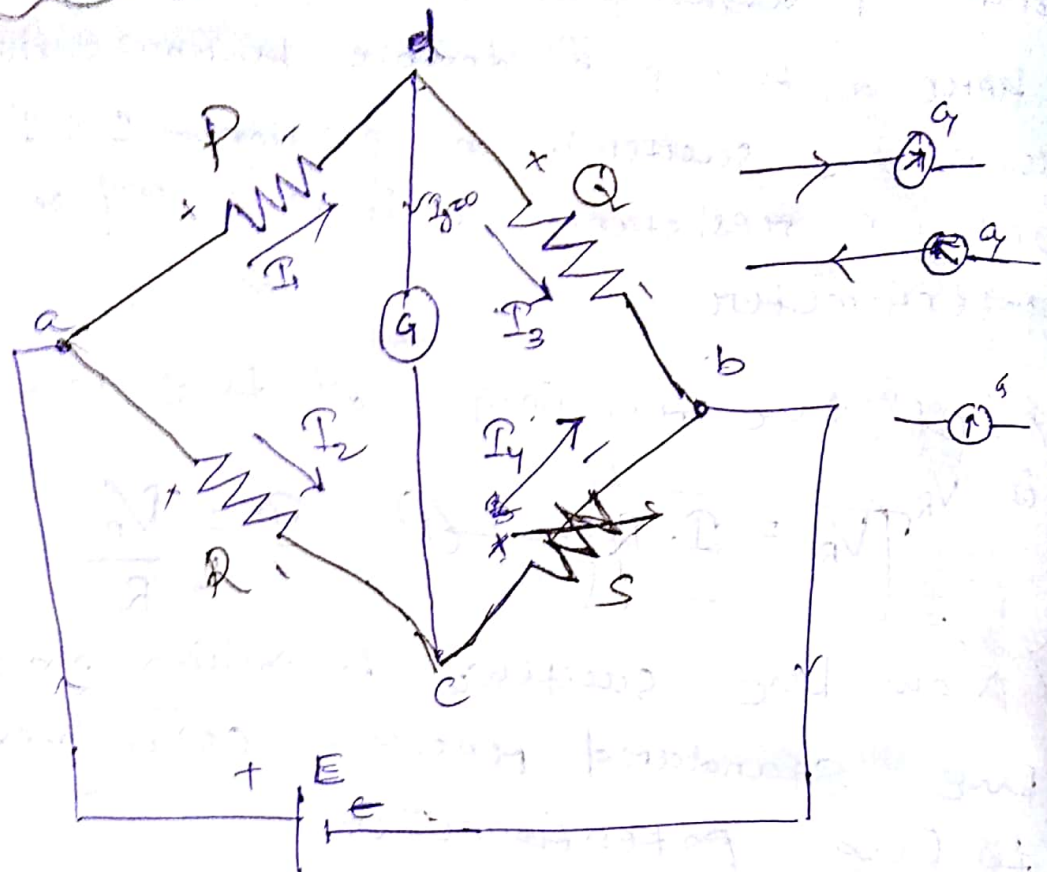
## (2) Measurement of medium Resistance by Wheat-Stone Bridge method



### (Wheatstone Bridge)

→ Wheatstone bridge is the ~~wheatstone~~ <sup>very</sup> important device which is used in the measurement of medium resistance.

→ This is the simplest & the most basic bridge circuit used in measurement studies.

→ It mainly consists of four arms of resistance 'P', 'Q', 'R' & 'S'. where 'R' is the unknown resistance which is to be measured, while 'S' is a standard



variable resistance & 'P' & 'Q' are known as the ratio arms.

→ An emf source 'E' is connected b/w points 'a' & 'b' while a galvanometer is connected b/w points 'c' & 'd'.

→ A bridge circuit always works on the principle of null indication or null detector, i.e. - we vary a parameter until the detector shows zero & then use a mathematical relation to determine the varying parameter & other constants.

→ The standard resistance, 'S' is varied in order to obtain null deflection in the galvanometer (G).

→ This null deflection implies no current flows from point 'c' to 'd', which means potential of point 'c' & 'd' is same. i.e. - the bridge is in balanced condition.

Hence  $I_1 P = I_2 R$  — (1)

For galvanometer current to be zero

also  $I_1 = I_3 = \frac{E}{(P+Q)}$  — (2)

&  $I_2 = I_4 = \frac{E}{(R+S)}$  — (3)

Combining the above two equations we get the ~~or, we obtain~~


$$\frac{P}{Q} = \frac{R}{S}$$

$$R = \frac{P}{Q} \times S$$

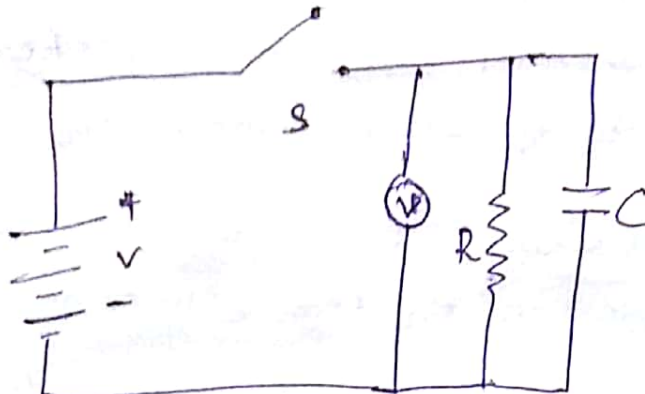
### ③ Measurement of high resistance by loss of charge method

~~There are few methods used for~~

→ In this method we utilize the emf of voltage across a discharging capacitor to find the value of unknown resistance  $R$ .



(a)

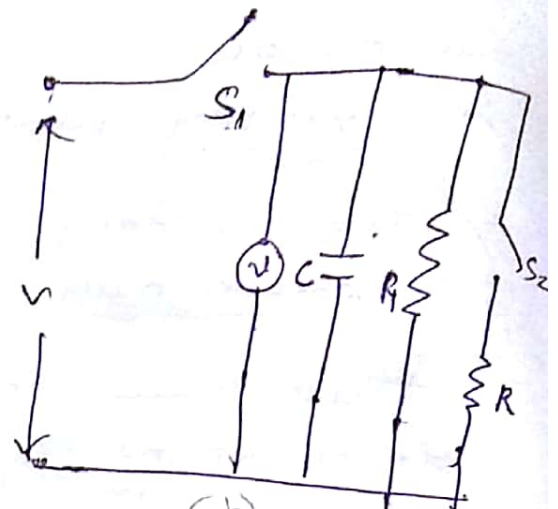

(b)

→ In this method the unknown resistance is  $R$  connected in parallel with a capacitor  $C$  & a electrostatic voltmeter.

→ The electrostatic voltmeter measure the voltage across the resistance  $R$  & through the voltage & current we can find out the unknown resistance.

→ The Capacitor  $C$  is allowed to charge through a ~~battery~~ voltage i.e. a battery is connected across it by switch  $S_1$ .

→ After that the Capacitor  $C$  is charged upto some voltage, the battery is disconnected ~~by switch  $S_1$~~  & the capacitor is allowed



to discharge through the unknown resistance  $R$ .

→ The relationship of the discharge or the loss of charge ~~through~~ <sup>in</sup> the capacitor  $C$  through that we can calculate the unknown resistance  $R$ . That is why it is called loss of charge method.

→ The capacitor is initially charged to some suitable voltage by means of a battery of voltage ' $V$ ' & then allowed to discharge through the unknown resistance.

→ The charging & discharging of capacitor can be expressed in ~~the~~ <sup>the</sup> form of an expression i.e.

→ The terminal voltage is observed during discharge →  $V = V_0 e^{(-t/CR)}$


$V = \text{emf of battery.}$

$V = \text{voltmeter reading.}$

$$\frac{V}{V_0} = e^{(-t/CR)}$$

$t = \text{time taken for full discharge of capacitor.}$

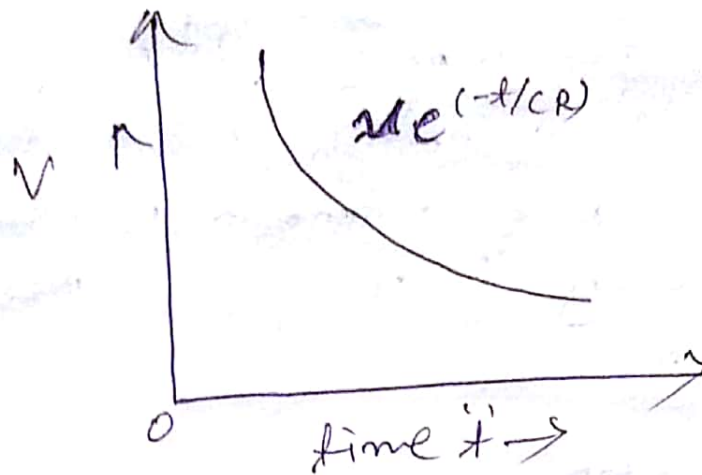→ The discharging of capacitor is in the form of exponential or the capacitor discharging exponentially



From the above expression <sup>unknown</sup>  $R$  high resistance  $R$  now we can find out

$$\cancel{R = \frac{t}{C \log_e \frac{V}{V_0}}} \quad \boxed{R = \frac{t}{C \log_e \left( \frac{V}{V_0} \right)}}$$

$$\boxed{R = 0.4343 \frac{t}{C \log_{10} \left( \frac{V}{V_0} \right)}}$$

$$\left( \log_e \rightarrow \log_{10} \right. \\ \left. = 0.4343 \right. \\ \left. \log_{10} \right)$$

→ If resistance  $R$  is very ~~high~~ large then the process becomes time consuming ~~to detect~~ therefore there are some factors which could occur error.

→ So Instead of measuring voltage across capacitor, ~~we measure~~ the diff. b/w voltage of battery  $V$  & voltage across voltmeter  $v$  is calculated.

$$\text{i.e. } \boxed{V - v = e}$$



So

$$R = \frac{0.4343}{C \log_{10} \frac{V}{V-e}}$$

where  $e$  = small difference b/w  $V$  &  $V'$

→ In this method measures high resistance but it requires a capacitor of very high leakage resistance as compared to the unknown resistance  $R$  so that no leakage current are produced.

→ So we have to consider the leakage resistance of capacitor also. & the ~~equation~~ becomes as shown in Fig (b)

Let  $R_1$  is the leakage resistance of the capacitor

$R'$  is the equiv. resistance of  $R$  &  $R_1$

$$R' = \frac{R \times R_1}{R + R_1}$$

Then discharge eq<sup>n</sup> will become when switch  $S_1$  &  $S_2$  closed 'C' discharges across equiv. Resistance  $R'$ .

$$R' = \frac{0.4343}{C \log_{10} \frac{V}{V'}}$$

Now when  $S_1$  = open &  $S_2$  also open

$$\text{Then } R_1 = \frac{0.4343}{C \log_{10} \frac{V}{V'}}$$

# Megger

(~~Ohmmeter~~)

- It is a special type of ohmmeter used to measure the electrical resistance of ~~insulators~~<sup>insulation</sup>. Insulating components i.e. cable jackets, winding resistance of motor, must be tested for ~~their~~ their insulation strength at the time of commission & as part of maintenance of high voltage electrical equipment & installations.
- Megger is adapted to application in portable instruments measuring insulation resistance. This is principle of ~~insulation~~ insulation testing instrument known as megger.


→ ~~Why~~ why is megger testing done?

→ The Insulation resistance needs to be tested to check the insulation quality (puncture in insulation) of the electrical system & to avoid any major or minor electrical shocks to operators.

~~Construction~~

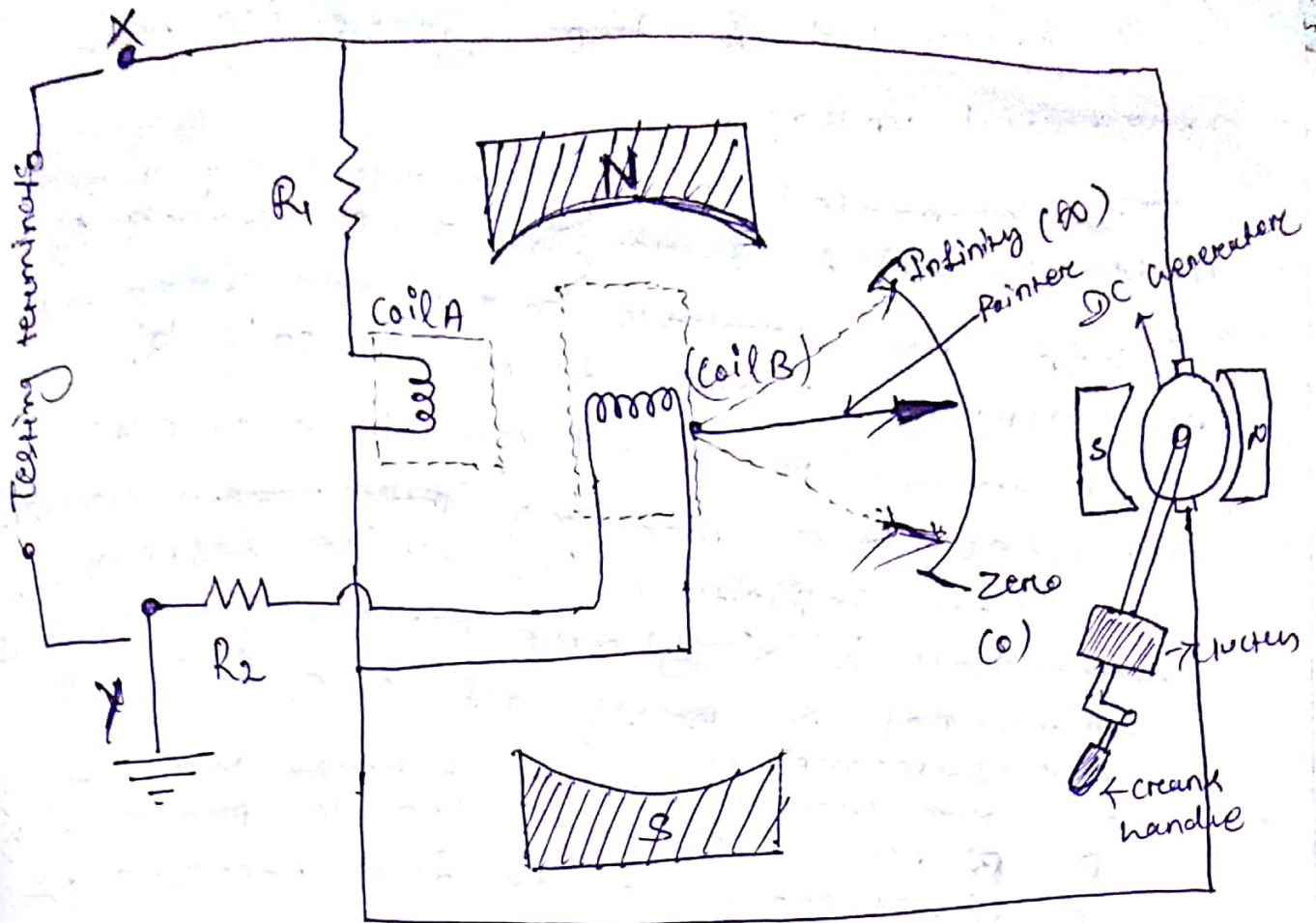- The parts of megger are shown in the Fig-1.
- The armature of the generator is rotated by the hand driven crank lever.
- The clutch mechanism is designed to slip at a predetermined speed. This facilitates





(Fig-1)

The generator to maintain a constant speed & hence the constant voltage while testing

→ The two coils 'A' & 'B' constitute a m.c voltmeter & an ammeter. Both are combined to form one instrument.

→ Coil A is voltage coil & coil 'B' is m.c as in PMMC instrument

→ The 'Hot' terminal of the equipment whose insulation resistance has to be measured is connected to the testing terminal 'X'.

→ The terminal 'Y' is connected to the body of the equipment, which is generally grounded

- when the crank handle is rotated, a voltage is generated in the generator, ~~the~~ generated voltage
- The generated voltage is applied across the voltage coil A through a resistance  $R_s$ .
- when the terminals 'n' & 'y' are free initially, no current flows through coil 'B'.
- The torque produced by the coil 'A' rotates the moving ~~element~~ element to show infinity ( $\infty$ ), while testing the terminals 'n' & 'y' are connected across the terminal & body of the M/C for measurement.
- Now the current passes through the deflection coil 'B'. The deflection torque produced by coil 'B' interacts with the torque of coil 'A' & rotates the moving element to indicate the resistance value.
- Voltage generated by this instrument is around 500 volts. Meggers are available to generate 1kV, 2.5kV & 5kV also.
- High voltage meggers are either motor operated or power operated.



# Earth Resistance Measurement

## Earth Tester



The instrument used for measuring the resistance of the earth is known as earth tester.

→ The Earth Tester is a special type of Meggare, & it has some additional constructional features & they are;

- (i) a rotating current reverser
- (ii) a rectifier.

→ Before providing the earthing to the equipment it is essential to determine the resistance of that particular area from where the earth pit can be dug. The earth should have low resistance so that the fault current easily passes ~~through~~ to the earth. The resistance of the earth can be ~~measured~~ determined by the help of earth tester instrument.

# Construction & Working Principle

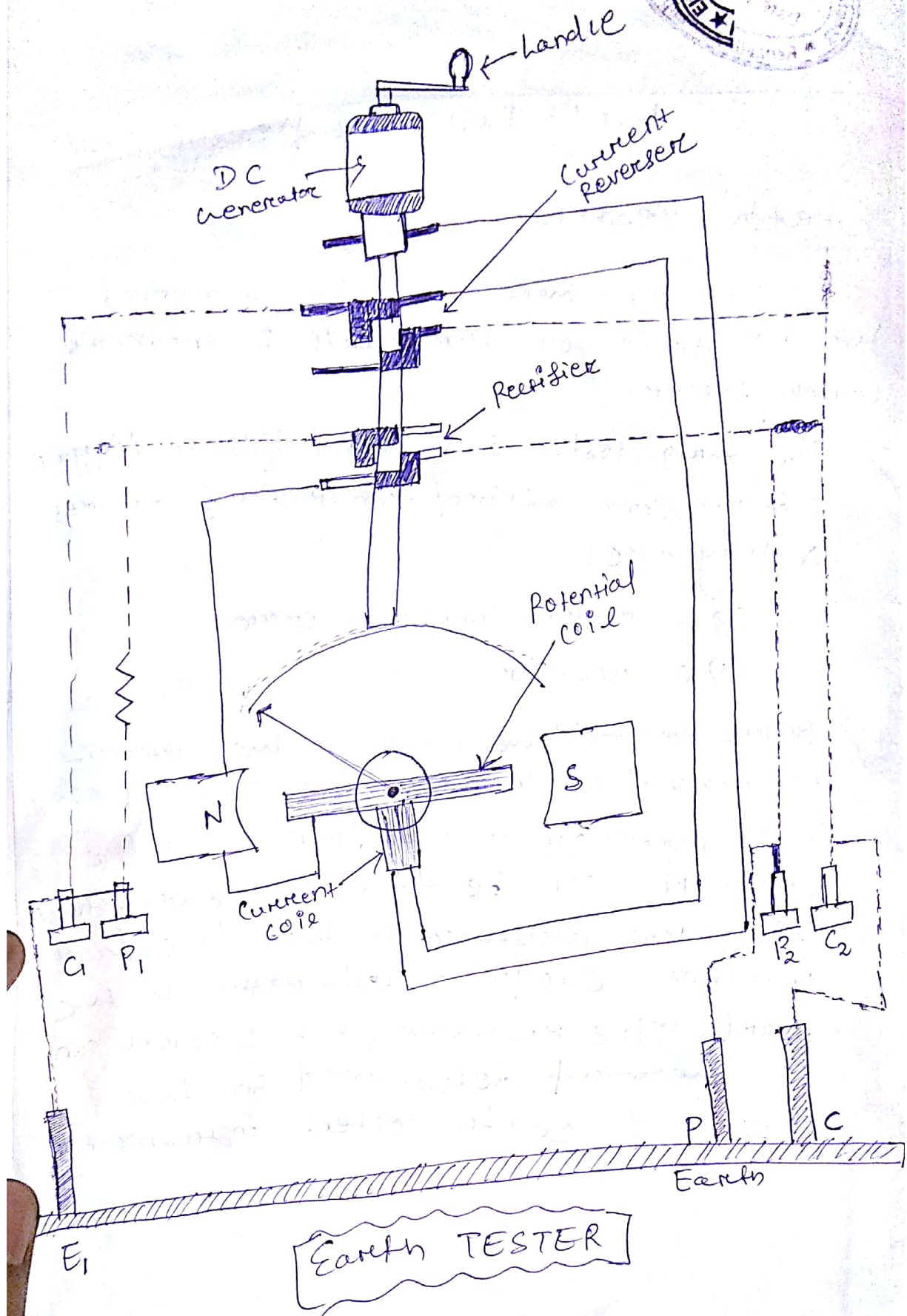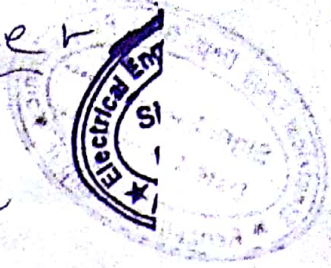



- The <sup>two</sup> additional features of earth tester consist of simple commutators made up of 'L' shaped segments.
- They are mounted on the shaft of hand driven generator.
- Each commutator has four lined brushes. One pair of each set of brushes is so positioned that they make contact alternately with one segment & then with other as the commutator rotates.
- The second pair of ~~brushes~~ each of set of brushes is so positioned on the commutator so that continuous contact is made with one segment whatever the position of the commutator.
- The earth Tester ~~has four terminals~~ consists of two pressure coils & two current coils. These are four terminals of earth tester  $P_1, P_2$  &  $G_1, G_2$ .
- Two terminals  $P_1$  &  $G_1$  are shorted to form a common point to be connected to the earth electrode. The other two terminals  $P_2$  &  $G_2$  are connected to auxiliary electrodes 'P' & 'C' respectively.
- The deflection of its pointer indicates the resistance earth directly. The deflection of the pointer depends upon the ratio of the voltage of P.C to the

## Current of the C.C.


→ Although the earth tester which is a PMMC instrument & can operate on d.c only, yet by including the reverser & the rectifying device it is possible to make measurements with a.c flowing in the soil.

→ The short ckt current passes through the equipment to the earth is alternating in nature. Thus, we can say that the Alternating current flows in the soil. This AC current reduces the unwanted effect of the soil, which occurs because of chemical action or because of the production of back emf.


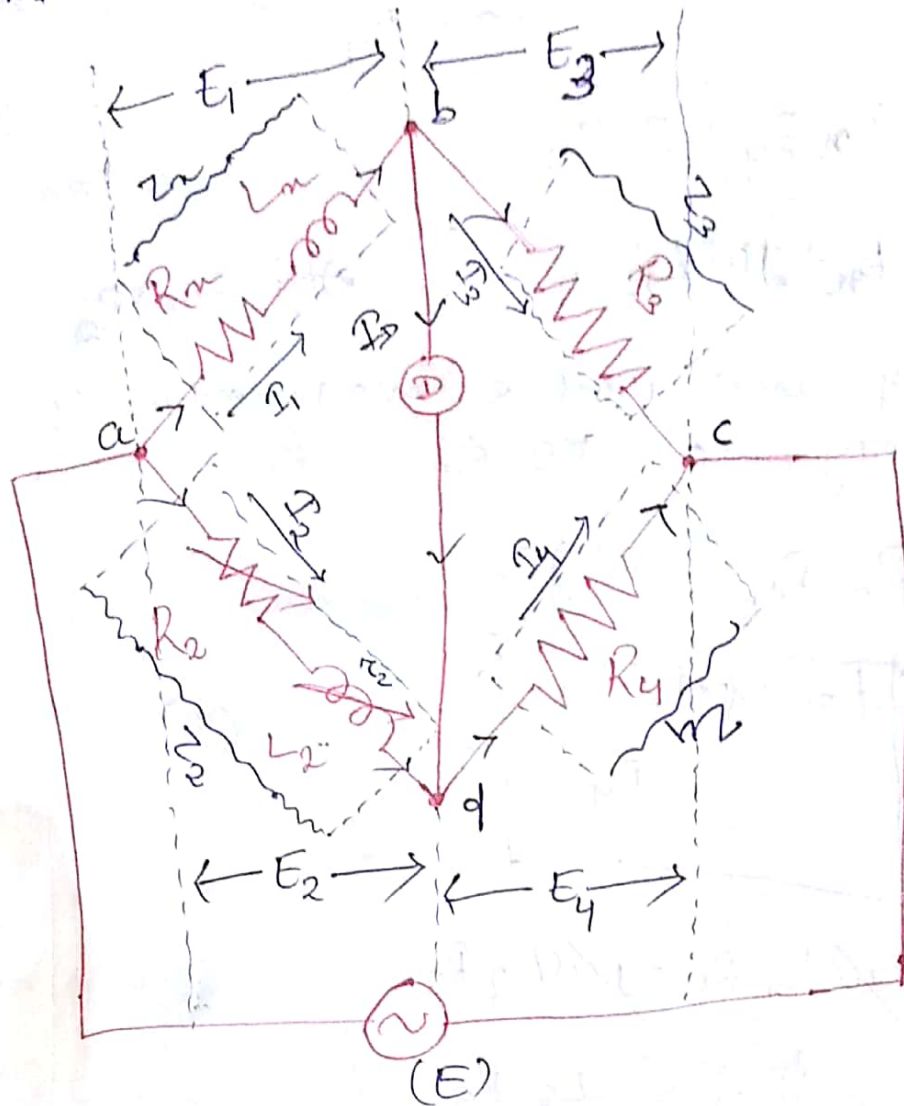
# Measurement of Inductance by Maxwell's Bridge Method:

> This bridge measures an inductance by comparison with a variable standard self-inductance.



The connection of the bridge as shown in above figure.

Let  $L_n$  = unknown inductance of  $R_n$

$L_2$  = Variable inductance of lined resistance  $R_2$ .

$R_2$  = variable resistance connected in series with inductor  $L_2$ .

$R_3$  &  $R_4$  = Known non-inductive resistances.

→ A detector  $D$  is connected across point  $b$  &  $d$  to detect the current  $I_D$  through it.

Therefore at balanced condition  $I_D = 0$

$$E_1 = E_2 \text{ or } E_3 = E_4$$

$$Z_n Z_4 = Z_2 Z_3$$

$$\text{or } (R_n + j\omega L_n) R_4 = (R_2 + j\omega L_2) R_3$$

Evaluating the real & imaginary parts separately, we have;

$$R_n R_4 = (R_2 + j\omega L_2) R_3$$

$$\Rightarrow \boxed{R_n = \frac{(R_2 + j\omega L_2) R_3}{R_4}} \quad \text{--- (1)}$$

$$\text{and } j\omega L_n R_4 = j\omega L_2 R_3$$

$$\Rightarrow \boxed{L_n = \frac{L_2 R_3}{R_4}} \quad \text{--- (11)}$$


Thus, the unknown value of inductance & resistance can be measured by using above expression i.e. eqn (1) & (11) in terms of  $R_2, R_3, R_4$  &  $L_2$ .


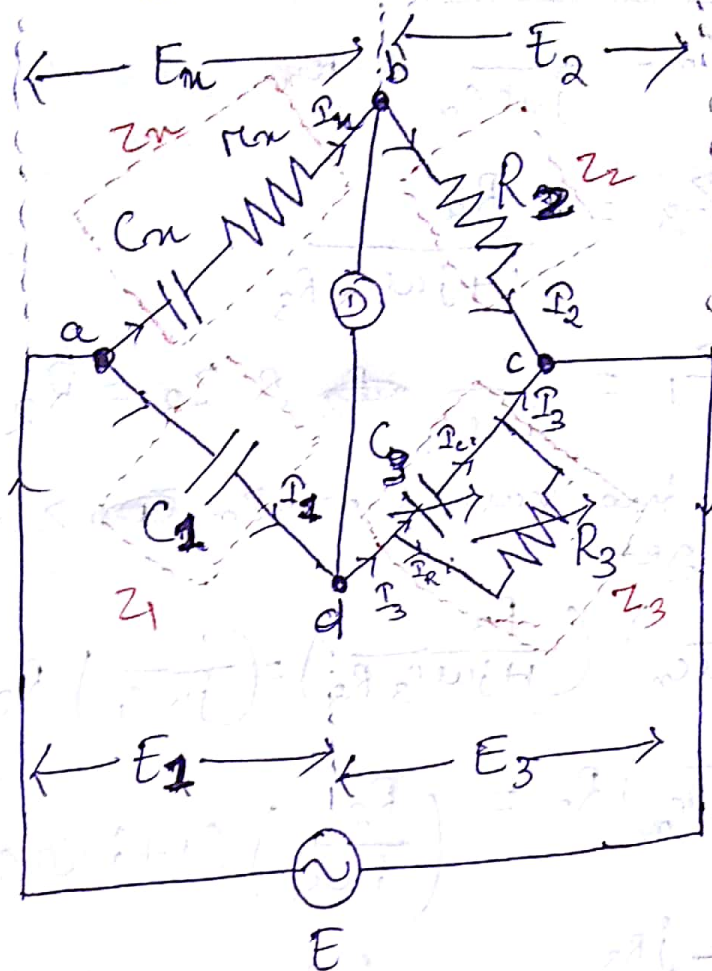
# Measurement of capacitance by Schering Bridge method

→ This bridge is widely used for measurement of capacitance & dissipation factor.

→ Let us consider the circuit of Schering bridge as shown in figure below



Here  $C_x$  = unknown capacitance whose value is to be determined with series resistance  $r_x$ .

$r_x$  = series resistance representing the loss in the capacitor 'C'.

$C_1$  = A standard capacitor

$C_3$  = A variable capacitor

$R_2$  = pure non-inductive resistor.

$R_3$  = variable non-inductive resistor.

in parallel with variable capacitor  $C_3$ .

Now the supply is given to the ~~the~~ bridge b/w the points 'a' & 'c'. The detector is connected b/w 'b' & 'd'.

Therefore at balanced condition

$$Z_m Z_3 = Z_1 Z_2$$

where  $Z_m = \frac{1}{j\omega C_m} + R_m$

$$Z_3 = \frac{R_3}{1 + j\omega C_3 R_3}$$

$$Z_1 = \frac{1}{j\omega C_1} \text{ \& } Z_2 = R_2$$

substituting the values of  $Z_m$ ,  $Z_1$ ,  $Z_2$  &  $Z_3$ , we get

$$\left(R_m + \frac{1}{j\omega C_m}\right) \left(\frac{R_3}{1 + j\omega C_3 R_3}\right) = \left(\frac{1}{j\omega C_1}\right) R_2$$

$$\left(R_m + \frac{1}{j\omega C_m}\right) R_3 = \left(\frac{R_2}{j\omega C_1}\right) (1 + j\omega C_3 R_3)$$

$$R_m R_3 - \frac{j R_3}{\omega C_m} = -\frac{j R_2}{\omega C_1} + \frac{R_2 R_3 C_3}{C_1}$$

Evaluating the real & imaginary parts, we get;

$$R_m = \frac{R_2 C_3}{C_1} \quad \text{--- (I)}$$

$$C_m = C_1 \frac{R_3}{R_2} \quad \text{--- (II)}$$

Dissipation factor:-

$$D_1 = \tan \delta = \omega C_m R_m$$

$$= \omega \left(C_1 \frac{R_3}{R_2}\right) \times \left(\frac{R_2 C_3}{C_1}\right) = \omega C_3 R_3$$



# Digital Multimeter

→ It is an instrument which measures a.c & d.c voltages, a.c & d.c currents & resistances over a wide range.

Digital

↓  
Indicates that the device has a digital or LCD output.

Multimeter

↓  
Indicates that a single device can be used for multiple measurements.

(LCD = Liquid crystal Display)

Parts of Digital Multimeter

① Display screen :- It has illuminated display screen for better visualization.

→ Five digits — one for sign value  
Display or Sign — ~~one~~ four for number representation.

$\overline{1}$   $\frac{0}{9}$   $\frac{0}{9}$   $\frac{0}{9}$   $\frac{0}{9}$   
1 2 3 4 5

② Selection knob + multimeter is used for several voltage, current & resistance.  
→ The selection knob allow the user to select the diff. measurement.

### ③ Port + Two Port

→ There are Two ports

(i) mAVS2 port

(ii) COM port.

→ One is milli-amp, volt & ohm to measure current, voltage & resistances. & another is common port.


→ In multimeter there having two probes i.e one Red probe (+) & one Black probe (-)

→ Red Probe is (+ve) & connected to mAVS2 port

→ Black Probe is (-ve) & connected to common port.

→ In this multimeter a '10A' port also available & this port current port can measures large currents.

### Block Diagram of Digital Multimeter

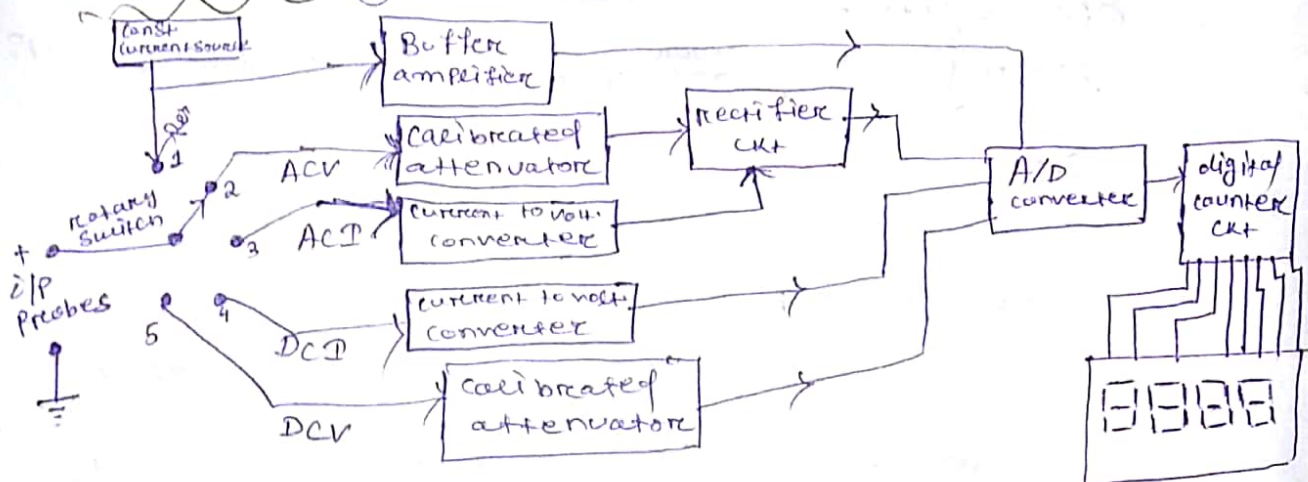

1. Resistance

2. ACV (AC voltage)

3. ACI (AC current)

4. DCI (DC current)

5. DCV (DC voltage)

Digital Display



→ The current is converted into voltage by passing it through low shunt resistance.

→ The AC quantities are converted into DC quantities by employing various rectifier & filtering circuits.

→ The resistance measurements consist of a low current source that is applied across an unknown resistance.

### Measurement of voltage

→ For measurement of A.C voltage, the i/p voltage is fed through a calibrated compensated attenuator, to a precision full wave rectifier followed by a ripple reduction filter & then converted by A/D converter to show digital form of voltage on display.

### Measurement of Current:-

→ For current measurement, the drop across an internal calibrated shunt is measured directly by the A/D converter in terms of "DC current mode" & after AC to DC conversion in the "ac current mode".

### Measurement of Resistance

→ Digital multimeter measures the voltage across the externally connected resistance, resulting from a current forced through it from a calibrated current source.

$$V = IR$$


$$R = \frac{V}{I}$$



## \* Analog Multimeter:
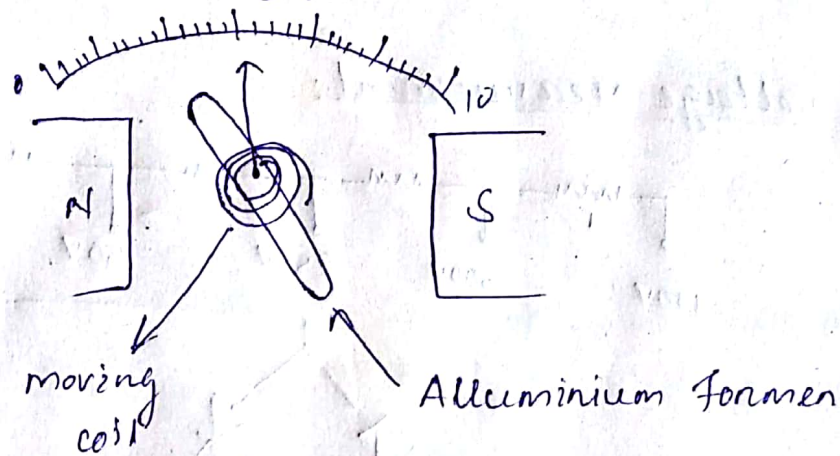
### \* Construction & Working Principle:

- It is an galvanometer of PMMC type.
- It consists of a moving coil and a permanent magnet. The moving coil is wound on an aluminium former.
- The pointer is attached on the moving coil and moves <sup>due to influence of</sup> in the magnetic field.
- The pointer is calibrated over the scale.



- Two spiral springs are attached to the coil assembly (at the top and bottom) to provide controlling torque.
- Galvanometer is converted into a voltmeter, ammeter & ohmmeter with the help of suitable ckt's for measuring voltage, current and resistance.


### \* Voltage measurement by multimeter:

High voltages are measured by connecting resistance in series with galvanometer.




- \* Multimeter having two lead 
 $\swarrow$  Red (+ve)  
 $\searrow$  Black (-ve)
- \* One lead is connected in voltage range socket  
 other lead  $\rightarrow$  common socket

### AC voltage Measurement:

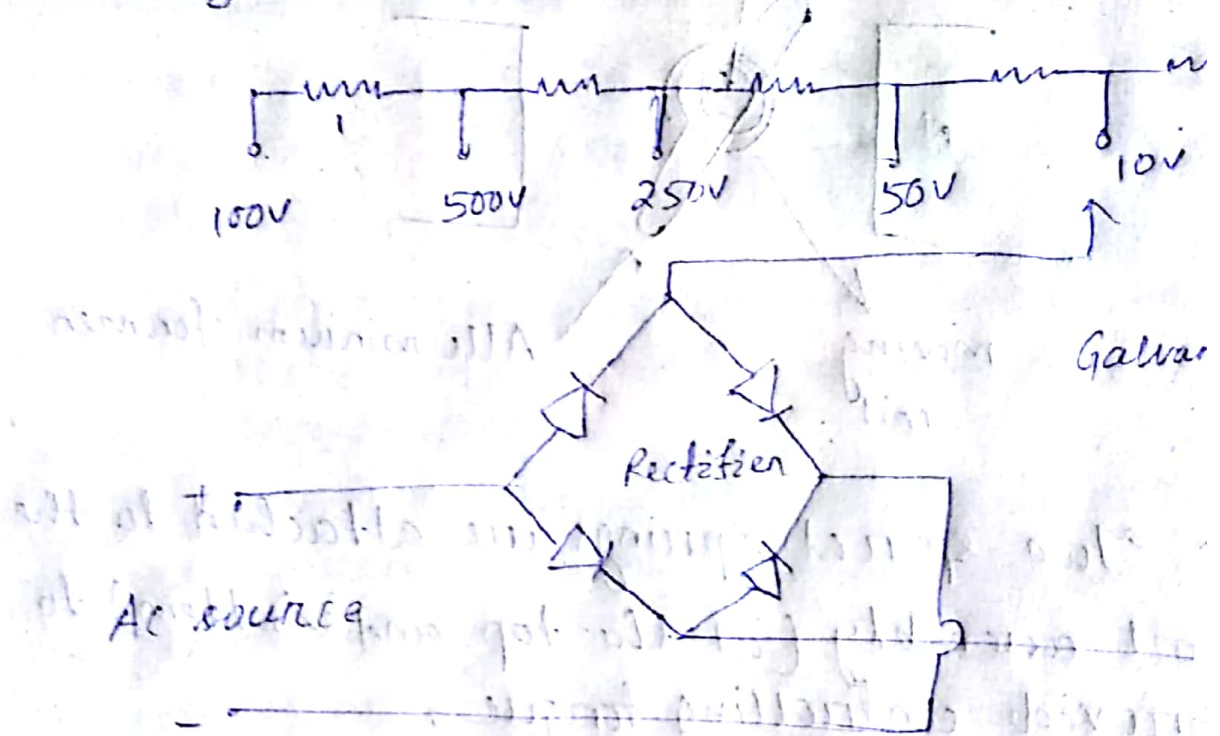

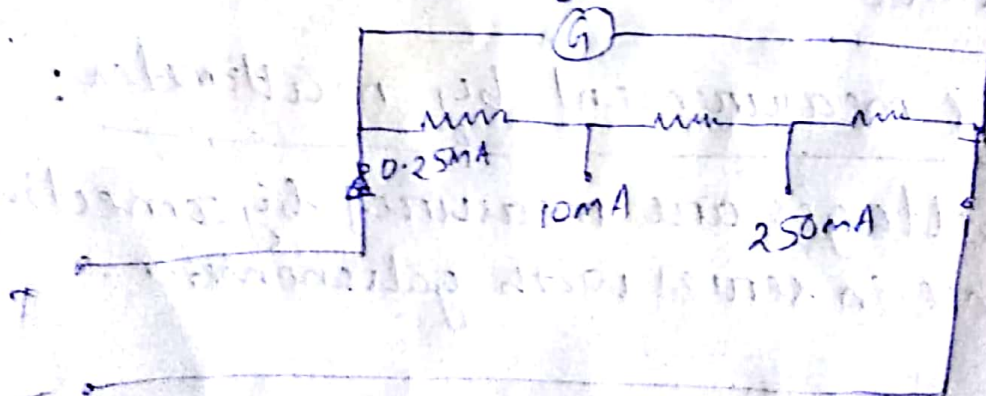
- $\rightarrow$  A rectifier is connected during the measurement of AC voltage source
- \* Current measurement by Multimeter



→ As the value of the current to be measured is increasing the shunt resistance value should be decreased.
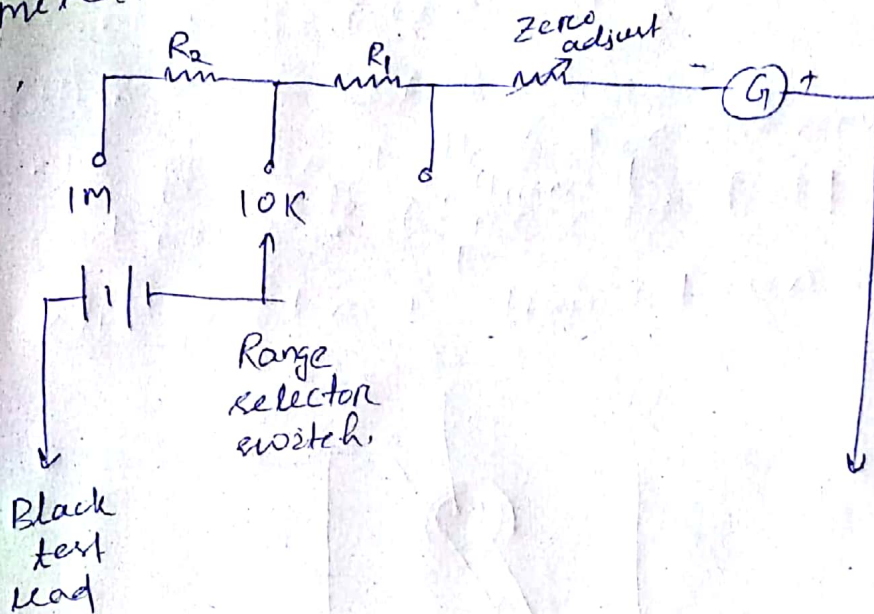
### Resistance Measurement by Multimeter:

→ Here the Galvanometer is converted as an ohm meter.



→ Here to measure the resistance value we have to make the voltage and current to be constant

→ The zero adjustment control is valid until the meter reads zero resistance.



# OSCILLOSCOPE:-

→ Oscilloscopes are commonly used to measure shape of a waveform, measure amplitude & frequency of a signal & detect error & noise in a signal.

## Cathode Ray Tube:-

→ CRT is one of the main parts of CRO


→ The entire CRT is enclosed in an evacuated glass envelope.

→ It consists of 3 main sections

(1) Electron gun assembly

(2) Deflection plates

(3) Phosphor screen.

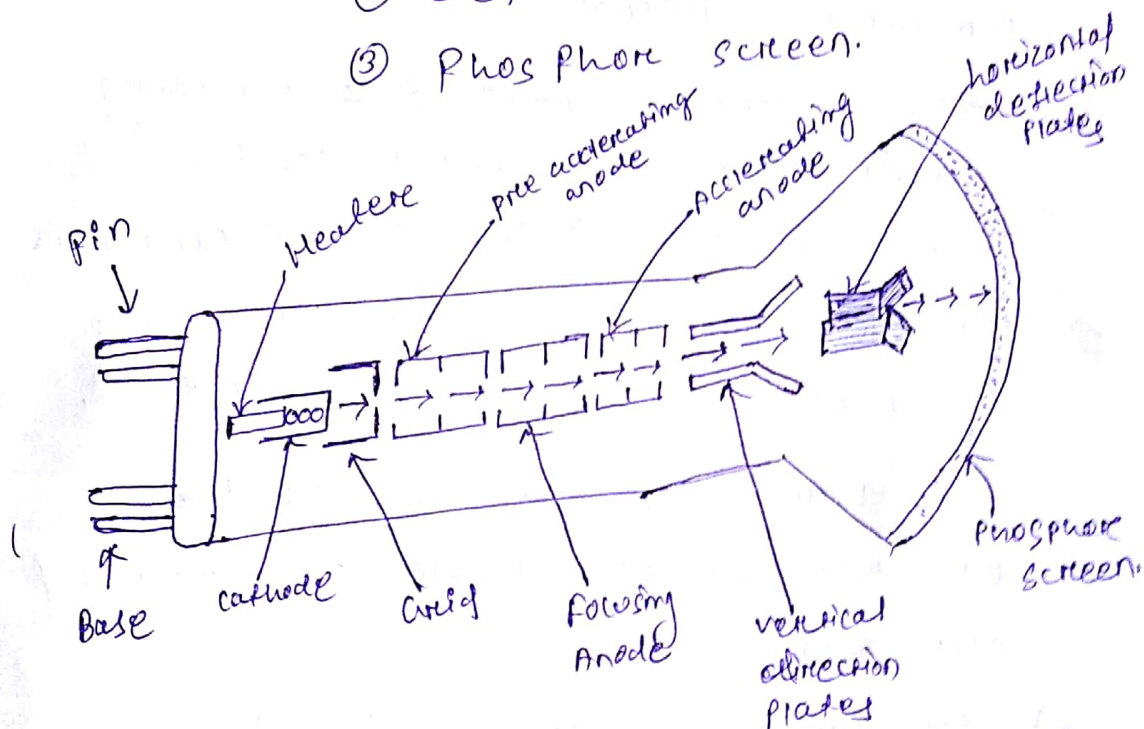

→ Electron gun assembly consists of a heater, cathode, grid, pre-accelerating & accelerating anodes, focusing anode.

- Cathode is indirectly heated <sup>by heater</sup> to emit electrons.
- These electrons then pass through the grid.
- The grid has a centrally located hole (or) aligns with the axis of tube.
- The grid focuses the <sup>emitted</sup> electrons produced by the cathode towards anode.

- The grid's potential is -ve w.r.t cathode.
- Then the emitted electrons pass through the accelerating anodes.

- The preaccelerating anode is a hollow cylindrical shape & its potential is more +ve w.r.t cathode.

- The preaccelerating anode has an electric field to accelerate the electrons to a particular direction.

- The focusing anode & accelerating anode provide particular speed to the electrons & focus the electrons.

- In CRT, two vertical direction plates are used also ~~are~~ known as Y-plates,


- The vertical plates move the electrons either upward or downward direction.

- If upper plate is more '+ve' as compare to lower plate then electron beam moves upper direction & vice-versa.



- CRT consists of another two plates known as horizontal plates also known as X-plates.
- The horizontal plates move the electrons towards right or left side.
- If backward plate is more '+'ve as compared to lower plate then the electron beam moves towards right direction & vice versa.
- At the end a phosphor screen is placed. In this way the electron beams strike on the phosphor screen & produce a picture.
- Phosphor is one type of substance which emits the lights ~~when~~ & produce particular colour. The lights produce on the screen are in dotted form.
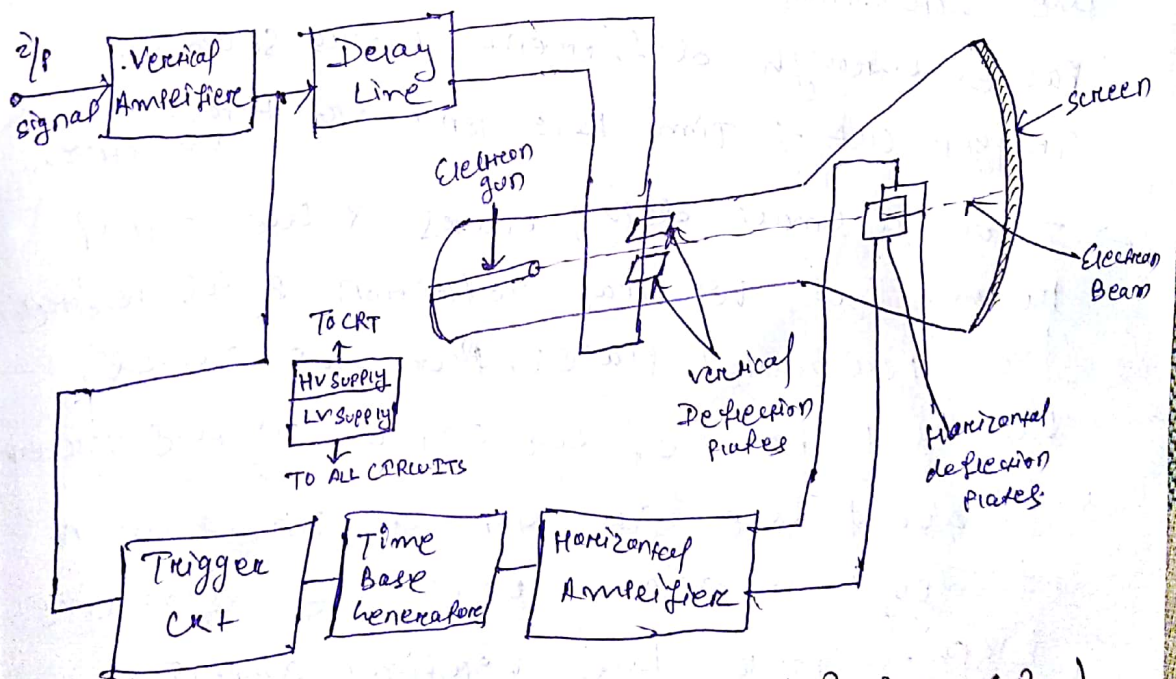
### Principle of Operation of Oscilloscope



[Block diagram of general Purpose CRO]

→ CRO widely used as measuring instrument in college laboratories & also well as in industries.

→ It is made of diff. blocks such as (a) Vertical Amplifier, (b) Delay Line, (c) Trigger ckt, (d) Time Base generator, (e) Horizontal Amplifier, (f) Cathode Ray Tube (CRT) (g) Power supply

(a) Vertical Amplifier :- The amp

→ It is the 1<sup>st</sup> block of CRO. The i/p signal to be displayed on screen of the CRO is applied to the vertical amplifier.

→ This amplifier amplifies the weak signal that they produce measurable deflection on the screen

→ It decides the sensitivity & bandwidth of CRO.  
→ It op is given as i/p to delay line block.

(b) Delay Line :-

→ The i/p signal is applied to the horizontal as well as vertical deflection plates, but before reaching the horizontal deflection plates the signal passes through different blocks such as; Trigger ckt → Time base generator → Horizontal amplifier.

→ Thus a small delay occurs & the signal reaches the vertical deflection plates before the horizontal plates, But this causes the distortion of the signal on the screen.


→ To avoid the situation a small amount of delay is added using the delay line block after the vertical amplifier.



### ③ Trigger ckt

→ This ckt generates trigger pulses, which keeps the synchronization b/w the e/p signal & the horizontal deflection ckt.

### ④ Time Base generator

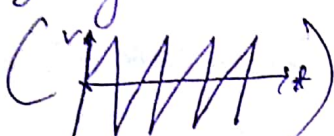→ It generates sawtooth waveforms &  & applies it b/w the horizontal deflection plates.

→ As the sawtooth wave varies linearly with time the movement of the spot on the screen takes place at a constant velocity, hence x-axis of the CRO is calibrated in terms of time & e/p can be displayed w.r.t time.

### ⑤ Horizontal Amplifier

→ The ~~sawtooth~~ strength of sawtooth signal is available at the o/p of a Time based generator is not sufficient, thus before applying it to horizontal plates the signal is amplified using a horizontal amplifier.

### ⑥ Power Supply

→ The power supply section of CRO generates two levels of DC voltage.

→ Low voltage ~~used~~ used for warming of electronic circuits & high voltage used as Anode for CRT

→ The high voltage generated is of the order of 1000 to 1500 volts.

## Measurement of voltage, current & frequency by oscilloscope

### (1) Voltage measurement

- The oscilloscope is mainly voltage oriented device or it's a voltage measuring device.
- The simplest way to measure signal is to set the trigger button to auto lie- oscilloscope start to measure the voltage signal by identifying the zero voltage point or peak voltage by itself.
- As any of these two points identified the oscilloscope triggers & measures the range of the voltage signal.
- vertical & horizontal controls are adjusted so that the displayed image of the sine wave is clear & stable.
- Now ~~the~~ voltage can be measured along the center vertical line which has the smallest divisions.
- Reading of the voltage signal is ~~will~~ be given by vertical control.



## ② Current Measurement

→ Electrical current can't be measured directly by an oscilloscope. However it could be measured indirectly ~~with a scope~~ by attaching probes or resistors.

→ Resistor measures the voltage across the points & then substituting the value of voltage & resistance in ohm's law & calculates the value of electric current.

→ To measure current first attach a probe with the resistor to an electrical circuit.

→ Make sure that resistor's power rating ~~now~~ should be equal or greater than the power o/p of the system.

→ Now take the value of resistance & plug into ohm's law to calculate the current.

→ Acc<sup>n</sup> to ohm's law

$$\text{Current (I)} = \frac{\text{Voltage (V)}}{\text{Resistance (R)}}$$

### ③ Method to measure frequency

→ Frequency can be measured on an oscilloscope by investigating the frequency spectrum of a signal on the screen & making small calculation.

→ The maximum frequency of an ~~oscilloscope~~ oscilloscope can measure may vary but it always in the 100's of MHz range.

→ To check the performance of response of signals in a circuit, oscilloscope measures the rise & fall of the wave.



## TRANSducers:

In general form, Transducer may be defined as a device, which converts energy from one form to another.

However according to electrical instrumentation, transducer may be defined as a "device which converts a physical quantity or a physical condition into an electrical signal".

### Advantages of electrical transducer:-

- (1) Electrical amplification and attenuation can be done easily.
- (2) The mass-inertia effects are minimized. In fact, when dealing with electrical or electronic signals, the inertia effects are due to electrons which have negligible mass.
- (3) The effect of friction is minimized.
- (4) The electrical and electronic system can be controlled with a very small power level.
- (5) The electrical output can be easily used.
- (6) It can be used in telemetry. In short, Telemetry is used in almost all sophisticated measurement systems.



## TRANSducers:

In general form, Transducer may be defined as a device, which converts energy from one form to another.

However according to electrical instrumentation, transducer may be defined as a "device which converts a physical quantity or a physical condition into an electrical signal".

### Advantages of electrical transducer:-

- (1) Electrical amplification and attenuation can be done easily.
- (2) The mass-inertia effects are minimized. In fact, when dealing with electrical or electronic signals, the inertia effects are due to electrons which have negligible mass.
- (3) The effect of friction are minimized.
- (4) The electrical and electronic system can be controlled with a very small power level.
- (5) The electrical output can be easily used.
- (6) It can be used in telemetry. In short Telemetry is used in almost all sophisticated measurement systems.



The entire aerospace research and development is based upon telemetry and remote control.

(vii).

In short, it can be said that the transforming a physical phenomenon into electrical form can be easily used, transmitted and processed for the purpose of measurement.

The transducer consist of two important part: These two part are:-

(1) Sensing element.

(2) Transduction element.

(1) Sensing element or Detector element:

A detector or a sensing element is that part of a transducer, which respond to a physical phenomenon or a change in physical phenomenon.

(2) Transduction element:

A transduction element transform the output of a sensing element to an electrical output.




## Classification of transducers:

- (b) The transducer can be classified as
- (1) on the basis of transduction from used,
  - (2) as primary and secondary transducers,
  - (3) as positive and active transducer,
  - (4) as analog and digital transducer,
  - (5) as transducers and Inverse transducers.

- (1) on the basis of principle of transduction
- transducers may be
- (1) Resistive transducer
  - (2) Inductive transducer
  - (3) Capacitive transducer

Depending upon how they convert the i/p quality into resistance, inductance and capacitance they can be classified as piezoelectric, thermoelectric, magneto-resistive, electro-kinetic and optical.
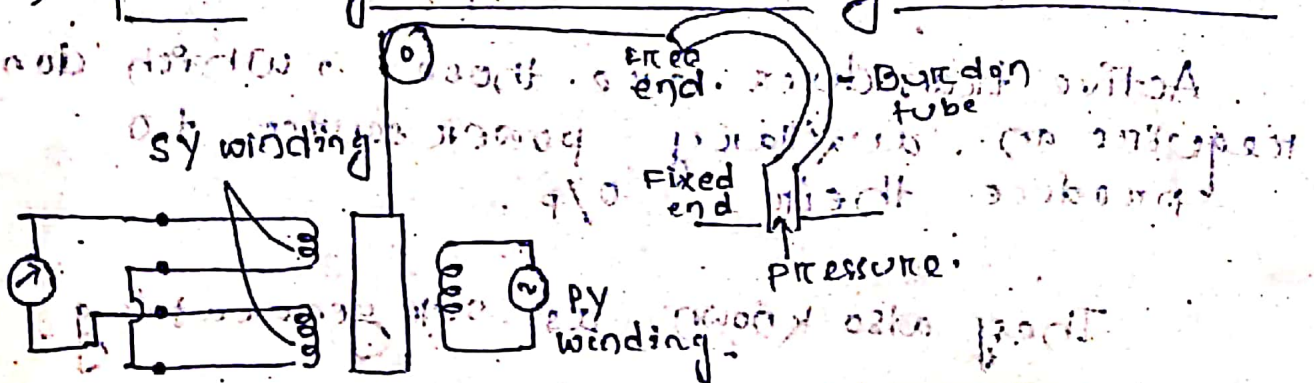
### (2) primary and secondary transducer:





The ~~bored~~ Bourdon tube acting as a sensor senses the pressure and converts the pressure into a displacement of its free end. Then the displacement of the free end moves the core of a linear differential transformer (LVDT), which produces an  $o/p$ .

Thus there are 2 stages of induction, the  $P$  is converted into displacement by Bourdon tube. then the displacement is converted into an analogous voltage by LVDT. The Bourdon tube is called primary transducer, while the LVDT is called a secondary transducer.

### (3) passive and active transducers:

Passive transducers derive the power required for transduction from an auxiliary power source.

They also known as externally powered transducers.

ex:- resistive transducer, inductive transducer, and capacitive transducer.

Active transducer are those, which don't require an auxiliary power source to produce their  $o/p$ .

They also known as self generating type transducer.

ex:- Accelerometer is a transducer



accelerometer transducers converts acceleration into electrical 'v'. does n't need any auxillary power source to convert a physical phenomenon into electrical, o/p.

#### [4] Analog and digital transducer:

The transducers can be classified on the basis of the o/p which may be a continuous function of time or the output may be discrete type steps.

##### 1. Analog transducer

These transducers convert the i/p quantity into an analog o/p which is a continuous function of time.

ex:- A strain gauge, LVDT, thermocouple, are analog transducer.

##### 2. Digital transducer:

These transducers convert the i/p quantity into an electrical o/p which is in the form of pulses. Coded digital signals and its output is represented by 0 and 1.  
example: digital tachometer.

#### [5] Transducer and Inverse transducer:

##### Transducer:

(i) A transducer can be defined as a device which converts a non electrical quantity into an electrical quantity.



## 2. Inverse transducer:

A inverse transducer is defined as a device, which converts a electrical quantity into a non-electrical quantity.

ex:- A 'I' carrying coil moving in a magnetic field is a inverse transducer, because 'I' carried by it is converted into a force, which cause rotational displacement.

## Resistive transducer:

### Thermistors:

Thermistor is a type of resistor whose resistance is dependent on temperature.

Thermistor is a contraction of a term thermal resistor. (short form)

Thermistor is generally composed of semi-conductor material.

Although +ve temp. coefficient of unit are available, most of the thermistor have -ve temp. coefficient. i.e. resistance decreases with increase in temperature.

— Thermistor is high sensitivity to temperature change.

Thermistor is widely used in the applications which involves measurement in the range of  $-60^{\circ}\text{C}$  to  $15^{\circ}\text{C}$ .

Resistance of thermistor ranges from  $\infty$  to  $0.75\Omega$ .




- Thermistor is highly sensitive device.
- Thermistor exhibits a highly non linear characteristics of resistance vs temp.

### Construction:

Thermistors are composed of mixture of metallic oxides such as manganese, nickel, cobalt, copper, iron and uranium.

They are available in variety of shapes and sizes.

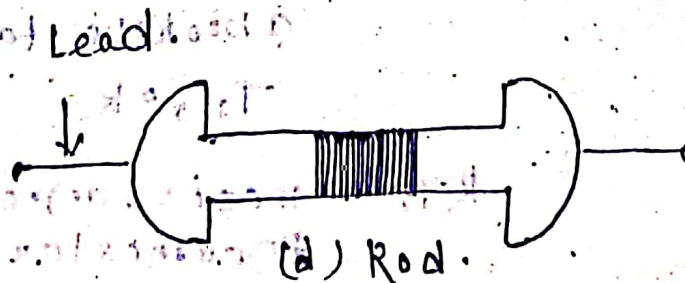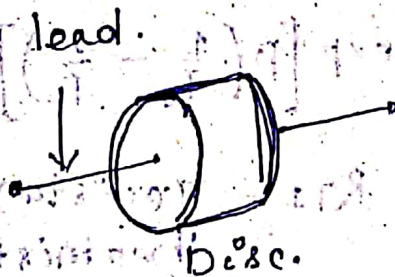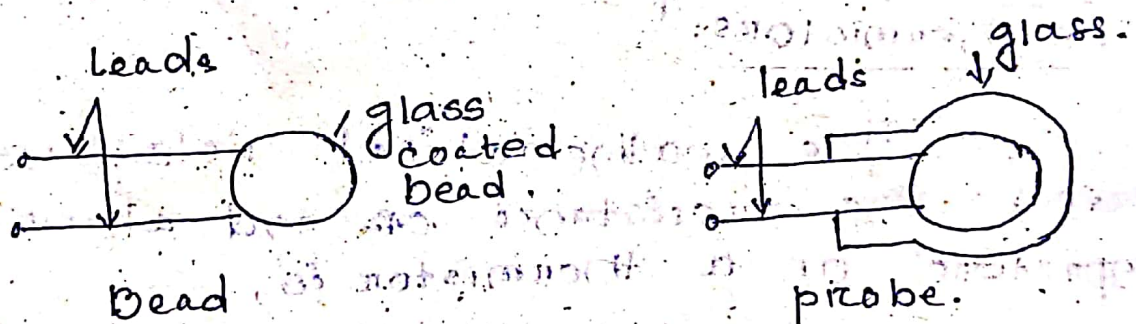- Thermistors may be in the form of beads, rods and discs.





A thermistor in the form of a bead is smallest in size and bead may have a diameter of 0.015 mm to 0.1.25 mm.

- Beads may be sealed in the tips of solid glass rods to form probes which may be easier to mount than the beads. glass probe have a diameter of about 2.5 mm and length varies from 5 mm - 50 mm.

- Disc are made by pressing material under high pressure into cylindrical flat shape under high pressure with diameter from 2.5 mm - 25 mm.

### Resistance-temperature characteristics of thermistors:

The mathematical relationship between the resistance of and absolute temperature of a thermistor is,


is the temp. of an object of scale where 0 is taken as absolute.

$$R_{T_1} = R_{T_2} \exp \left[ \beta \left( \frac{1}{T_1} - \frac{1}{T_2} \right) \right]$$

Where,  $R_{T_1}$  - resistance of the thermistor at absolute temperature  $T_1, ^\circ K$ .

$R_{T_2}$  - resistance of the thermistor at absolute temperature  $T_2, ^\circ K$ .

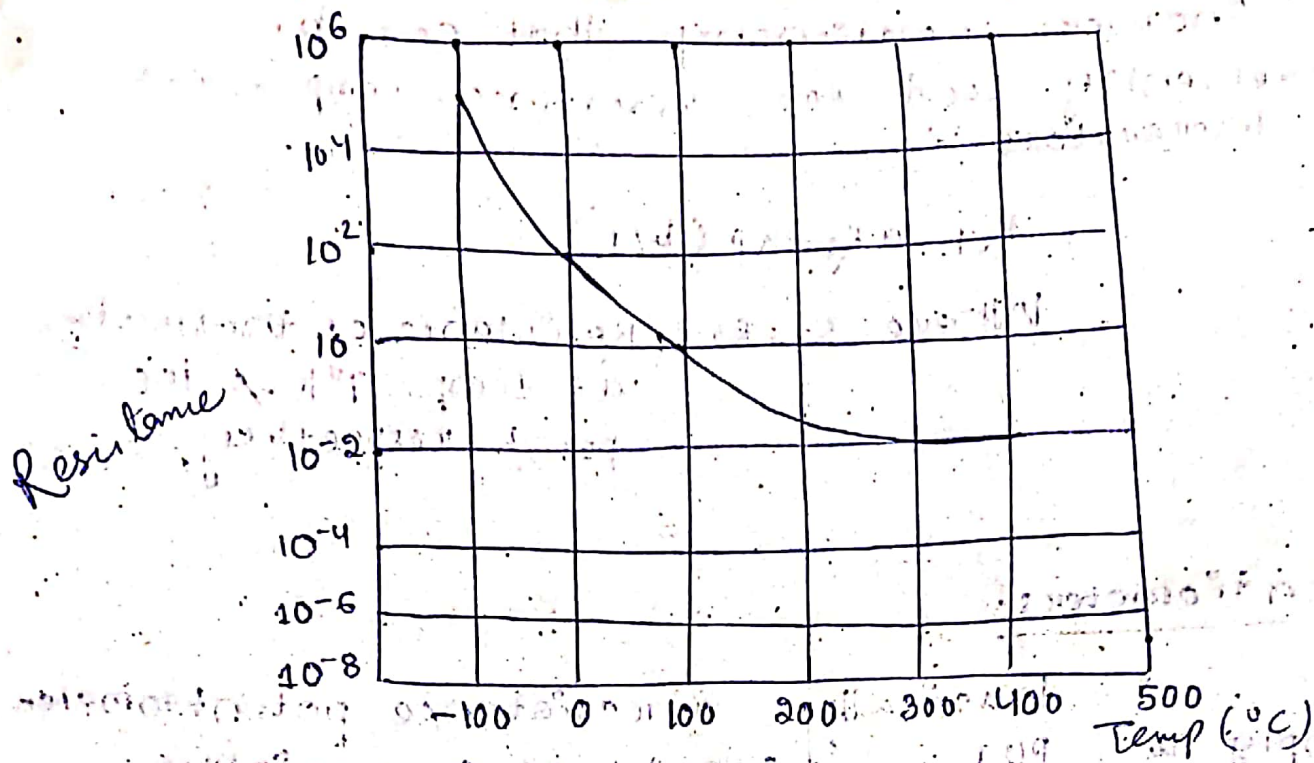$\beta$  - a constant depending upon the material of thermistor, typically.



Resistance temperature characteristics of a typical thermistor.

Figure 1 shows that, a thermistor has a very high negative temperature co-efficient of resistance.

The characteristic resistance temperature of a thermistor is not non linear but a linear approximation of the temp. resistance-temp. curve can be obtained over a small range of temp.

Thus for a limited range of temperature, the resistance of a thermistor varies as,

$$R_\theta = R_{\theta_0} [1 + \alpha_{\theta_0} \Delta \theta]$$

A thermistor exhibits a -ve resistance temp. co-efficient which is typically about 0.05%/°C.



er relationship that can be  
y used for resistance-temp. curve  
stone's,

$$R_T = a R_0 \exp(b/T)$$

Where  $R_T, R_0$  = Resistance of thermistor  
at temp.  $T^\circ K$  & ice  
point respectively.

## Platinum resistance thermometer:

The resistance of a conductor changes when its temperature changed. This property is utilized for the measurement of temperature.

The variation of resistance  $R$  with temperature  $T$  (ok) can be represented by following relationship for most of the metals as,

$$R = R_0 (1 + \alpha_1 T + \alpha_2 T^2 + \dots + \alpha_n T^n + \dots)$$

Where,  $R_0$  = resistance at temp.  $\theta T = 0$   
and  $\alpha_1, \alpha_2, \alpha_3, \dots, \alpha_n$  are constants.

Platinum is especially suited for this purpose, as it can withstand high temperature.

Resistance thermometers are also called resistance temperature detectors (RTDs).

The requirements of conductor material to be used in RTD are:

- (i) The change in resistance of material per unit change in temperature should be as large as possible.
- (ii) The material should have high value of resistivity so that minimum volume of material is used for the construction of RTD.
- (iii) The resistance of material should have a stable relationship with temp.




- Gold and silver rarely used for construction of RTDs on account of their low resistivities.
- Tungsten has relatively high resistivity, but it is reserved for high temperature. & it is difficult to work.
- Copper is used occasionally as RTD element.

The most common RTDs are made of either platinum, nickel or nickel alloys. Nickel wires are used over a limited temperature range.

The common values of resistance for a platinum RTD range from  $10\ \Omega$  to several thousand  $\Omega$ .

The single most common value is  $100\ \Omega$  at  $0^\circ\text{C}$  with a resistance temp. coefficient of  $0.00385/^\circ\text{C}$ .

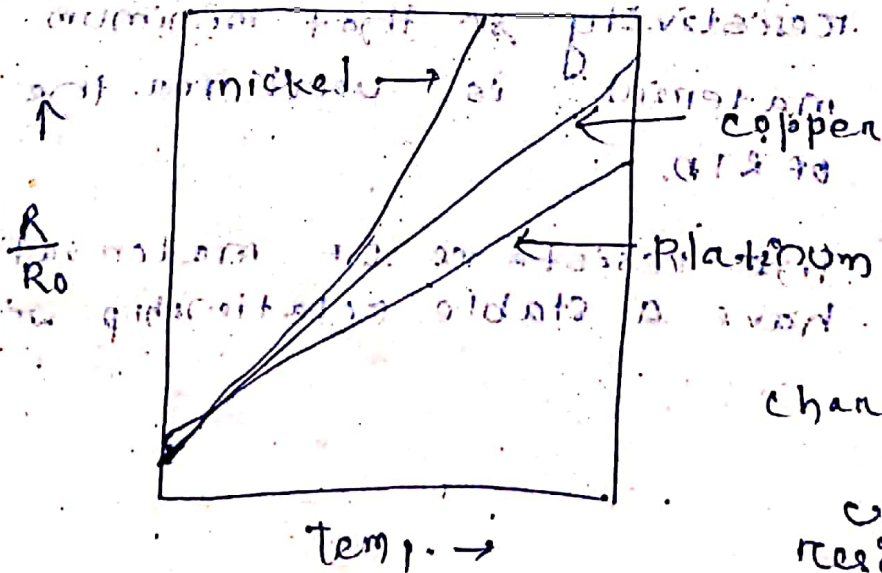The more chemically pure platinum wire has a resistance temp. coefficient of  $0.00392/^\circ\text{C}$ .



Characteristics of material used for resistance thermometer





## Constructional Features of bonded strain gauge:

1. It consists of a grid of fine resistance wire of about  $0.025 \text{ mm}$  in diameter or less.
  2. The grid is cemented to carrier (base) which may be a thin sheet of paper.
  3. The wire is covered with a thin sheet of material in order to protect from mechanical damage.
  4. The spreading of the wires permits a uniform distribution of stress.
  5. The carrier is bonded with an adhesive material structure, so that it permits a good transfer of strain from carrier to wires.
- For excellent results, the bonded strain gauge should have following properties:

- (i) It should have high value of gauge factor. ( $G_f$ )
- (ii) The resistance of strain gauge should have as high as possible.  
(since this minimizes the effects of undesirable variations of resistance in the measurement) Ckt.
- (iii) The strain gauge should have a low resistance temp. co-efficient.  
(This is essential to minimize error on account of temp. variation, which effect the accuracy of measurement)

## 15 UNBONDED STRAIN GAUGE

An unbonded strain gauge is consist of a wire stretched between 2 points in an insulating medium such as air.

The diameter of the wire is about 25  $\mu\text{m}$  and can be strained depending on the w

The wire may be made of various copper, nickel, chrome nickel or nickel iron alloys.

They are about 0.003 mm in diameter, have a gauge factor of 2-4 and sustain a force 2 mN. The length of the wire is 25 mm or less.

The spring element is connected via a rod to diaphragm, the spring which is used for pressure measurement.

\* The unbonded metal wire gauges, used almost exclusively in transducers application, employ preloaded resistance wires connected in a wheatstone bridge, \*

( At initial, the strain & resistance of 4 arms are normally equal, ) with the result the o/p 'v' of the bridge,  $e_0 = 0$ .



As when 'p' is applied, there is a small displacement which is about 0.004 mm, the displacement increases tension in 2 wires and decreases it in the other 2.



16

thereby increasing the resistance in 2 wires which are in tension and decreasing the resistance in the other two.

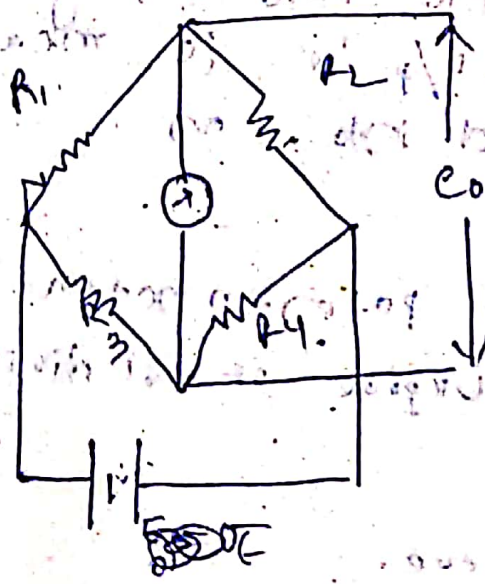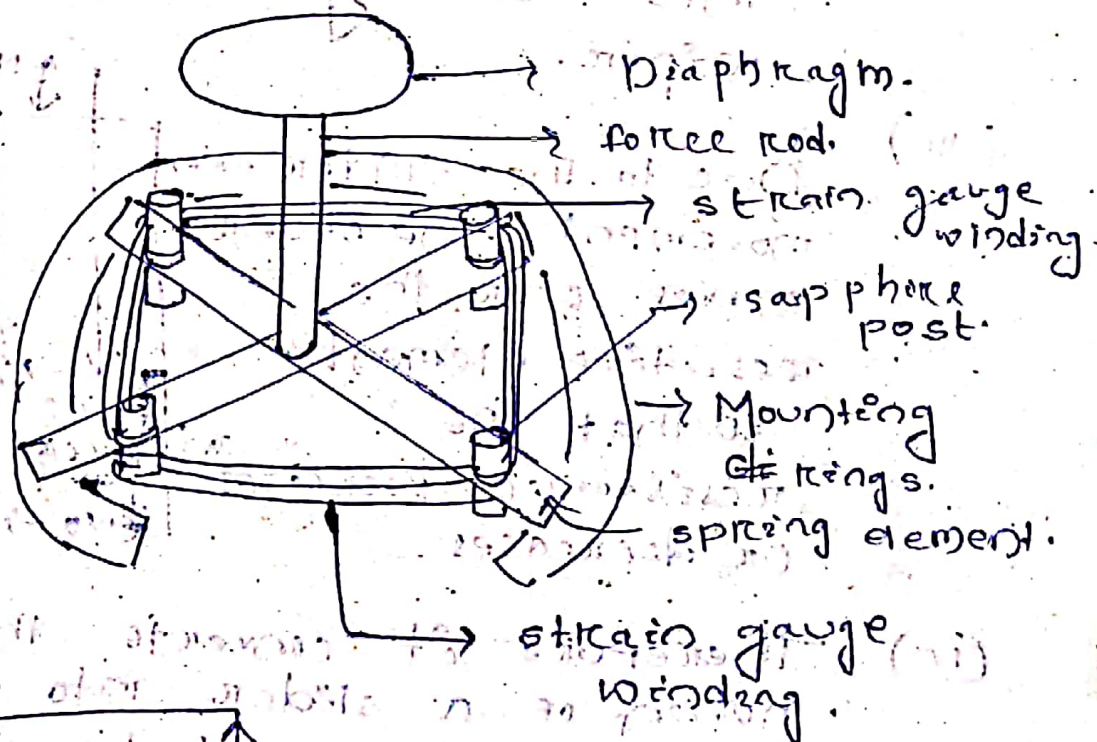This causes an unbalance of the bridge producing an o/p 'v'.




## 17 Potentiometers: (POT)

(i) It is a passive transducer, so it requires an external power source for its operation.

(ii) POT consists of a resistive element provided with sliding contact. This sliding contact is called a wiper.

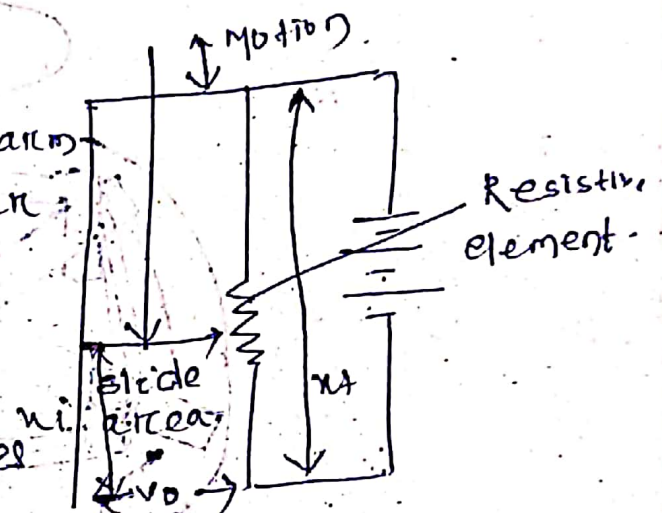(iii) Due to the slider arm movement, the slider moves over the resistive element so that the resistance increases or decreases.



(iv) Therefore it converts the linear motion of a slider into changes in resistance, and the o/p  $V_o$  is measured directly or fed into an amplifier.

(v) Thus, a resistance potentiometer is used for the purpose of  $V_i$  division.

### Advantages:-

- (1) They are inexpensive.
- (2) Simple to operate.
- (3) very useful for measurement of large amplitude.
- (4) electrical efficiency is very high.



## Disadvantages:

- (1) They require a large force to move their sliding contacts.
- (2) sliding contact may be contaminated, can wear out, & generate noise.

Let,


$e_i$  = input voltage

$e_o$  = o/p voltage

$x_t$  = Total displacement of translator pot

$x_i$  = Displacement of wiper from its zero position.

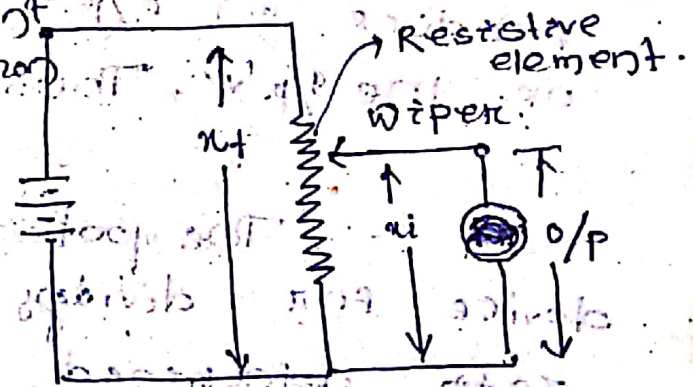$R_p$  = total resistance of potentiometer.



The o/p ( $v$ ) under

$$e_o = \left( \frac{\text{Resistance at o/p terminals}}{\text{Resistance at i/p terminals}} \right) \times e_i$$

$$= \left[ \frac{R_p \left( \frac{x_i}{x_t} \right)}{R_p} \right] \times e_i$$

$$= \frac{x_i}{x_t} \times e_i$$

19 Thus o/p 'v' varies linearly with displacement.

Let  $\theta_i = \text{i/p angular displacement in degree}$

$\theta_t = \text{total travel of wiper in degree}$

$$\text{o/p } v = e_o = e_i (\theta_i / \theta_t)$$

Thus the ckt are called potentiometer dividers since they produce an o/p 'v' which is a fraction of the i/p 'v'. Thus 'i/p' 'v' is divided.

The potential divider is a device for dividing the potential in a ratio determined by the position of sliding contact.



→ The linear variable differential transformer is an inductive transducer.

→ The "LVDT" use to measure linear motion into an electrical signal.

→ construction

→ It consist of one primary winding ( $P_1$ ) and two secondary winding  $S_1$  and  $S_2$ .

→ A ferromagnetic core of cylindrical shape is attached to the transducer sensing shaft.

→ The  $S_1$  winding have equal number of turns and are identically placed on another either side of the  $P_1$  winding.

The  $P_1$  winding is connected to an alternating current source.

→ \* The core is made of high permeability.

→ The magnetic core is free to move inside the coil and motion being measured ~~and each~~ mechanically.

→ The 2 secondary  $S_1$  &  $S_2$  have equal no of turns but they are connected in series opposition to that emfs ( $E_1$  &  $E_2$ ).

→ The primary is energized from a suitable A.C source.

## 2) Working:

When the core is in the centre, the induced voltages  $E_1$  &  $E_2$  are equal and opposite.  $\therefore E_1 = E_2 \Rightarrow V_0 = 0$

- when the external force applied moves the core & when core moved towards the coil  $S_1$ ,  $E_1$  increased but  $E_2$  decreased in magnitude.  $\therefore$

$$V_0 = E_{S1} - E_{S2} \text{ and the net } (V_0)$$

is in phase with  $S_1$

- similarly when the magnetic core moves towards coil  $S_2$ ,  $E_2 > E_1$ .  $V_0 = E_{S2} - E_{S1}$  and is  $180^\circ$  out of phase with  $S_1$

## Conclusion:-


Thus we find that the magnitude of O/P ( $V_0$ ) is a function of the distance moved by the core & its phase indicates in which direction it has moved.

uses:-

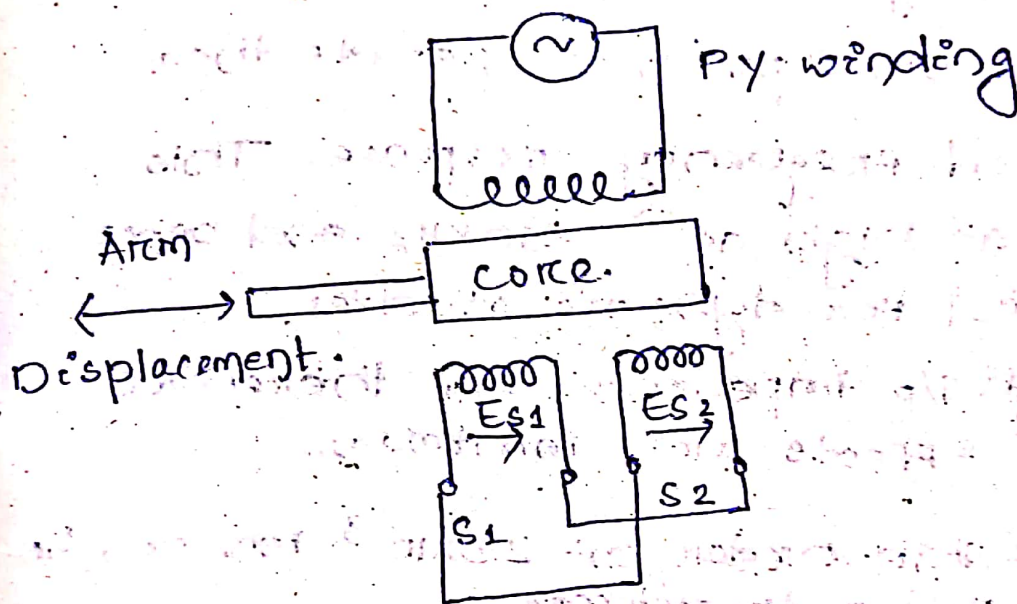1. LVDT can be used in all applications where displacement ranging from  $\frac{1}{1000}$  mm to a fraction of  $\mu$  mm to few cm.
2. Act as a secondary transducer. It can be used as a device to measure force, weight, & pressure etc.



- 22 → force - load cell  
→ fluid pressure - Borden tube  
- use to measurement & control of thickness of a metal sheet.



## 23 Capacitive transducer.

The principle of operation of capacitive transducers is based on the equation

$$C = \frac{A\epsilon}{d}$$

$$C = \epsilon_r \epsilon_0 \frac{A}{d}$$

Where,  $A$  = Overlapping area of plates,  $m^2$   
 $d$  = distance between 2 plates,  $m$

$\epsilon = \epsilon_r \epsilon_0$  = permittivity of medium,  $F/m$ .

$\epsilon_r$  - relative permittivity.

$\epsilon_0$  = Permittivity of free space.  
 $= 8.85 \times 10^{-12} F/m$

The capacitive transducer works on the principle of change of capacitance which may be caused by,

- (1) change in overlapping area  $A$ ,
- (2) change in distance ' $d$ ' between the plates.
- (3). change in dielectric constant.


Transducer using change in Area of plates  
(variable area capacitive transducer)

The principle of operation of capacitive transducer is based on the equation of parallel plate capacitor,

$$C = \frac{A\epsilon}{d}$$



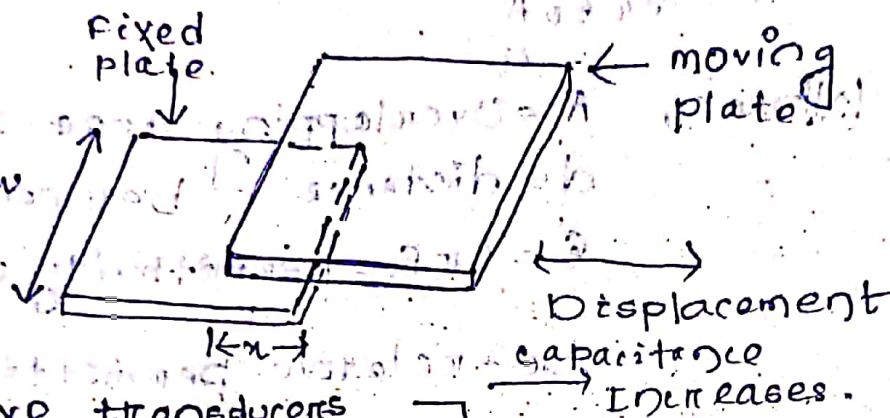Where  $A$  = overlapping area  
 $d$  = distance between 2 plates  
 $\epsilon$  = permittivity.



capacitive transducers working on the principle of change of capacitance with change in Area.

Displacement  
 Capacitance increases.  
 ← decreases

If the moving plate is moved right ward then overlapping area will increase such that capacitance will increase and vice

If the moving plate is moved left towards left, the overlapping area will decrease such that capacitance is decrease.

Transducer using change in distance between 2 plates:


The principle of operation of parallel capacitive transducer based on the equation,

$$C = \frac{A\epsilon}{d}$$

Where,  $A$  = overlapping area between the plate.


$d$  = distance between the plate

$\epsilon$  = dielectric strength.

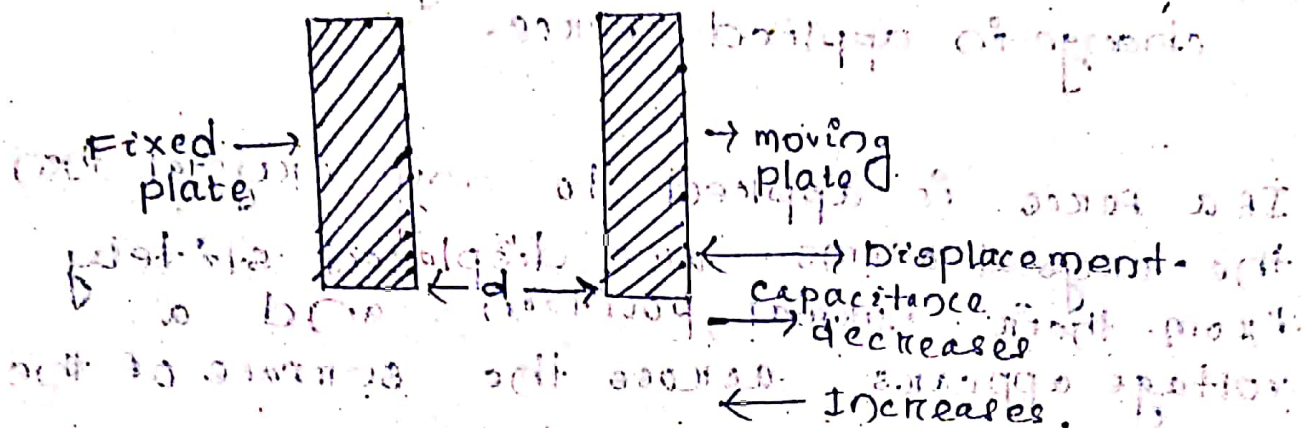

If the moving plate is moves towards to the right direction, distance increases, since distance is inverse proportional to capacitance, so capacitance decreases.

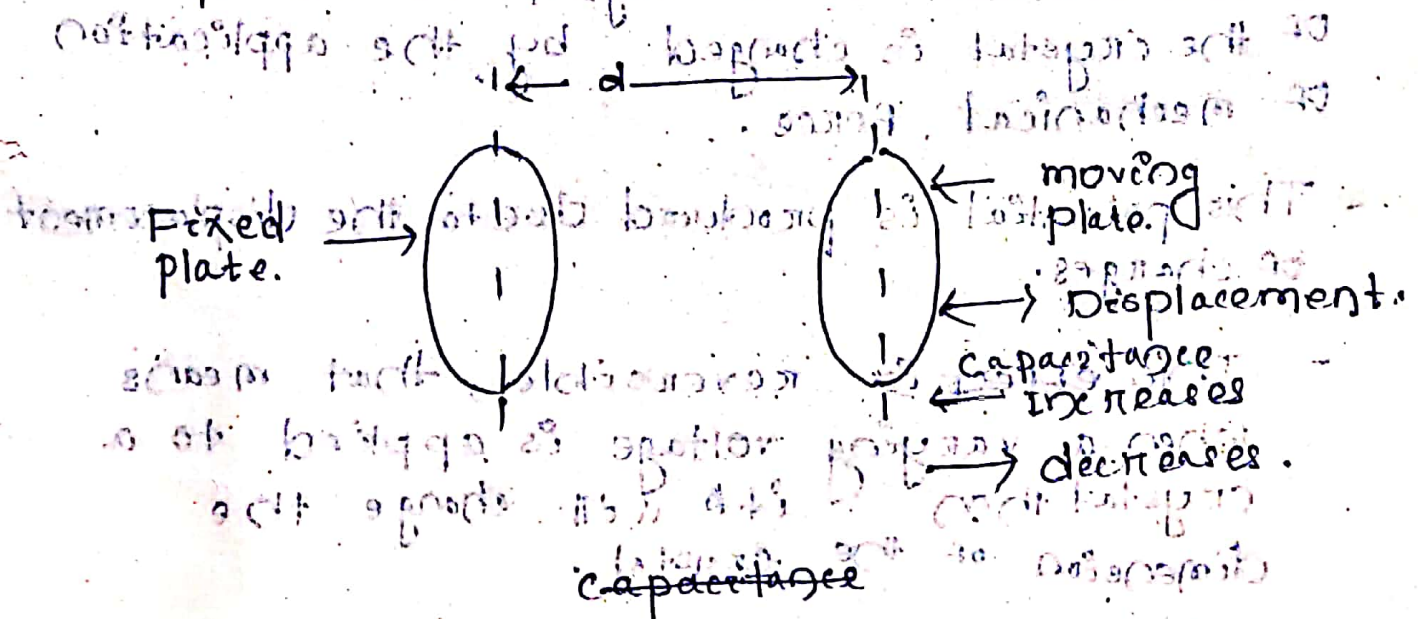If the moving plate is moves towards the left, distance between 2 plate decrease, so capacitance increases.



capacitive transducer using the principle of change of capacitance with change of distance between plates.



## 26 Advantages of Capacitive transducer:-

- (i) They require extremely small force to operate them and hence are very useful for use in small system.
- (ii) They are extremely sensitive.
- (iii) They require small power to operate them.
- (iv) They have good frequency response. This response is as high as 50 kHz and hence they are useful for dynamic studies.
- (v) They have a high  $s/p$  impedance and therefore loading effects are minimum.
- (vi) A resolution of the order of  $2.5 \times 10^{-3}$  mm can be obtained with these transducers.
- (vii) The capacitive transducers can be used for applications where stray magnetic fields render the inductive transducers useless.

## Disadvantages:-

- (i) The metallic parts of the capacitive transducer must be insulated from each other.
- (ii) It shows non-linear behaviour many times.
- (iii) The  $o/p$  impedance of capacitive transducers tends to be high due to small capacitance value.

\* Piezo-electric means change due to applied force.

### Principle:

A piezoelectric material is one in which an electric potential appears across certain surface of a crystal, if the dimension of the crystal is changed by the application of mechanical force.

- This potential is produced due to the displacement of charges.
- This effect is reversible, that means when a varying voltage is applied to a crystal then it will change the dimension of the crystal.

This effect is known as piezoelectric effect.

Example of piezoelectric material are :-

Quartz, Lithium sulphate, dipotassium tetrates, potassium dihydrogen phosphate, Rochelle salt, and ceramics.



## Optoelectronic transducers:

Optoelectronic transducer operates on the principle that it produces an electrical output response to the light input.

### Application:-

~~These are use~~


It is used in.

- (1) satellite use in space research;
- (2) solar batteries as sources of electric power for rocket
- (3) photographic exposure meter.
- (4) for counting packages moving on a conveyor belt.

Lecture notes on  
Generation transmission & Distribution  
4th sem  
Electrical Engg.


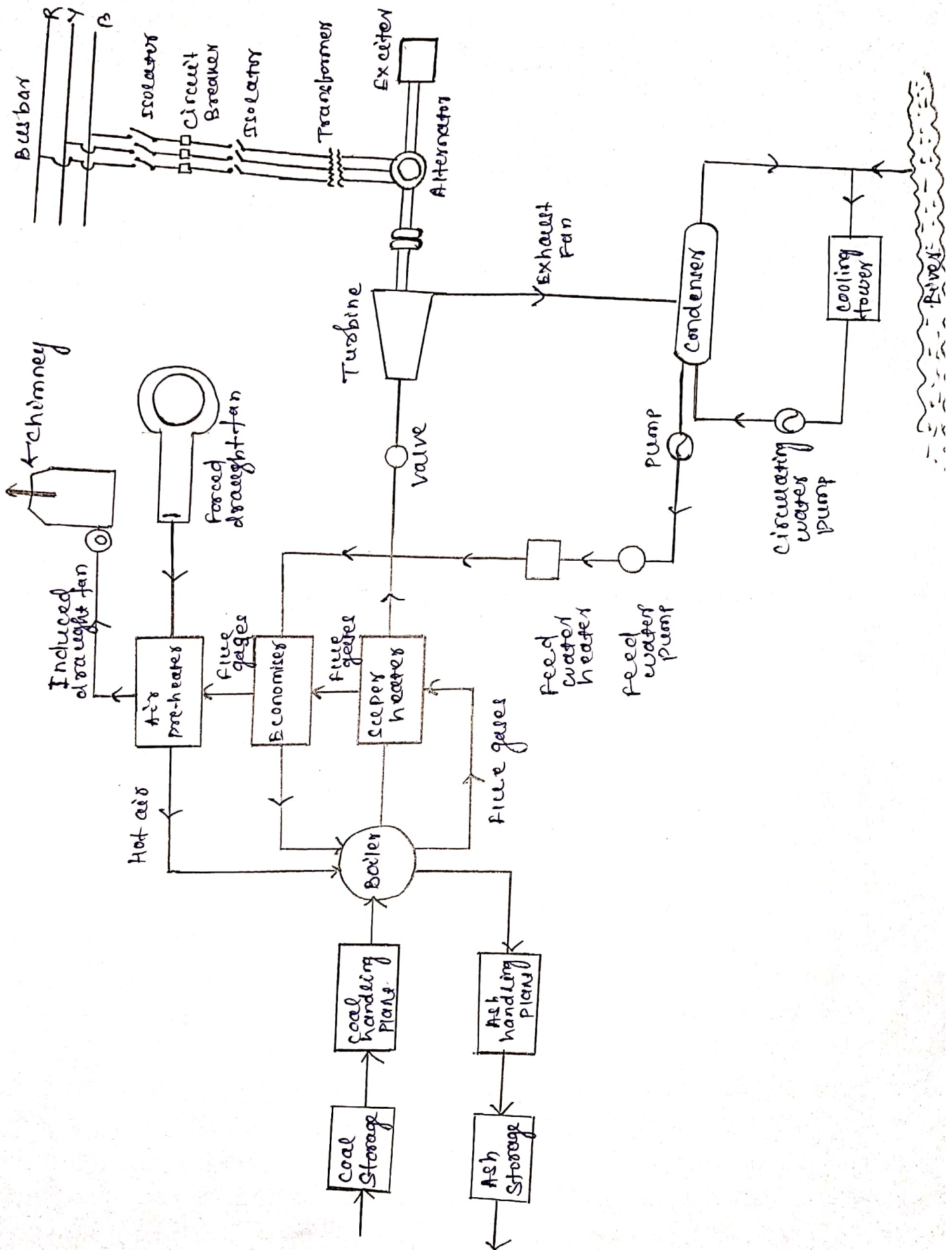
# Steam power station / Thermal power station



# Thermal Power Plant

In thermal power plant, the whole arrangement can be divided into the following stages for the sake of simplicity.

- ① coal and ash handling arrangement
- ② steam generating plant
- ③ steam turbine
- ④ alternator
- ⑤ feed water
- ⑥ cooling arrangement

## ① coal and ash handling arrangement

- The coal is transported to the power station by road or rail and is stored in the coal storage plant.
- From the coal storage plant, coal is delivered to the coal handling plant where it is pulverised. (Crushed into small pieces)
- Then the pulverised coal is fed to the boiler by belt conveyors.
- The coal is burnt in the boiler and the ash produced after the complete combustion of coal is removed to the ash handling plant and then delivered to the ash storage plant for disposal.

## ② steam generating plant

The steam generating plant consist of a boiler for the production of steam.



(a) Boiler! →

The heat of combustion of coal in the boiler is utilised to convert water into steam at high temperature and pressure.

(b) Superheater! →

→ The steam produced in the boiler is wet and is passed through a superheater where it is dried and superheated by the flue gases on their way of chimney.

→ The main function of superheater is to increase the overall efficiency of plant.

→ The superheated steam from the superheater is fed to steam turbine through the main valve.

(c) Economiser! →

The feed water from condenser is fed to the economiser before supplying to the boiler, the economiser extracts a part of heat of flue gases to increase the feed water temperature.

(d) Air-preheater

→ The air preheater extracts heat from flue gases and increases the temperature of air used for coal combustion and overall it increases the efficiency of plant.

(3) Steam turbine

→ The dry and superheated steam from the superheater is fed to the steam turbine through main valve. Heat energy of steam when passing over the blades of turbine is converted into mechanical energy.

→ After giving heat energy to the turbine, the steam is exhausted to the condenser where it is converted into water.

#### ④ Alternator! →

The steam turbine is coupled to an alternator, The alternator convert mechanical energy of turbine into electrical energy. The electrical output from the alternator is delivered to the busbar through T/F, CB and isolator.

#### ⑤ cooling Arrangement! →

Due to scarcity of water in river, hot water from the condenser is passed on to the cooling towers where it is cooled.

#### Advantages


- ① The fuel (coal) is cheaper
- ② Less initial cost as compared to other generating plants.
- ③ It required less space.
- ④ It can be installed at any place irrespective of the existence of coal.

#### Disadvantages

- High maintenance and operating cost.
- Pollution of atmosphere due to fuel (coal)
- A huge quantity of water is required.



# 19 Hydro-electric plant

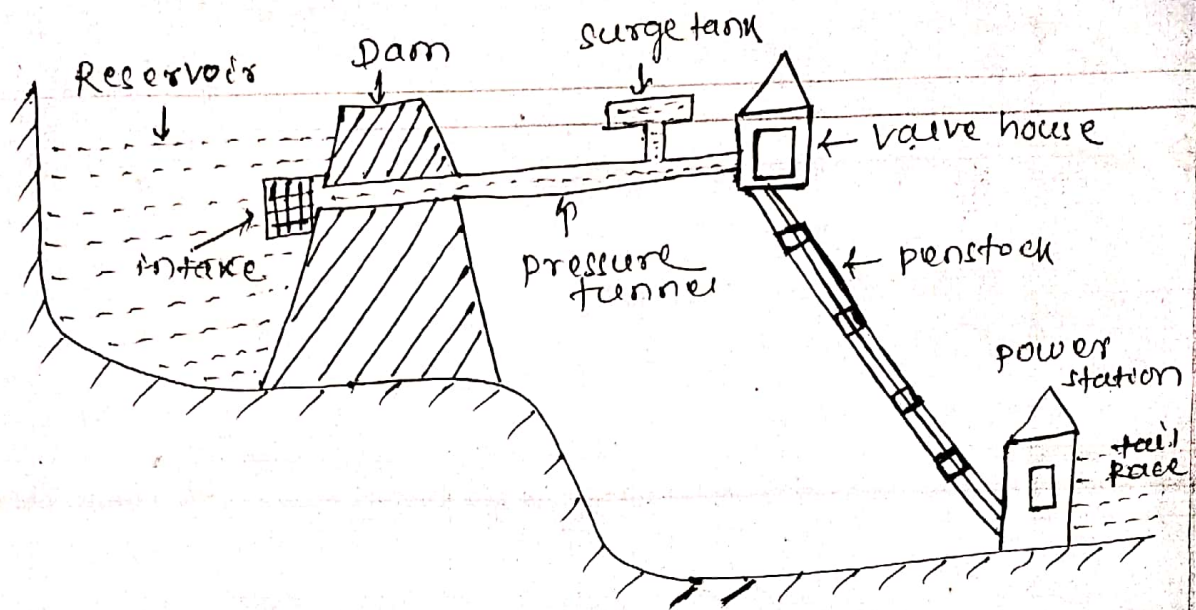

## Elements of hydro-electric power plants

### ① Storage Reservoir : →

→ Its purpose is to store water.

### ② Dam : →

→ The Dam used to raise the water surface of the stream to increase an artificial head.

### ③ penstock : →

→ A penstock is the long pipe that carries the water, flowing from the reservoir towards the power generation unit.

### ④ Intake : →

→ These are the gates built on the inside of the dam to controlled water flow through water tunnel from Reservoir.

### ⑤ Surge tank : →

→ surge tank is used to avoid a hammering effect <sup>water</sup> and to save penstock.



- \* → For hydro-electric power plant, a huge quantity of water is required which is store in Reservoir.
- There is a pressure tunnel which connect reservoir to the valve house, so water from reservoir to valve house passes through pressure tunnel.
- Valve house contain main sluice valve for controlling water flow to the power station.
- A surge tank is provided to avoid water hammering effect on penstock which is placed before valve house.
- Then the water from valve house flow into the power station through penstock.
- in power station turbine coupled with generator
- in power station, water from penstock fall on blade of turbine, where kinetic energy and potential energy of water is converted into the rotational motion of blade.
- Because of rotation of blade, shaft of turbine and also coupled generator rotate which produce Alternating current.

### Advantages : →


- They donot pollute atmosphere.
- The lake's water can be used for irrigation purpose.
- Hydro power project control flood.
- Cheapest in operation and maintenance.

### disadvantages : →

- Dam are extremely expensive to build.
- It depends on rain.
- It requires large area.



# Nuclear power plant

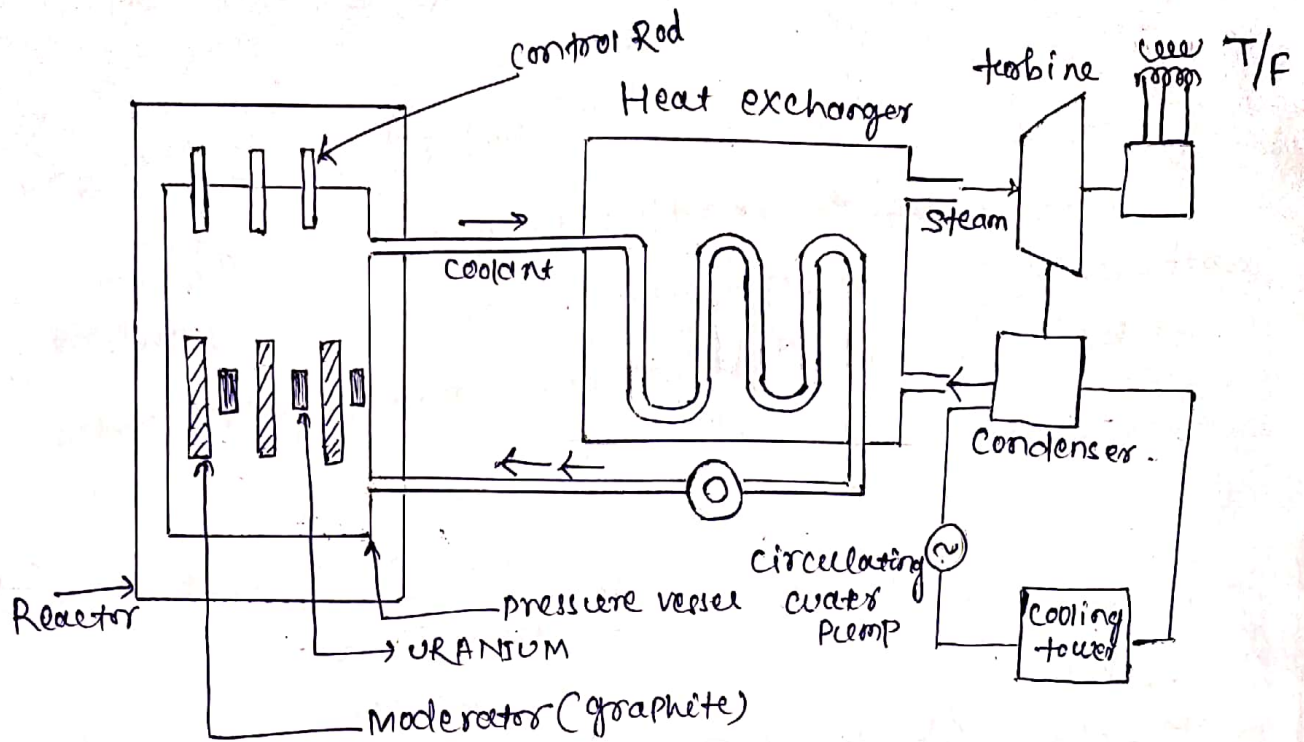

The whole arrangement of Nuclear power plant can be divided into!

- ① Nuclear Reactor
- ② Heat exchanger
- ③ steam turbine
- ④ condenser
- ⑤ Alternator

## Nuclear Reactor

A nuclear reactor is consist of uranium rods (fuel rods), moderators and control rods.

→ In nuclear power plant, reactor used for heat generator. A huge quantity of heat energy is produced by breaking of uranium ( $U_{235}$ ) a result of fission reaction and passes the heat to the heat exchanger through coolant.

→ control rods are made up of cadmium which is a strong neutron absorber and used to regulate the supply of neutron for fission.

### ② Heat exchanger :-

The coolant gives up heat to the heat exchanger which is utilised in raising the steam. After giving up heat, the coolant is again fed to reactor.

### ③ Steam turbine :-

The steam produced in the heat exchanger is supplied to the steam turbine through valve. After doing a useful work in the turbine, the steam is exhausted to condenser.

### ④ Condenser :-

In condenser, steam is converted into water and fed to the heat-exchanger for reuse.

### ⑤ Alternators :-

The steam turbine drives the alternator which converts mechanical energy into electrical energy.

### Advantages :-

- The amount of fuel required is quite small.
- A nuclear power plant requires less space as compare to other power plant.
- It's more reliable, cheaper for running cost.



### Disadvantages

- fuel is expensive and not abundantly available every where.
- It has high capital cost.
- maintenance charge is high
- Nuclear waste disposal may cause a dangerous amount of radio active pollution.

## Ch-2 Transmission of Electric Power

### Electric supply system

→ The conveyance of Electric Power from a power station to consumer's premises is known as Electric supply system.

→ An Electric supply system consist of 3 principal components

① power station → Electric power is produced at the power station which are located at favourable places, generally quite away from the consumers.

② Transmission line → It is then transmitted over large distance to load centres with the help of conductors known as transmission line.


③ Distribution system → Finally, it is distributed to a large no. of small and big consumer's through a distribution network.

The Electric supply system can be classified into

- ① AC or D.C system
- ② overhead or underground system
- ③  $3\phi$ , 3 wire system (generally adopted for generation and transmission purpose)
- ④  $3\phi$ , 4 wire system (adopted for distribution purpose)



# A. C Power supply scheme

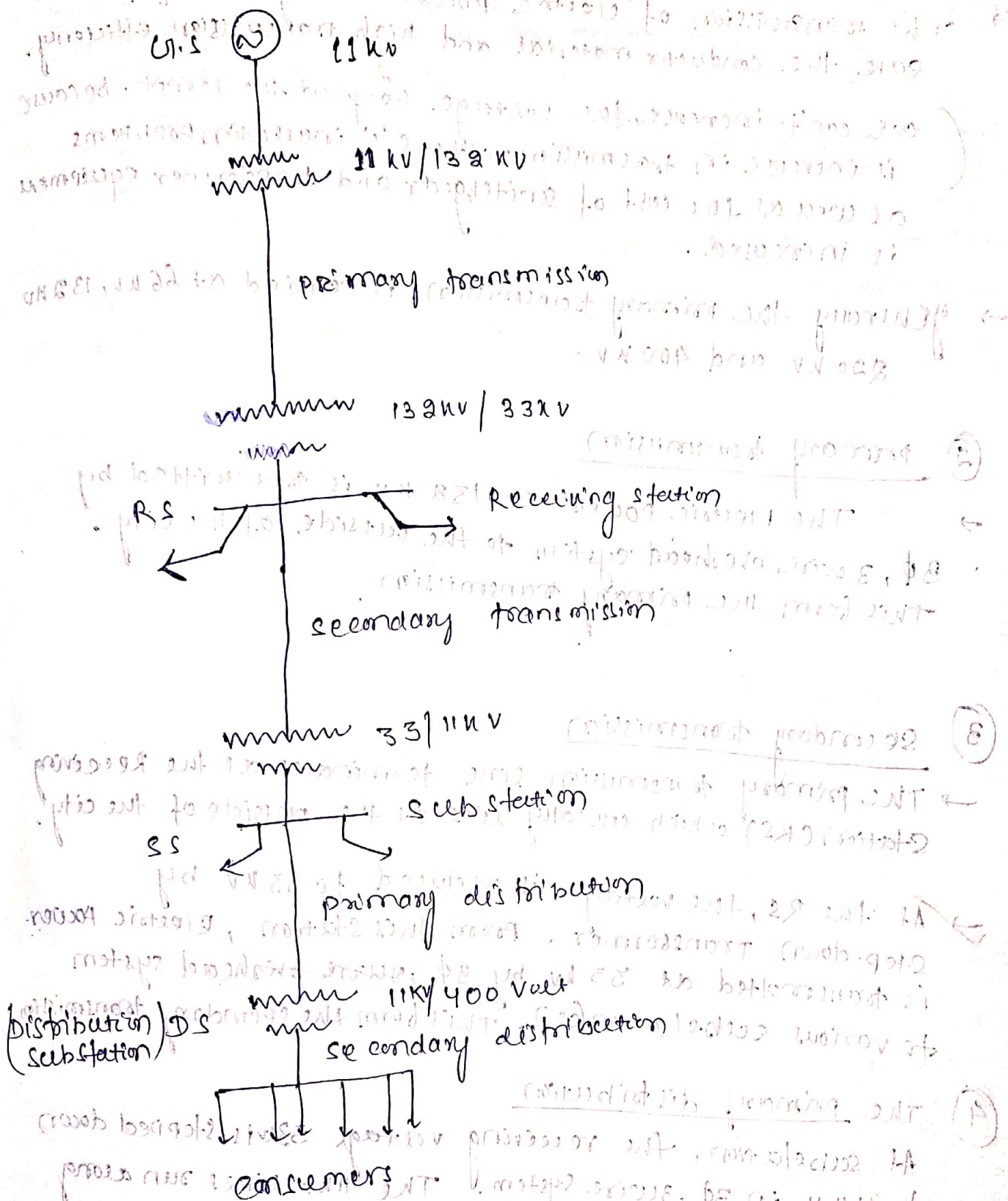

## ① Generating station :-

It represents the generating station where electric power is produced by 3 $\phi$  alternators operating in parallel. The usual generation voltage is 11 kV. This 11 kV is

- stepped up to 132 kV at the generating station with the help of 3- $\phi$  transformers.
- The transmission of electric power at high voltage save the conductor material and high transmission efficiency.  
( we can't increase the voltage beyond the limit, because it increase in transmission voltage's insulation problems as well as the cost of switchgear and transformer equipment is increased.
- generally the primary transmission is carried at 66 kV, 132 kV, 220 kV and 400 kV.

### ② primary transmission

- The Electric Power at 132 kV is transmitted by 3 $\phi$ , 3 wire overhead system to the outside of the city. This form the primary transmission.

### ③ secondary transmission

- The primary transmission line terminates at the Receiving Station (RS) which usually lies at the outside of the city.
- ✓ At the RS, the voltage is reduced to 33 kV by step-down transformer. From this station, electric power is transmitted at 33 kV by 3 $\phi$ , 3 wire overhead system to various substation (S). This form the secondary transmission.

### ④ The primary distribution

At substation, the receiving voltage 33 kV is stepped down to 11 kV in 3 $\phi$ , 3 wire system. The 11 kV lines run along the important road sides of the city. This form the primary distribution.




## ⑤ secondary Distribution

- The 11 kV distribution line is delivered to distribution sub-station (DS), which is located near the consumer's localities and step down the voltage to 400 volt, 3  $\phi$  4 wire for secondary distribution.
- The voltage b/w any two phases is 400 volt and voltage b/w any phase and neutral is 230 volt.
- The single-phase residential lighting load is connected b/w any phase and neutral, whereas 3-phase, 400 volt motor load is connected across 3 phase lines directly.

\* The secondary distribution system consists of service mains.

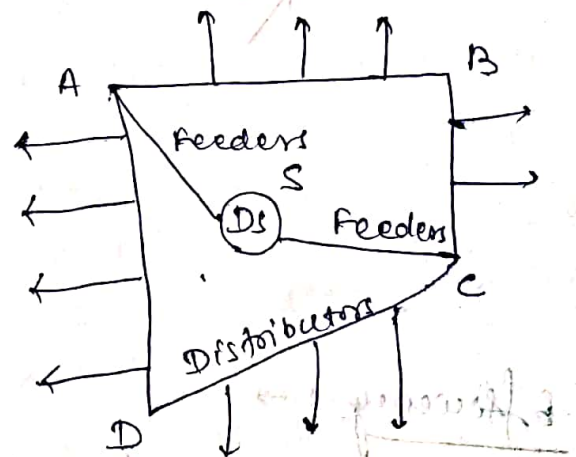- ① Feeders
- ② Distributors
- ③ service mains



## Voltage Regulation

→ It is used to maintain a constant voltage in the transmission line.

→ Voltage Regulation is defined as the difference of <sup>sending</sup> supply voltage to the receiving voltage.

$$\%VR = \frac{V_S - V_R}{V_R} \times 100$$


① saving of conductor material

② high transmission efficiency

where,

$V_S$  = sending voltage

$V_R$  = receiving voltage.

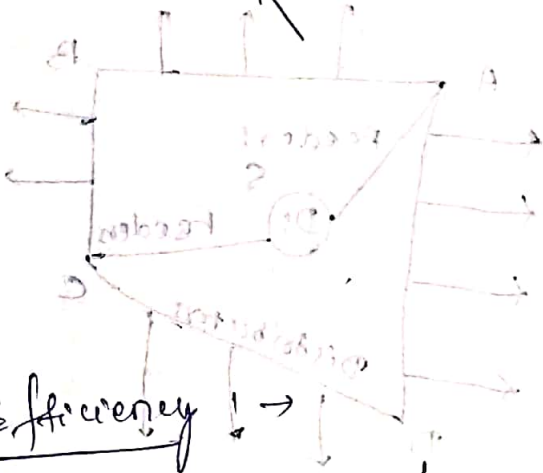

Efficiency →

it is defined as the ratio of the power delivered at the receiving end to the power sent from sending end.

$$\text{power efficiency } (\eta) = \frac{P_R}{P_R + (\text{loss})} = \frac{P_R}{P_R + \alpha(I^2 R)}$$

$$\eta = \frac{\text{o/p}}{\text{i/p}} = \frac{V_R}{V_S} = \frac{P_R}{P_S}$$

$\alpha = 1$  (1 $\phi$ )  
 $\alpha = 3$  (3 $\phi$ )



## Economics of Power Transmission

The following two fundamental economic principles which closely influence the electrical design of a transmission line will be discussed.

① Economic choice of conductor size

② Economic choice of transmission voltage

### ① Economic choice of conductor size (Kelvin's law)

It states that, the most economical area of conductor is that for which the total annual cost of transmission line is minimum.

→ The total annual cost of transmission line can be divided broadly into two parts

(a) Annual charge on capital outlay

(b) Annual cost of energy wasted in the conductor.

#### (a) Annual charge on capital outlay

→ In case of overhead system, it will be the annual interest and depreciation on the capital cost of conductors, supports and insulators and the cost of their erection.

→ So, Annual charge on an overhead transmission line can be expressed as:

$$\text{Annual charge} = P_1 + P_2 a \quad \rightarrow \text{eqn } ①$$

$P_1, P_2 = \text{constant}$ ,  $a = \text{area of x-section of conductor}$ .

(b) Annual cost of energy wasted : →

- The amount of energy lost in a conductor due to  $I^2 R$  loss.
- The energy lost in the conductor is proportional to 'R' and thus 'R' is inversely proportional to the area of x-section of conductor.
- Therefore, the energy lost in the conductor is inversely proportional to area of x-section.

∴ Annual cost of energy wasted in an overhead transmission line can be expressed as,

$$\text{Annual cost of energy wasted} = \frac{P_3}{a} \rightarrow \text{eqn } (2)$$

where  $P_3 = \text{constant}$

$$\text{Total Annual cost } C = \text{eqn } (1) + \text{eqn } (2)$$

$$C = P_1 + P_2 a + \frac{P_3}{a}$$

only  $a = \text{variable}$

Total annual cost of transmission line will be minimum if differentiation of 'C' w.r.t. 'a' is zero

$$\frac{d(C)}{da} = 0$$

$$P \propto R \propto \frac{1}{A}$$

$$\Rightarrow \frac{d\left(P_1 + P_2 a + \frac{P_3}{a}\right)}{da} = 0$$

$$\Rightarrow 0 + P_2 - \frac{P_3}{a^2} = 0$$

$$\Rightarrow P_2 = \frac{P_3}{a^2} \Rightarrow \boxed{P_2 a = \frac{P_3}{a}}$$


Variable part of annual charge = Annual cost of energy wasted.

Kelvin's law can be stated that : →

The most economical area of conductor is that for which the variable part of annual charge is equal to the cost of energy losses per year.


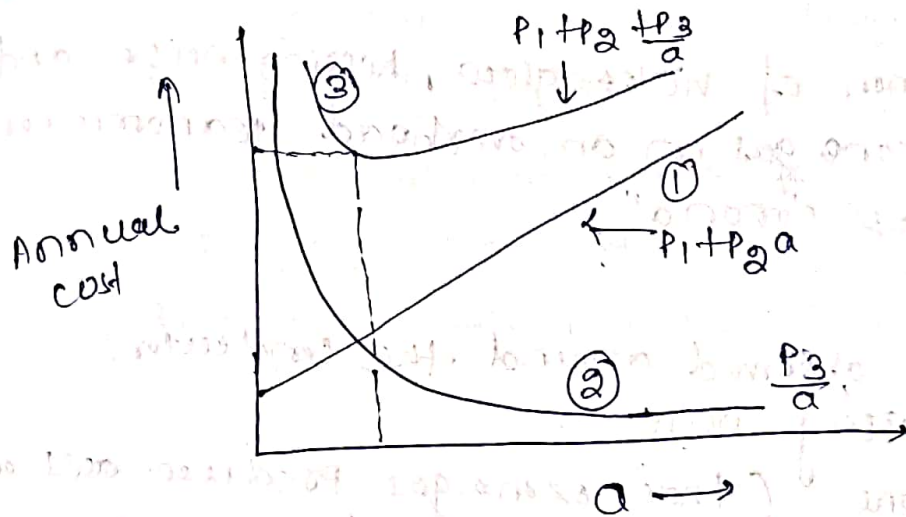
## Graphical illustration of Kelvin's law



- It is the graph b/w annual cost and the area of x-section of conductor.
- The straight line (1) represents the relation b/w annual charge  $(P_1 + P_2 a)$  and the area of x-section of the conductor.
- The graph (2) represents the relation b/w annual cost of energy wasted and area of x-section 'a'.
- The graph (3) represents the relation b/w total annual cost  $(P_1 + P_2 a + \frac{P_3}{a})$  of transmission line and area of x-section 'a'.

## CORONA

"The phenomenon of violet glow, hissing noise and production of ozone gas in an overhead transmission line is known as corona"

- A violet glow is observed around the conductor.
- It produces a hissing noise.
- It produces ozone (that ozone gas produces acid which corrodes the surface of conductor)
- The glow is maximum over rough and dirty surfaces of the conductor.
- It is accompanied by power loss in the form of light, heat, sound and chemical action.  
(If wattmeter is connected in the ckt. then it shows the reading)
- The charging current under corona condition increases because the corona induces harmonics current.

## Factors affecting corona

Since corona occurs due to the ionization of the air surrounding the line conductor, it is affected by the physical state of the atmosphere as well as by the condition of the line. The corona is affected by the following factors.

### ① Atmosphere →

In the stormy weather, the no. of ions is more than normal and as such corona occurs at much less voltage as compared with fair weather.

### ② Conductor size! →

→ The corona is affected by the size (diameter), shape (stranded or smooth) and surface condition (dirty/clean) of the conductor.



- The rough and irregular surface will give rise to more corona because unevenness of the surface decreases the value of breakdown voltage.
- Thus a stranded conductor has irregular surface and hence gives rise to more corona than a solid conductor.
- Corona decreases with increase in diameter of conductor.

### ③ Spacing b/w conductors : →

With the increase in spacing b/w the conductors the electrostatic stresses are reduced and therefore, the corona effect is reduced.

### ④ Line voltage : →

At low voltage, there is no corona effect, but when the line voltage is increased to such a value that electrostatic stresses developed at the conductor surface make the atmospheric air surrounding the conductor conducting, corona effect appears.

## Advantages of corona

- ① Due to corona formation, the air surrounding the conductor becomes conducting and hence virtual diameter of the conductor is increased. The increased diameter reduces the electro-static stresses b/w the conductors.
- ② Corona reduces the effects of transients produced by surges.

## Disadvantages of corona

- ① corona is accompanied by a loss of energy. This affects the transmission efficiency of the line.
- ② ozone is produced by corona and may cause corrosion of the conductors due to chemical action.
- ③ The current drawn by the line due to corona is non-sinusoidal and hence non-sinusoidal voltage drop occurs in the line. This may cause inductive interference with neighbouring communication lines.

## Methods of reducing corona effects

- ① By increasing conductor size! → By increasing the conductor size  $V_{do}$  is increased and corona effect can be reduced. mainly ACSR conductor is used which have a large X-sectional area.
- ② By increasing conductor spacing! → By increasing the spacing b/w conductors, the voltage at which corona occurs is raised and hence corona effects can be eliminated.



⑤ By using bundled conductors also corona effects can be avoided because effective diameter of the bundled conductor is much larger than that of the equivalent single conductor.

## Ch-3 overhead line

### Main components of overhead line

An overhead line may be used to transmit or distribute electric power. In general, the main components of an overhead line are! →

#### (i) conductors! →

Conductors which carry electric power from the sending end station to the receiving end station.

#### (ii) Supports! →

Supports which may be poles or towers and keep the conductors at a suitable level above the ground.

#### (iii) cross-arms and clamps! →

These are used on pole structures to support the insulators and conductors.

#### (iv) Insulators! →

Insulators which are attached to support and insulate the conductors from the ground.


#### (v) Guy's and stays! →

\* Stay wires are galvanised steel wire strands that are used for sustaining mechanical load.  
\* These are used to stay power poles and tower with the help of stay wire.
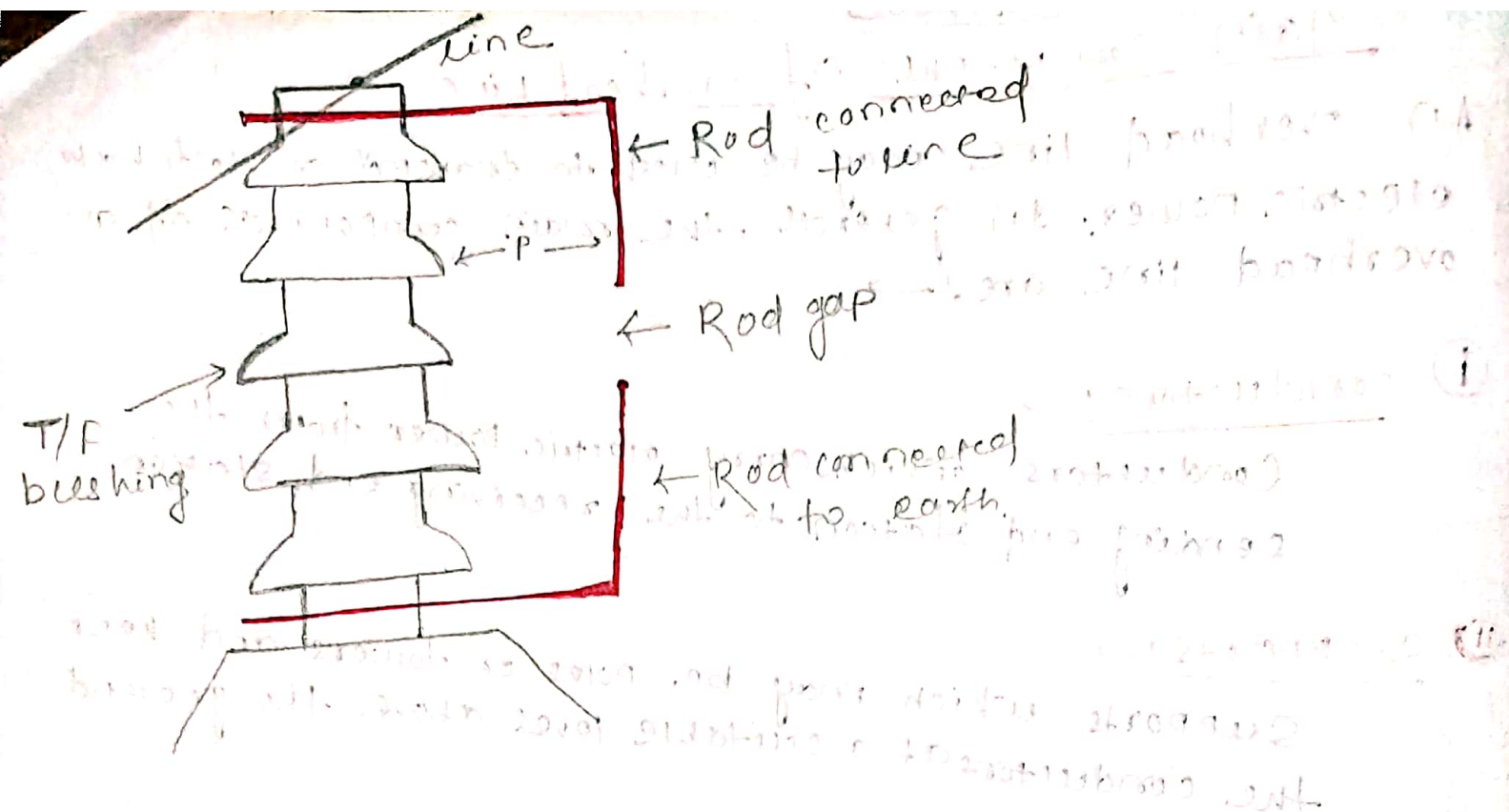
#### (vi) Lightning arrestors! →

A lightning arrester is a device used on electrical power systems and telecommunications system to protect the insulator and conductors from the effects of lightning.





(VII) Earth wire! →  
 Earth wire is run on the top of the towers to protect the line against lightning discharges.

(VIII) Vee-Guards! →  
 V-guards are often provided below bare overhead lines running along or across public streets to make the line safe if it should break.

(IX) Creand wires! →  
 guard wires are provided above or below power lines while crossing telephone or telegraph lines. The guard wires and steel structures are solidly connected to earth.

## ⑧ Miscellaneous items! →

Such as plate phase plates, danger plates, lightning arrestors, anti-climbing wires etc.

## Line supports: →

The line supports should have the following properties

- (i) High mechanical strength to withstand the weight of conductors and wind load etc.
- (ii) Light in weight without the loss of mechanical strength
- (iii) cheap in cost and economical to maintain.
- (iv) Longer life
- (v) Good looking
- (vi) Easy accessibility for erection of line conductor.

## ① wooden poles! →

→ These supports are cheapest, easily available, provide insulating properties and therefore these are widely used for distribution purpose in rural areas.

→ The pole below the ground level is impregnated with preservative compound like creosote oil in order to prevent it from rot.

→ 'A' and 'H' shape poles are used for distribution purpose.

→ Length of wooden pole is 10-12m, span length is upto 50m.

## The main drawbacks of wooden supports! →

- (i) Tendency to rot below the ground level,
- (ii) comparatively smaller life span (20-25 yr.)
- (iii) less mechanical strength
- (iv) Required periodical inspection.
- (v) cannot be used for voltage higher than 33kV.



## ② Steel Poles ! →

- The wooden poles are replaced by steel poles due to its several disadvantages.
- steel poles possess greater mechanical strength, longer life and permit longer spans length (50-80m).
- such poles are generally used for distribution purposes in the cities.
- These type of supports need to be galvanised or painted in order to increase its life. (lifetime is more than 40 yr.)
- steel poles are used for transmission purposes for 11 kV - 33 kV.
- steel poles are 3 types
  - (i) Rail poles
  - (ii) Tubular poles
  - (iii) Rolled steel joints

### ③ RCC poles! → (Reinforced cement concrete)

- It is used in distribution line upto 33 kV.
- RCC poles give good appearance, require no maintenance, have good insulating properties and resistance against chemical action, very strong, have longer life and can be used for longer span (80-200 m).
- These pole may be manufactured at site itself to avoid heavy cost of transportation.  
(RCC poles are very bulky and heavy)  
(It need care in handling and erection)



#### ④ Steel tower : → (Lattice steel tower)

wooden pole  
steel pole  
RCC pole

→ Used for distribution line

steel tower} → It is used for Transmission line.

→ steel towers have greater mechanical strength, longer life, can withstand most severe climate condition and permit the use of longer span lengths (300m or more)

→ Narrow-base, lattice steel towers are used for transmission at 11 kV to 33 kV and broad-base, lattice steel towers are used for transmission purposes at 66 kV and above.

## Types of Conductor Materials! →

The conductor material used for transmission and distribution of electric power must have the following characteristics! →

- (i) High electric conductivity.
- (ii) High tensile strength in order to withstand mechanical stress.
- (iii) Low cost so that it can be used for long distance.
- (iv) Easy availability.
- (v) should not be brittle.
- (vi) Low specific gravity in order to give low weight per unit volume.



## ② Aluminium! —

- Aluminium is cheaper in cost and lighter in weight and easily available.
- It has smaller conductivity and tensile strength.
  - \* (Conductivity of Al. is 60% of co.)
  - \* (Tensile strength of Al is 45% to that of co.)
- \* Specific gravity of Al. is 2.71 gm/cc, is lower than that of co. (8.9 gm/cc), therefore, Al weight is lower than co.
- \* The Al. conductor being liable to swing, requires larger X-arms.
- Due to lower tensile strength and higher co-efficient of linear expansion of Aluminium, the sag is greater in Aluminium conductor.
- Due to low melting point of Al., it cannot withstand short-circuit etc. Joining of Aluminium is also difficult as compared to that of copper.
- \* **AAC**! → All Aluminium conductor.
- \* All aluminium stranded conductors are mainly used for low voltage distribution overhead line having short spans of upto 65m.


### ③ Steel-cored Aluminium

(ACSR - Aluminium conductor steel reinforced)

- Due to low tensile strength, Aluminium conductors produce greater sag, so that Al. conductor unsuitable for long distance transmission line.
- In order to increase the tensile strength, the Al. conductor is reinforced with a core of galvanised steel wires and composite conductor is known as steel-cored aluminium.
- ACSR has high tensile strength and lighter in weight produces small sag and therefore longer spans can be used.
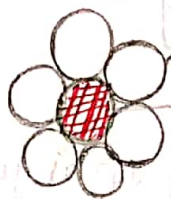
#### Advantages of ACSR:

- ACSR has high tensile strength and lighter in weight produces small sag; therefore it can be used for longer span length.
- Due to smaller sag with steel cored aluminium conductors, towers of smaller heights can be used.
- ACSR conductor reduces skin effects.
- ACSR conductor reduces corona losses.
- Because of use of larger span, the number of line supports may be reduced (about 25%). Thus the overall cost of supports, foundations, insulators and erection is considerably reduced. Maintenance cost is also reduced.





## ① copper! →

- copper has high electrical conductivity
- It has greater tensile strength.
- due to its high current density, smaller x-sectional area is required for conductivity and secondly, the area offered by the conductor to wind load is reduced
- It is durable and has high scrap value.

## drawback! →

- It is costly.
- and it is rarely not available:

→ coat (iron/steel) with a protective layer of zinc. have very high

## ④ galvanised steel! →

- Galvanised steel has poor conductivity but high tensile strength.
- Due to high tensile strength, galvanised steel can be used for extremely long span.
- Due to its poor conductivity, it is used to transmit a small power over a small distance.

## properties of galvanised steel! →

- ① poor conductivity, 15% that of copper.
  - ② High internal reactance
  - ③ It is subjected to eddy current and hysteresis.
- and wire! → galvanised steel wire is limited to telecommunication lines, stay wire, earth wire, guard wire.

- Stranded galvanised steel wires are used as guy wires and earth/ground wire.
- In 11 kV and 33 kV lines, the earth wire is provided below the line conductors for the safety of personnel, cattle and material moving under the line as a precaution in case a line conductor snaps.
- In case of extra-high voltage lines of 66 kV, 132 or 220 kV, the ground wire is provided above the line conductors for protection against lightning.

### ⑤ Cadmium Copper : →

- In some cases, 1-2% of cadmium is added with copper to increase the tensile strength by 50% but its conductivity is reduced by 15%.
- Use of cadmium copper will be economical for a line with long spans and small cross section, i.e. where the cost of conductor material is comparatively small in comparison to that of supports.
- Cadmium-copper conductors are also employed for telephone and telegraph lines where current involved are quite small.
- But due to scarcity of copper, cadmium-copper conductors on communication lines are being replaced by ACSR conductors.



## Insulators

The insulators provide necessary insulation between the conductors and supports and prevent any leakage current from conductors to earth.

For an insulator, the general properties are

- (i) High mechanical strength in order to withstand conductor load, wind load etc.
- (ii) High electrical resistance of insulator material in order to avoid leakage current to earth.
- (iii) High relative permittivity so as to provide high dielectric strength.
- (iv) High ratio of rupture strength to flash-over voltage.
- (v) The insulator material should not be porous, free from impurities and cracks otherwise the permittivity will be lowered.
- (vi) Ability to withstand large temperature variations.  
i.e. It should not crack when subjected to high temperature during summer and low temp. during winter.





## Types of Insulators

①

Various type of insulators are used for overhead transmission and distribution lines are

- (1) pin type insulator.
  - (2) suspension type insulator
  - (3) strain insulator
  - (4) shackle insulator
  - (5) stay insulator
  - (6) post insulator.
- String insulator.

### (i) pin type-insulators

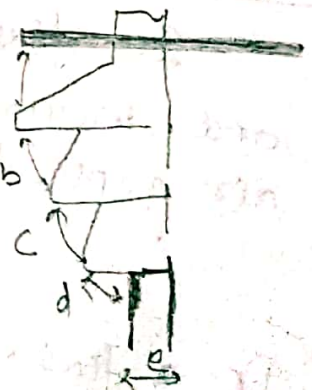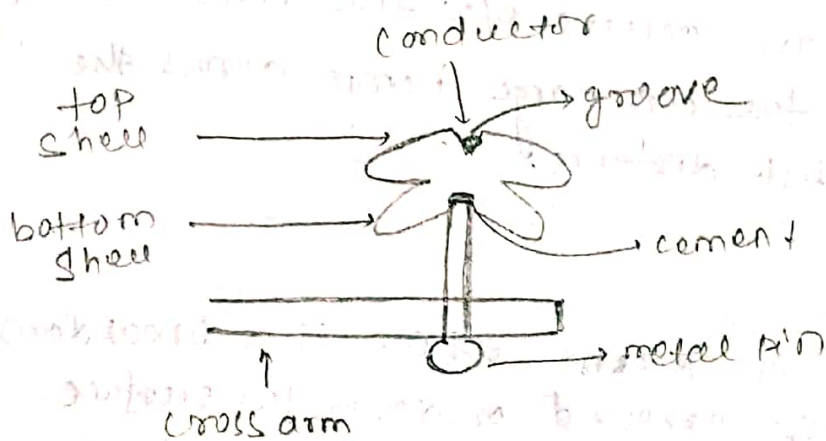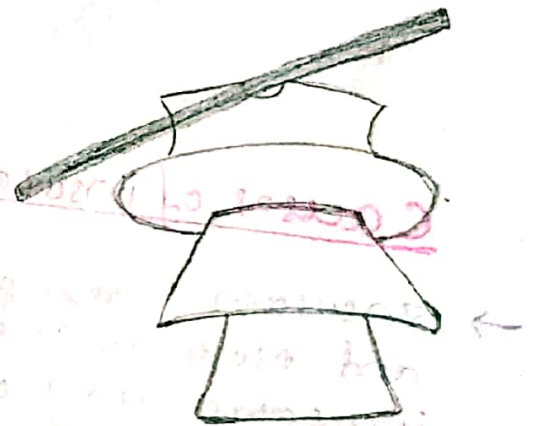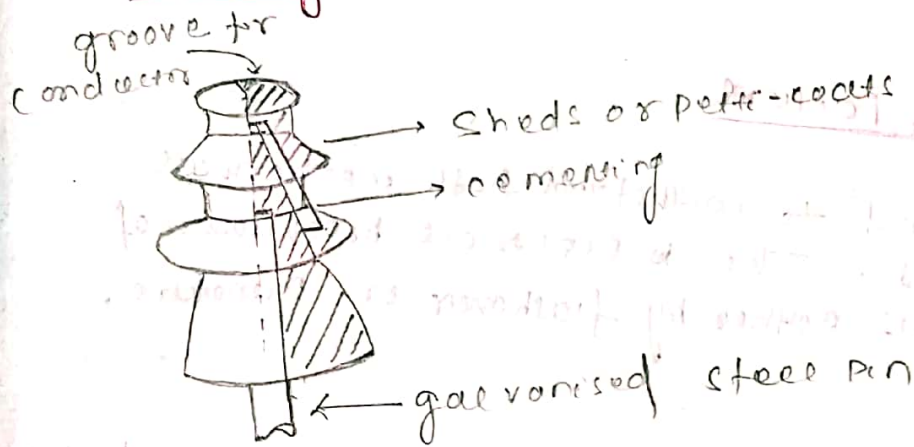



- Pin type insulators are used for transmission and distribution of electric power at voltage upto 33 kV. Beyond the 33 kV the pin insulators becomes too bulky and hence uneconomical.
- There is a groove on the upper end of the insulator for placing the conductor. The conductor passes through this groove and is bounded by the annealed wire of the same material as the conductor.







### Causes of insulator Failure

- Insulators are required to withstand both mechanical and electrical stresses. The electrical breakdown of insulators may occur either by flashover or puncture.
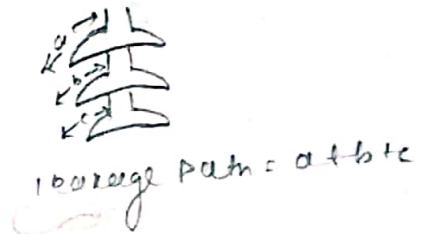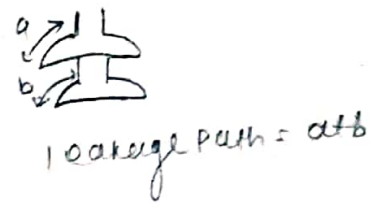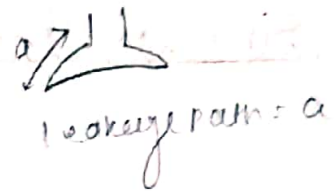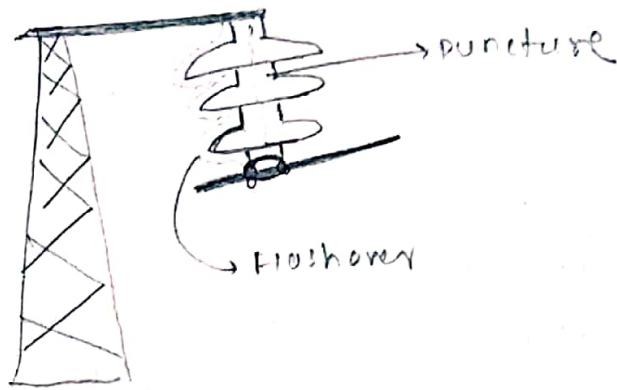
#### Flash-over

In flash over, an arc occurs b/w the line conductor and insulator pin and the discharge jumps across the air gaps, following shortest distance.



### Puncture

- In case of puncture the discharge occurs from conductor to pin through the body of insulator. under this condition the insulator is permanently destroy due to excessive heat.
- In practice sufficient thickness of porcelain is provided in the insulator to avoid puncture by line voltage.


\* The ratio of puncture strength to the flashover voltage is known as safety factor

$$S.F = \frac{\text{puncture strength}}{\text{Flashover voltage}}$$

- \* For the pin type insulator the value of S.F is about 10
- \* with increase in no. of sheds the leakage path increases.  
leakage current  $\propto \frac{1}{\text{length of leakage path}}$




## ② Shackle Insulator

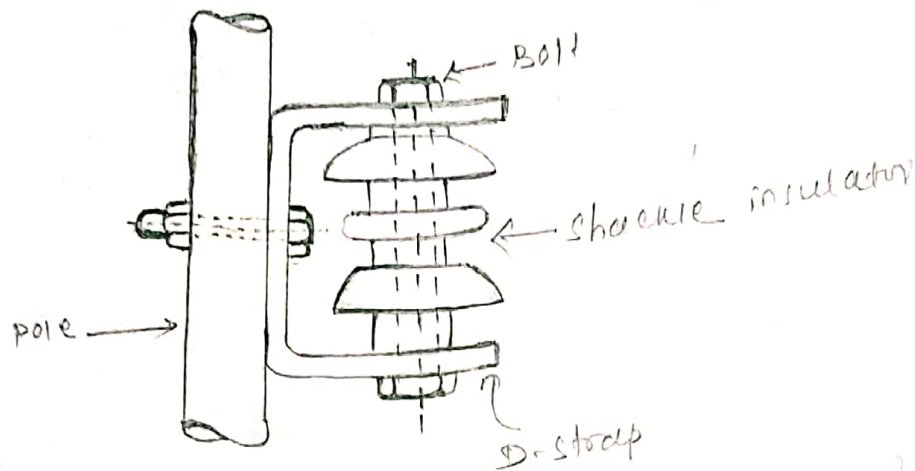

- It is used up to 25kV.
- shackle insulators are frequently used for low voltage distribution line. Each insulator can be used either in horizontal position or vertical position.
- They can be directly fixed to the pole with a bolt or to the cross-arm.


## ③ Stay insulator / Egg Insulator

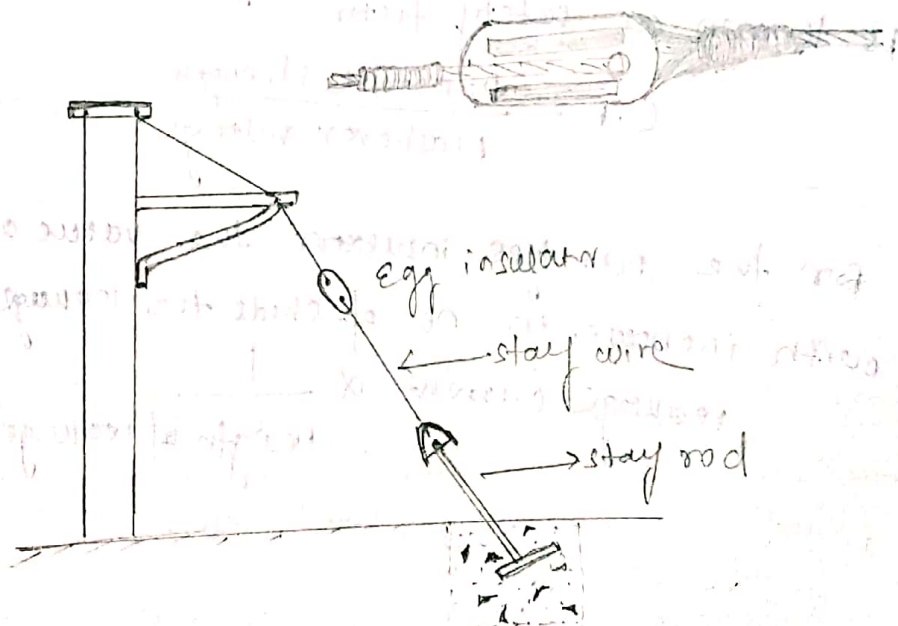

It provide the insulation b/w stay wire and cross-arm (pole & earth)
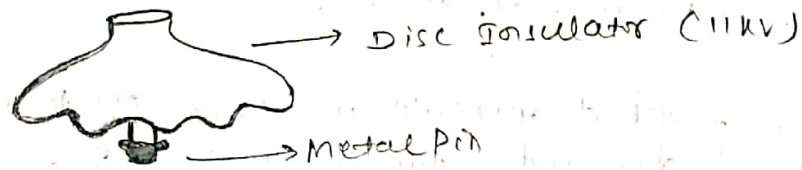
#### ④ String insulator

A number of disc insulators are connected in cascade (series) & each disc is rated at 11 kV.




① suspension type

② strain type insulator.
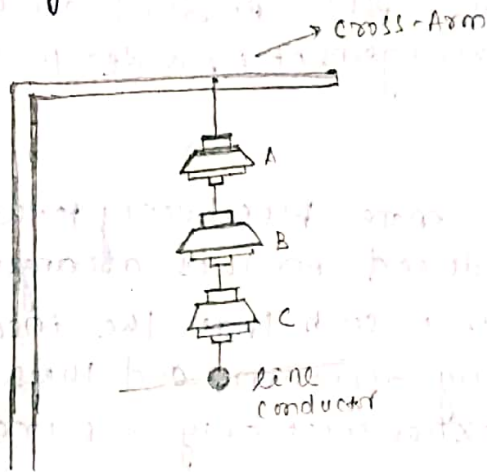
#### ① suspension type insulator

→ Above 33 kV, the pin-type insulator becomes bulky and costly so it is not economical to use.



→ for high voltage (> 33 kV) it is a usual practice to use suspension type insulator.

→ It consists of a no. of porcelain discs connected in series by metal link in the form of a string. The conductor is suspended at the bottom end of the string while the other end of the string is connected to the cross-arm of the tower.

→ Each unit or disc is design for low voltage (upto 11 kV) i.e. 11 kV.

#### Advantages


→ suspension type insulators are cheaper than pin type insulator for voltage beyond 33 kV.

→ if any one disc is damaged, then that disc can be replaced instead of the whole string.



- Each unit or disc of suspension type insulator is designed for low voltage, usually 11 kV. Depending upon the working voltage, the desired no. of discs can be connected in series.
- In case of rapid increase in load on transmission line, the increased demand can be met by raising the line voltage than to provide another set of conductors. With suspension type insulators, additional line insulation required can be obtained easily by adding one or more discs to the string.
- The suspension type insulators are generally used with steel towers. As the conductors run below the earthed cross-arm of the tower, therefore, this arrangement provides partial protection from lightning.
- Suspension type insulators give more flexibility to the line and mechanical stresses are reduced in this arrangement. The connection at the cross-arm is such that the insulator string is free to swing in any direction, and thus takes up a position where it experiences only a pure tensile strength.

### b) Strain Insulation

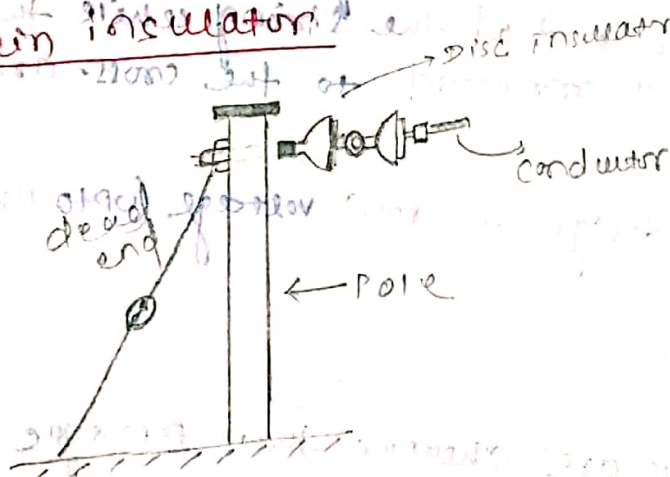

→ where there is a dead end of the line, or there is a corner or a sharp curve, diversion or the line crosses river etc. The line is subjected to greater tension.

- In order to relieve the line of excessive tension, strain insulators are used.
- For low voltage (25 kV) shackle type insulators are used as strain insulator. However for high voltage transmission line

strain insulator consist of a no. of disc insulator which are horizontally placed.


No. of Disc in strain type insulator = 1 + No. of Disc in suspension type insulator

| Voltage level (L-L) | No. of Disc |
|---------------------|-------------|
| 11 kV               | 1           |
| 33 kV               | 3           |
| 66 kV               | 5           |
| 132 kV              | 9           |
| 220 kV              | 13-15       |
| 400 kV              | 20          |


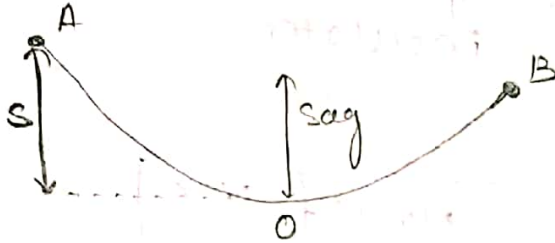
# Sag

The difference in level between points of supports and the lowest point on the conductor is called sag.



When the conductor is suspended b/w 2 supports at the same level, it takes the shape of catenary.

Factors affecting the sag in an overhead line are given below! →

(i) Weight of the conductor! →

Heavier the conductor, greater will be the sag. In locations where ice formation takes place on the conductor, this will also cause increase in the sag.

(ii) Length of span! →

Sag is directly proportional to the square of the span length.

(iii) Working tension, working tensile strength! →

The sag is inversely proportional to the working tensile strength of conductor.

(iv) Temperature! →

Length of conductor increases with the rise in temp. and so that sag form.

(a) The weight  $w x$  of conductor acting at a distance  $\frac{x}{2}$  from  $O'$ .

(b) The tension  $T$  acting at  $O'$ .

Equating the moments of above 2 forces about point  $O'$ , we get.

$$T y = w x \times \frac{x}{2}$$

$$y = \frac{w x^2}{2 T}$$

The maximum sag is represented by the value of  $y$  at either of the supports 'A' and 'B'.

At support A,  $x = \frac{l}{2}$ ,  $y = s$

$$\text{Sag } s = \frac{w \left(\frac{l}{2}\right)^2}{2 T} = \frac{w l^2}{4 \cdot 2 T} = \frac{w l^2}{8 T}$$

$$\boxed{s = \frac{w l^2}{8 T}}$$



## Calculation of sag and Tension

② When supports are at unequal level

Generally in hilly area, these type of sags are occurring on overhead lines.

Let a conductor suspended b/w 2 supports A' and B' which are at different levels.

The lowest point on the conductor is 'O'.


Let  $L$  = span length

$h$  = difference in levels b/w 2 supports.

$x_1$  = Distance of supports at lower level (i.e. A) from O

$x_2$  = Distance of supports at higher level (i.e. B) from O

$T$  = Tension in the conductor.

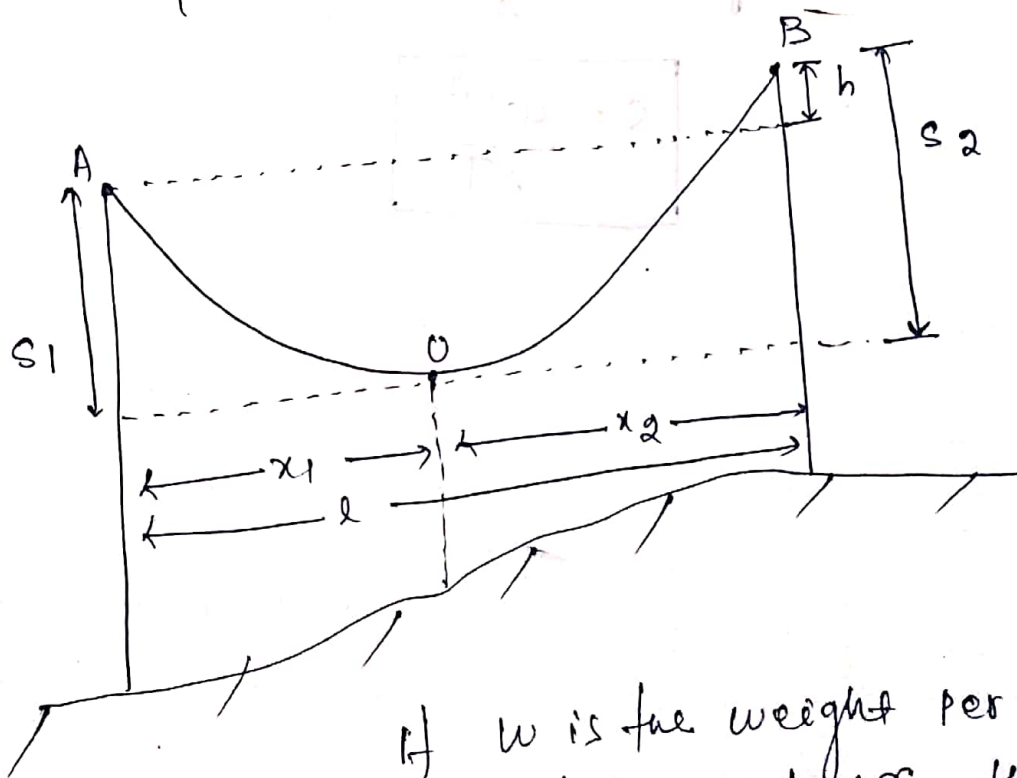

If  $w$  is the weight per unit length of the conductor, then.

$$\text{Sag } S_1 = \frac{w x_1^2}{2T}$$

and sag  $s_2 = \frac{wx_2^2}{2T}$

$$x_1 + x_2 = l \longrightarrow \text{eqn (1)}$$

$$s_2 - s_1 = \frac{wx_2^2}{2T} - \frac{wx_1^2}{2T}$$

$$\Rightarrow h = \frac{w}{2T} (x_2^2 - x_1^2)$$

$$\Rightarrow h = \frac{w}{2T} (x_2 + x_1)(x_2 - x_1)$$

$$\Rightarrow h = \frac{wl}{2T} (x_2 - x_1)$$

$$\Rightarrow x_2 - x_1 = \frac{2Th}{wl} \longrightarrow \text{eqn (2)}$$

from eqn (1) and eqn (2), we get

|   |   |
|---|---|
| $\begin{aligned} x_2 + x_1 &= l \\ x_2 - x_1 &= \frac{2Th}{wl} \end{aligned}$ <hr/> $2x_2 = l + \frac{2Th}{wl}$ $\Rightarrow \boxed{x_2 = \frac{l}{2} + \frac{Th}{wl}}$ | $\begin{aligned} x_1 + x_2 &= l \\ x_1 &= l - x_2 \\ &= l - \left( \frac{l}{2} + \frac{Th}{wl} \right) \\ &= l - \frac{l}{2} - \frac{Th}{wl} \\ &= \frac{l}{2} - \frac{Th}{wl} \end{aligned}$ $\boxed{x_1 = \frac{l}{2} - \frac{Th}{wl}}$ |
|---|---|



from  $x_1$  and  $x_2$  we can easily find out the value of  $s_1$  and  $s_2$ .


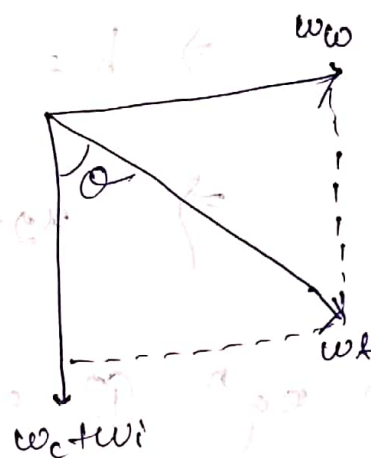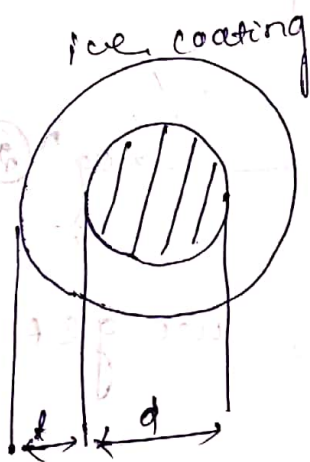
## Effect of wind and ice loading

Here the weight of ice acts vertically downward i.e., in the same direction as the weight of conductor, the force due to the wind is assumed to act horizontally i.e. at right angle to the projected surface of the conductor.

Hence total force on the conductor is the vector sum of horizontal and vertical forces i.e.



Total weight of conductor per unit length is

$$w_r = \sqrt{(w_c + w_i)^2 + (w_w)^2}$$

$w_c$  = weight of conductor per unit length  
 = conductor material density  $\times$  volume per unit length

$w_i$  = weight of ice per unit length  
 = density of ice  $\times$  volume of ice per unit length  
 = density of ice  $\times \left\{ \frac{\pi}{4} [(d+t)^2 - d^2] \times 1 \right\}$

$$\frac{\pi}{4} [(d+t)^2 - d^2] = \frac{\pi}{4} (d^2 + 4dt + 4t^2 - d^2)$$


$$= \frac{\pi}{4} 4t(d+t) = \pi t(d+t)$$

$$w_i = \text{density of ice} \times [\pi t(d+t) \times 1]$$


$w_w = \text{wind force per unit length}$   
 $= \text{wind pressure per unit area} \times \text{projected area per unit length}$   
 $= \text{wind pressure} \times [(d+t) \times 1]$

$$w_w = p \times [(d+t) \times 1]$$

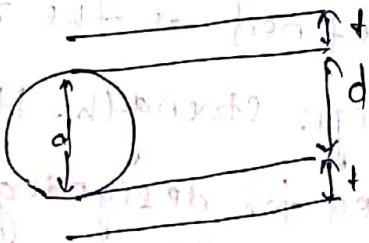where  $d = \text{diameter of conductor}$   
 and  $t = \text{Radial thickness of ice coating in m}$



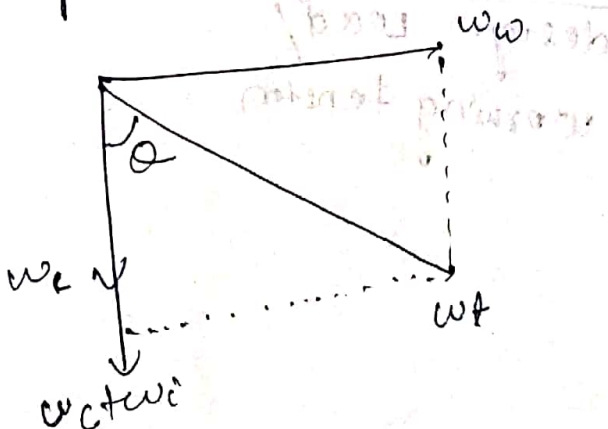When the ice and wind are acting simultaneously, the lowest point of the conductor does not remain vertically down but away from it at an angle  $\alpha$ , i.e.



$$\cos \alpha = \frac{w_c}{w_{ctwd}}$$

$$\alpha = \cos^{-1} \left( \frac{w_c}{w_{ctwd}} \right)$$




for slant sag, the formula is

$$S = \frac{wL^2}{8T}$$

where the vertical sag =  $S \cos \theta$

### Ultimate strength

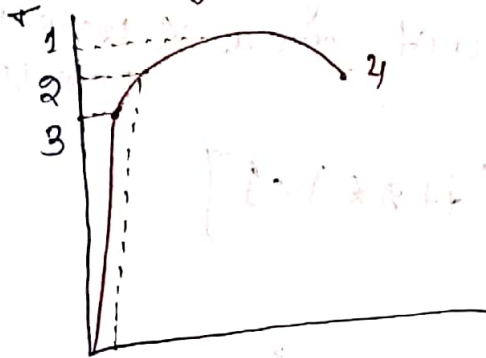

$$\tan \theta = \frac{wL}{w_{ctw}}$$

$$\text{vertical sag} = S \cos \theta$$

$$\theta = \tan^{-1} \frac{wL}{w_{ctw}}$$

ultimate strength is measured by the maximum stress that a material can withstand while being stretched or pulled before breaking.

### Safety of factor

factor of safety can be defined as the ratio of ultimate strength to the design strength. It is a constant factor that is considered for designing of machine components or structure beyond its working strength.

$$F.O.S = \frac{\text{ultimate strength}}{\text{design load / working tension}}$$

Q.1

A 132 kV transmission line has the following data:

w.t. of conductor =  $680 \text{ kg/km}$

Length of span =  $260 \text{ m}$ .

ultimate strength =  $3100 \text{ kg}$

Safety factor =  $2$

calculate the height above ground at which the conductor should be supported. ground clearance required is  $10 \text{ m}$ .


working tension,  $T = \frac{\text{ultimate strength}}{\text{safety factor}}$

$$= \frac{3100}{2} = 1550 \text{ kg}$$

weight of conductor per m. length,  $w_c = \frac{680}{1000}$   
 $w_c = 0.68 \text{ kg}$

$$\begin{aligned} \text{maximum sag, } S' &= \frac{wL^2}{8T} \\ &= \frac{0.68 \times (260)^2}{8 \times 1550} \\ &= 3.7 \text{ m} \end{aligned}$$

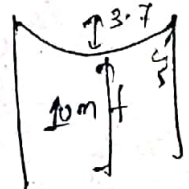The height above ground at which the conductor should be supported  
= clearance + sag  
=  $10 + 3.7$   
=  $13.7 \text{ m}$ .





Q.2

A transmission line has a span of 150 mt. b/w level supports. The conductor has a cross-sectional area of  $2 \text{ cm}^2$ . The tension in the conductor is 2000 kg. if the specific gravity of the conductor material is  $9.9 \text{ gm/cm}^3$  and wind pressure is  $1.5 \text{ kg/m}$  length, calculate the sag. what is the vertical sag.

Span length,  $l = 150 \text{ mt.}$

working tension  $T = 2000 \text{ kg}$

wind force / m length of conductor,  $w_w = 1.5 \text{ kg/m}$

wt. of conductor / m length

$w_c = \text{sp. gravity} \times \text{volume of 1 mt. conductor}$

$$= 9.9 \times 2 \times 100$$

$$= 1980 \text{ gm} = 1.98 \text{ kg}$$


Total weight of 1 mt. length of conductor is

$$wt = \sqrt{w_c^2 + w_w^2}$$
$$= \sqrt{(1.98)^2 + (1.5)^2}$$

$$= 2.48 \text{ kg}$$

$$\text{sag, } S = \frac{w l^2}{8T} = \frac{2.48 \times (150)^2}{8 \times 2000} = 3.48 \text{ m}$$

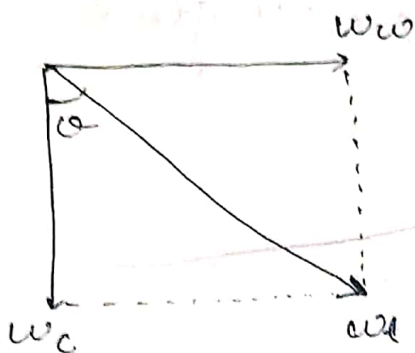This is the value of least sag in a direction making an angle  $\theta$  with the vertical.



$$\cos \theta = \frac{b}{h} = \frac{w_c}{w_t}$$

$$\cos \theta = \frac{1.98}{2.48}$$

$$\cos \theta = 0.796$$

$$\begin{aligned} \text{vertical sag} &= 3 \cos \theta \\ &= 3.48 \times 0.796 \\ &= 2.77 \text{ m.} \end{aligned}$$


OR  $\tan \theta = \frac{w_w}{w_c} = \frac{1.5}{1.98} = 0.76$

$$\theta = \tan^{-1} 0.76 = 37.25^\circ$$

$$\begin{aligned} \text{vertical sag} &= 3 \cos \theta \\ &= 3.48 \times \cos 37.25^\circ \\ &= 2.77 \text{ m.} \end{aligned}$$



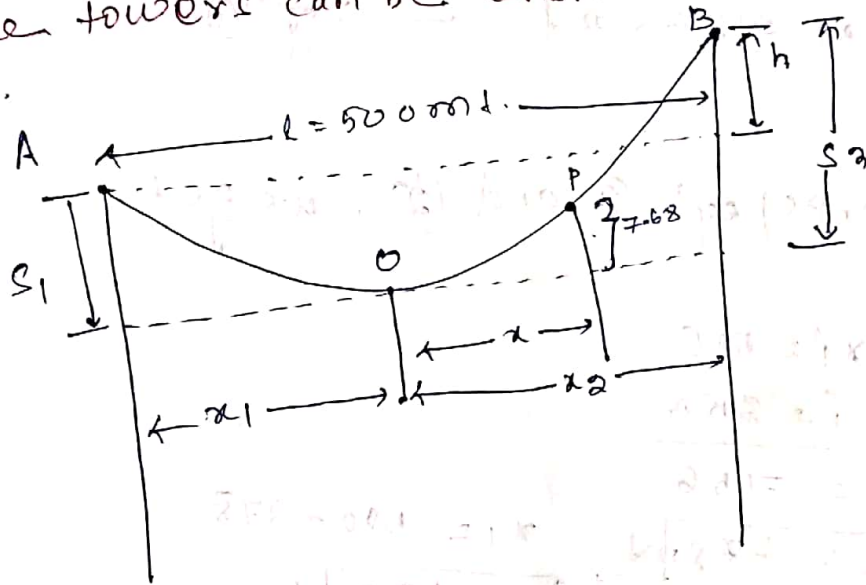Q.7 The tower of height 30 m and 90 m. respectively support a transmission line conductor at water crossing. The horizontal distance b/w the tower is 500 m. If the tension in the conductor is 1600 kg. find the minimum clearance of the conductor and water and clearance mid-way b/w the supports. weight of conductor is  $1.5 \text{ kg/m}$ . Bases of the towers can be considered to be at water level.



Here  $l = 500 \text{ m}$ .  
 $w = 1.5 \text{ kg/m}$   
 $T = 1600 \text{ kg}$

Difference in level b/w supports  $h_1 = 90 - 30 = 60 \text{ m}$ .  
 Let, The distance b/w support 'A' and 'O' is  $x_1$   
 and the distance b/w support 'B' and 'O' is  $x_2$

$$x_1 + x_2 = 500 \text{ m} \quad \text{--- eqn (1)}$$

and

$$\text{sag } s_1 = \frac{wx_1^2}{2T}, \quad \text{sag } s_2 = \frac{wx_2^2}{2T}$$

$$h = s_2 - s_1 = \frac{wx_2^2}{2T} - \frac{wx_1^2}{2T}$$

$$\Rightarrow h = \frac{w}{2T} (x_2^2 - x_1^2)$$

$$\Rightarrow G_0 = \frac{w_c}{2T} (x_1 + x_2)(x_2 - x_1)$$

$$\Rightarrow 60 = \frac{w_c}{2T} \times 500(x_2 - x_1)$$

$$\Rightarrow x_2 - x_1 = \frac{60 \times 2 \times T}{w \times 500} = \frac{60 \times 2 \times 1600}{1.5 \times 500}$$

$$\Rightarrow x_2 - x_1 = 256 \text{ m} \rightarrow \text{eqn ①}$$

Solving eqs | eqn ① and ②, we get

$$\begin{array}{r} x_2 + x_1 = 500 \\ x_2 - x_1 = 256 \\ \hline 2x_2 = 756 \\ \boxed{x_2 = 378 \text{ m}}, \quad \boxed{x_1 = 122 \text{ m}} \end{array}$$

Now,  $S_1 = \frac{w x_1^2}{2T} = \frac{1.5 \times (122)^2}{2 \times 1600} = 7 \text{ m}$

Now, clearance of the lowest point 'O' from water level,  $= 30 - 7 = 23 \text{ m}$ .

Let mid-point 'P' be at a distance 'x' from the lowest point O.

$$\text{So } x = 250 - x_1 = 250 - 122 = 128 \text{ m}$$

$$\text{Sag at mid-point P, } S_{\text{mid}} = \frac{w x^2}{2T} = \frac{1.5 \times (128)^2}{2 \times 1600} = 7.68 \text{ m}$$

clearance of mid point 'P' from water level  $= 23 + 7.68 = 30.68 \text{ m}$



Q.8 An over-head transmission line conductor having a parabolic configuration weight  $1.925 \text{ kg per metre of length}$ . The area of x-section of the conductor is  $2.2 \text{ cm}^2$  and the ultimate strength is  $8000 \text{ kg/cm}^2$ . The supports are  $600 \text{ m}$  apart having  $15 \text{ m}$  difference of levels. calculate the sag from the taller of the two supports which must be allowed so that the factor of safety shall be 5. Assume that ice load is  $1 \text{ kg per mt. run}$  and there is no wind pressure.

$$l = 600 \text{ mt.}, w_i = 1 \text{ kg}, h = 15 \text{ mt.}$$

$$w_c = 1.925 \text{ kg}, T = \frac{8000 \times 2.2}{5}$$


$$T = 3520 \text{ kg}$$

Total weight of  $1 \text{ mt}$  length of conductor is (Length of con/mt)

$$w_t = w_c + w_i$$

$$w_t = 1.925 + 1 = 2.925 \text{ kg}$$

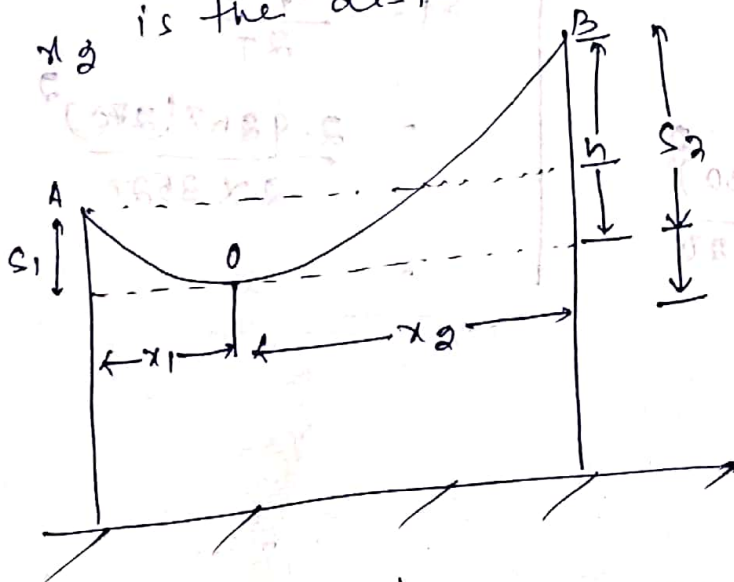Let  $x_1$  is the distance from point  $O'$  to support 'A'  
 $x_2$  is the distance from point  $O'$  to support B.



$$s_1 = \frac{w_t x_1^2}{2T}, s_2 = \frac{w_t x_2^2}{2T}$$

$$x_1 + x_2 = 600 \text{ mt.} \quad \text{--- eqn ①}$$

$$h = \frac{w_t x_2^2}{2T} - \frac{w_t x_1^2}{2T} = \frac{w_t}{2T} (x_2^2 - x_1^2)$$

$$\Rightarrow h = \frac{w_t}{2T} (x_2 + x_1)(x_2 - x_1)$$

$$\Rightarrow h = \frac{w_t}{2T} \cdot l (x_2 - x_1)$$

$$\Rightarrow 15 = \frac{w_t}{2T} \cdot 600 (x_2 - x_1)$$

$$\Rightarrow x_2 - x_1 = \frac{15 \times 2 \times 3520}{2.926 \times 600}$$

$$\Rightarrow x_2 - x_1 = 60 \text{ m.} \rightarrow \text{eq}^n (2)$$

by solving eq<sup>n</sup> (1) and eq<sup>n</sup> (2), we get

$$x_2 + x_1 = 600$$

$$x_2 - x_1 = 60$$

$$2x_2 = 660$$

$$x_2 = 330 \text{ m}$$

$$x_2 + x_1 = l$$

$$\Rightarrow x_1 = l - x_2$$

$$\Rightarrow x_1 = 600 - 330$$

$$\Rightarrow x_1 = 270 \text{ m.}$$

Ans

$$S_2 = \frac{w_t x_2^2}{2T}$$

$$= \frac{2.926 \times (330)^2}{2 \times 3520}$$

$$= 45.24 \text{ m.}$$

$$S_1 = \frac{w_t x_1^2}{2T}$$

$$= \frac{2.926 \times (270)^2}{2 \times 3520}$$

=

$$= 35.24 \text{ m.}$$



Q. 9 An overhead transmission line at a river crossing is supported from two towers at heights of 40m and 90m. above water level, the horizontal distance b/w the towers being 400m. if the maximum allowable tension is 2000 kg; find the clearance b/w the conductor and water at a point mid-way b/w the towers. weight of conductor is 1 kg/m.

here

$$h = 90 - 40 = 50 \text{ m.}$$

$$l = 400 \text{ m.}$$

$$T = 2000 \text{ kg}$$

$$w_c = 1 \text{ kg/m.}$$

$$x_1 + x_2 = 400 \text{ m.} \rightarrow \text{eqn (1)}$$

$$h = \frac{w_c x_2^2}{2T} - \frac{w_c x_1^2}{2T}$$

$$\Rightarrow h = \frac{w_c}{2T} (x_2^2 - x_1^2)$$

$$\Rightarrow h = \frac{w_c}{2T} (x_2 + x_1)(x_2 - x_1)$$

$$\Rightarrow h = \frac{w_c}{2T} \cdot l \cdot (x_2 - x_1)$$

$$\Rightarrow x_2 - x_1 = \frac{2T \cdot h}{w_c \cdot l}$$

$$\Rightarrow x_2 - x_1 = \frac{2 \times 2000 \times 50}{1 \times 400}$$

$$\Rightarrow x_2 - x_1 = 500 \text{ m.} \rightarrow \text{eqn (2)}$$

by solving eqn (1) and eqn (2) we get

$$x_2 + x_1 \rightarrow \text{eqn (1)}$$

$$x_2 - x_1 \rightarrow \text{eqn (2)}$$

$$x_2 + x_1 = 400$$

$$x_2 - x_1 = 500$$

$$2x_2 = 900$$


$$x_2 = 450 \text{ m.}$$

$$x_1 = l - x_2$$

$$= 400 - 450$$

$$x_1 = -50 \text{ m.}$$

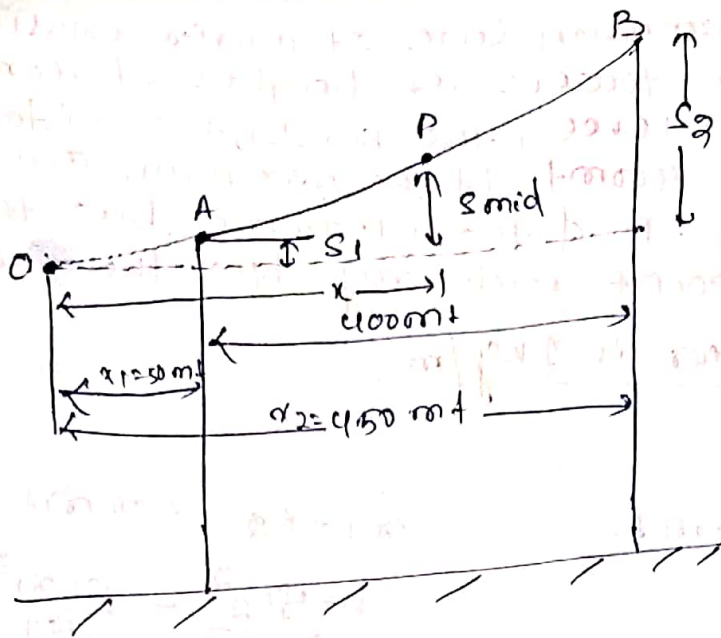Let  $x_1$  is the distance b/w point 'o' and support 'A'  
 &  $x_2$  is the distance b/w point 'o' and support 'B'



horizontal distance of mid-point 'P' from lowest point 'O' is

$$x = \text{Distance of A from } O' + \frac{400}{2}$$

$$= 50 + 200$$

$$\boxed{x = 250 \text{ m}}$$

Sag at point P,  $s_{\text{mid}} = \frac{wx^2}{2T} = \frac{1 \times (250)^2}{2 \times 2000}$

$$s_{\text{mid}} = 15.6 \text{ m}$$

Sag  $s_2 = \frac{wx_2^2}{2T} = \frac{1 \times (450)^2}{2 \times 2000} = 50.6 \text{ m}$

Height of point 'B' above mid-point P

$$= s_2 - s_{\text{mid}} = 50.6 - 15.6 = 35 \text{ m}$$

$\therefore$  clearance of mid-point 'P' above water level  
 $= 90 - 35 = 55 \text{ m}$



## Ch-4 performance of short & medium lines

- The design and operation of a transmission line are occurs to determine the voltage drop, line losses and efficiency of transmission.
- These values are greatly influenced by the line constant  $R$ ,  $L$  and  $C$  of the transmission line.
- In this chapter, we shall develop formula by which we can calculate voltage regulation, line losses and efficiency of transmission line.

### Classification of over-head lines

There are 3 types of transmission line according to Length and line voltage.

#### ① Short transmission line! →

- when the length of an overhead transmission line is upto 50 km and line voltage is comparatively low (20 kV), it is usually known as short transmission line.
- Due to smaller length and lower voltage, the capacitance effects are small and hence can be neglected.

#### ② Medium transmission line! →

- when the length of an overhead transmission line is about 50 - 150 km and the line voltage is moderately high (720 kV, < 100 kV), it is known as medium transmission line.

- Due to sufficient length and voltage of the line, the capacitance effects are taken into account.

\* All 3 constant  $R$ ,  $L$  &  $C$  are considered in medium transmission line.

## Long transmission line :-

When the length of an overhead transmission line is more than 160 km and line voltage is very high ( $> 100 \text{ kV}$ ), it is known as long transmission line.

## Important Terms

### ① Voltage Regulation :-

The difference in voltage at the receiving end of a transmission line with no-load and full-load condition is called as voltage regulation and it is expressed as a percentage (%) of the receiving end voltage.

$$\% V.R = \frac{V_S - V_R}{V_R} \times 100$$

→ So the voltage regulation of a transmission line should be low.

### ② Transmission Efficiency :-

The ratio of receiving end power to sending end power of a transmission line is known as transmission efficiency.

$$\% \eta = \frac{\text{Receiving end power}}{\text{Sending end power}} \times 100$$

$$\% \eta = \frac{V_R I_R \cos \phi_R}{V_S I_S \cos \phi_S} \times 100$$


$$\% \eta = \frac{V_R I_R \cos \phi_R}{V_S I_S \cos \phi_S} \times 100$$



$V_R$  = Receiving end voltage  
 $I_R$  = Receiving end current  
 $\cos \phi_R$  = Receiving end P.F

$V_S$  = sending end voltage  
 $I_S$  = sending end current  
 $\cos \phi_S$  = sending end P.F

Short transmission line :-

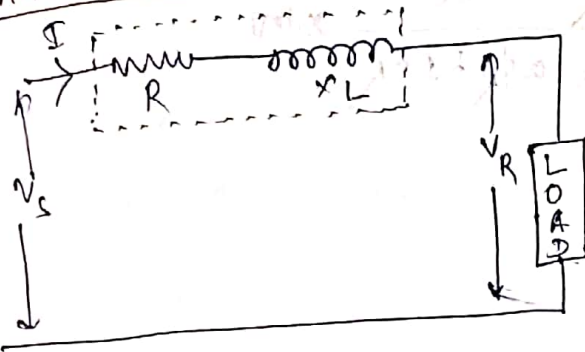


$V_S$  = sending end voltage  
 $V_R$  = Receiving end voltage

$I$  = load current  
 $R$  = loop Resistance  
 $X_L$  = loop Reactance

$\cos \phi_R$  = Receiving end P.F (lagging)  
 $\cos \phi_S$  = sending end P.F (lagging)

Phasor diagram

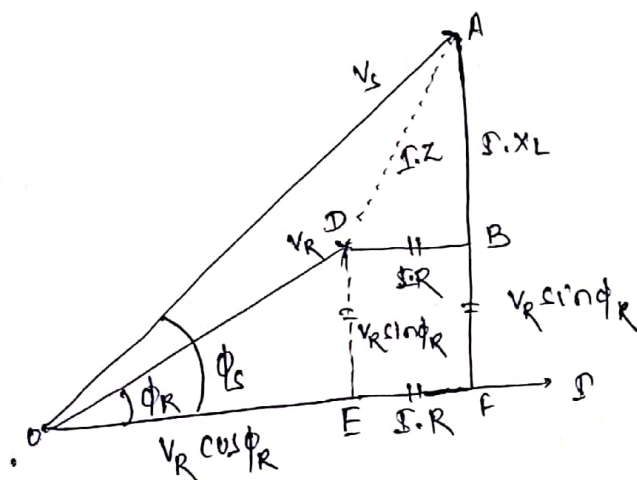

By applying Pythagorean theorem.

$$h^2 = p^2 + b^2 = b^2 + p^2$$

$$\Rightarrow (OA)^2 = (OF)^2 + (AF)^2$$

$$\Rightarrow V_S^2 = (OE + EF)^2 + (FB + BA)^2$$

$$\Rightarrow V_S = \sqrt{(V_R \cos \phi_R + I \cdot R)^2 + (V_R \sin \phi_R + I \cdot X_L)^2}$$

$$\therefore V_S = \sqrt{(V_R \cos \phi_R + I \cdot R)^2 + (V_R \sin \phi_R + I \cdot X_L)^2}$$

$$\therefore V_R = \frac{V_S - V_R}{V_R} \times 100$$

$$\text{sending end P.F} = \cos \phi_S = \frac{b}{h} = \frac{V_R \cos \phi_R + I R}{V_S}$$

$$\text{Power delivered} = V_R I_R \cos \phi_R$$

$$\text{Power loss} = I^2 R$$

$$\text{Sending power} = V_R I_R \cos \phi_R + I^2 R$$

$$\therefore \text{transmission efficiency} = \frac{O/P}{I/P}$$

$$= \frac{V_R I_R \cos \phi_R}{V_R I_R \cos \phi_R + I^2 R} \times 100$$



Q A single Phase overhead transmission line delivers 1100 kW at 33 kV at 0.8 pf, lagging. The total resistance and inductive reactance of the line are 10  $\Omega$  and 15  $\Omega$  respectively. Determine: (i) sending end voltage (ii) sending end p.f. (iii) transmission efficiency.

Ans

$$\cos \phi_R = 0.8 \text{ lagging}$$

$$\text{Total line impedance } Z = R + jX_L = 10 + j15$$

$$\text{Receiving end voltage, } V_R = 33 \text{ kV} = 33000 \text{ V}$$



$$\text{Line current, } I = \frac{\text{kW} \times 10^3}{V_R \cos \phi_R} = \frac{1100 \times 10^3}{33000 \times 0.8} = 41.67 \text{ Amp}$$

$$\cos \phi_R = 0.8 ; \sin \phi_R = 0.6$$

$$\begin{aligned} \text{(i)} \quad V_S &= \sqrt{(V_R \cos \phi_R + IR)^2 + (V_R \sin \phi_R + IX_L)^2} \\ &= \sqrt{(33000 \times 0.8 + 41.66 \times 10)^2 + (33000 \times 0.6 + 41.66 \times 15)^2} \\ &= 33709.14 \text{ V} \end{aligned}$$

$$\text{(ii)} \quad \cos \phi_S = \frac{V_R \cos \phi_R + IR}{V_S} = \frac{33000 \times 0.8 + 41.66 \times 10}{33709.14} = 0.795 \text{ (lagging)}$$
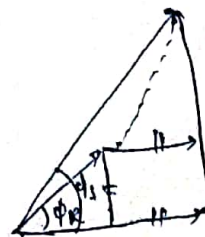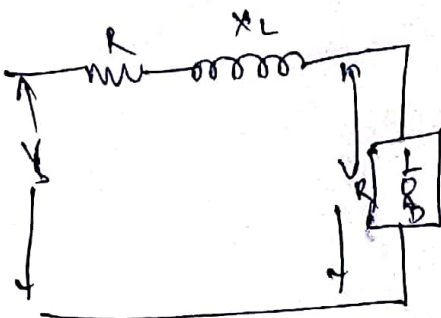
$$\begin{aligned} \text{(iii)} \quad \text{Efficiency} &= \left( \frac{V_R I \cos \phi_R}{V_S I \cos \phi_S + I^2 R} \right) \times 100 \\ &= \frac{33000 \times 41.66 \times 0.8}{33000 \times 41.66 \times 0.795 + (41.66)^2 \times 10} \times 100 \\ &= 98.44 \% \end{aligned}$$



Q what is the maximum length in km for a 1- $\phi$  transmission line having copper conductor of 0.775 cm<sup>2</sup> cross-section over which 200 kW at unity P.F. and at 3300 volts are to be delivered? The efficiency of transmission is 90%. Take specific resistance as  $1.725 \times 10^{-8} \Omega \text{ cm}$ .

Ans Receiving end power = 200 kW = 200,000 W  
 Transmission efficiency = 0.9  
 sending end power =  $\frac{200,000}{0.9} = 2,22,222 \text{ watt}$   
 (i/p power)  
 Line losses = 2,22,222 - 200,000 = 22,222 watt  
 Line current,  $I = \frac{200 \times 10^3}{3300 \times 1} = 60.6 \text{ amp}$

Let  $R/2$  be the resistance of one conductor,

$$\text{Line losses} = 2I^2R$$

$$\Rightarrow 22,222 = 2(60.6)^2 \times R$$

$$\Rightarrow R = \frac{22,222}{2(60.6)^2} = 3.025 \Omega$$

$$\Rightarrow \boxed{R = \frac{\rho l}{a}}$$

$$\Rightarrow l = \frac{Ra}{\rho} = \frac{3.025 \times 0.775}{1.725 \times 10^{-8}} = 1.36 \times 10^6 \text{ cm} = 13.6 \text{ km}$$




## Medium transmission line :-

There are 5 methods known as localised capacitance methods for the solution of medium transmission line are

- (1) End condenser method
- (2) Nominal T method
- (3) Nominal  $\pi$  method
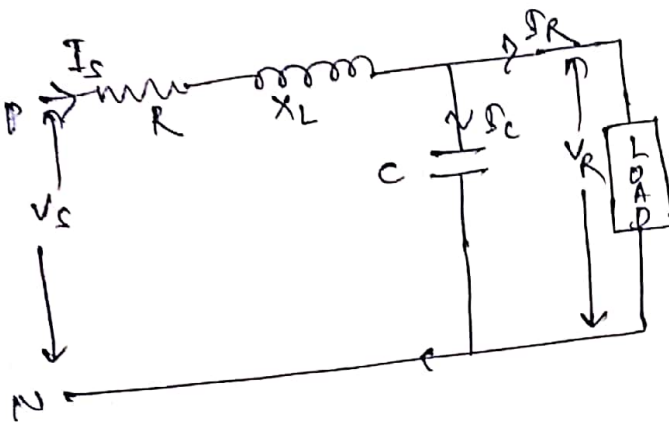
### (1) End condenser method

In this method the capacitance of the line is lumped or concentrated at the receiving or load end.



$I_R$  = load current per phase

$R$  = Resistance per phase

$X_L$  = inductive reactance per phase

$C$  = capacitance per phase


$\cos \phi_R$  = Receiving end P.F (lagging)

$V_S$  = Sending end voltage per phase

$\cos \phi_S$  = sending end P.F

$V_R$  = Receiving end voltage / phase

$I_S$  = sending end current

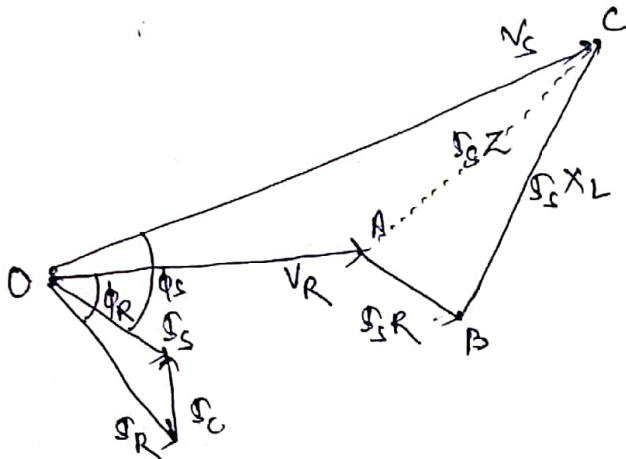

Let  $\vec{V}_R$  be the reference phasor.

$$\vec{V}_R = V_R + j0$$

load current,  $\vec{I}_R = I_R \angle -\phi_R = I_R (\cos \phi_R - j \sin \phi_R)$

capacitive current,  $\vec{I}_C = j \vec{V}_R \omega C = j 2\pi f C \vec{V}_R$

$$X_C = \frac{1}{j\omega C}$$

$$= \frac{1}{j 2\pi f C}$$

$$I_C = \frac{V_R}{X_C}$$

$$= \frac{V_R}{\frac{1}{j\omega C}} = j V_R \omega C$$

$$\vec{I}_S = \vec{I}_R + \vec{I}_C = I_R (\cos \phi_R - j \sin \phi_R) + j \omega C V_R$$

$$\text{voltage drop} = \vec{I}_S \vec{Z} = \vec{I}_S (R + jX_L)$$

$$\text{sending end voltage } \vec{V}_S = \vec{V}_R + \vec{I}_S \vec{Z} = \vec{V}_R + \vec{I}_S (R + jX_L)$$

$$\boxed{\% \text{ V.R} = \frac{V_S - V_R}{V_R} \times 100}$$

$$\% \text{ Voltage transmission efficiency} = \frac{\text{Power delivered/phase} \times 100}{\text{Power delivered/phase} + \text{losses/phase}}$$

$$\boxed{\% \text{ } = \frac{V_R I_R \cos \phi_R}{V_R I_R \cos \phi_R + I_S^2 R} \times 100}$$

- Q A (medium) single phase transmission line 100 km long has the following constants:
- Resistance/km =  $0.25 \Omega$ , Reactance/km =  $0.8 \Omega$
- Susceptance/km =  $14 \times 10^{-6}$  siemen Receiving end line voltage = 66 kV
- Assuming that the total capacitance of the line is localised at the receiving end alone, determine (i) sending end current (ii) The sending end voltage (iii) The V.R (iv) Supply P.F

The line is delivering 15,000 kW at 0.8 P.F lagging. Draw the Phasor diagram to illustrate your calculation.

Soln

$$\begin{aligned} \text{Total Resistance } R &= 0.25 \times 100 = 25 \Omega \\ \text{Total Reactance } X_L &= 0.8 \times 100 = 80 \Omega \\ \text{Total susceptance } B &= 14 \times 10^{-6} \times 100 = 14 \times 10^{-4} \text{ S} \end{aligned}$$

$$\begin{aligned} Z &= R + jX_L \\ Y &= \frac{1}{Z} = \frac{1}{R + jX_L} \\ G &= \frac{R}{R^2 + X_L^2} \\ B &= \frac{-X_L}{R^2 + X_L^2} \end{aligned}$$



Receiving end voltage  $V_R = 66000 \text{ V}$

$$\text{load current, } I_R = \frac{15,000 \times 10^3}{66000 \times 0.8} = 284 \text{ Amp}$$

$$\cos \phi_R = 0.8 \quad \sin \phi_R = 0.6$$

Taking receiving end voltage as the reference phasor,

$$\vec{V}_R = V_R + j0 = 66,000 \text{ volt}$$

$$\begin{aligned} \text{load current } \vec{I}_R &= I_R (\cos \phi_R - j \sin \phi_R) \\ &= 284 (0.8 - j0.6) = 227 - j170 \end{aligned}$$

$$\text{capacitive current } \vec{I}_C = j B \times V_R = j 14 \times 10^{-4} \times 66000 = j92$$

$$\begin{aligned} \text{i) sending end current } \vec{I}_S &= \vec{I}_R + \vec{I}_C = (227 - j170) + j92 \\ &= 227 - j78 \end{aligned}$$

$$\text{magnitude of } \vec{I}_S = \sqrt{(227)^2 + (78)^2}$$

$$= 240 \text{ Amp.}$$

$$\text{ii) voltage drop } = \vec{I}_S Z = \vec{I}_S (R + jX_L)$$

$$= (227 - j78) (25 + j80)$$

$$= 5675 + j18,160 - j1950 + 6240$$

$$= 11915 + j16,210$$

$$\begin{aligned} \text{sending end voltage, } \vec{V}_S &= V_R + \vec{I}_S Z = 66000 + 11915 + j16210 \\ &= 77915 + j16210 \end{aligned}$$

$$\begin{aligned} \text{magnitude of } V_S &= \sqrt{(77915)^2 + (16210)^2} \\ &= 79583 \text{ volt.} \end{aligned}$$

$$(iii). \% V.R = \frac{V_s - V_R}{V_R} \times 100 = \frac{74583 - 66000}{66000} \times 100 = 20.58\%$$

(iv) phase angle b/w  $\vec{V}_R$  &  $\vec{I}_R$

$$\alpha_1 = \tan^{-1} \left( \frac{-7.8}{22.7} \right) = \tan^{-1} (-0.3436) = -18.96^\circ$$


Phase angle b/w  $\vec{V}_R$  &  $\vec{V}_s$

$$\alpha_2 = \tan^{-1} \frac{16210}{77915} = \tan^{-1} (0.2036) = 11.57^\circ$$


supply power factor angle

$$\alpha_s = 18.96 + 11.57 = 30.46^\circ$$
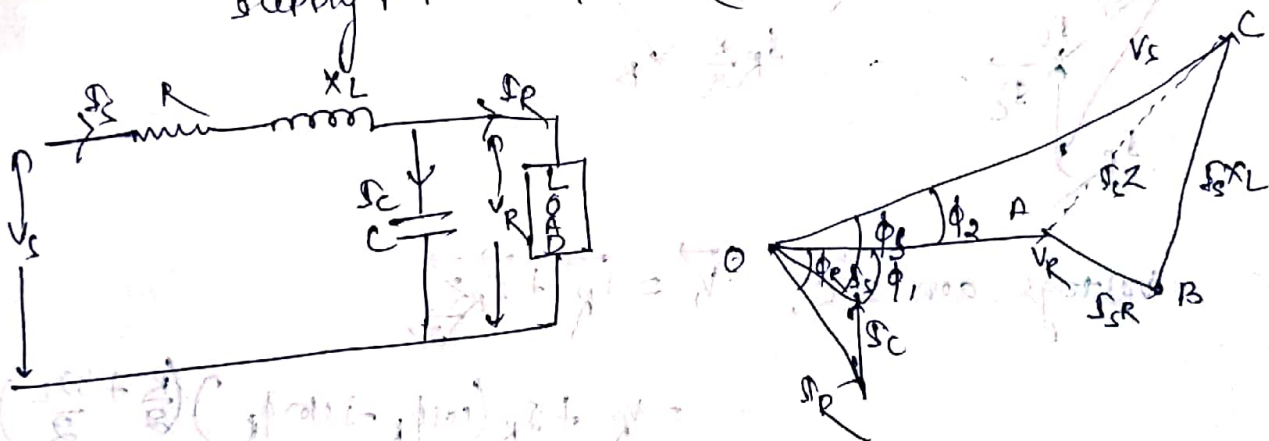
$$\text{supply P.F.} = \cos \phi_s = \cos (30.46^\circ) = 0.86 \text{ lag}$$



### Nominal T-Method

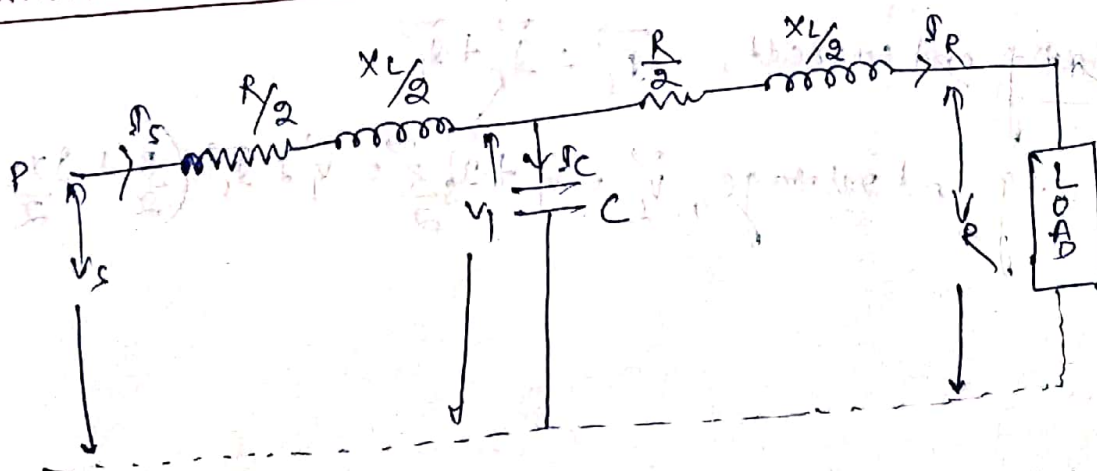

Neutral

$I_p$  = load current/phase

$X_L$  = inductive reactance/phase

$\cos \phi_R$  = receiving end P.F

increase across capacitor  $C$ .

$R$  = Resistance/Phase

$C$  = capacitance/phase


$V_s$  = sending end voltage/Ph



Taking receiving end voltage  $\vec{V}_R$  as the reference phasor

Receiving end voltage  $\vec{V}_R = V_R \angle 0^\circ$

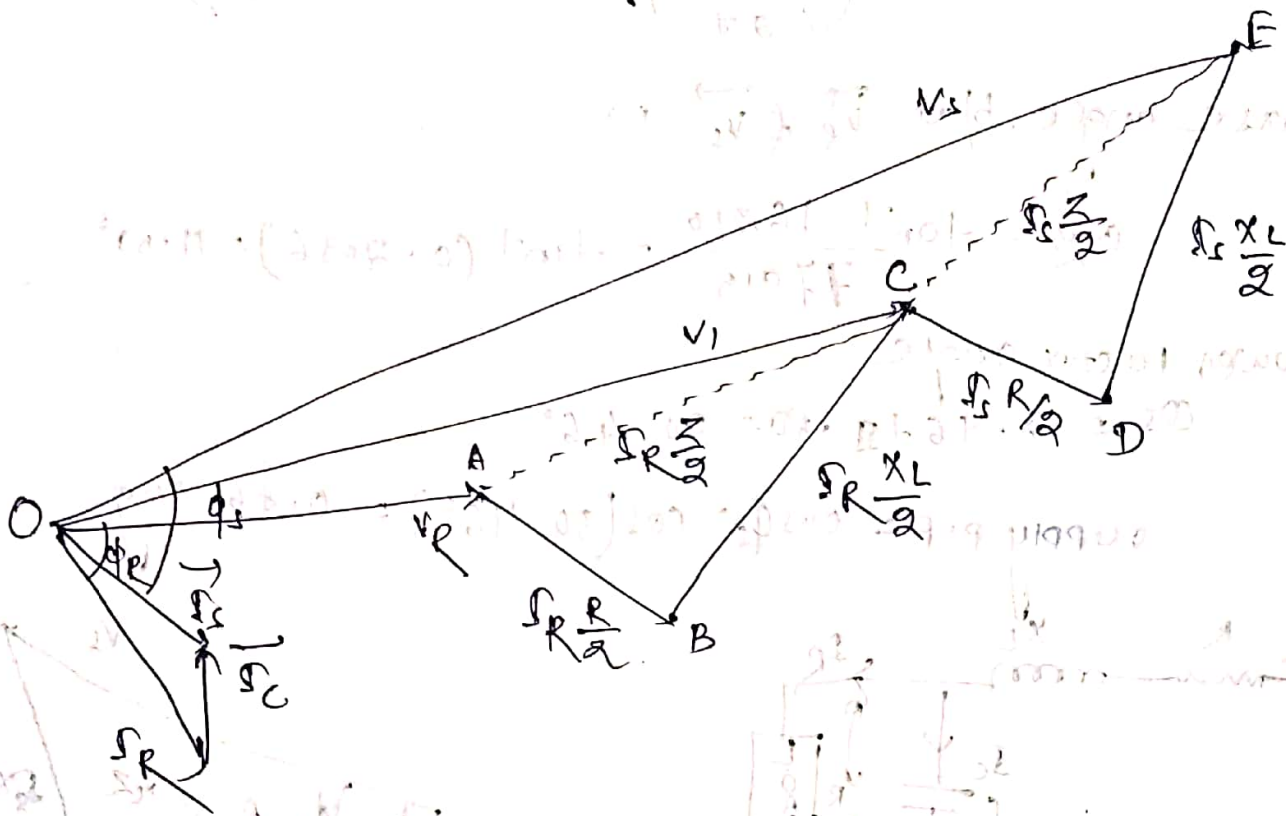load current  $\vec{I}_R = I_R (\cos \phi_R - j \sin \phi_R)$



voltage across C,  $\vec{V}_1 = \vec{V}_R + \vec{I}_R \frac{Z}{2}$

$$= V_R + I_R (\cos \phi_R - j \sin \phi_R) \left( \frac{R}{2} + j \frac{X_L}{2} \right)$$

capacitive current,  $\vec{I}_C = j \omega C \vec{V}_1 = j 2\pi f C \vec{V}_1$

sending end current,  $\vec{I}_s = \vec{I}_R + \vec{I}_C$

sending end voltage,  $\vec{V}_s = \vec{V}_1 + \vec{I}_s \frac{Z}{2} = \vec{V}_1 + \vec{I}_s \left( \frac{R}{2} + j \frac{X_L}{2} \right)$

Q A 3- $\phi$ , 50 Hz overhead transmission line 100 km long has the following constants;

Resistance / km / phase =  $0.1 \Omega$

inductive reactance / km / phase =  $0.2 \Omega$

capacitive susceptance / km / phase =  $0.04 \times 10^{-4}$  siemen

determine (i) The sending end current



(ii) sending end voltage

(iii) sending end power factor

(iv) transmission efficiency when supplying a

balanced load of 10,000 kW at 66 kV, P.f 0.8 lagging.

use nominal T-method!  $\rightarrow$

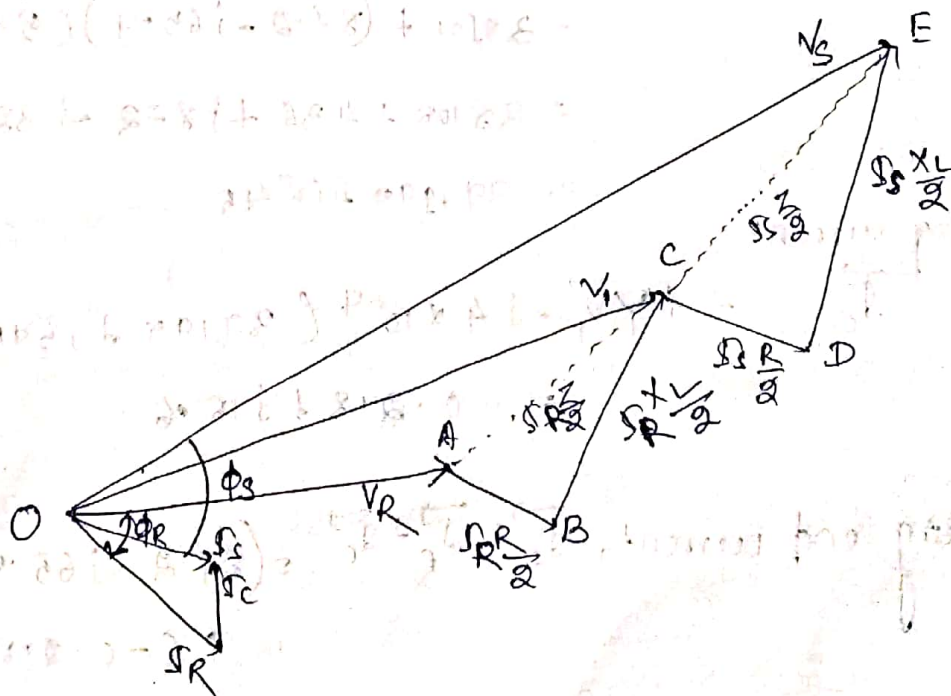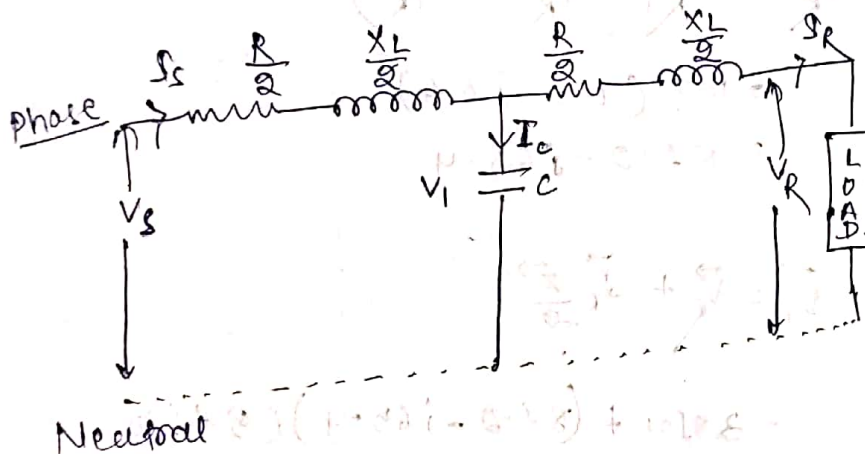



$$\text{Total resistance/ph } R = 0.1 \times 100 = 10 \Omega$$

$$\text{Total reactance/ph } X_L = 0.2 \times 100 = 20 \Omega$$

$$\text{capacitive susceptance } Y = 0.04 \times 10^{-4} \times 100 = 4 \times 10^{-4} \text{ S}$$

$$\text{Receiving end voltage/ph } V_R = \frac{66000}{\sqrt{3}} = 38105 \text{ volt}$$

$$\text{load current, } I_R = \frac{10000 \times 10^3}{\sqrt{3} \times 66 \times 10^3 \times 0.8} = 109 \text{ Amp}$$

$$\cos \phi_R = 0.8 \quad \sin \phi_R = 0.6$$

$$\text{impedance/ph } Z = R + jX_L = 10 + j20$$

$$(i) \text{ Receiving end voltage, } \vec{V}_R = V_R + j0 = 38105 \text{ volt}$$

$$\text{load current } \vec{I}_R = I_R (\cos \phi_R - j \sin \phi_R)$$

$$= 109 (0.8 - j0.6)$$

$$= 87.2 - j65.4$$

$$\text{voltage across 'c', } \vec{V}_1 = \vec{V}_R + \vec{I}_R Z$$

$$= 38105 + (87.2 - j65.4)(10 + j20)$$

$$= 38105 + 436 + j872 - j327 + 654$$

$$= 39199 + j545$$

Charging current

$$\vec{I}_C = jY \vec{V}_1 = j4 \times 10^{-4} (39199 + j545)$$

$$= -0.218 + j15.6$$

$$\text{Sending end current, } \vec{I}_S = \vec{I}_R + \vec{I}_C = (87.2 - j65.4) + (-0.218 + j15.6)$$

$$= 87.0 - j49.8$$

$$= 100 \angle -29.47^\circ \text{ Amp}$$

∴ sending end current  $(I_s) = 100 \text{ Amp}$

(ii) sending end voltage  $\vec{V}_s = \vec{V}_r + I_s \vec{Z}$

$$= (39.195 + j545) + (87.0 - j49.8)(5 + j10)$$


$$= 39.195 + j545 + 434.9 + j870 - j249 + 498$$

$$= 401.28 + j1170 = 401.45 \angle 1^\circ 40' \text{ Volt}$$

∴ line value of sending end voltage  $= \sqrt{3} \times 401.45$

$$= 69.533 \text{ kV}$$

(iii) Referring to phasor diagram,

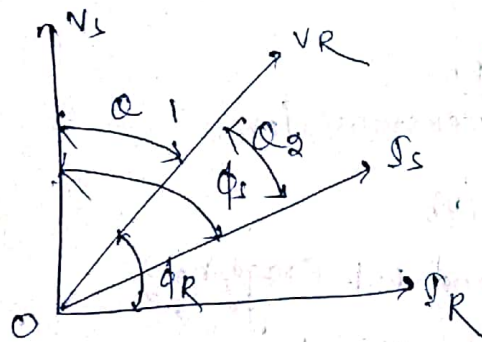

$\alpha_1 = \text{angle b/w } \vec{V}_r \text{ \& } \vec{V}_s = 1^\circ 40'$

$\alpha_2 = \text{angle b/w } \vec{V}_r \text{ \& } \vec{I}_s$   
 $29^\circ, 47'$

$$\phi_s = \alpha_1 + \alpha_2$$

$$= 1^\circ 40' + 29^\circ 47'$$

$$= 31^\circ 27'$$

sending end p.f  $\cos \phi_s = \cos(31^\circ 27') = 0.8531$  lagging

(iv) sending end power  $= 3 V_s I_s \cos \phi_s = 3 \times 401.45 \times 100 \times 0.853$

$$= 10273105 \text{ watt} = 10273.105 \text{ kW}$$


Power delivered  $= 10,000 \text{ kW}$

∴ Transmission efficiency  $= \frac{10000}{10273.105} \times 100 = 97.34 \%$


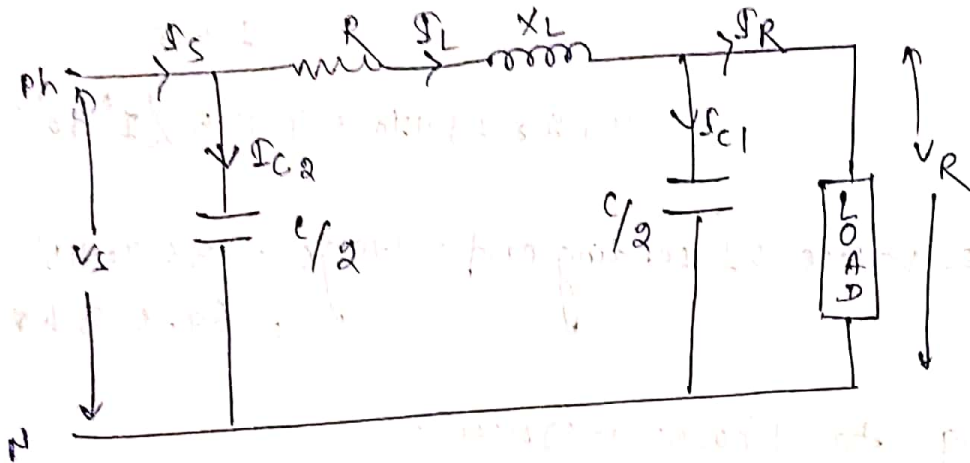
## Nominal $\pi$ -method

In this method, capacitance of each conductor (core line to neutral) is divided into two halves; one half being lumped at the sending end and the other half at the receiving end.



$S_P$  = load current / ph

$R$  = Resistance / ph


$X_L$  = inductive reactance / ph

$C$  = capacitance / ph

$\cos \phi_R$  = receiving end p.f. (lagging)

$V_S$  = sending end voltage / ph

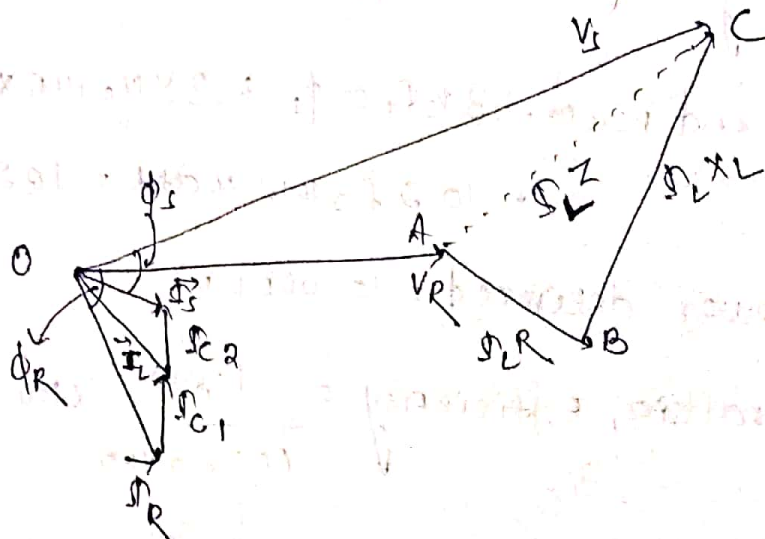Taking  $\vec{V}_R$  as the reference phasor.



$$\vec{V}_R = V_R + j0$$

$$\text{load current } \vec{I}_R = I_R (\cos \phi_R - j \sin \phi_R)$$

charging current at load end is

$$\vec{I}_{C1} = j\omega\left(\frac{C}{2}\right) \vec{V}_R = j\pi f C \vec{V}_R$$

$$\text{line current, } \vec{I}_L = \vec{I}_R + \vec{I}_{C1}$$

$$\begin{aligned} \text{sending end voltage, } \vec{V}_S &= \vec{V}_R + \vec{I}_L \vec{Z} \\ &= \vec{V}_R + \vec{I}_L (R + jX_L) \end{aligned}$$

charging current at the sending end is

$$\vec{I}_{C2} = j\omega\left(\frac{C}{2}\right) \vec{V}_S = j\pi f C \vec{V}_S$$

$$\text{sending end current } \vec{I}_S = \vec{I}_L + \vec{I}_{C2}$$

Q A 3 $\phi$ , 50 Hz, 150 km line has a resistance, inductive reactance and capacitive shunt admittance of 0.1 $\Omega$ , 0.5 $\Omega$  and  $3 \times 10^{-6}$  S per km per phase. If the line delivers 50 MW at 110 kV and 0.8 pf lagging, determine the sending end voltage and current. Assume a nominal  $\pi$  circuit for the line.

Ans

$$\text{Total resistance / ph} = R = 0.1 \times 150 = 15 \Omega$$

$$\text{Total reactance / ph} = X_L = 0.5 \times 150 = 75 \Omega$$


$$\text{capacitive admittance / ph} = Y = 3 \times 10^{-6} \times 150 = 45 \times 10^{-5} \text{ S}$$



Receiving end voltage / ph  $V_R = \frac{110 \times 10^3}{\sqrt{3}} = 63508 \text{ volts}$

load current  $I_R = \frac{50 \times 10^6}{\sqrt{3} \times 110 \times 10^3 \times 0.8} = 328 \text{ Amp}$

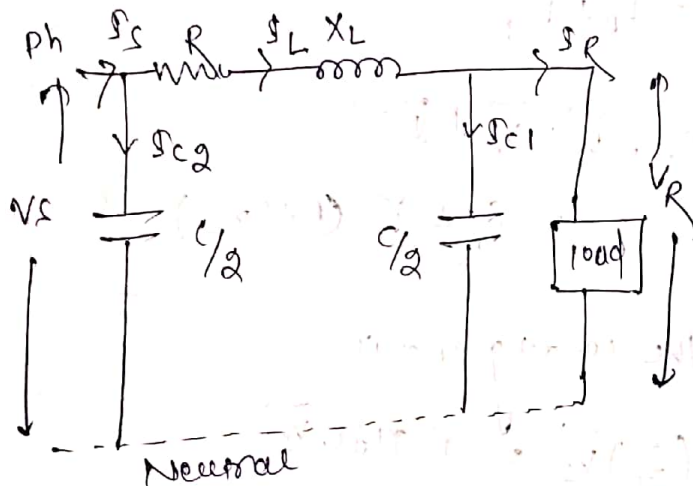$\cos \phi_R = 0.8 \quad \sin \phi_R = 0.6$



Taking Receiving end voltage as the reference phasor, we have

$\vec{V}_R = V_R + j0 = 63508 \text{ volts}$

load current  $\vec{I}_R = I_R (\cos \phi_R - j \sin \phi_R) = 328 (0.8 - j0.6) = 262.4 - j196.8$

charging current at the load end is

$\vec{I}_{C1} = \vec{V}_R j \frac{Y}{2} = 63508 \times j \frac{45 \times 10^{-6}}{2} = j14.3$

line current  $\vec{I}_L = \vec{I}_R + \vec{I}_{C1} = (262.4 - j196.8) + j14.3 = 262.4 - j182.5$

sending end voltage  $\vec{V}_s = \vec{V}_R + \vec{I}_L \vec{Z}$

$$= \vec{V}_R + \vec{I}_L (R + jX_L)$$
$$= 63508 + (262.4 - j182.5) (15 + j75)$$
$$= 63508 + 3936 + j19680 - j27375$$
$$= 67444 + j12305 = 69111 \angle 10.4^\circ$$

$$\therefore \text{line to line sending end voltage} = 82881 \times \sqrt{3} \\ = 143550 \text{ volt} \\ = 143.55 \text{ kV}$$

charging current at the sending end is

$$I_{C2} = j \vec{V}_S \frac{Y}{2} = (81131 + j16942.5) j \frac{45 \times 10^{-5}}{2} \\ = -3.81 + j18.25$$

$$\text{sending end current } \vec{I}_S = \vec{I}_L + \vec{I}_{C2} = (262.4 - j182.5) \\ + (-3.81 + j18.25)$$

$$= 258.6 - j164.25 \\ = 306.4 \angle -32.4^\circ \text{ Amp} \\ = 306.4 \text{ Amp}$$

sending end current  $I_S$



## Ch-5 EHV Transmission

### 5.1 EHV AC transmission

#### 5.1.1 Reasons for adoption of EHV AC transmission

##### ① Reduction of electrical losses

→ Line losses are reduced since line losses are inversely proportional to the transmission voltage.

$$I^2 R \propto \frac{1}{V}$$

##### ② Increase in transmission efficiency

Transmission efficiency increases because of reduction in line losses.

##### ③ Improvement of voltage regulation

→ Improvement of voltage regulation because of reduction of voltage drop.

##### ④ Reduction of conductor material Requirement.

→ Lesser conductor material is required because current is inversely proportional to voltage.

$$I \propto \frac{1}{V}$$

##### ⑤ Interconnection of power system in a large network can be possible.


##### ⑥ Increase in transmission capacity of the line.

#### 5.1.2 problems involved in EHV transmission

① corona loss and Radio interference.

② Heavy supporting structures and Erection difficulties.

③ Insulation Requirement.

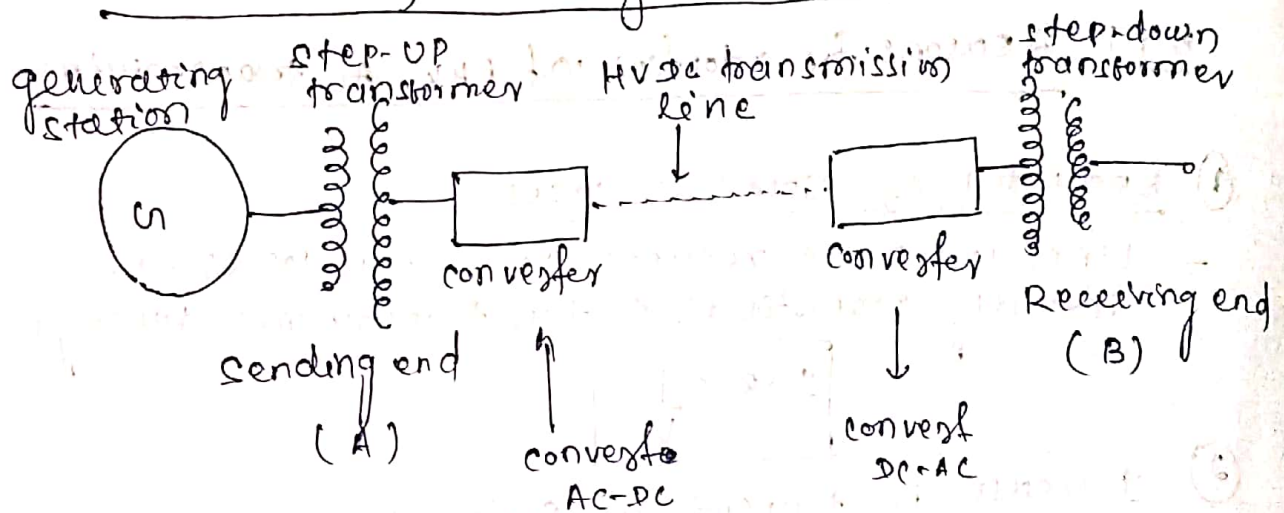Principle of HVDC system operation5.2.1 Advantages of HVDC transmission system

① Cheaper in cost! →

→ The HVDC transmission line requires two conductors while 'ac' system requires 3 conductors to carry power.

② No skin and ferranti effect.

③ Lower Transmission Losses! →

→ HVDC transmission system requires only two conductors and therefore, the power losses in a 'dc' line are lesser than the 'ac' line system.

④ Better Voltage Regulation! →

→ There is no inductance, hence the voltage drop due to inductive reactance does not exist in 'dc' transmission line. Thus voltage regulation is better in 'dc' system.

⑤ Ground can be used as a return conductor.

⑥ No charging current.

⑦ No switching transient



- ⑧ No stability limit.
- ⑨ It requires less space as compared to HVAC transmission with same voltage rating and size.
- ⑩ Lesser corona losses and Radio interference.

→ The corona loss is directly proportional to  $(f+25)$  where  $f$  is the frequency. So corona loss in 'dc' system are lesser than in 'ac' system.

### Limitation of HVDC transmission

- ① costly terminal equipments! →  
→ The HVDC transmission system require expensive components like converters, filters
- ② more maintenance of line insulators
- ③ converter control is quite complex.
- ④ Additional filters are required at various stages of HVDC transmission system. to remove harmonics.
- ⑤ DC circuit breaking system is costlier than ac circuit breaking system.

## (Ch-6) Distribution System

→ That part of power system which distribute electric power for local use is known as distribution system. Distribution system is nothing is a conductor.

→ It is generally consist of

- (i) Feeders
- (ii) distributors
- (iii) service connection / service main ✓

In general, the distribution system is the electrical system b/w the sub-station fed by the transmission system and the consumers meters.


### Feeders

- (i) A Feeder is a conductor which connects the substation to the area where power is to be distributed.
- (ii) Generally, no tapping are taken from the feeder so that current in it remains the same throughout
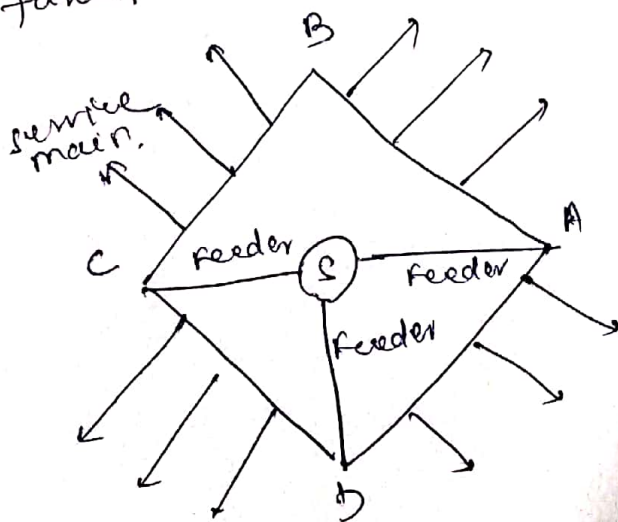
### Distributor

A distributor is a conductor from which tappings are taken for supply to the consumers.

→ The current is not constant because tappings are taken at various places along its length.



AB, BC, CD, AD  
are distributors.



## Service main :

A service main is generally a small cable which connects the distributor to the consumer's terminals.

## Classification of distribution systems

A distribution system may be classified according to :

(i) Nature of current : According to nature of current it is 2 types

- ① AC distribution system
- ② DC distribution system.

AC system is adopted for distribution of electric power as it is simpler and more economical than direct current method.

## (ii) Types of construction :

According to construction it is classified as

(a) overhead system

(b) under ground system.

\* overhead system is generally employed for distribution as it is 5 to 10 times cheaper than equivalent underground system.

## (iii) scheme of connection

According to scheme of connection, the distribution system may be classified as

(a) Radial system

(b) ring main system.

(c) interconnected system.

## Ac distribution (Nature of current)

Ac system is generally prefer in generation, transmission and distribution. The main behind that is (i) Alternating voltage can be conveniently changed in magnitude by using T/F.

(ii) High transmission and distribution voltage reduce the current in the conductor and the losses in line is less.

The a.c. distribution system is classified into


- (i) primary distribution system
- (ii) secondary distribution system

### ① primary distribution system

- This voltage is generally higher than utilization and handles large blocks of electrical energy than the average low-voltage consumers uses
- primary distribution voltages are 11 kV, 6.6 kV and 3.3 kV.
- primary distribution is carried out by 3-phase 3-wire system.

(industry, workshop, substation)



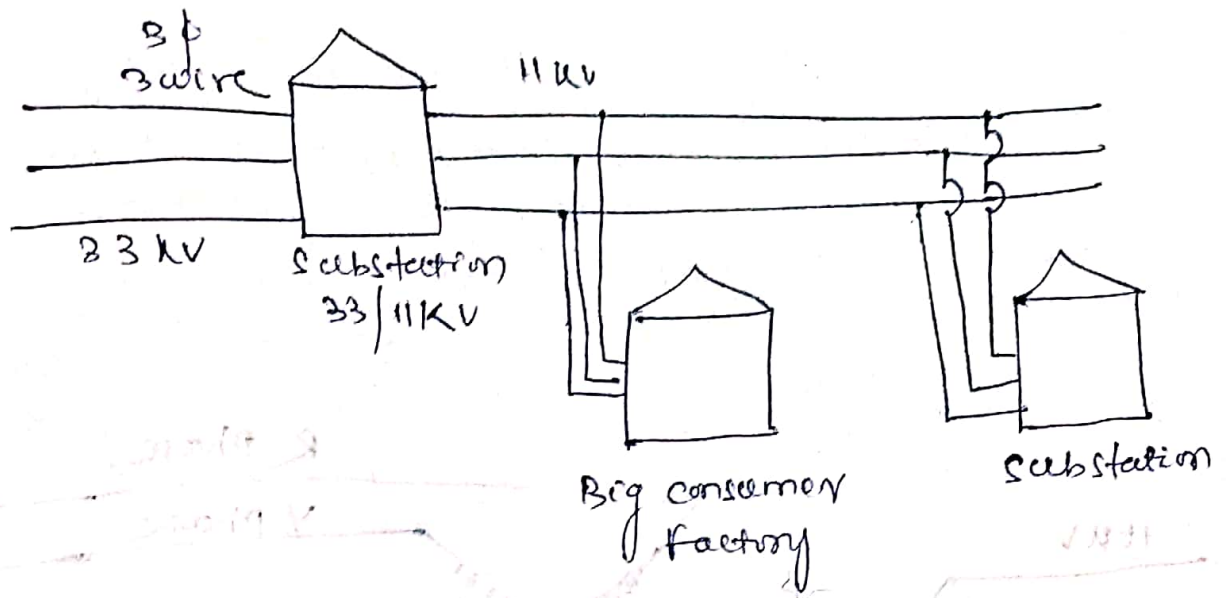


## (2) secondary distribution system

- This distribution system includes the range of voltage at which the ultimate consumer utilises the electrical energy delivered to him.
- The secondary distribution employs 400/230 volt. (3φ, 4 wire system)
- The primary distribution circuit delivered power to various substation, called distribution substation.
- \* The substations are situated near the consumer's localities and contain step down T/F.
- \* At distribution substation, the voltage is stepped down to 400 volt and the system is 3φ, 4 wire.

Phase - Phase  
Phase - Neutral  
400 volt

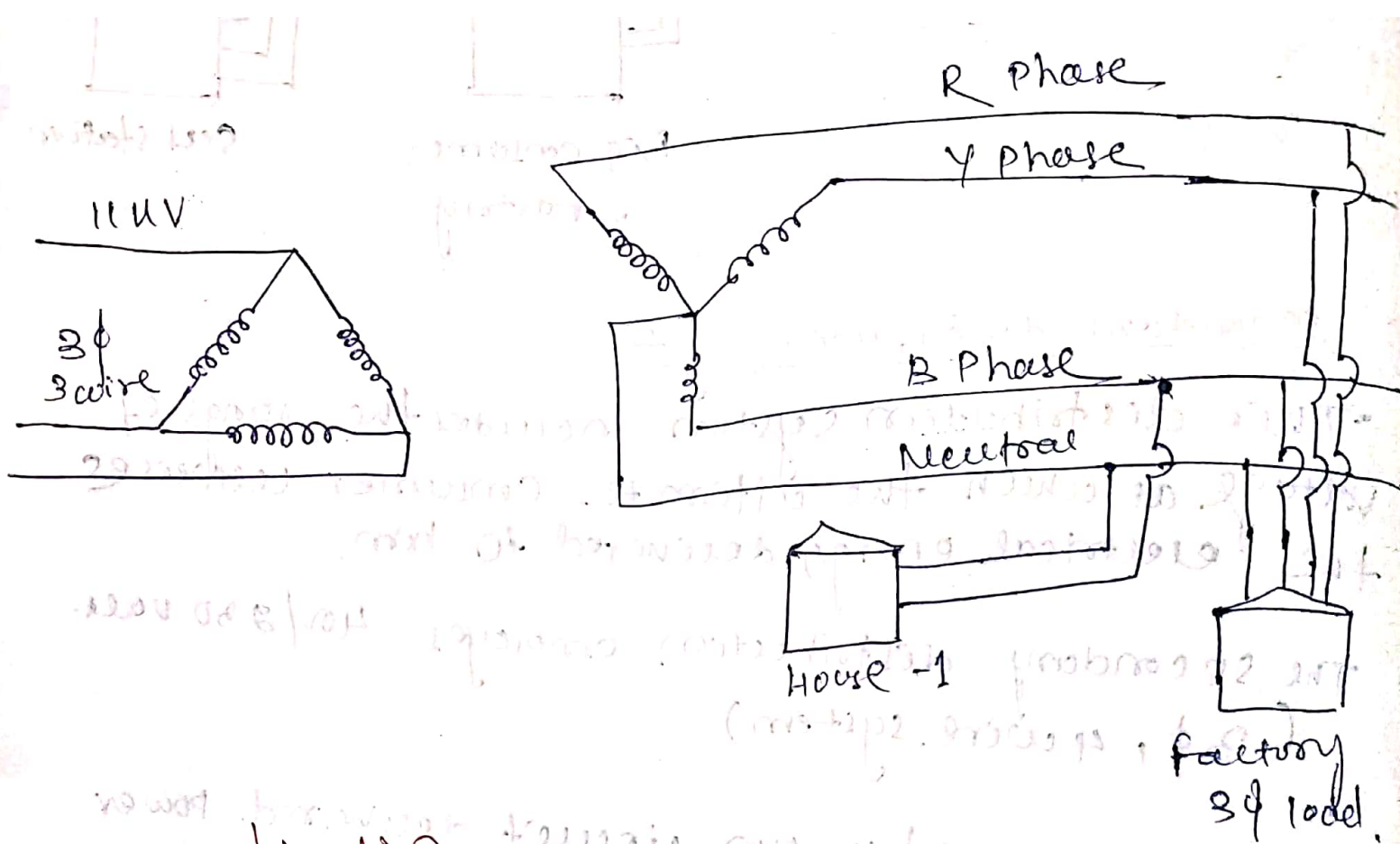230  
Phase, N → connected to load (1φ)  
3φ → connected to 3 Phase load, Motor



### D.C. distribution

For certain application, d.c. supply is absolutely necessary. D.C. supply is required for the certain operation of variable speed machinery (i.e. d.c. Motor).


→ The d.c. supply from the substation may be obtained in the form of (i) 2 wire or (ii) 3-wire for distribution.



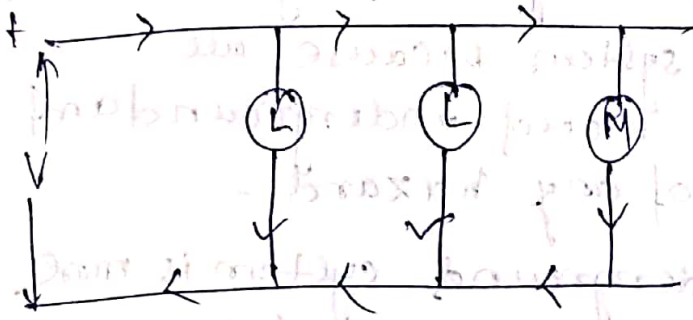
### (i) 2 wire d.c. system

It consists of 2 wire i.e. positive and negative

- The loads such as lamps, motors etc. are connected in parallel b/w the two wires.
- This system is never used for transmission purposes due to low efficiency but may be employed for distribution of d.c. power.



### (ii) 3 wire d.c. system

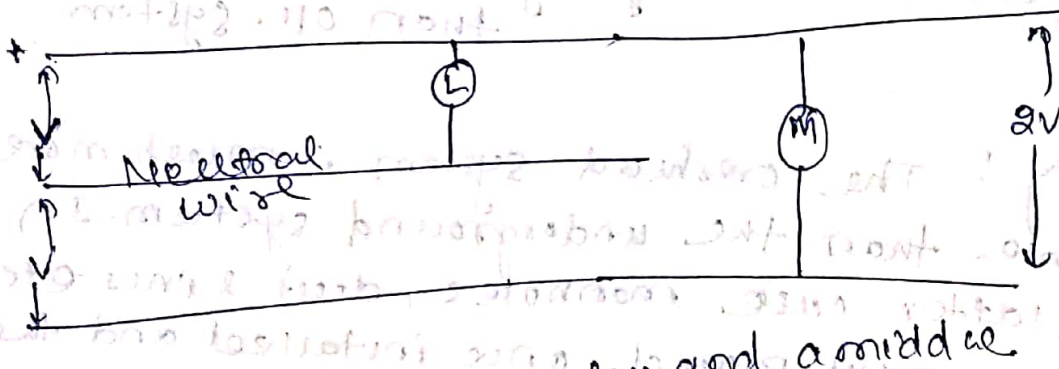

- It consists of two outer and a middle or neutral wire which is earthed at substation.

## Overhead versus underground system

\* overhead lines are generally mounted on wooden, concrete or steel poles which are arranged to carry distribution T/F in addition to the conductors.

\* The underground system uses conduits, cables and manholes under the surface of street and sidewalks.

\* the comparison b/w OH and U.G. cables:

(i) Public safety: The underground system is more safe than overhead system because all distribution wiring placed underground and are little chance of any hazard.

(ii) Initial cost: The underground system is more expensive due to the high cost of trenching, conduits, cables, manholes and other special equipments. U.G. system is 5 times more than OH system.

(iii)

Flexibility: The overhead system is much more flexible than the underground system. In the latter case manholes, duct lines etc. are permanently placed once installed and the load expansion can only be met by laying new lines. However on an overhead system, poles, wires, transformers etc, can be easily shifted to meet the changes in load conditions.

(iv) Faults: The chances of faults in underground system are very rare as the cables are laid underground and are generally provided with better insulation.



# Connection schemes of distribution system

## ① Radial system

All distribution of electrical energy is done by constant voltage system.


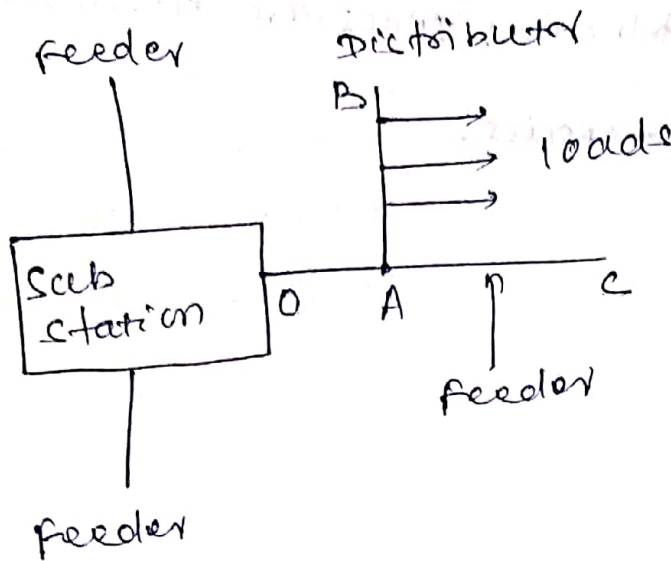


Fig. (1) (DC-distribution)

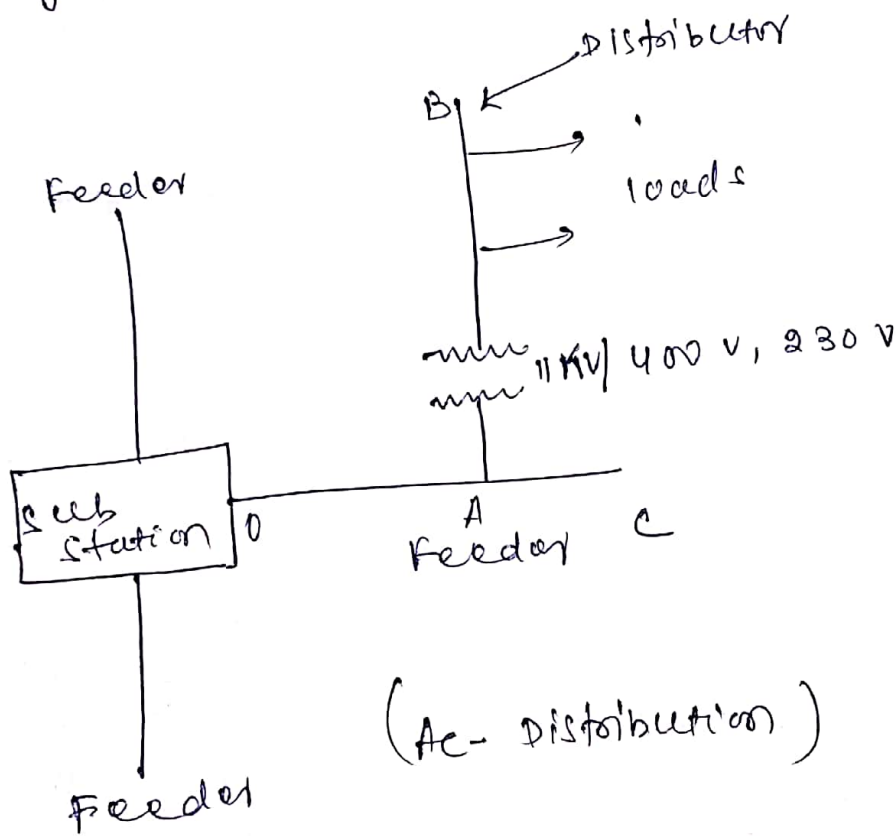

(AC-distribution)

(Fig-2)

- In this system, separate feeders radiate from a single sub-station and feed the distributors at one end only.
- In single line diagram OC is the feeder, supplies a distributor AB at point A.

→ The radial system is employed only when power is generated at low voltage and the substation is located at the centre of the load.

Advantages ① simplest distribution. ckt & lowest initial cost.


disadvantages ① The end of the distributor nearest to the feeding point will be heavily loaded.

② The consumers are dependent on a single feeder and single distributor. Therefore, any fault on the feeder or distributor cuts off supply to the consumers who are on the side of the fault away from the substation.

③ The consumers at the distant end of the distributor would be subjected to serious voltage fluctuation when the load on the distributor changes.

\* Due to these limitations, this system is used for short distance only.

## ② Ring mains system

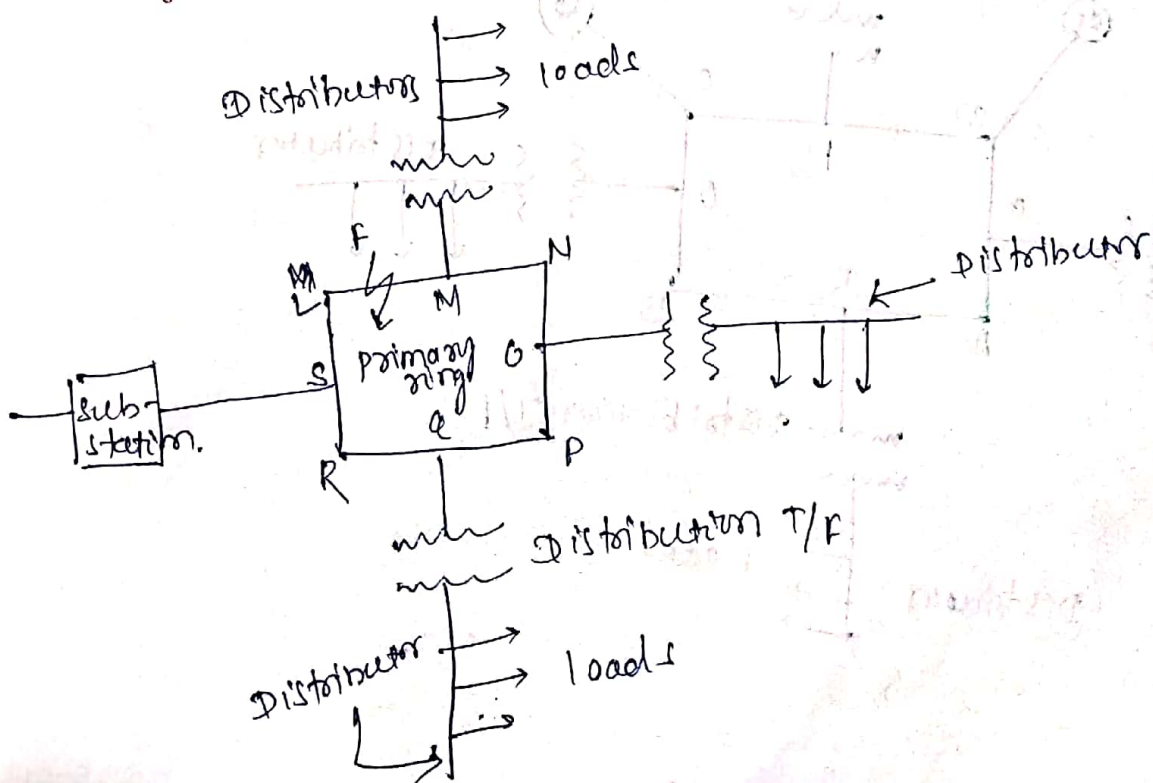




- In this system, the primaries of distribution T/F form a loop. The loop cut starts from the sub-station bus-bars, make a loop through the area to be served, and returns to the substation.
- In the single line diagram LMNOPQRS form a closed feeder.
- Then the distributors are tapped from different point M, O & Q of the feeder through distribution T/F.

### Advantages

- There are less voltage fluctuation at consumer's terminals.
- The system is very reliable as each distributor is fed through two-feeders. In the event of fault on any section of the feeder, The continuity of supply is maintained.

### Interconnected system

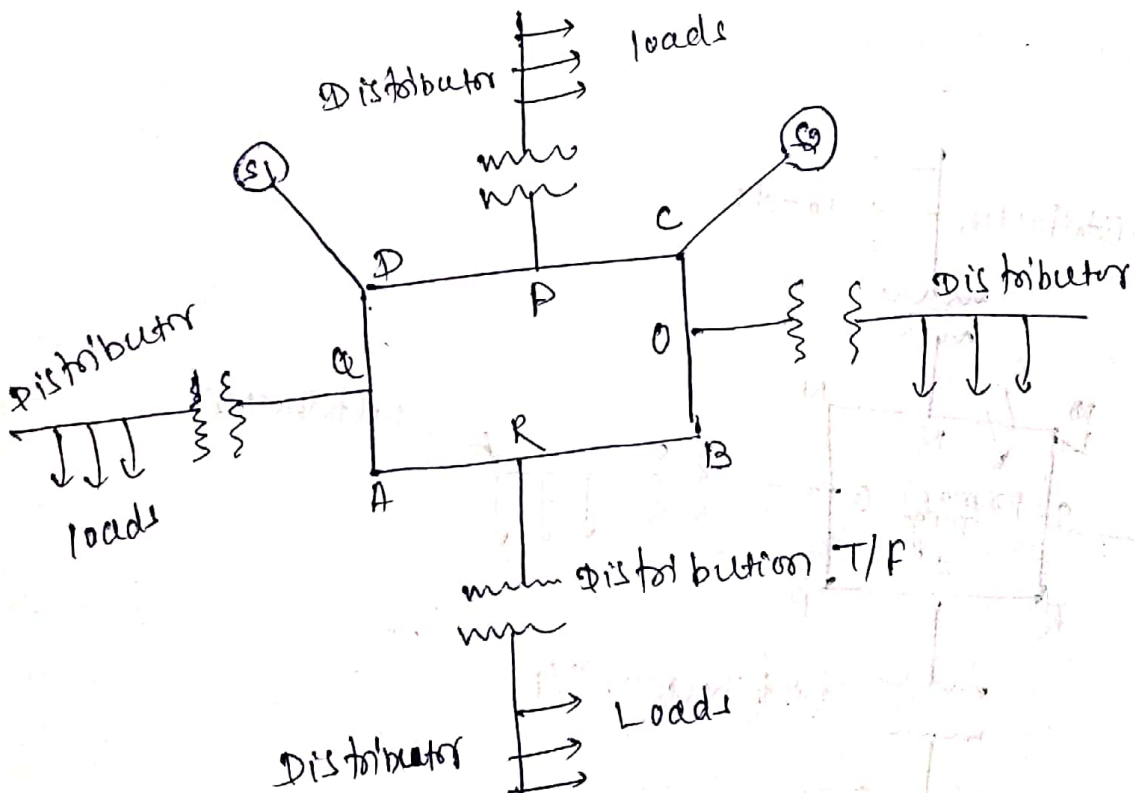

- when the feeder ring is energized by two or more than two generating station or sub-station, it is called inter-connected system.
- In single line diagram, the closed feeder ring ABCD is supplied by two substations  $S_1$  and  $S_2$  at point 'b' and 'c' respectively.
- distributors are connected to points O, P, Q, and R of the feeder ring through distribution T/F.

### Advantages

- It increases the service reliability.
  - Any area fed from one generating station during peak load hours can be fed from the other generating station.
- This reduces reserve power capacity and increase efficiency of the system.



## DC distribution system

However, for certain applications, DC supply is absolutely necessary. For example, DC supply is required for the operation of variable speed machinery (e.g. DC motors), electrochemical work and electric traction.

→ For this purpose AC power is converted into DC power at the sub-station by using converting machinery e.g. mercury are rectifiers, rotary converters and motor-generator sets.


→ The DC supply from the sub-station is conveyed to the required places for distribution.

## Types of D.C Distributors

The most general method of classifying d.c distributors is the way they are fed by the feeders. On this basis, d.c distributors are classified as:

- ① Distributor fed at one end
- ② Distributor fed at both end
- ③ Ring distributor

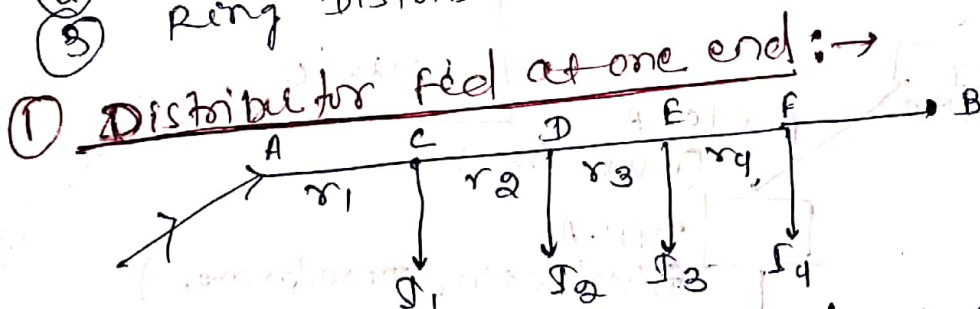\* It is easy to see that the minimum potential will occur at point 'F' which is furthest from the feeding point A



Let  $r_1, r_2, r_3$  &  $r_4$  be the resistance of both wires (go & return) of the sections AC, CD, DE, EF of the distributor respectively.

current fed from point A =  $I_1 + I_2 + I_3 + I_4$

current in section AC =  $I_1 + I_2 + I_3 + I_4$

current in section CD =  $I_2 + I_3 + I_4$

current in section DE =  $I_3 + I_4$

current in section EF =  $I_4$

So Total voltage drop in distributor

$$= r_1(I_1 + I_2 + I_3 + I_4) + r_2(I_2 + I_3 + I_4) + r_3(I_3 + I_4) + r_4 I_4$$

voltage drop in section AC =  $r_1(I_1 + I_2 + I_3 + I_4)$

CD =  $r_2(I_2 + I_3 + I_4)$

DE =  $r_3(I_3 + I_4)$

EF =  $r_4 I_4$

Q: A two wire DC distributor cable AB is 2 km long and supplies loads of 100A, 150A, 200A and 50 Amp situated 500m, 1000m, 1600m and 2000m from the feeding point A. Each conductor has a resistance of  $0.01 \Omega$  per 1000 m. Calculate the p.d at each load point if a p.d of 300V is maintained at point A.

Resistance per 1000 m of distributor  
 $2 \times 0.01 = 0.02 \Omega$

Resistance of section AC,  $R_{AC} = 0.02 \times \frac{500}{1000}$   
 $= 0.01 \Omega$

Resistance of section CD,  $R_{CD} = 0.02 \times \frac{500}{1000} = 0.01 \Omega$

Resistance of section DE,  $R_{DE} = 0.02 \times \frac{600}{1000} = 0.012 \Omega$


Resistance of section EB,  $R_{EB} = 0.02 \times \frac{400}{1000} = 0.008 \Omega$

$I_{EB} = 50 \text{ A}$

$I_{DE} = 50 + 200 = 250 \text{ A}$

$I_{CD} = 250 + 150 = 400 \text{ A}$

$I_{AC} = 400 + 100 = 500 \text{ A}$

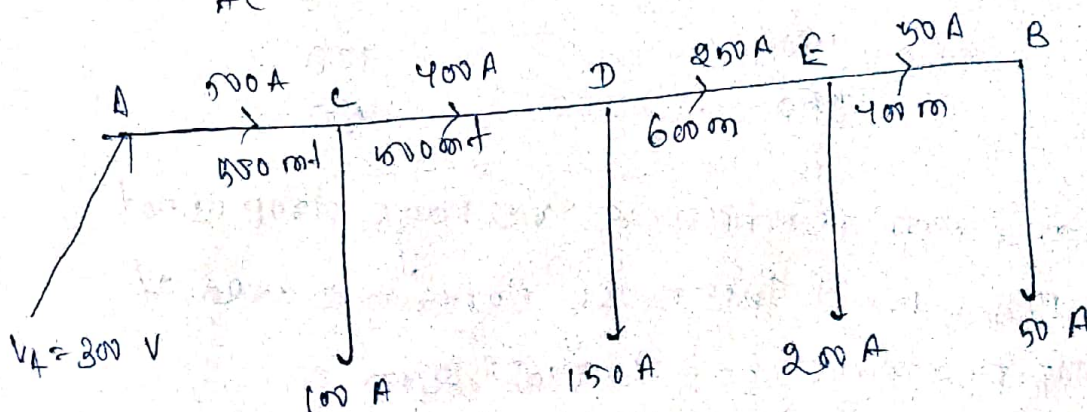



P.D at load point C,  $V_C = \text{voltage at A} - \text{voltage drop in AC}$

$$= V_A - I_{AC} R_{AC}$$

$$= 300 - 500 \times 0.01 = 295 \text{ V}$$

P.D at load point D,  $V_D = V_C - I_{CD} R_{CD}$

$$= 295 - 400 \times 0.01 = 291 \text{ V}$$

P.D at load point E,  $V_E = V_D - I_{DE} R_{DE}$

$$= 291 - 250 \times 0.012 = 288 \text{ V}$$

P.D at load point B,  $V_B = V_E - I_{EB} R_{EB}$

$$= 288 - 50 \times 0.008 = 287.6 \text{ V}$$

Q.2 A 2-wire d.c distributor AB is 300 m long. It is fed at point A. The various loads and their positions are given below.

| At point | distance from A in m. | Concentrated load in Amps |
|----------|-----------------------|---------------------------|
|          | 40                    | 30                        |
| C        | 100                   | 40                        |
| D        | 150                   | 100                       |
| E        | 250                   | 50                        |
| F        |                       |                           |

If the maximum permissible voltage drop is not to exceed 10 V, find the cross-sectional area of the distributor. Take  $\rho = 1.78 \times 10^{-8} \Omega \text{ m}$ .

Ans

suppose that resistance of 100m length of the distributor is  $r$  ohms.


Then resistance of various sections of the distributor is

$$R_{AC} = 0.4r \Omega$$

$$R_{EF} = 1r \Omega$$

$$R_{CD} = 0.6r \Omega$$

$$R_{DE} = 0.5r \Omega$$

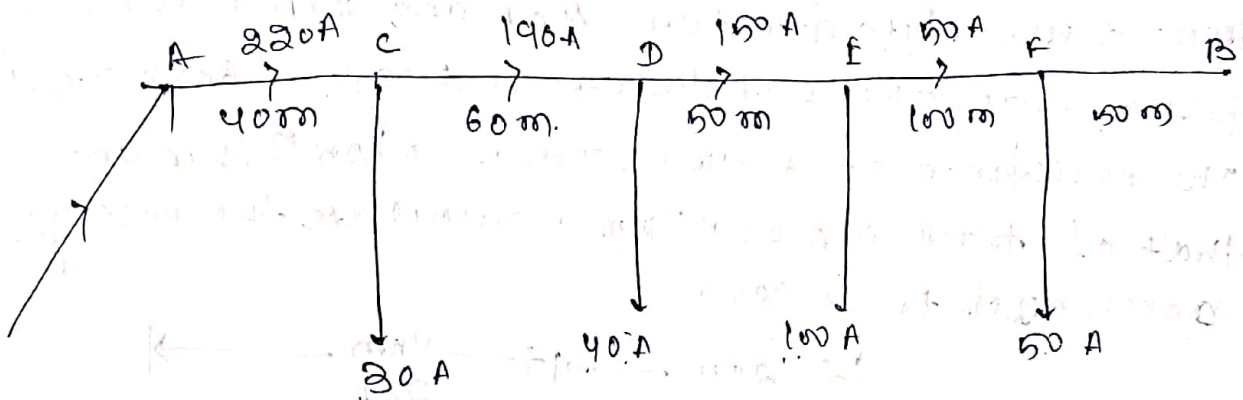

$$I_{AC} = 220 \text{ Amp}$$

$$I_{DE} = 150 \text{ Amp}$$

$$I_{CD} = 190 \text{ Amp}$$

$$I_{EF} = 50 \text{ Amp}$$

Total voltage drop over the distributor

$$\begin{aligned} &= I_{AC} R_{AC} + I_{CD} R_{CD} + I_{DE} R_{DE} + I_{EF} R_{EF} \\ &= 220 \times 0.4r \Omega + 190 \times 0.6r + 150 \times 0.5r \\ &\quad + 50 \times r \end{aligned}$$

$$= 327r$$

As the maximum permissible drop in the distributor is 10 volt.

$$10 = 327r \quad \checkmark$$



$$r = 10/327 = 0.03058 \Omega \checkmark$$

X. sectional area of conductor

$$(a) = \frac{\rho l}{r/2} = \frac{1.78 \times 10^{-8} \times 100}{\frac{0.03058}{2}} = 116.4 \times 10^{-6} \text{ m}^2$$


$$= 1.164 \text{ cm}^2$$

$$\frac{\rho}{2} = \frac{\rho L}{A}$$

$$A = \frac{\rho L}{(\rho/2)}$$

③

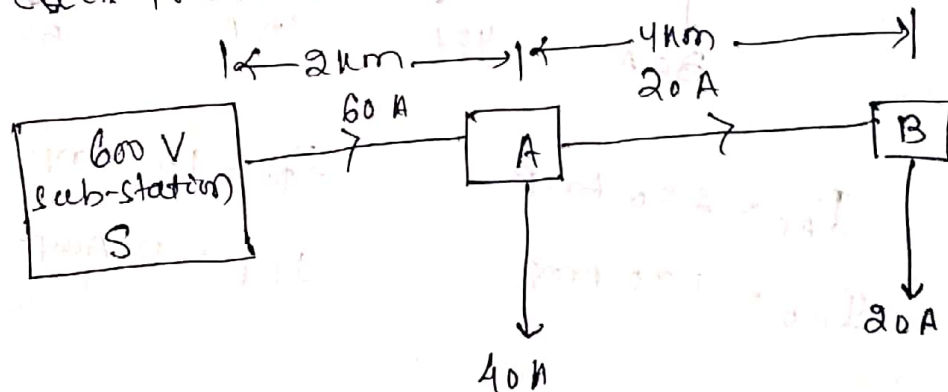Two tram cars (A & B) 2 km and 4 km away from a sub-station return 40 A and 20 A respectively to the rails. The substation voltage is 600 V d.c. The resistance of trolley wire is  $0.25 \Omega/\text{km}$  and that of track is  $0.03 \Omega/\text{km}$ . Calculate the voltage across each tram car.



Resistance of trolley wire and track/km  
 $= 0.25 + 0.03 = 0.28 \Omega$

current in section SA =  $40 + 20 = 60 \text{ A}$

current in section AB =  $20 \text{ A}$

voltage drop in section SA =  $60 \times 0.28 \times 2 = 33.6 \text{ V}$

voltage drop in section AB =  $20 \times 0.28 \times 4 = 22.4 \text{ V}$

voltage across tram A =  $600 - 33.6 = 566.4 \text{ V}$

voltage across tram B =  $566.4 - 22.4 = 544 \text{ V}$

distribution fed at both ends

concentrated loading


① Two ends fed with equal voltages! →

② Two ends fed with unequal voltages! →

Whenever possible, it is desirable that a long distributor should be fed at both ends instead of at one end only. Since total voltage drop can be considerably reduced without increasing the cross-section of the conductor. The two ends of the distributor may be supplied with ① equal voltage  
② unequal voltage.

① Two ends fed with equal voltages! →

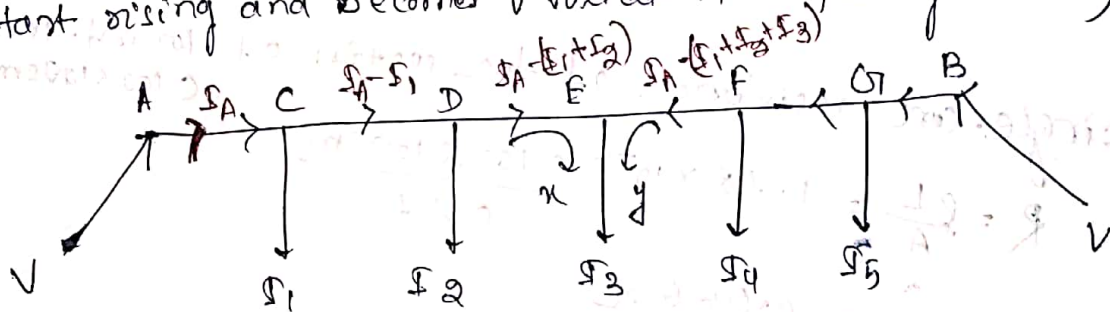Let a AB distributor fed at both ends with equal voltage 'V' with and having concentrated load  $I_1, I_2, I_3, I_4$  and  $I_5$  at points C, D, E, F & G respectively. (As we move away from one of the feeding points 'A', P.d. goes on decreasing till it reaches the minimum value at some load point say E, and then again start rising and becomes 'V' volt at other feeding point B)



The current  $I_1$  &  $I_2$  supplies from feeding point 'A'

The load current  $I_4$  &  $I_5$  supplies from feeding point 'B'

and the load current  $I_3$  supplies from both feeding point 'A' & 'B'

$$I_3 = x + y$$

∴ at point of minimum potential (E), the current comes from both ends of the distributor.

$$I_{AC} = I_A, I_{CD} = I_A - I_1, I_{DE} = I_A - (I_1 + I_2)$$


$$I_{EF} = I_A - (I_1 + I_2 + I_3), I_{FG} = I_A - (I_1 + I_2 + I_3 + I_4)$$



→ Voltage at point 'B' is

$$V_B = V_A - [I_{AC} R_{AC} + I_{CD} R_{CD} + I_{DE} R_{DE} + I_{EF} R_{EF} + I_{FB} R_{FB} + I_{NB} R_{NB}]$$
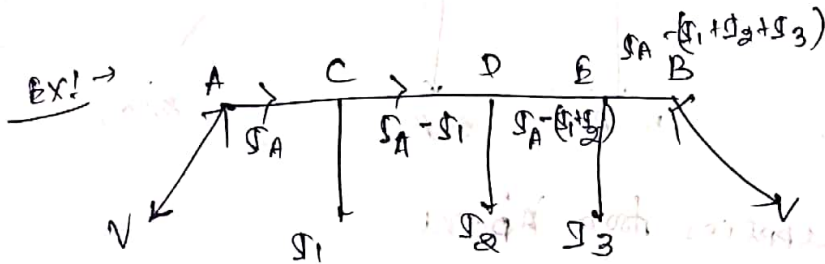
$$\Rightarrow V_B = V_A - \left\{ [I_A R_{AC}] + (I_A - I_1) R_{CD} + [I_A - (I_1 + I_2)] R_{DE} + [I_A - (I_1 + I_2 + I_3)] R_{EF} + [I_A - (I_1 + I_2 + I_3 + I_4)] R_{FB} + [I_A - (I_1 + I_2 + I_3 + I_4 + I_5)] R_{NB} \right\}$$



$$I_{AC} = I_A$$

$$I_{CD} = I_A - I_1$$

$$I_{DE} = I_A - (I_1 + I_2)$$


$$I_{EB} = I_A - I_1 - I_2 - I_3$$

$$= I_A - (I_1 + I_2 + I_3)$$

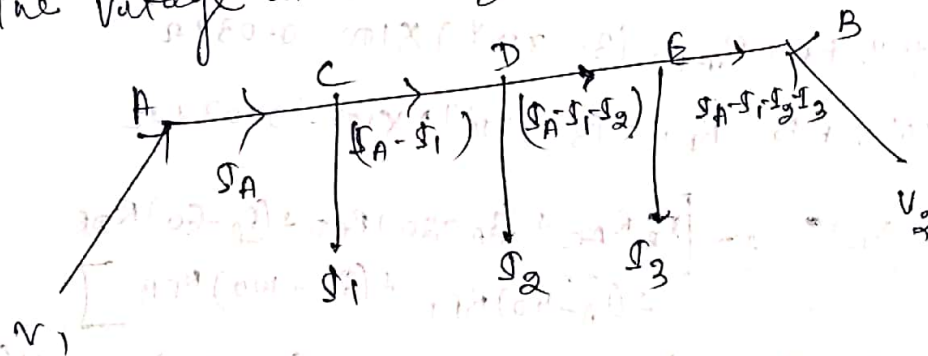
Q2) Two end feeds with unequal voltages! →

Let AB distributor fed with unequal voltage.  
At point 'A' it is fed with  $V_1$  volt and  
B is fed with  $V_2$  volt

The voltage at B is  $V_B = V_1 - (I_A R_{AC} + I_{CD} R_{CD} + I_{DE} R_{DE} + I_{EB} R_{EB})$



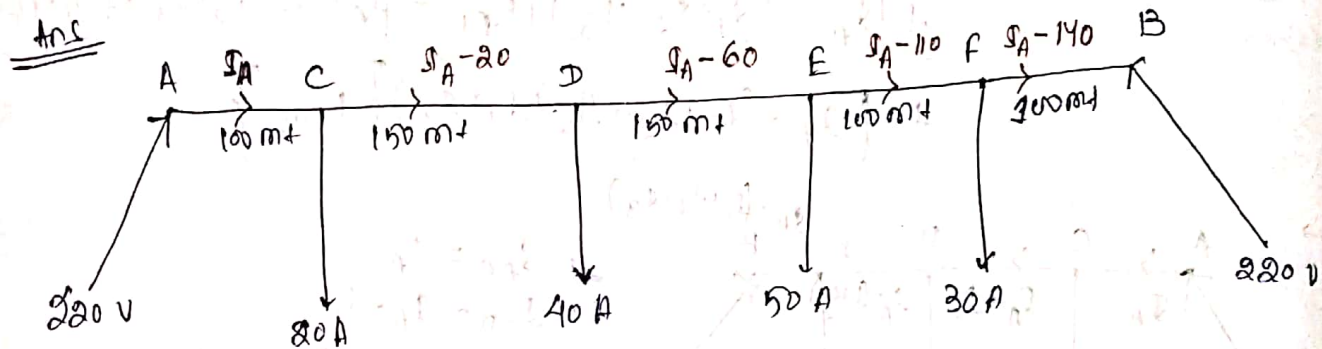Q.1 A 2-wire, d.c. street mains AB, 600 m long is fed from both ends at 220V. Loads of 20A, 40A, 50A and 30A are tapped at distance of 100m, 250m, 400m and 500m from the end A respectively. If the area of X-section of distributor is  $1 \text{ cm}^2$ . find the minimum consumer voltage.  
Take  $\rho = 1.7 \times 10^{-6} \Omega \text{ cm}$ .



Let  $I_A$  Amp current supplies from A point

Resistance of 1m length of distributor (go & Return)

$$R = \frac{2\rho L}{A} = \frac{2 \times 1.7 \times 10^{-6} \times 100 \text{ cm}}{1 \text{ cm}^2} = 3.4 \times 10^{-4} \Omega$$

Resistance of section AC,  $R_{AC} = (3.4 \times 10^{-4}) \times 100 = 0.034 \Omega$

Resistance of section CD,  $R_{CD} = (3.4 \times 10^{-4}) \times 150 = 0.051 \Omega$

Resistance of section DE,  $R_{DE} = (3.4 \times 10^{-4}) \times 150 = 0.051 \Omega$

Resistance of section EF,  $R_{EF} = (3.4 \times 10^{-4}) \times 100 = 0.034 \Omega$

Resistance of section FB,  $R_{FB} = (3.4 \times 10^{-4}) \times 100 = 0.034 \Omega$

Voltage at 'B'  $V_B = V_A - [I_A R_{AC} + (I_A - 20) R_{CD} + (I_A - 60) R_{DE} + (I_A - 110) R_{EF} + (I_A - 140) R_{FB}]$


$$220 = 220 - [0.034 I_A + 0.051 (I_A - 20) + 0.051 (I_A - 60) + 0.034 (I_A - 110) + 0.034 (I_A - 140)]$$

$$\Rightarrow 220 = 220 - [0.204 I_A - 12.58]$$

$$\Rightarrow 0.204 I_A = 12.58$$
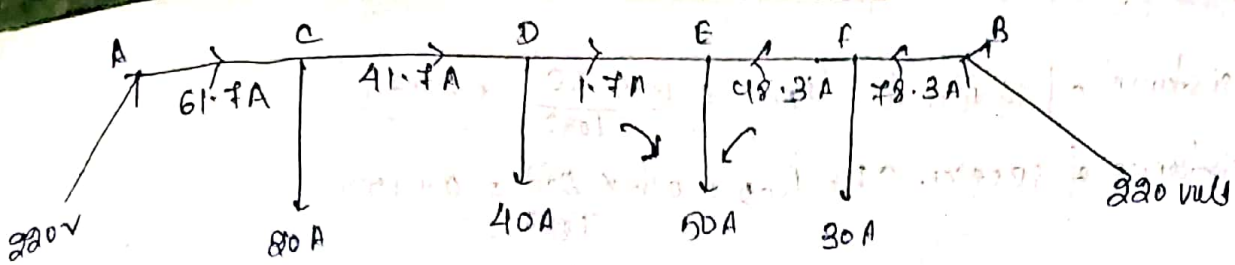
$$\Rightarrow I_A = \frac{12.58}{0.204} = 61.7 \text{ Amp}$$





'E' is the point of minimum potential.

∴ minimum consumer voltage

$$V_E = V_A - (I_{AC} R_{AC} + I_{CD} R_{CD} + I_{DE} R_{DE})$$

$$= 220 - (61.7 \times 0.034 + 41.7 \times 0.051 + 1.7 \times 0.051)$$

$$= 220 - 4.31$$

$$= 215.69 \text{ volt}$$

Q.2

A 2-wire DC distributor AB is fed from both ends. At feeding point A, the voltage is maintained at 220V and at B 235V. The total length of the distributor is 200 mt and loads are tapped off as under:


- 25A at 50 mt. from A
- 50A at 75 mt. from A
- 30A at 100 mt. from A
- 40A at 150 mt. from A

The resistance per kilometre of one conductor is 0.3Ω calculate;  
 (i) currents in various sections of the distributor

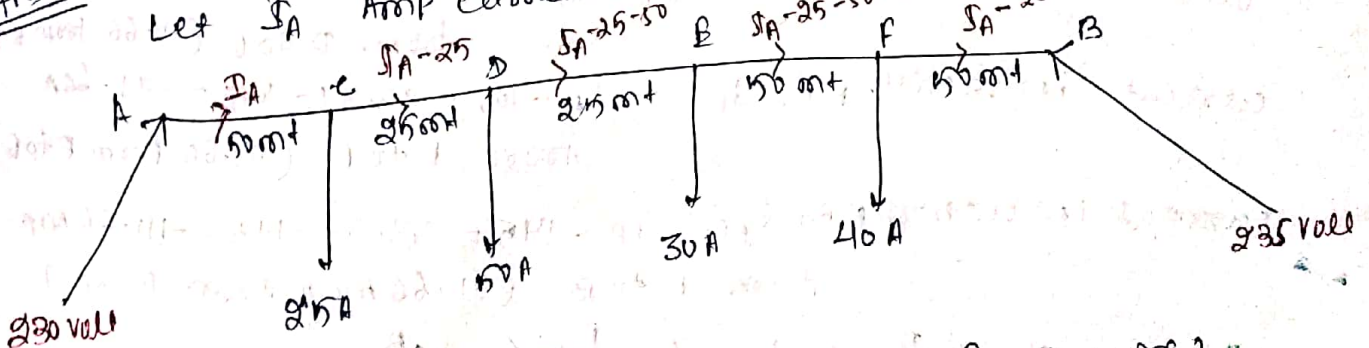(ii) minimum voltage and the point at which it occurs.

Ans

Let  $I_A$  Amp current is supplied from feeding point A.



Resistance of 1000 mt. length of distributor (both wire)  
 $= 2 \times 0.3 = 0.6 \Omega$

Resistance of section AC,  $R_{AC} = 0.6 \times \frac{50}{1000} = 0.03 \Omega$

Resistance of section CD,  $R_{CD} = 0.6 \times \frac{25}{1000} = 0.015 \Omega$

Resistance of section DE,  $R_{DE} = 0.6 \times \frac{25}{1000} = 0.015 \Omega$

Resistance of section EF,  $R_{EF} = 0.6 \times \frac{50}{1000} = 0.03 \Omega$

Resistance of section FB,  $R_{FB} = 0.6 \times \frac{50}{1000} = 0.03 \Omega$

Voltage at point 'B'  $V_B = V_A - [I_A R_{AC} + (I_A - 25) R_{CD} + (I_A - 75) R_{DE} + (I_A - 105) R_{EF} + (I_A - 145) R_{FB}]$

$$\rightarrow 235 = 230 - [0.03 I_A + 0.015 (I_A - 25) + 0.015 (I_A - 75) + 0.03 (I_A - 105) + 0.03 (I_A - 145)]$$

$$\rightarrow 235 = 230 - [0.12 I_A - 9]$$

$$\Rightarrow I_A = \frac{239 - 235}{0.12} = 33.34 \text{ Amp}$$


(i) current in section AC,  $I_{AC} = I_A = 33.34 \text{ Amp}$

current in section CD,  $I_{CD} = I_A - 25 = 33.34 - 25 = 8.34 \text{ Amp}$

current in section DE,  $I_{DE} = I_A - 75 = 33.34 - 75 = -41.66 \text{ Amp}$   
from D to E (41.66 Amp from E to D)

current in section EF,  $I_{EF} = I_A - 105 = 33.34 - 105 = -71.66 \text{ Amp}$   
from E to F (71.66 Amp from F to E)

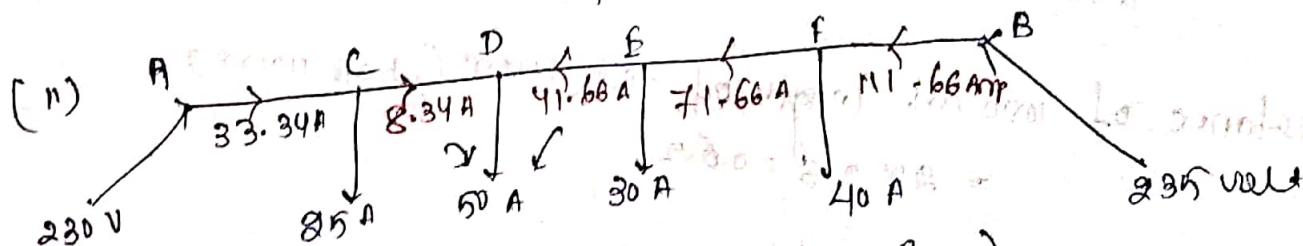current in section FB,  $I_{FB} = I_A - 145 = 33.34 - 145 = -111.66 \text{ Amp}$   
from F to B (111.66 Amp from B to F)



Voltage at D,  $V_D = V_A - [I_{AC} R_{AC} + I_{CD} R_{CD}]$   
 $= 230 - (33.34 \times 0.03 + 8.34 \times 0.015)$   
 $= 230 - 1.125 = 228.875 \text{ Volt}$



## Ring distributor

- (i) A distributor arranged to form a closed loop and fed at one or more point is called a ring distributor.
- (ii) Such a distributor starts from one point, makes a loop through the area to be served, and return to original point.

Advantages!  $\rightarrow$  The main advantages of ring distributor is that by proper choice in the no. of feeding points, great economy in copper can be affected.

\* Ring distributor is equivalent to a straight distributor fed at both ends with equal voltages.

Q.1

A 2 wire d.c. ring distributor is 300 m long and is fed at 240 V at point 'A'. At point B, 150 m from A, a load of 120 Amp is taken and at 'C', 100 m in the opposite direction, a load of 80 Amp is taken. If the resistance per 100 m of single conductor is  $0.03 \Omega$ , find,

- (i) current in each section of distributor  
(ii) voltage at point B and 'C'


Solution

Resistance per 100 m of distributor  
 $= 2 \times 0.03 = 0.06 \Omega$

Resistance of section (AB)  $R_{AB} = 0.06 \times \frac{150}{100} = 0.09 \Omega$

Resistance of section BC,  $R_{BC} = 0.06 \times \frac{50}{100} = 0.03 \Omega$

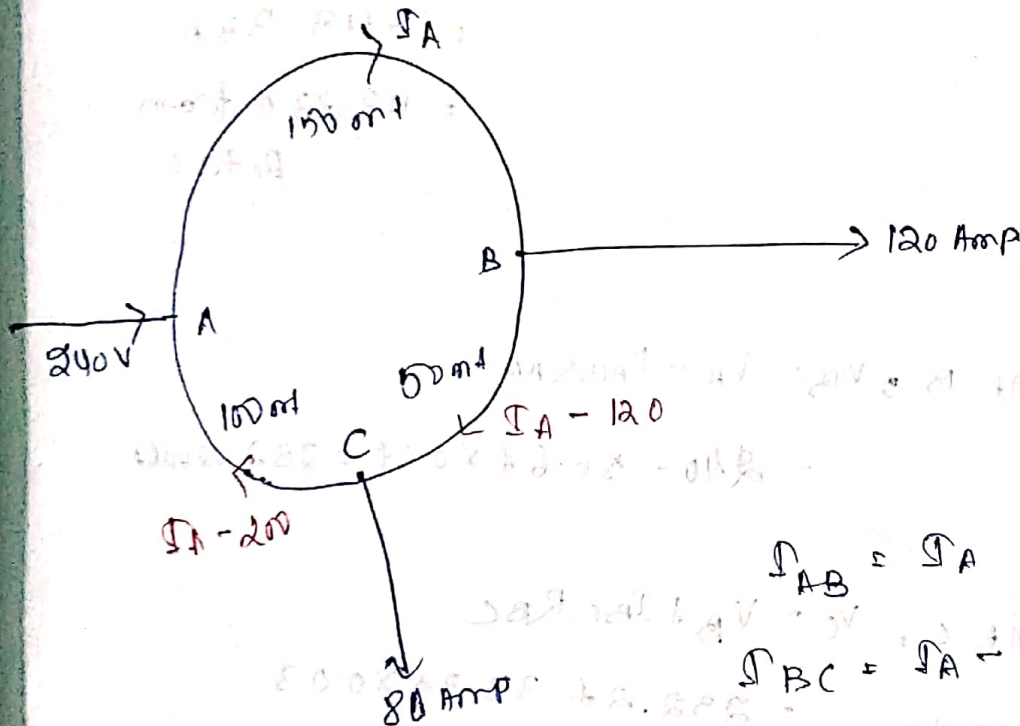Resistance of section CA,  $R_{CA} = 0.06 \times \frac{100}{100} = 0.06 \Omega$



$$I_{AB} = I_A$$

$$I_{BC} = I_A - 120$$

$$I_{CA} = I_A - 200$$

According to Kirchhoff's voltage law, the voltage drop in the closed loop ABCA is zero i.e.

$$I_{AB} R_{AB} + I_{BC} R_{BC} + I_{CA} R_{CA} = 0$$

$$\Rightarrow 0.09 I_A + 0.03 (I_A - 120) + 0.06 (I_A - 200) = 0$$

$$\Rightarrow -0.18 I_A = 15.6$$


$$\Rightarrow I_A = \frac{15.6}{-0.18} = -86.67 \text{ Amp}$$




current at section AB,  $I_{AB} = I_A = 86.64 \text{ A}$  from A to B  
 current at section BC,  $I_{BC} = I_A - I_B = 86.64 - 10 = 76.64 \text{ A}$   
 $= 76.64 \text{ A}$   
 $= 76.64 \text{ A}$   
 current at section CD,  $I_{CD} = I_A - 20 = 86.64 - 20 = 66.64 \text{ A}$   
 $= 66.64 \text{ A}$   
 $= 66.64 \text{ A}$  from B to C

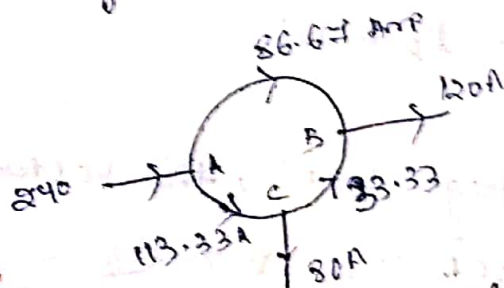(ii) voltage at point B,  $V_B = V_A - I_{AB} R_{AB}$   
 $= 240 - 86.64 \times 0.09 = 232.2 \text{ V}$

voltage at point C,  $V_C = V_B - I_{BC} R_{BC}$   
 $= 232.2 + 76.64 \times 0.03$   
 $= 234.6 \text{ V}$



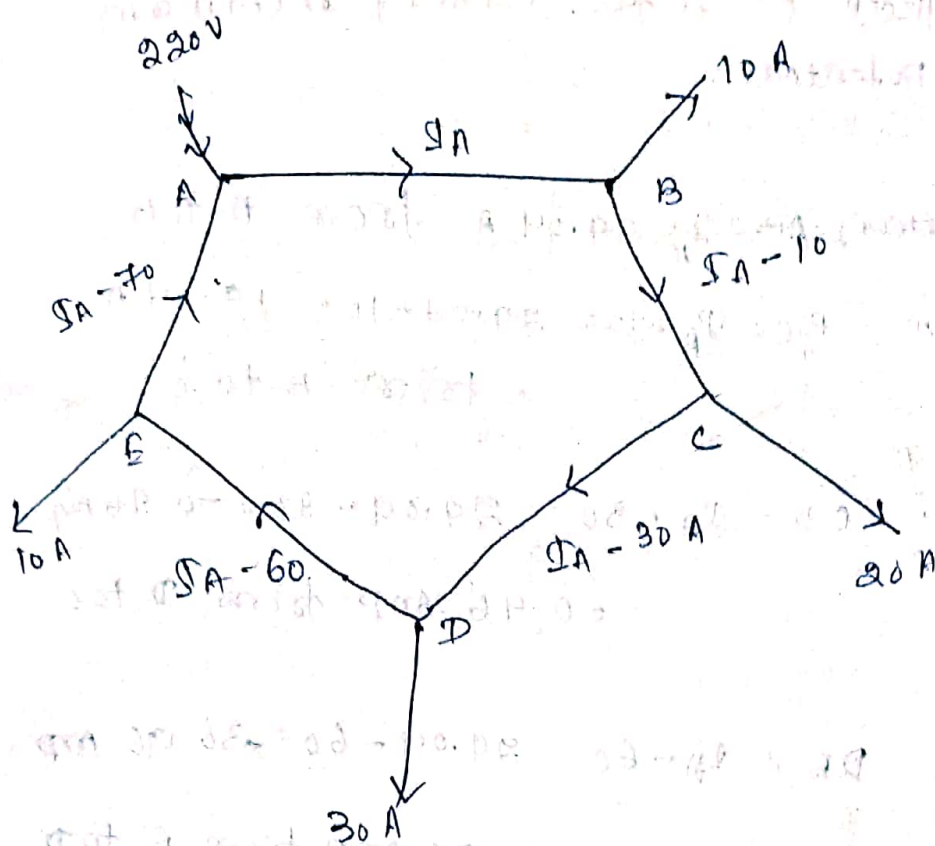Q.2  
 A wire, d.c. distributor ABCDEA in the form of a ring main is fed at point A at 240 V and is located as under:  
 10 A at B, 20 A at C, 30 A at D and 10 A at E  
 The resistance of various sections (go and return) are  $AB = 0.1 \Omega$ ,  $BC = 0.05 \Omega$ ,  $CD = 0.01 \Omega$ ,  $DE = 0.025 \Omega$  and  $EA = 0.075 \Omega$   
 Determine (i) The point of minimum potential  
 (ii) current in each section of distributor



$$I_{EA} = I_A - 70$$

$$I_{CD} = I_A - 30$$

$$I_{AB} = I_A$$

$$I_{DE} = I_A - 60$$

$$I_{BC} = I_A - 10$$

$$R_{EA} = 0.075 \Omega$$

$$R_{CD} = 0.01 \Omega$$

$$R_{AB} = 0.01 \Omega$$

$$R_{DE} = 0.025 \Omega$$

$$R_{BC} = 0.05 \Omega$$

i) According to KVL, the sum of the closed loop is zero i.e.

$$I_{AB} R_{AB} + I_{BC} R_{BC} + I_{CD} R_{CD} + I_{DE} R_{DE} + I_{EA} R_{EA} = 0$$

$$\Rightarrow 0.01 I_A + 0.05 (I_A - 10) + 0.01 (I_A - 30) + 0.025 (I_A - 60) + 0.075 (I_A - 70) = 0$$

$$\Rightarrow 0.26 I_A = 7.55$$

$$= 29.04 \text{ amp}$$

$$\Rightarrow I_A = 7.55 / 0.26$$



It is clear that 'c' is the point of minimum potential.

(11)


Current in section AB =  $I_A = 29.04$  A from A to B

" " BC =  $I_A - 10 = 29.04 - 10 = 19.04$  A from B to c

" " CD =  $I_A - 30 = 29.04 - 30 = -0.96$  Amp  
= 0.96 Amp from D to C

" " DE =  $I_A - 60 = 29.04 - 60 = -30.96$  Amp  
= 30.96 Amp from E to D

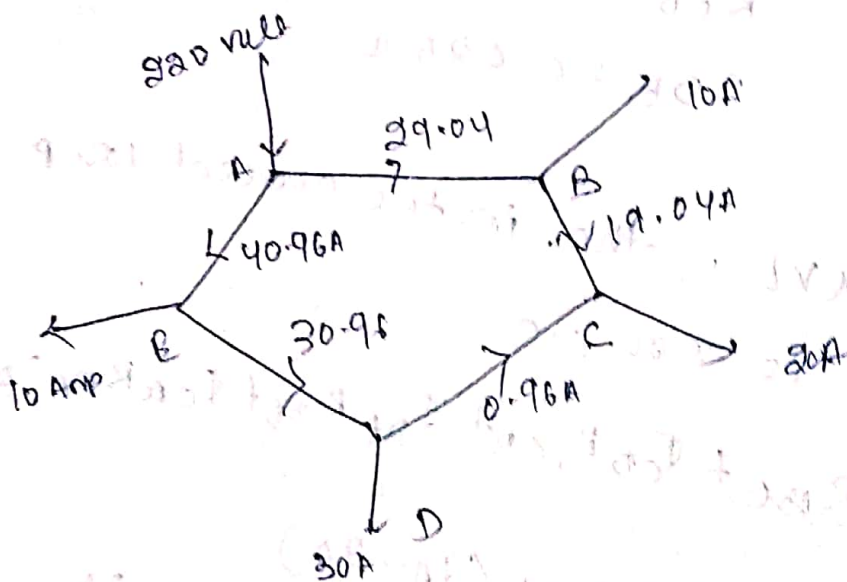" " EA =  $I_A - 70 = 29.04 - 70 = -40.96$   
= 40.96 Amp from A to E



## AC distribution calculation

Ac distribution calculations differ from D.C distribution in the following respects.


- (i) In d.c. distribution system, the voltage drop is due to resistance alone. However in a.c system, the voltage drops are due to the combined effect of resistance, inductance and capacitance.
- (ii) In d.c. system, addition and subtraction of current or voltage are done arithmetically but in a.c system, these operations are done vectorially (Phasor sum).
- (iii) In a.c system P.F. is considered.
- (iv) It may be referred to supply or receiving end voltage which is regarded as the reference vector.
- (v) It may be referred to the voltage at the load point itself.
- \* In this method, voltage current and impedances are expressed in complex notation and the calculation are made exactly as in d.c. distribution.

## Methods of solving AC distribution problems

- (1) In ac distribution calculation, P.F. of various load currents have to be considered, since current in different sections of the distributor will be the vector sum of load currents and not the arithmetic sum.
- The P.F. of load current may be given
- (i) w.r.to receiving or sending end voltage
  - (ii) w.r.to load voltage itself.


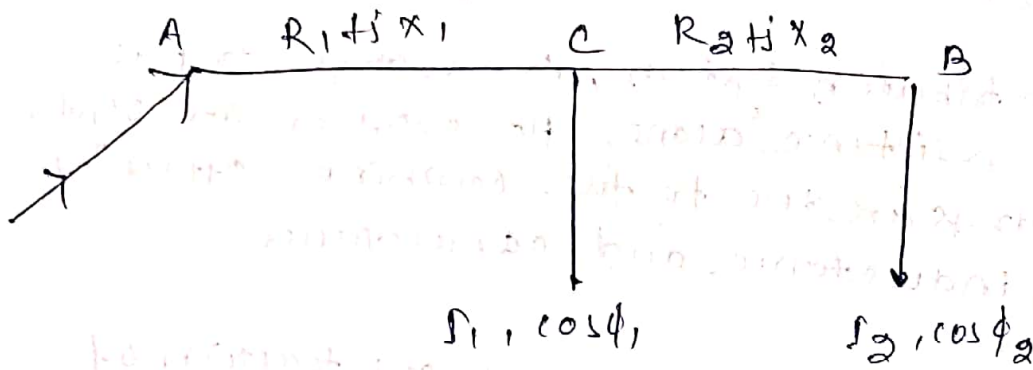
# ① Power factors referred at receiving end voltage



Let  $I_1, I_2$  are tapped off at point C & B

$\cos \phi_1, \cos \phi_2$  = p.f. at 'C' and 'B' (lagging pf)

$R_1, X_1, R_2, X_2$  = Resistance and reactance of section AC & CB

$V_B$  = Receiving end voltage ( $V_R$ ) as the reference vector.

Impedance of section

$$AC, \vec{Z}_{AC} = R_1 + jX_1$$

impedance of section CB,  $\vec{Z}_{CB} = R_2 + jX_2$

load current at point C,  $\vec{I}_1 = I_1(\cos \phi_1 - j\sin \phi_1)$

load current at point B,  $\vec{I}_2 = I_2(\cos \phi_2 - j\sin \phi_2)$

current in section CB,  $\vec{I}_{CB} = \vec{I}_2 = I_2(\cos \phi_2 - j\sin \phi_2)$

current in section AC =  $\vec{I}_{AC} = \vec{I}_1 + \vec{I}_2$

$$\vec{I}_{AC} = \vec{I}_1 + \vec{I}_2$$

$$= I_1(\cos \phi_1 - j \sin \phi_1) + I_2(\cos \phi_2 - j \sin \phi_2)$$

voltage drop on section CB,

$$\vec{V}_{CB} = \vec{I}_{CB} \vec{Z}_{CB} = I_2(\cos \phi_2 - j \sin \phi_2)(R_2 + jX_2)$$

voltage drop on section AC,

$$\vec{V}_{AC} = \vec{I}_{AC} \vec{Z}_{AC} = (\vec{I}_1 + \vec{I}_2) \vec{Z}_{AC}$$


$$= (I_1 \cos \phi_1 - j I_1 \sin \phi_1) + I_2(\cos \phi_2 - j \sin \phi_2)(R_1 + jX_1)$$

$$\vec{V}_A = \vec{V}_B + \vec{V}_{CB} + \vec{V}_{AC}$$

Sending end voltage

$$\text{sending end current} = \vec{I}_1 + \vec{I}_2$$

$$(\vec{I}_A)$$

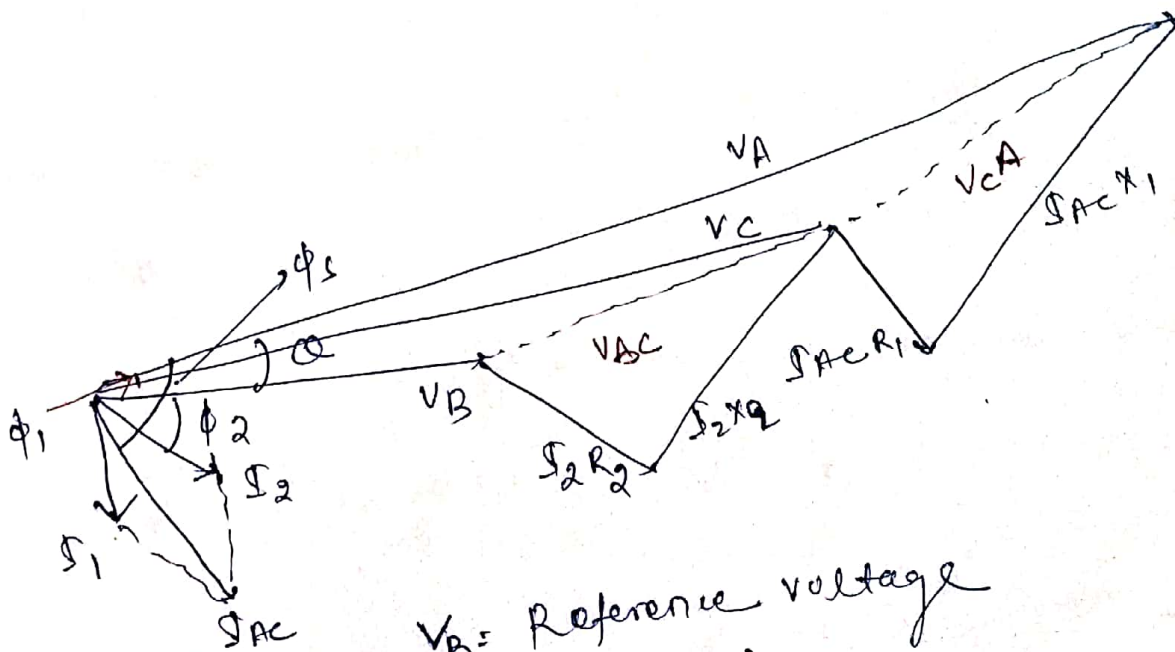

$V_B$  = Reference voltage  
( $V_C$  and  $V_A$ )



Q.1


A single phase a.c. distributor AB 300 m long is fed from end A and is loaded as under.

(i) 200 A at 0.707 p.f. lagging 200 m from point A

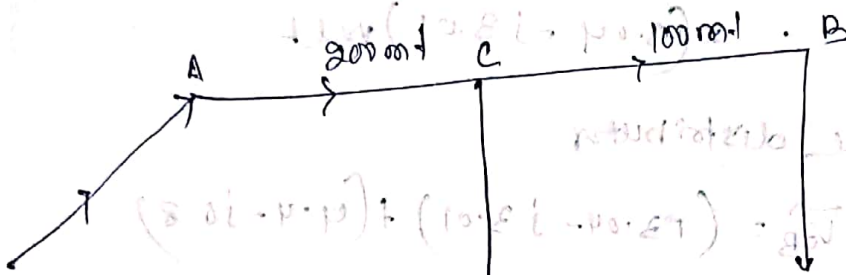(ii) 200 A at 0.8 p.f. lagging 300 m from point A

The load resistance and reactance of the distributor is  $0.2 \Omega$  and  $0.1 \Omega$  per kilometre. Calculate the total voltage drop in the distributor. The load power factor refers to the voltage at the far end.

Ans impedance of distributor / km =  $(0.2 + j0.1) \Omega$



$$I_1 = 200 \text{ A} \quad \cos \phi_1 = 0.707 \text{ lag}$$

$$I_2 = 200 \text{ A} \quad \cos \phi_2 = 0.8 \text{ lag}$$

impedance of section AC,  $\vec{Z}_{AC} = (0.2 + j0.1) \times \frac{200}{1000} = (0.04 + j0.02) \Omega$

impedance of " CB,  $\vec{Z}_{CB} = (0.2 + j0.1) \times \frac{100}{1000} = (0.02 + j0.01) \Omega$

$V_B$  (voltage at B) is the reference voltage

load current at point B =  $I_2 = I_2 (\cos \phi_2 - j \sin \phi_2) = 200 (0.8 - j0.6)$   
 $= (160 - j120) \text{ A}$

load current at point C =  $I_1 = I_1 (\cos \phi_1 - j \sin \phi_1) = 200 (0.707 - j0.707)$   
 $= (141.4 - j141.4) \text{ A}$

current in section CB,  $\vec{I}_{CB} = \vec{I}_2 = (160 - j120)A$

current in section AC,  $\vec{I}_{AC} = \vec{I}_1 + \vec{I}_2$

$$= (70.7 - j40.7) + j(160 - j120)$$

$$= (230.7 - j190.7)A$$

voltage drop in section CB,

$$\vec{V}_{CB} = \vec{I}_{CB} \vec{Z}_{CB} = (160 - j120)(0.02 + j0.01)$$

$$= (4.4 - j0.8) \text{ volts}$$

voltage drop in section AC,

$$\vec{V}_{AC} = \vec{I}_{AC} \vec{Z}_{AC} = (230.7 - j190.7)(0.04 + j0.02)$$

$$= (13.04 - j3.01) \text{ volt}$$

voltage drop in the distributor

$$= \vec{V}_{AC} + \vec{V}_{CB} = (13.04 - j3.01) + (4.4 - j0.8)$$

$$= (17.44 - j3.81) \text{ volt}$$

$$= \sqrt{(17.44)^2 + (3.81)^2} = 17.85 \text{ volt}$$



## Ch-7

## underground cables

### Advantages of underground cables →

- less lightning effect.
- less maintenance cost
- less chance of fault
- smaller voltage drop
- better general appearance.

### Disadvantages of underground cables →

- greater installation cost
- Introduce insulation problem for high voltage.
- fault finding is difficult.


### Properties of underground cables →

An underground cable essentially consist of one or more conductors covered with suitable insulation and surrounded by a protecting cover.

In general, a cable must fulfil the following necessary requirement:

- The conductor used in cables should be tinned stranded copper or aluminium of high conductivity.
- The conductor should be stranded which increase its flexibility.
- conductor should have suitable size that carry desire load current without over heating.
- limited voltage drop
- cable must have proper thickness of insulation in order to give high degree of safety and reliability at the voltage for which it is designed.
- The cable must be provided with suitable mechanical protection, so that it may withstand the rough use in laying it.

# Construction of cable

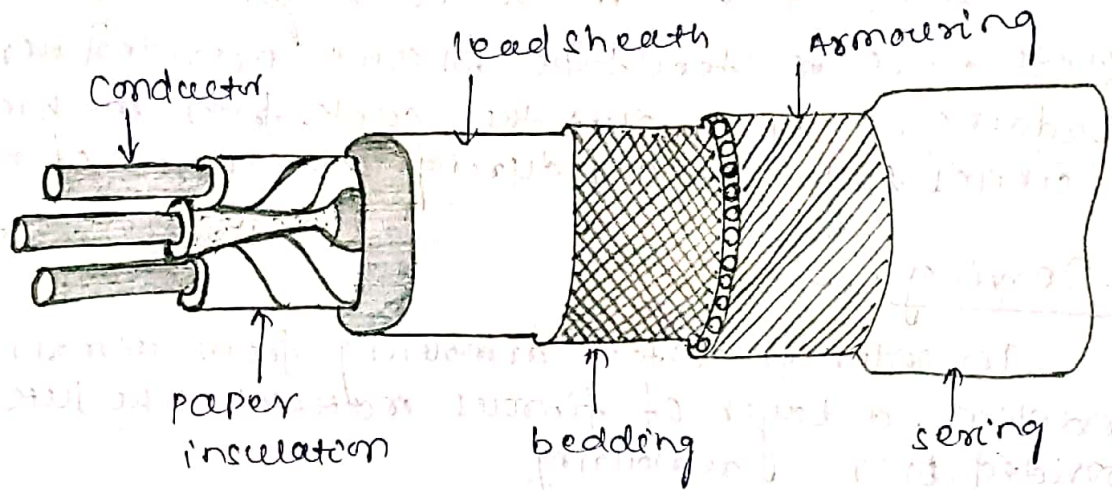

## ① Core or conductor ! →

- A cable may have one or more than one conductor depending upon the type of service for which it is used.
- The conductors are made of tinned copper or aluminium and are stranded in order to provide flexibility to the cable.

## ② Insulation ! →

- Each conductor is provided with a suitable thickness of insulation. The thickness of layer depending upon the voltage to be withstood by the cable.

## ③ Metallic sheath ! →

- A metallic sheath of lead or aluminium is provided over the insulation to protect the cable from moisture, gases or ~~any~~ other damaging liquid (acid & alkalis).

## ④ Bedding ! →

- A layer of fibrous material like jute is applied over the metallic sheath which is called a bedding.
- It protects the metallic sheath from corrosion and mechanical injury due to armouring.



⑤ Armouring! →

→ It consists of one or two layers of galvanised steel wire or steel tape which is provided over the bedding. It protects the cable from mechanical injury while laying it and during the course of handling.

⑥ Sewing! →

In order to protect armouring from atmospheric condition, a layer of fibrous material like jute is provided over armouring.

## Insulating material for cable

In general the insulating material used in cable should have the following properties: →

- (i) High insulation resistance to avoid leakage current
- (ii) High dielectric strength to avoid electrical breakdown of the cable.
- (iii) High mechanical strength to withstand the mechanical handling of cables.
- (iv) Non-hygroscopic (it should not absorb moisture from air or soil)
- (v) non-inflammable
- (vi) Low cost so as to make the underground system a variable proposition
- (vii) unaffected by acid or alkalis to avoid and prevent the cable from chemical action.

## Types of insulating Materials

### ① Rubber

- Rubber has high dielectric strength which is about  $30 \text{ kV/mm}$  and resistivity of insulation is  $10^{17} \Omega/\text{cm}$
- It has high insulating properties
- But in pure rubber the major drawbacks are
  - \* It's maximum safe temp is low i.e.  $38^\circ\text{C}$
  - \* It absorb moisture



\* As it is very soft, so there is a chance of damage due to rough handling and ages when exposed to light.

\* deform when warm and brittle when cold

\* sticky

So that pure rubber is not used for insulation,

## ② VSR (Vulcanised India Rubber)

\* It is a mixture of pure rubber and mineral material such as zinc oxide, red lead etc and 3-5% of sulphur.

\* The compound so formed is rolled into thin sheets and cut into strips.

\* The rubber compound is then applied to the conductor and is heated to a temp. of about  $150^{\circ}\text{C}$ .

\* The whole process is called vulcanisation and that product is known as VSR.

### Advantages! →

→ It has greater mechanical strength,

→ good electrical insulator

→ does not absorb moisture from atmosphere naturally

### ③ Impregnated paper (Saturated paper)

- It has high dielectric strength (50 kV per mm)
- It has good insulation resistance
- It has low cost.

#### disadvantages

- It absorbs moisture (hygroscopic in nature), so that it always provided with some protective covering and never left unsealed.

- To make it non-inflammable, paper is impregnated with some compound like Paraffin, naphthenic and resin

(It consists of chemically pulped paper made from wood chippings and impregnated with some compound such as paraffinic or naphthenic material)

### ④ Varnished cambric

- \* It is a cotton cloth impregnated and coated with varnish.
- \* The cambric is lapped on to the conductor in the form of a tape and its surface are coated with potassium jelly compound to allow for the sliding of one turn over another turn as the cable is bent.
- \* As the varnished cambric is hygroscopic, therefore steel cables are always provided with metallic sheath.

### ⑤ PVC (Poly-vinyl chloride)

- \* It is obtained from polymerisation of acetylene and is in the form of white powder.
- \* Then it is combined with plasticizer which make the compound in liquid form in high boiling point.



# Classification of cable

Cable for underground service may be classified into 2 way

- (1) The type of insulating material is used for their manufacture
- (2) The voltage for which they are manufacture

According to the voltage, the cables are

- (1) Low-tension (L.T) cables - upto 1000 V
- (2) High-tension (H.T) cables - upto 11 kV
- (3) Super-tension cable (S.T) → from 22 kV to 33 kV
- (4) Extra high tension (E.H.T) cables → from 33 kV to 66 kV
- (5) Extra super tension (E.S.T) cables → beyond 132 kV.  
(Extra super voltage cable)

Accordinging to no. of conductor

(1) Single core cable

(2) Multi core cable

↓  
2-core

3-core


4-core

} depend upon the service.

Single core cable / (Low-Tension cable)

\* It has ordinary construction because the stresses developed in the cable for low-voltages are generally small.

- \* It consists of one circular core of tinned & stranded copper or aluminium insulated by layer of impregnated paper.
- \* The insulation is surrounded by a lead sheath which prevent the entry of moisture.
- \* In order to protect the lead sheath from corrosion, a serving is provided over the lead sheath.
- C. The single core cables are not usually armoured in order to avoid excessive sheath losses.)

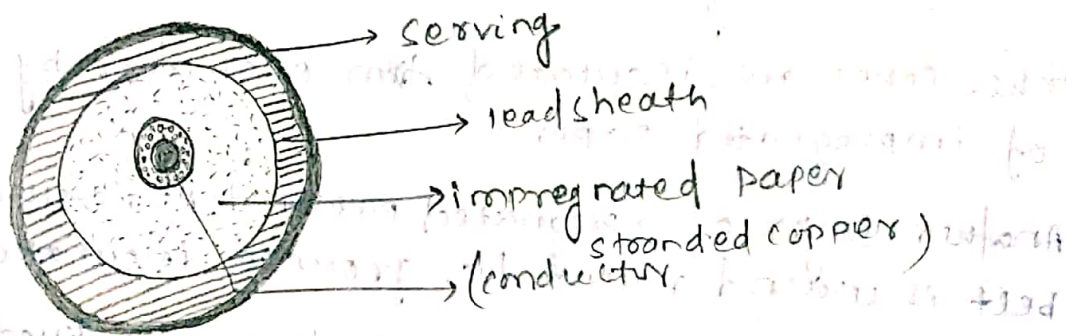

- 3-core cables → (For 3- $\phi$  services)
- \* For power supply either 3-core cable or 3-single core cable may be used.
  - \* For voltage up to 66 kV, 3-core cable is preferred due to economic reason.
  - \* For voltage beyond 66 kV, 3-core cables become too larger and unwieldy and therefore, single-core cables are used.




## Types of cables, generally used for 3- $\phi$ supply service

- ① Belted cables - (upto 11 kV)
- ② screened cables - (from 22 kV - 66 kV)
- ③ pressure cables - (beyond 66 kV)
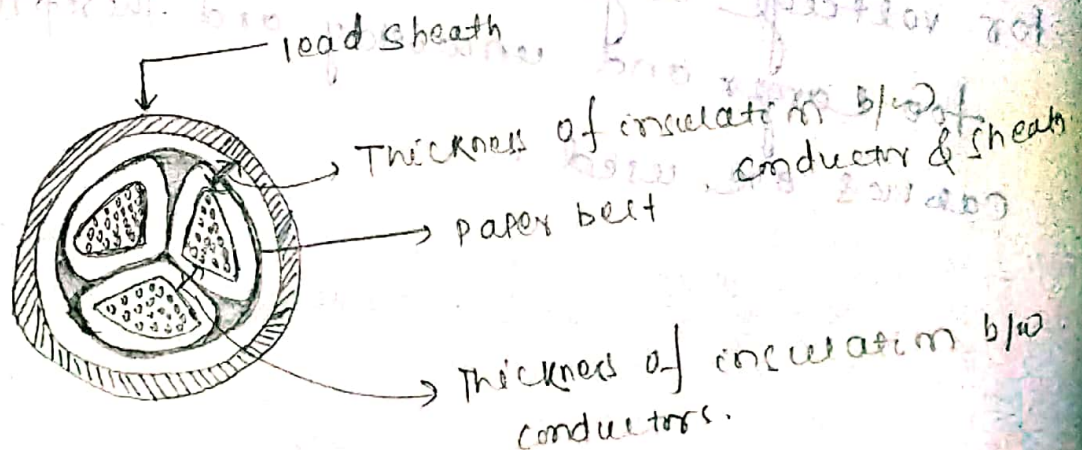
### ① Belted cables : →

- Belted cables are used for voltage upto 11 kV. but in extraordinary cases it is used upto 22 kV.
- The cores are insulated from each other by layers of impregnated paper.
- Another layer of impregnated paper tape, called paper belt is wound round the grouped insulated cores.
- A gap between insulated conductor is filled with fibrous insulating material to give a circular X-section to the cable.
- The belt is covered with lead sheath to protect the cable against moisture and mechanical injury.
- The lead sheath is covered with one or a layer of armouring with an outer serving.
- This type of cable is suitable for low and medium voltage.



## ② screened cables! →

These cables are used upto 33 kV, but in particular cases these are extended upto 66 kV.

It is 2 types ① H-type cable ← designed by H. Hochstadter  
② S.L type cable

### ① H-type cable! -

- In this cable, each core is insulated by layer of impregnated paper.
- The insulation on each core is covered with a metallic screen which usually consist of a perforated aluminium foil.
- (The cores are laid in such away that metallic screens make contact with one another)
- The three cores are then wrapped around using a conducting belt made of copper woven fabric tape.
- H-type cable does not have an insulating belt; however it has the lead sheath followed by bedding, cransoling and then a serving.
- The core screens in the cable are all electrically connected to both the conducting belt and the lead sheath. This ensures that they are at the earth




Potential and all the electrical stresses are therefore purely radial, hence reduced dielectric losses.

### Advantages of H-type cables

- ① Metallic screen improve the heat dissipation of the cable.
- ② No-formation of air pocket and voids in the dielectric, hence a high breakdown strength and less dielectric losses.
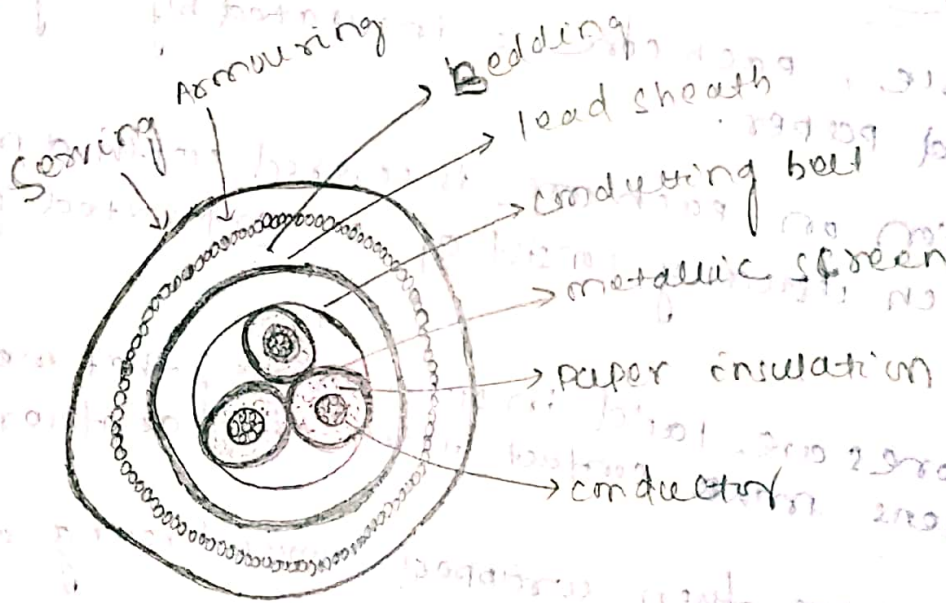
### disadvantages! →

These cables are only suitable for low and medium voltage of up to 33 kV, but can reach 66 kV at times.



## ② S.L type cable. (Separately lead sheath)


- \* It is basically H-type cable, each core is first insulated with an impregnated paper then each insulated core is covered by its own lead sheath.
- \* Then all 3 cores are covered with cotton tape, then armouring and serving are provided over the cotton tape.
- (No-lead covering is provided surrounding all the 3-cores in addition to their individual lead sheath.)

### The advantages of S.L type cable over H-type cable.

- \* Bending of cables becomes easy due to the elimination of overall lead sheath.
- \* The separate sheaths minimise the possibility of core-to-core breakdown.
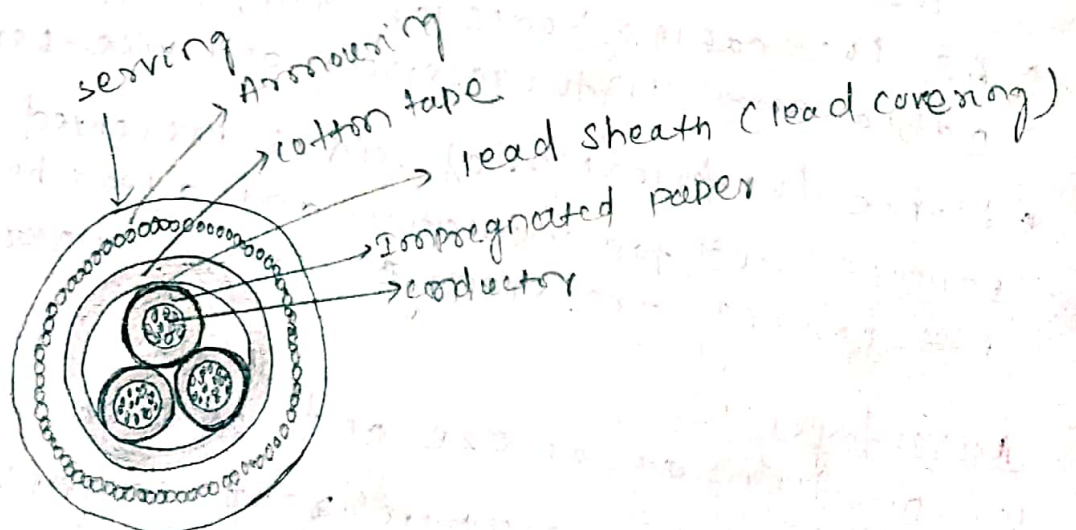
### disadvantages:-

- \* The disadvantages of S.L type cable is that the manufacturing is difficult because of thinner lead sheath which is thinner than single sheath of H-cable.





## Pressure cable →

For voltage beyond 66 kV, solid type cables are unreliable because there is a danger of breakdown of insulation due to the presence of voids. When the operating voltages are greater than 66 kV, pressure cables are used. In such cables, voids are eliminated by increasing the pressure of compound and for this reason they are called pressure cables.

### 2 types of pressure cables

- ① oil-filled cables
- ② gas pressure cables

#### ① Oil-filled cables →

- \* In this type of cable, a hollow conductor of soft-drawn stranded copper, fed by oil reservoirs placed at interval along the route of the cable.
- \* The oil is maintained under pressure by these reservoirs.
- \* As the cable heats on load, oil is driven from the cable into the reservoir and vice-versa.
- \* Hence the formation of void is prevented. Impregnated paper is used for insulation and a lead sheath and a jute covering are employed to give waterproof.

#### Advantages →


- 1) smaller overall size and smaller weight.
- 2) increased temperature range in service possible
- 3) No ionisation, oxidation and formation of voids
- 4) High current rating (voltage rating)
- 5) High maximum permissible stress.

## disadvantages :-

- \* High cost
- \* Laying of cable and maintenance are complicated.


It is 3 types

### ① single core conductor channel

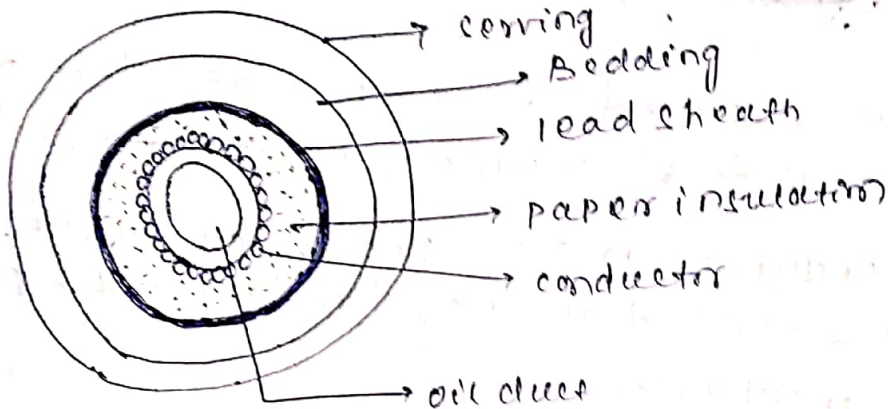


- \* Here the oil pressure compresses the layer of paper insulation and prevents the possibilities of void formation.
- \* The system is so designed that when the oil gets expanded due to increase in cable temp. the extra oil collects in the reservoir. However when the temp falls during light load condition, the oil from the reservoir flows to the channel.
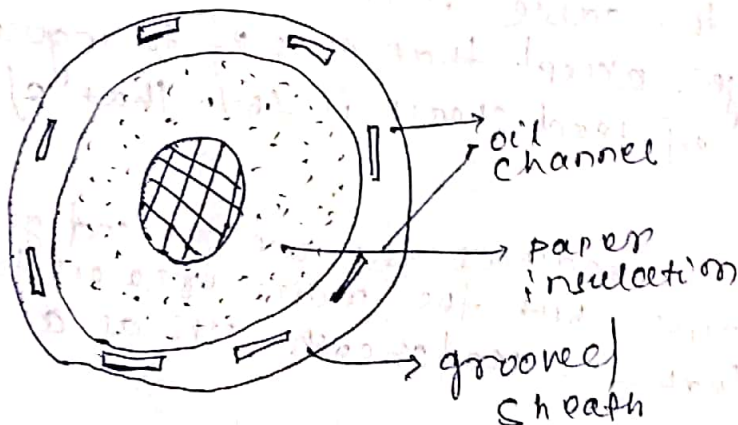
### ② single-core sheath channel oil filled cable



- \* The conductor is solid similar to that of solid cable and it's paper insulated and oil ducts are provided in the metallic sheath.


### ③ 3-core oil-filled cable

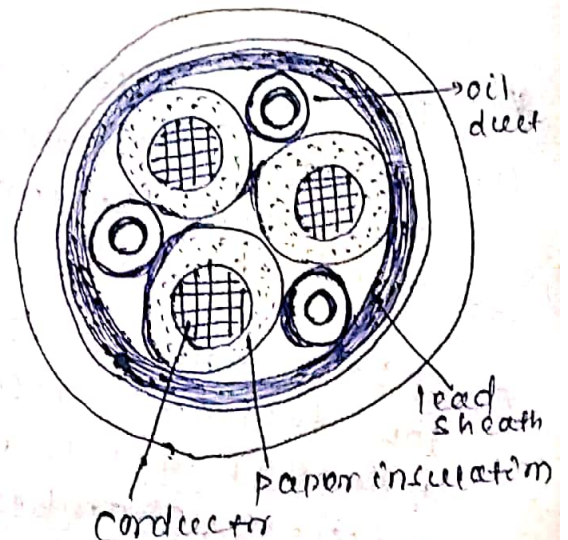

- \* The oil ducts are located in the filler spaces.



## Gas Pressure cable : →

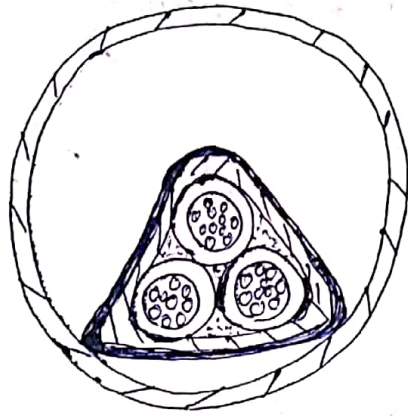

- \* The cable is placed in a gas tight steel pipe, The pipe is filled with dry nitrogen gas.
- \* The gas pressure produce radial compression and closes the voids that may formed b/w the layers of paper insulation.

### \* Advt. : →

- \* such cables can carry more load current and operate at higher voltage than a normal cable.
- \* maintenance cost is small and the nitrogen gas helps in quenching any flame.

### dis-adv : →

- \* overall cost is very high
- \* The construction of the cable is similar to that of an ordinary solid type except that it is of triangular shape and thickness of lead sheath is 75% that of solid cable.
- \* The triangular section reduces the weight and gives low thermal resistance but the main reason for triangular shape is that the lead sheath acts as a pressure chamber.

## Laying of underground cables

There are 3 main methods of laying underground cables.

- ① direct laying
- ② draw-in system
- ③ solid system

### ① Direct laying

- In this method, a trench of about 1.5 m deep and 45 cm wide is dug.
- Then the trench is covered with a layer of fine sand (about 10 cm thickness) and a cable is laid over this sand bed.
- The sand prevents the entry of moisture from the ground and protect the cable from corrosion.
- After the cable has been laid in the trench, it is covered with another layer of sand of about 10 cm thickness.
- The trench is then covered with bricks and other materials in order to protect the cable from mechanical injury.
- When more than one cable is to be laid in the same trench the minimum spacing b/w them is about 30-40 cm.
- It reduce the effect of mutual heating and fault occurring in one cable doesnot affect the other.

### Advantages: →


- It is a simple and cheap method
- It provide better condition for heat dissipation.





→ It is a clean and safe method as the cable is invisible and free from external disturbances.
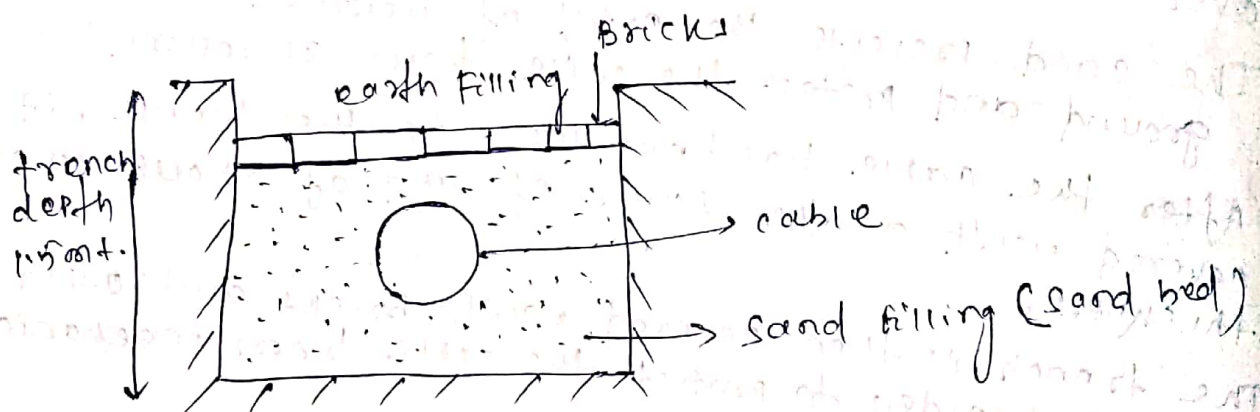
### disadvantages:

- Localisation of fault is difficult.
- The maintenance cost is very high
- It cannot be used in congested areas (where excavation is expensive and inconvenient)
- The cable sheath may sometimes undergo chemical changes and get damaged due to impurities present in the soil.
- Extension of load is possible only by a completely new excavation which may cost as much as the original work.



### ② Draw-in system

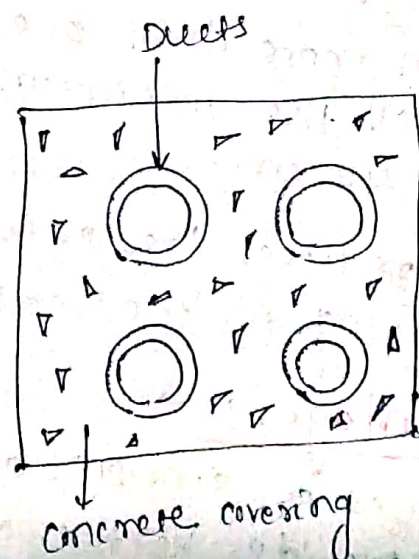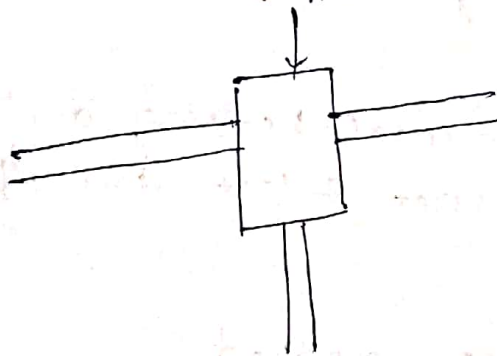

- \* In this method a line of conduit or tube made of either iron, clay or cement concrete are laid in the trench side by side.
- \* separate pipes are provided for each cables laid in the same trench.
- \* The diameter of the pipe must be greater than the diameter of cable.
- \* The width of the trench depends upon the no. of pipes to be used.
- \* Normally spacing of 0.25 to 0.75 is maintained b/w two pipes.
- \* The pipes terminate in a underground chamber known as man hole.
- \* It is employed for pulling-in cable through the pipe and jointing the incoming cable and out going cable.
- \* In this system, cables are not provided with armouring only serving is given in order to protect them when being pulled into the ducts.

### Advantages:-

- As armouring is not present joint becomes simpler and maintenance cost is reduced.
- cable repair, alteration and addition to the cable network are possible through digging soil.
- There is very less chance of fault occurrence due to strong mechanical protection provided by the system.
- This system offers long life to cable.



### disadvantages


- Initial cost is very high.
- Unfavourable conditions for dissipation of heat.
- current carrying capacity of the cables is reduced due to the close grouping of cables.

### ③ Solid System: →

- In this method of laying the cable is laid in open pipes made of cast iron or treated wood.
- After the cable is laid in position the pipe is filled with a bituminous compound.
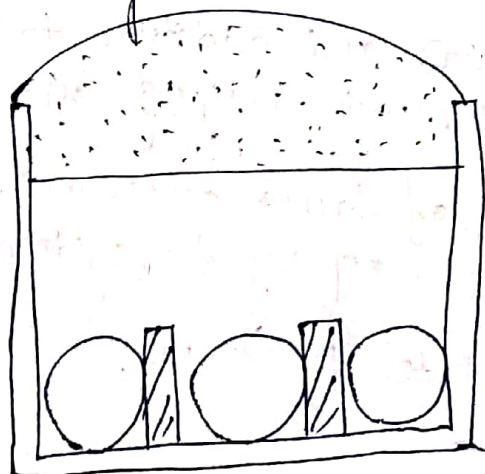
### disadvantages: →

- It's more expensive
  - It requires skilled labour and favourable weather condition.
  - Due to poor heat dissipation facility the current carrying capacity of the cable is reduced.
- ∴ due to all these disadvantages, this method of laying underground cables is rarely used now days.



- \* laying and repair require more time.
- \* laying and repair cannot be carried out in rainy season

## Types of Cable faults

∴ If a fault does occur, it is difficult to locate and repair the fault because conductors are not visible.

There are 3 types of fault which occur in underground cable.

- ① open-circuit fault
- ② short-circuit fault
- ③ Earth-fault

Loop tests for location of Fault in underground cables

There are several methods for locating the faults in underground cables. However, two popular methods known as loop tests are:

- ① Murray loop test
- ② Varley loop test

These simple tests can be used to locate the earth fault or short-circuit fault in underground cable.


### ① Murray loop test

(i) Earth fault : → Earth fault by murray loop test.

AB = sound cable  
CD = faulty cable

F = Earth fault occurs at point F.

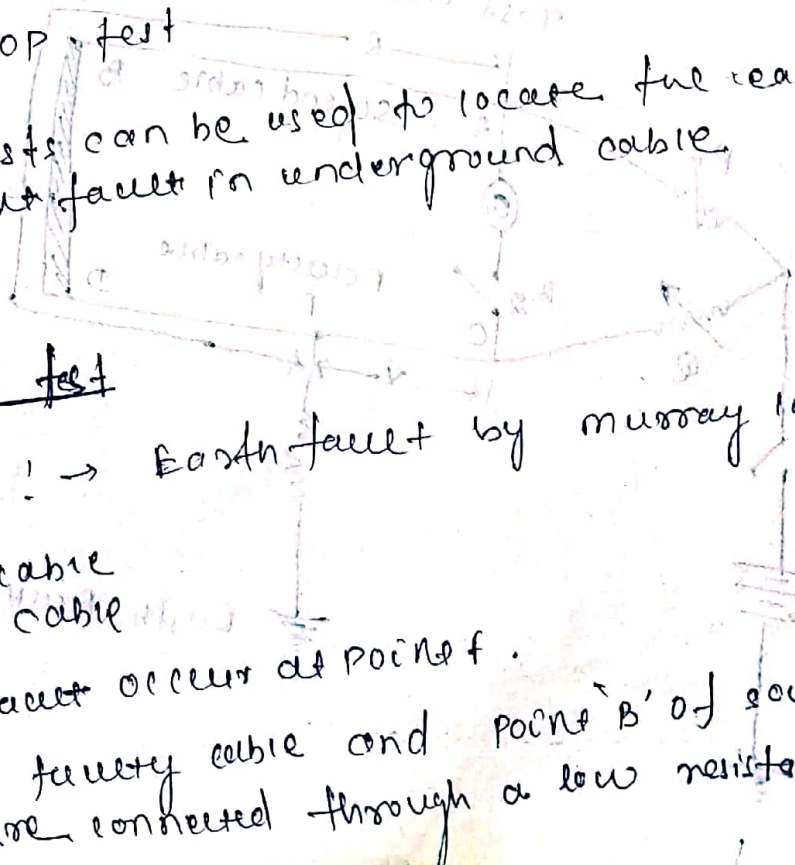The point D of faulty cable and point B' of sound cable are connected through a low resistance





# Murray Loop test

The murray loop test is the most common and accurate method of locating earth fault or short-circuit fault in under-ground cables.

## ① Earth-fault

Location of earth fault by murray loop test.

AB = sound cable


CD = faulty cable

F = fault occurs at point 'F'

- The point D of faulty cable is joined to the point of B of the sound cable through a low resistance link.
- Two variable resistance P and Q are joined to ends of 'A' and 'C' respectively and serve as the ratio arms of the wheatstone bridge.

$R$  = Resistance of the conductor from point 'A' to 'F'

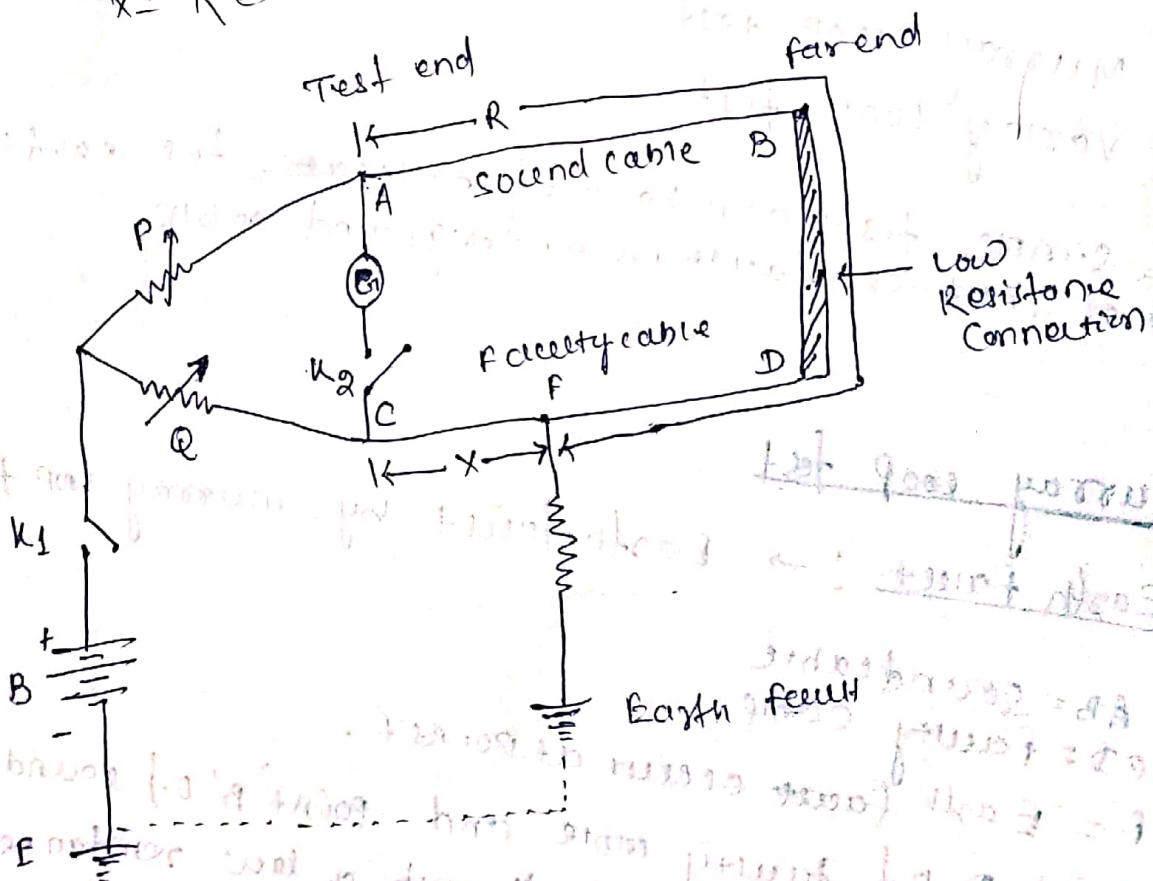$X$  = Resistance of the conductor from point 'C' to 'F'



P, Q, R and X are the four arms of wheatstone bridge  
 → The resistance p and q are varied till the galvanometer indicates zero deflection.

under balanced condition, we have

$$\frac{P}{Q} = \frac{R}{X}$$

$$\Rightarrow \frac{P}{Q} + 1 = \frac{R}{X} + 1$$

$$\Rightarrow \frac{P+Q}{Q} = \frac{R+X}{X}$$

if 'r' is the resistance of each cable,

$$\text{then } R+X = 2r$$

$$\frac{P+Q}{Q} = \frac{2r}{X}$$

$$\Rightarrow \boxed{X = \frac{Q}{P+Q} \times 2r}$$

if 'l' is the length of each cable in mt.  
 resistance per mt. =  $\frac{r}{l}$

then of cable

∴ distance of fault point from test end is


$$d = \frac{X}{(\frac{r}{l})} = \frac{Q}{P+Q} \times 2r \times \frac{l}{r} = \frac{Q}{P+Q} \times 2l$$

$$\boxed{d = \frac{Q}{P+Q} \times \text{loop length in mt.}}$$

Thus position of the fault is located.



## 11) Short cut Fault

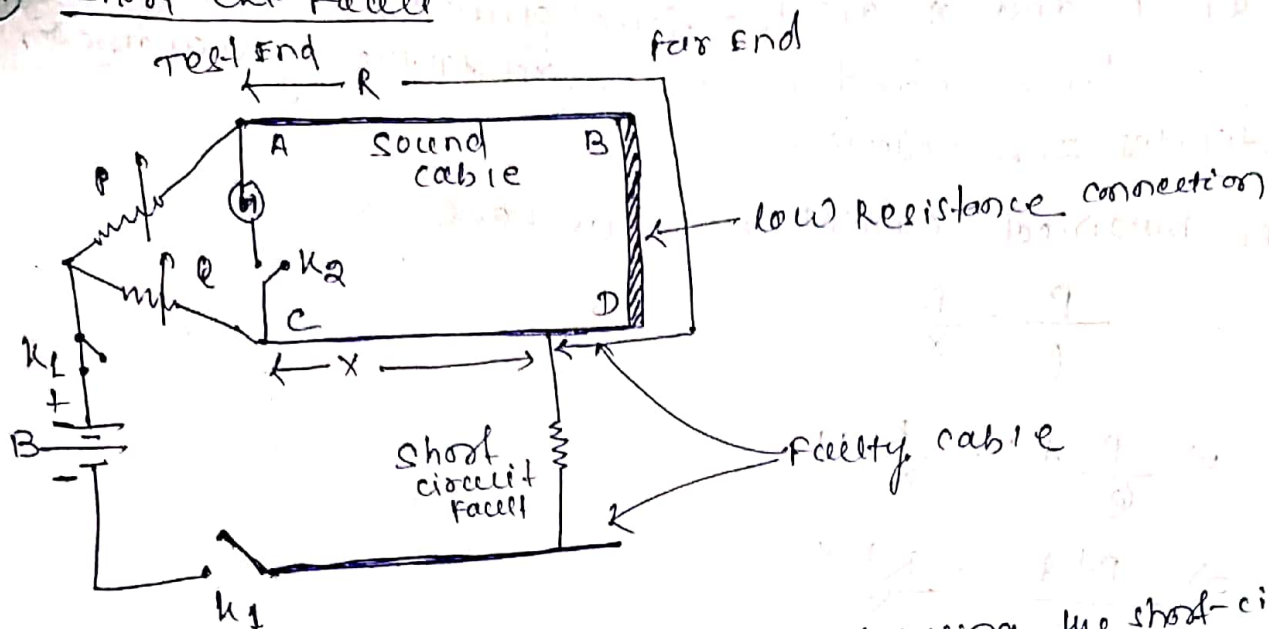

- This is the circuit connection for locating the short-circuit fault by Murray loop test. Again  $P$ ,  $Q$ ,  $R$ , and  $X$  are the four arms of the bridge. (Fault resistance is in the battery circuit and not in the bridge circuit)
- The bridge is balanced by adjusting the resistance  $P$  and  $Q$
- For balanced position of the bridge we get

$$\frac{P}{Q} = \frac{R}{X} \Rightarrow \frac{P}{Q} + 1 = \frac{R}{X} + 1$$

$$\Rightarrow \frac{P+Q}{Q} = \frac{R+X}{X} = \frac{2R}{X}$$


$$\Rightarrow X = \frac{Q}{P+Q} \times 2R$$

$$\Rightarrow d = \frac{Q}{P+Q} \times (\text{loop length}) \text{ in m.}$$


Thus position of the fault is located.
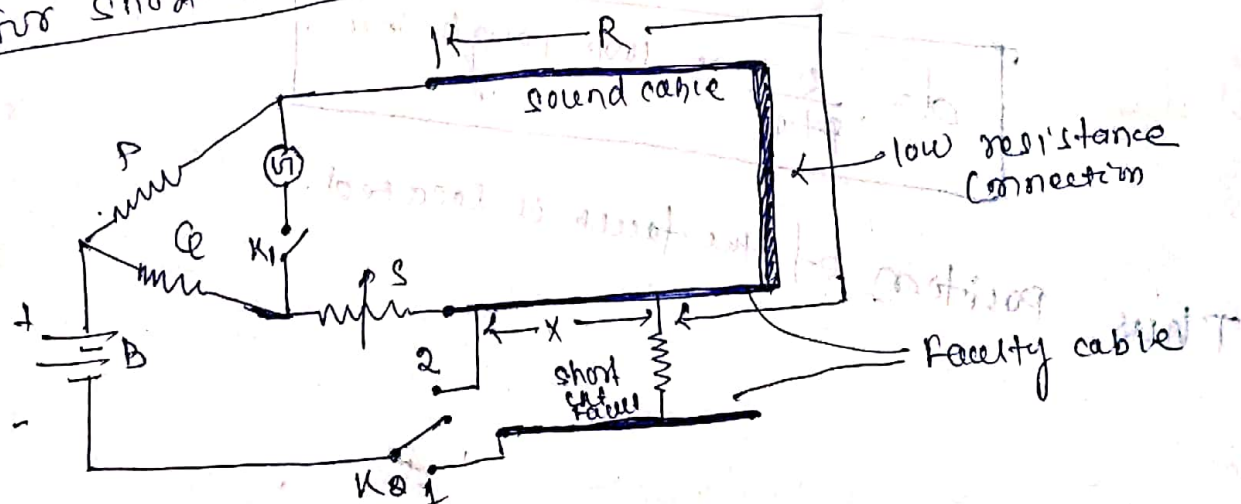
### Variety loop test

- Here, the ratio arms  $P$  and  $Q$  are fixed resistance, Balance is obtained by adjusting the variable resistance  $S$  connected to the test end of the faulty cable.
- for short cut test diagram



# for Fault Fault test Diagram

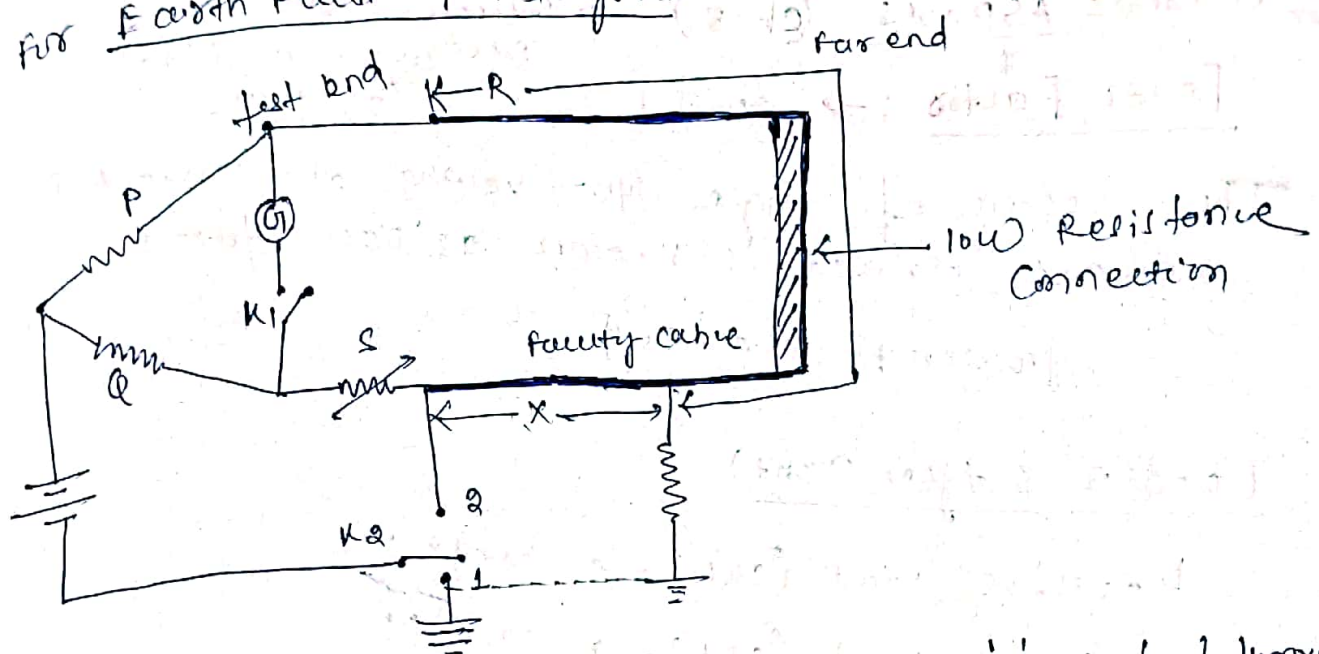

for Earth fault or short cut fault, the key 'K2' is first thrown to position '1'. The variable resistance 'S' is varied till the bridge is balanced for resistance value of  $S_1$ . Then

$$\frac{P}{Q} = \frac{R}{x + S_1}$$

$$\Rightarrow \frac{P+Q}{Q} = \frac{R+x+S_1}{x+S_1}$$

$$\Rightarrow x = \frac{Q(R+x) - PS_1}{P+Q} \quad \text{--- (1)}$$

Now, key K2 is thrown to position 2 and bridge is balanced with new value of resistance  $S_2$ . Then

$$\frac{P}{Q} = \frac{R+x}{S_2}$$

$$\Rightarrow (R+x)Q = PS_2 \quad \text{--- (2)}$$

from eqn (1) & (2), we get

$$x = \frac{P(S_2 - S_1)}{P+Q}$$

Since the values of P, Q,  $S_1$  and  $S_2$  are known, the value of 'x' can be determined.

Loop resistance =  $R+x = \frac{P}{Q} S_2$

if  $r$  is the resistance of the cable per mt., Then distance of fault from test end is  $d = \frac{x}{r}$  m.



Economics ASPECTS <sup>→ particular parts</sup> (Ch-8) → studies about economic activities of a man.

Power Factor : →  $\cos \phi$

The cosine of angle b/w voltage and current in an a.c. circuit is known as power factor.

$$\text{Power Factor} = \cos \phi$$

Load is 3 types (cmt)

Resistive load (cmt) →  $\cos \phi = 1$


Inductive load (cmt) →  $\cos \phi < 1$

Capacitive load (cmt) →  $\cos \phi > 1$

- \* If the cmt is inductive, then current lags behind the voltage and the P.F. is referred to as lagging.
- \* If the cmt is capacitive, then current leads the voltage and the P.F. is referred to as leading.
- \* If the cmt is resistive, then current overlaps the voltage and the P.F. is referred to as unity.

\* Lagging P.F.

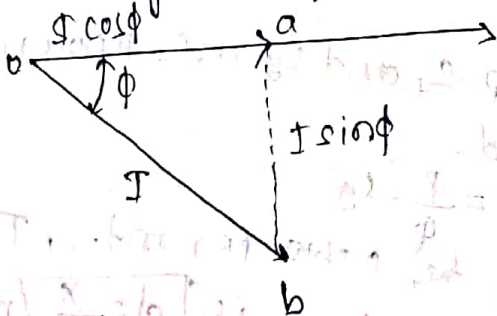Let the inductive cmt taking a lagging current  $I$  from supply voltage  $V$ ;



## Disadvantages of low power factor

\*  $P = V_L I_L \cos \phi$  (for single phase supply)

$$I_L = \frac{P}{V_L \cos \phi}$$

✓  $P = \sqrt{3} V_L I_L \cos \phi$  (for 3- $\phi$  supply)

$$I_L = \frac{P}{\sqrt{3} V_L \cos \phi}$$

Here 'P' depend on 'cos  $\phi$ ', where 'P' is the power consumed in the ckt.

So, cos  $\phi$  play an important role in a.c ckt.

$$P = V_{ph} I_{ph} \cos \phi$$

$$P = 3 V_{ph} I_{ph} \cos \phi$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

\* for constant 'P' and 'V'  
current 'I' is inversely proportional to the P.F

$$I \propto \frac{1}{P.F}$$

$$\boxed{I \propto \frac{1}{\cos \phi}}$$

when cos  $\phi \downarrow$ ,  $I \uparrow$  (higher the load current)  
cos  $\phi \uparrow$ ,  $I \downarrow$  (lower the load current)

A power factor less than unity results in the following disadvantages

① Large kVA rating of equipment.

The electrical machinery (i.e. alternators, transformers, switchgear) is always rated in kVA.



$$\cos \phi = \frac{\text{Active Power}}{\text{Apparent Power}} = \frac{\text{KW}}{\text{KVA}}$$

$$\Rightarrow \uparrow \text{KVA} = \frac{\text{KW}}{\cos \phi} \downarrow$$

∴ It is clear that KVA rating of the equipment is inversely proportional to P.F.

∴ Therefore, at low P.F, the rating of KVA of the equipment has to be made more, making the equipment larger and expensive.

② greater conductor size →

$$I_L = \frac{P}{\sqrt{3} V_L \cos \phi}$$

if P &  $V_L$  is constant then

$$I_L \propto \frac{1}{\cos \phi}$$

\* Here P.F is inversely proportional to  $I_L$

so that load current will high at low P.F

\* so that conductor will have to carry more current at low power factor.

Ex! → For 1- $\phi$ , AC motor, The i/p power is  $\frac{10 \text{ KW}}{250 \text{ volt}}$  at full-load. The terminal voltage is 250 volt

At unity P.F, the load current =  $I_L = \frac{10 \times 10^3}{250 \times 1} = 40 \text{ A}$

At 0.8 lag P.F, the load current =  $I_L = \frac{10 \times 10^3}{250 \times 0.8} = 50 \text{ A}$

when P.F ↓, the current value ↑, we required greater size conductors.

### (iii) Large copper losses : →

- \* The large current at low P.F. causes more  $I^2R$  losses in all the elements of the supply system.
- \* This results in poor efficiency.  $\eta = \frac{o/p}{i/p}$

### (iv) Poor voltage regulation : →

The large current at low lagging P.F. causes greater voltage drops in alternators, transformers, transmission lines and distributors. So the voltage regulation ~~is~~ <sup>more</sup> ~~is increased~~ due to this voltage drop. & to maintain voltage drop within permissible limits, extra equipments is required (Voltage Regulator).

### (v) Reduced handling capacity of system

The lagging P.F. reduces the handling capacity of all the elements of the system. It is because the reactive component of current prevents the full utilisation of installed capacity.

## Causes of low P.F

Normally, the P.F. of the whole load on the supply system is lower than 0.8.

- ① Most of the a.c. motors are of induction type (1 $\phi$ , 3 $\phi$  induction motor) which have low lagging P.F.




These motors work at a power factor which is extremely small on light load (0.2-0.3) and rises to 0.8-0.9 at full-load.



- (ii) Arc lamps, electric discharge lamps and industrial heating furnaces operate at low lagging power factor.
- (iii) The load on the power system is varying; being high during morning and evening and low at other times. During low load period, supply voltage is increased which increases the magnetisation current. This results in the decreased power factor.
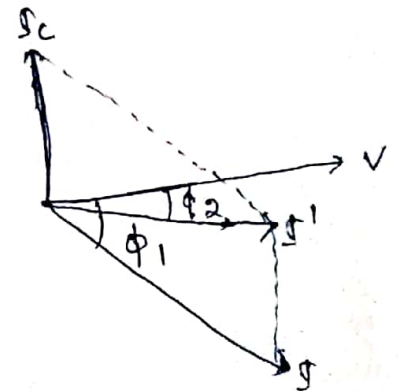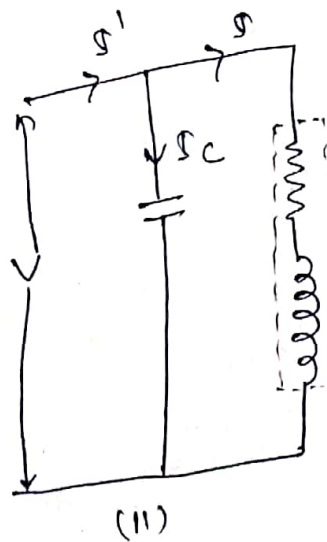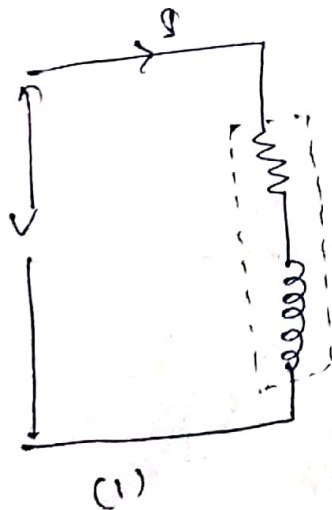
### Power factor improvement

- \* The low power factor is mainly due to that most of the power loads are inductive and therefore, take lagging currents. In order to improve the P.F., some device taking leading power should be connected in parallel with load. One of such devices can be a capacitor.
- \* The capacitor draws a leading current and partly or completely neutralises the lagging reactive component of load current. This raises the P.F. of the load.



$\phi_1 > \phi_2$   
 so  $\cos \phi_1 < \cos \phi_2$   
 so P.F. improved.



# Power factor improvement equipment

Normally, P.F. of the whole load on a large generating station is in the region of 0.8 to 0.9. However it is lower and in such cases it is generally desirable to take special steps to improve the P.F.

There are 3 methods / equipments! →

- ① static capacitor
- ② synchronous condenser
- ③ phase advancers

## ① static capacitor! →

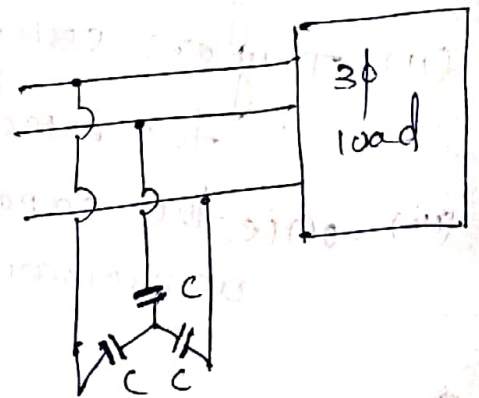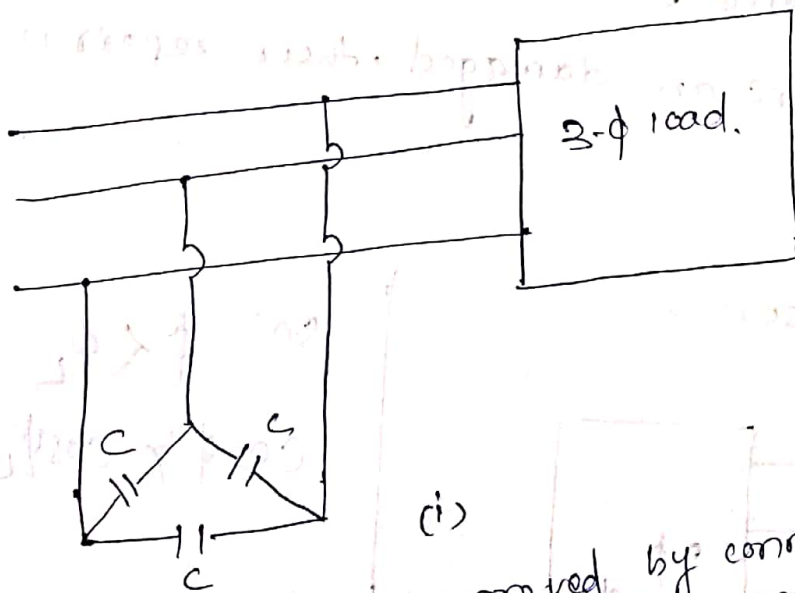

- (i)
- The P.F. can be improved by connecting capacitors in parallel with the equipment operating at lagging P.F.
  - The capacitor (static capacitor) draws a leading current and partly or completely neutralises the lagging reactive component of load current. This raises the P.F. of the load.
  - For 3- $\phi$  load, the capacitors can be connected in delta or star.
- (ii)




## 1) Advantages! →

- ① They have low losses
- ② They require little maintenance as there are no rotating parts
- ③ They can be easily installed as they are light and require no foundation.
- ④ They can work under ordinary atmospheric condition.


## disadvantages! →

- (i) They have short service life ranging from 8 to 9 yrs.
- (ii) They are easily damaged if the voltage exceeds the rated value.
- (iii) Once the capacitors are damaged, their repair is uneconomical.

## ② synchronous condenser! →

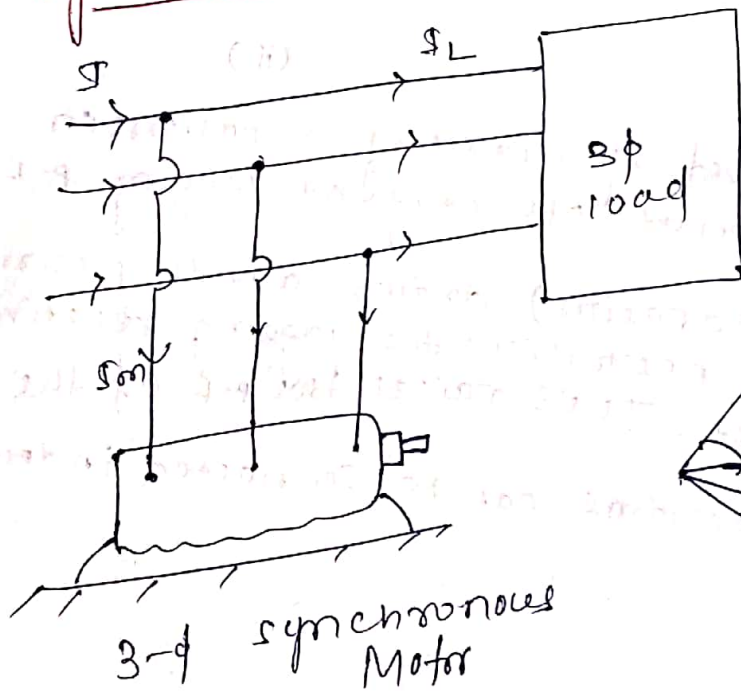

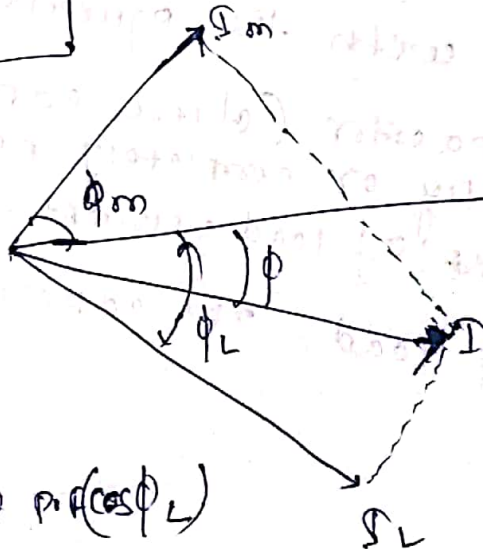so:  $\phi < \phi_L$   
 $\cos \phi > \cos \phi_L$



\* 3φ load taking current  $I_L$  at  $P.F.(\cos \phi_L)$   
 The synchronous condenser takes the current  $I_m$  at leading  $P.F. \cos \phi_m$   
 'm' is the sum of  $I_L$  &  $I_m$  and lag  $V$  by  $\phi'$

\* A synchronous motor takes a leading current when over-excited and therefore, behaves as a capacitor.


\* An over-excited synchronous motor running on no-load is known as synchronous condenser, and under this condition it behaves as a capacitor, which draws leading current.

\* when such a machine is connected in parallel with the supply, it takes a leading current which partly neutralises the lagging reactive component of the load. Thus the P.F. is improved.

\* synchronous condensers are generally used at major bulk supply substations for P.F. improvement.

### Advantages: →

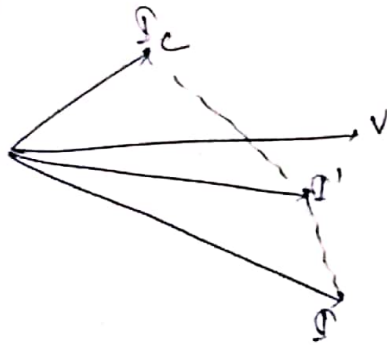(i) By varying the field excitation, the magnitude of current drawn by the motor can be changed by any ~~small~~ amount.



(2) The motor windings have high thermal stability to short circuit currents.

(3) The fault can be removed easily.

### Disadvantages: →

(i) There are considerable losses in the motor.

(ii) maintenance cost is high

(iii) It produces noise

(iv) Except in sizes above 500 kVA, the cost is greater than that of static capacitors of the same rating.

(v) As a synchronous motor has no self-starting torque, therefore, an auxiliary equipment has to be provided for this purpose.



## ① Load curve! →

The curve showing the variation of load on the power station w.r. to time is known as a load curve.

OR

Load curve is the graphical representation of load (in kW or MW) in proper time sequence and the time in hours. It shows the variation of load on the power station.

load curve is 3 types


### ① Daily load curve! →

When the load curve is plotted for 24 hours a day, then it is called daily load curve.
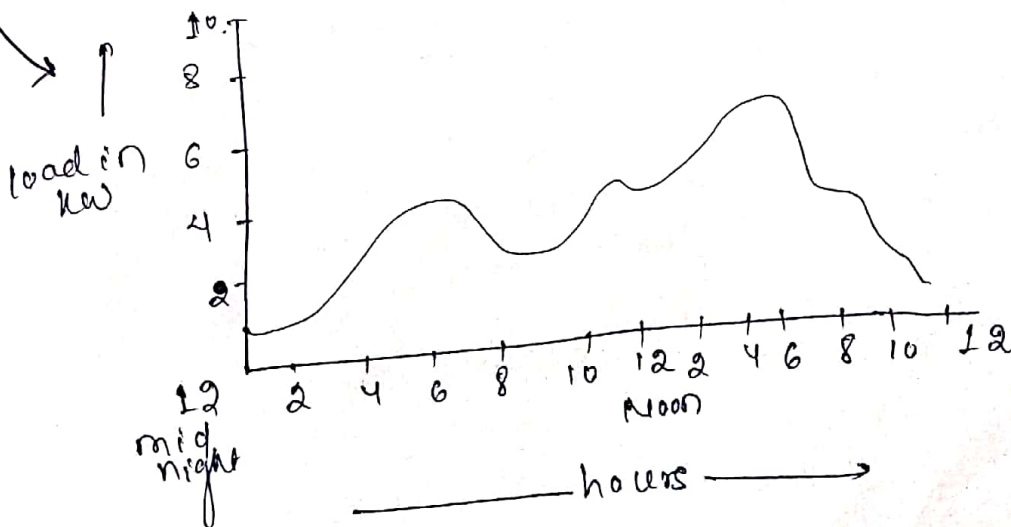
### ② Monthly load curve! →

\* When the load curve is plotted for a month, then it is called monthly load curve and it is obtained from the daily load curves of that month.

\* For this purpose, average values of power over a month at different times of the day are calculated and then plotted on the graph.



### ⑧ Maximum demand ! →

\* It is the greatest demand of load on the power station during a given period.  
(OR)

- \* The maximum demand is the power consumed over a predetermined period of time, which is usually b/w 8-30 minutes.
- \* maximum demand is generally less than the connected load because all the consumers do not switch on their connected load to the system at a time.
- \* The knowledge of maximum demand is very important as it helps in determining the installed capacity of the station.
- \* The station must be capable of meeting the maximum demand.

### ⑨ Connected load ! →

- \* It is the sum of continuous rating of all the equipments connected to supply system.
- A power station supplies load to thousand of consumers. Each consumer has certain equipment installed in his premises. The sum of the continuous rating of all the equipments in the consumer's premises is the "connected load" of the consumers.
- \* The sum of the connected loads of all the consumers is the connected load to the power station.  
 $5 \times 100 + 500 = 1000 \text{ watt}$



#### ④ Demand Factor →

It is the ratio of maximum demand on the power station to its connected load i.e.

$$\text{Demand factor} = \frac{\text{Maximum demand}}{\text{Connected load}}$$

$$\text{D.F.} < 1$$

The value of demand factor is usually less than 1. It is expected because maximum demand on the power station is generally less than the connected load.

$$\text{Demand factor} < 1$$

because maximum demand < connected load.

EX! →

$$\text{maximum demand} = 80 \text{ MW}$$

$$\text{connected load} = 100 \text{ MW}$$

$$\text{Demand factor} = \frac{80}{100} = 0.8$$

\* It helps in determining the capacity of the plant equipment.

#### ⑤ Average load! →

The average of loads occurring on the power station in a given period (day / month / year) is known as average load or average demand.

$$\text{Daily average load} = \frac{\text{No. of units (kwh) generated in a day}}{24 \text{ hours.}}$$

$$\text{Monthly average load} = \frac{\text{No. of units (kwh) generated in a month}}{\text{No. of hours in a month.}}$$

Yearly average load =  $\frac{\text{No. of units (kwh) generated in a year}}{8760 \text{ hours}}$

### ⑥ Load Factor :-

The ratio of average load to the maximum demand during a given period is known as load factor i.e.

$$\text{Load factor} = \frac{\text{Average load}}{\text{maximum demand}} = \frac{\text{Average load} \times T}{\text{max. demand} \times T}$$

= units generated in T hours

Load factor is always less than 1.

because Average load < maximum demand.  
\* Higher the load factor of power station, lesser will be the cost per unit generated.

### ⑦ Diversity Factor

The ratio of the sum of individual maximum demands to the maximum demand on power station is known as diversity factor i.e.

$$\text{Diversity factor} = \frac{\text{sum of individual maximum demands}}{\text{max. demand on power station}}$$

The diversity factor always greater than 1.

$$\boxed{D.F. > 1}$$

because sum of individual max. demand > max. demand on power station.

The greater the diversity factor, the lesser is the cost of generation of power.

A power station supplies load to various types of consumers whose maximum demands generally do not occurs at the same time.



8

### Plant capacity factor

It is the ratio of actual energy produced to the maximum possible energy that could have been produced during a given period i.e.

$$\text{Plant capacity factor} = \frac{\text{actual energy produced}}{\text{max. energy that could have been produced}}$$

$$= \frac{\text{average demand} \times T}{\text{plant capacity} \times T}$$


$$= \frac{\text{average demand}}{\text{plant capacity}}$$

Plant capacity! → The max<sup>m</sup> energy that could have been produced.

$$\text{Plant capacity factor} = \frac{\text{actual energy produced}}{\text{plant capacity}}$$

Load on the Power station can be considered in two parts, namely

- ① Base load
- ② peak load

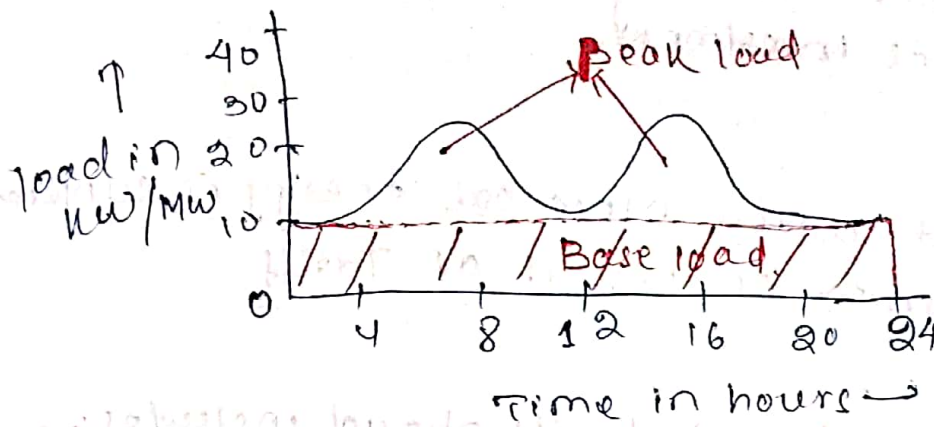

① Base load ! → The <sup>an</sup> ~~all~~ varying load which occurs almost the whole day on the station is known as base load.

\* in figure 10 MW is the base load of the station  
\* As base load on the station is almost of constant nature, therefore it can be suitably supplied without facing the problems of variable load.

② peak load ! → The variable peak demands of load over and above the base load of the station is known as peak load.



## Ch-9 Tariff

The supply company has to ensure that the tariff is such that it not only recovers the total cost of producing electrical energy but also earns profit on the capital investment.

\* The rate at which electrical energy is supplied to a consumer is known as Tariff.

Objectives of Tariff :- A tariff should include the following items

- (i) Recovery of cost of producing electrical energy at the power station.
- (ii) Recovery of cost on the capital investment in transmission and distribution systems.
- (iii) Recovery of cost of operation and maintenance of supply of electrical energy i.e. metering equipments, billing etc.
- (iv) A suitable profit on the capital investment.

## Different type of tariff

### ① Simple tariff! →

- \* Where there is a fixed rate per unit of energy consumed, it is called a simple tariff or uniform rate tariff.
- \* The price does not vary with increase or decrease in no. of units consumed.

### ~~Disadvantages~~

### ② Flat rate Tariff! →

When different types of consumers are charged at different uniform per unit rate, it is called a flat rate tariff.

### Advantages! →

The advantage of such a tariff is that it is more fair to different types of consumers and is quite simple in calculation.

### Disadvantages! →

- Since the flat rate tariff varies according to the way the supplies is used, separate meters are required for lighting load, power load etc. This makes the application of such a tariff expensive and complicated.
- A particular class of consumers is charged at the same rate irrespective of the magnitude of energy consumed. However a big consumers should be charged at a lower rate as in his case the fixed charges per unit are reduced.



### (3) Block rate tariff! →

when a given block of energy is charged at a specific rate and the succeeding block of energy are charged at progressively reduced rates, it is called a block rate tariff.

- In block rate tariff, the energy consumption is divided into blocks and the price per unit is fixed in each block.
- The price per unit in the first block is the highest, and it is progressively reduced for the succeeding blocks of energy.

EX! → For first 30 units → 60 paise per unit

Next 20 units → 55 paise per unit

and the remaining addl. unit → 30 paise per unit  
may be charged at the rate of 30 paise per unit

#### ④ Two Part Tariff! →

when the rate of electrical energy is charged on the basis of maximum demand of the consumer and the units consumed, it is called a two-part tariff.

→ In two-part tariff, the total charge to be made from the consumer is split into two components.

- ① Fixed charges → depends upon the maximum demand of the consumer is while
- ② Running charges, → depends upon the no. of units consumed by the consumers.

$$\text{Total charge} = Rs (b \times kW + c \times kWh)$$

$b$  = charge per kW of maximum demand

$c$  = charge per kWh of energy consumed.

→ This type of tariff is mostly applicable to industrial consumers who have appreciable maximum demand.

#### Advantages! →

- (i) It is easily understood by the consumers
- (ii) It recovers the fixed charges which depend upon the maximum demand of the consumers but are independent of the units consumed.

#### Disadvantages

- (i) The consumer has to pay the fixed charges irrespective of the fact whether he has consumed or not consumed the electrical energy.
- (ii) There is always error in assessing the maximum demand of the consumers.



Q.1

A consumer has a maximum demand of 200 kW at 40% load factor. if the tariff is Rs. 100 per kW of maximum demand plus 10 paise per kWh, find the overall cost per kWh.

$$\text{Load Factor} = \frac{\text{average load}}{\text{maximum demand}}$$

$$\text{average load for yr.} = \frac{\text{No. of units consumed (kWh)}}{8760 \text{ hrs.}}$$

$$\Rightarrow \text{Load factor} = \frac{\text{No. of units consumed (kWh)}}{\text{max}^m \text{ demand} \times 8760}$$

$$\begin{aligned} \Rightarrow \text{No. of units consumed (kWh)} &= \text{Load factor} \times \text{max}^m \text{ demand} \times 8760 \\ &= 0.4 \times 200 \times 8760 \\ &= 700800 \text{ kWh} \end{aligned}$$

$$\begin{aligned} \text{Annual charges} &= \text{Annual Max}^m \text{ demand} + \text{Annual energy consumed} \\ &= (a \times \text{kW} + b \times \text{kWh}) \\ &= (100 \times 200 + 0.1 \times 700800) \\ &= 90080 \end{aligned}$$

$$\text{overall cost/kWh} = \text{Rs. } \frac{90080}{700800} = 0.1285 \approx 12.85 \text{ paise}$$

## Ch-10 substation

### Bus-Bar Arrangements in sub-station

→ There are several bus-bar arrangements that can be used in a sub-station. This arrangement depends upon various factors such as system voltage, position of sub-station, degree of reliability, cost, etc.

#### (1) Single Bus-bar arrangement: →

→ It consists of a single bus-bar and all the incoming and outgoing lines are connected to it.

##### Advantages


- (i) low initial cost.
- (ii) Less maintenance.
- (iii) simple operation.

##### disadvantages

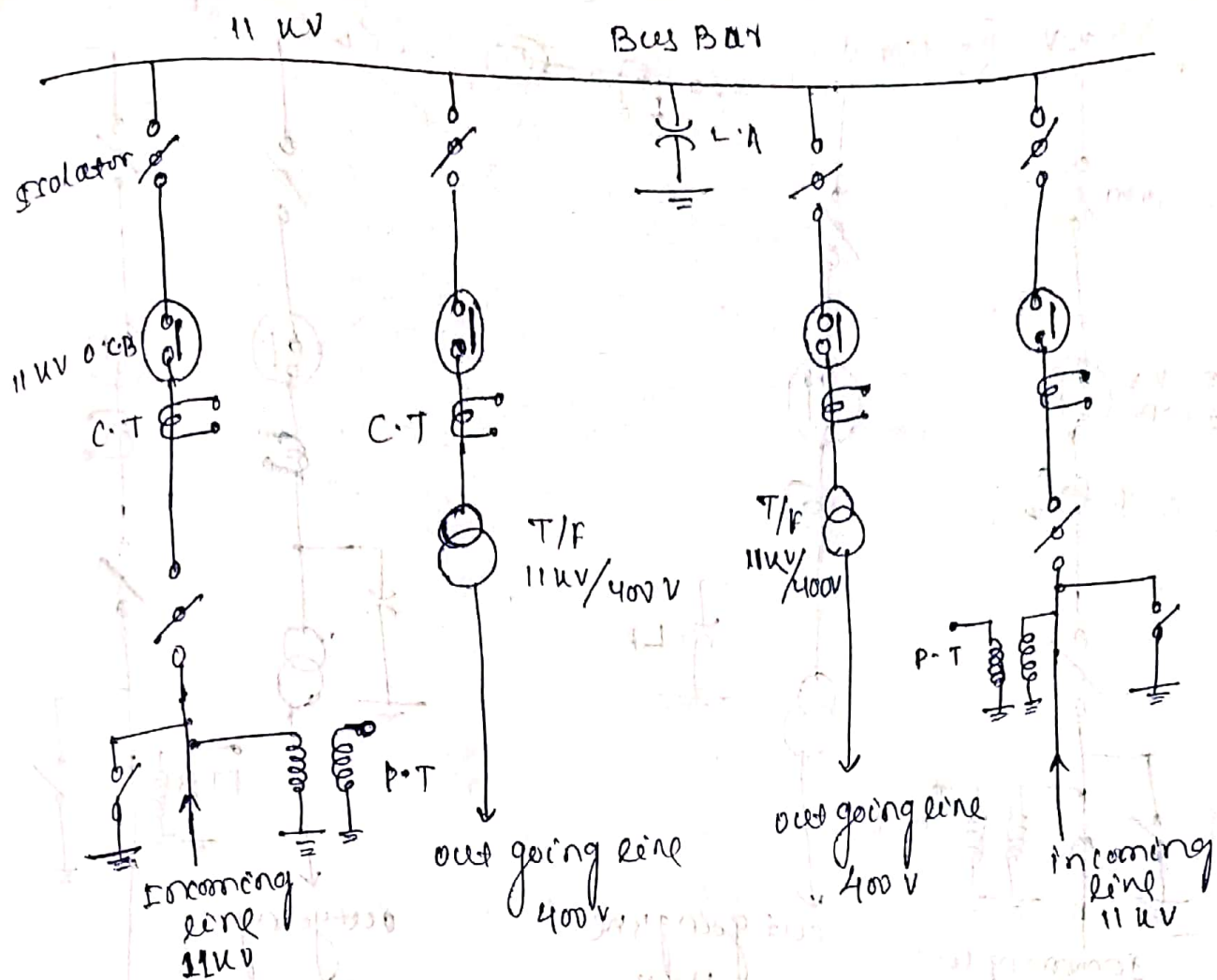- (i) If repair is to be done on the bus-bar or a fault occurs on the bus, there is a complete interruption of the supply.
- (ii) This arrangement is not used for voltage above 33 kV.

Here 2, 11 kV incoming line and 2, 400 V outgoing line connected to single bus.






(b) Single bus-bar system with sectionalisation  
 → In this arrangement, the single bus-bar is divided into two sections with circuit CB and isolator. and load is equally distributed on all the section.

### Advantages

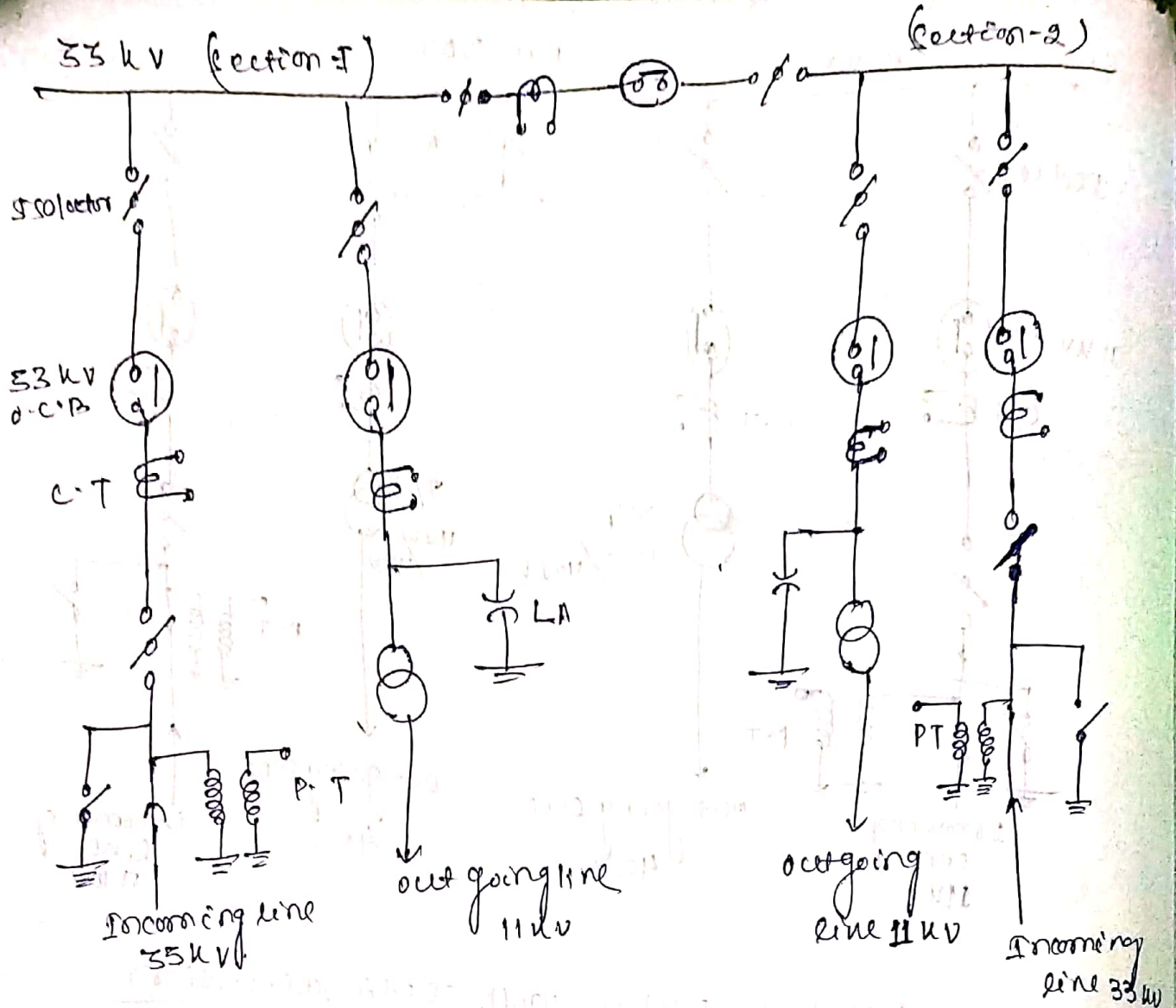- (i) If a fault occurs on any section of the bus, then that section can be isolated without affecting the supply from other section.
- (ii) Repair and maintenance of any section of the bus bar can be carried out by de-energising that section only, eliminating the possibility of complete shut-down.


→ This arrangement is used for voltage upto 33 kV.


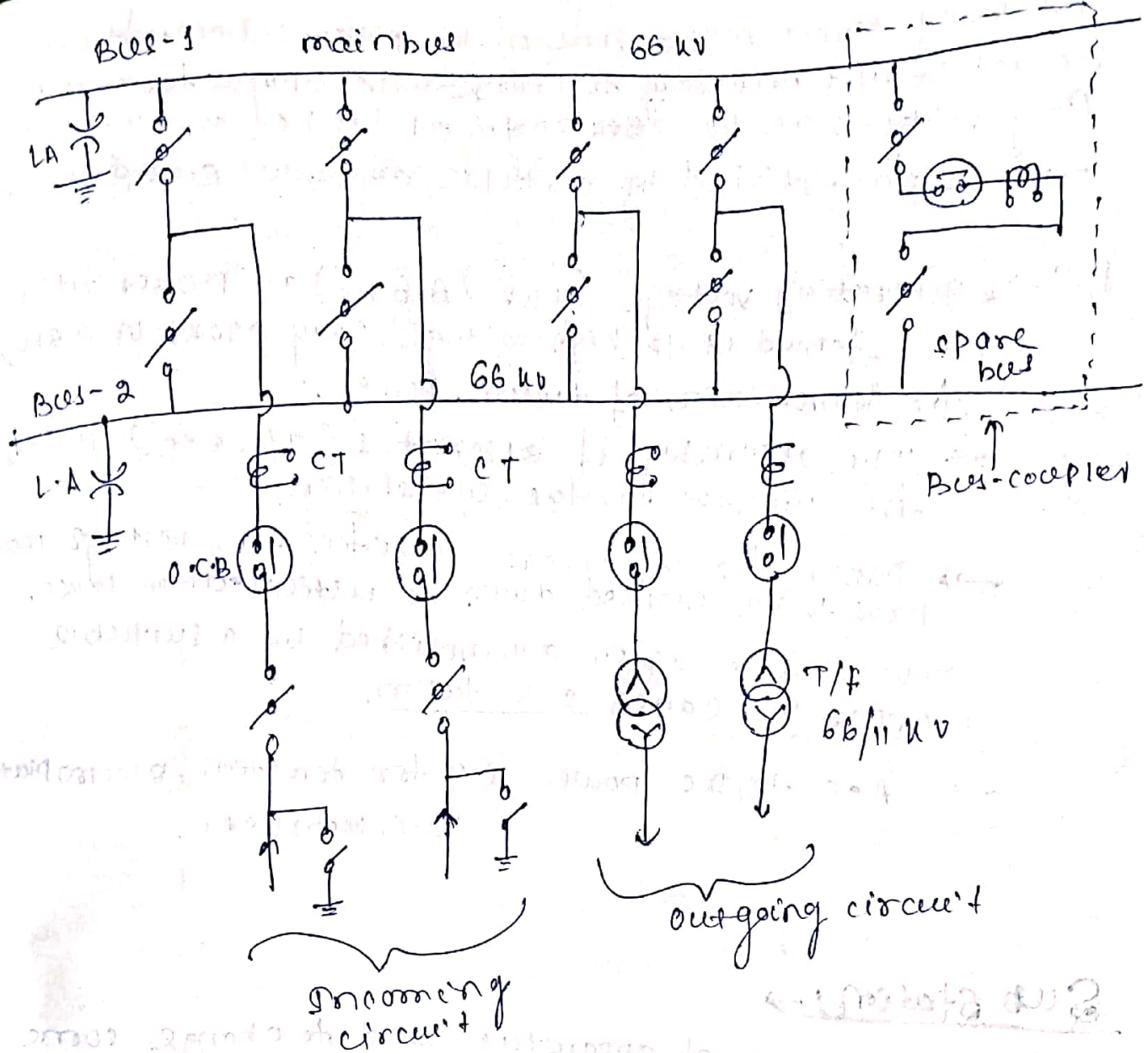
### (iii) Duplicate-bus-bar arrangements: →

- In this system, it consists of 2 bus-bars:
  - (i) main bus-bar and
  - (ii) spare bus-bar.
- Ordinarily, the incoming and out-going line always connected to the main bus-bar, but whenever in case of repair or fault occurring on main bus, the continuity of supply to the circuit can be maintained by transferring it to the spare bus by using bus-coupler.
- For voltage above 33 kV, duplicate bus-bar system is frequently used.





## Substation :-

→ Main function of substations are to receive energy transmitted at high voltage from the generating station, reduce the voltage to a value appropriate for local distribution and provide facilities for switching.

- receive energy
- Reduce energy
- switching operation

EX:- 11 kV or 6.6 kV

11 kV / 6.6 kV → 132 kV / 220 kV

132 kV → 440 volt.

- \* some sub-stations are simply switching stations where different connections b/w various transmission line are made, others are converting sub-stations which either convert ac into dc or vice versa or convert frequency from higher to lower or vice versa.
- \* It disconnect the cut or equipments during fault time.
- \* outgoing voltage can be regulated. For street light, switching control can be installed at sub-station.

\* At many places in the line of the power system, it may be desirable and necessary to change some characteristics (e.g. voltage, ac-dc, frequency, p.f etc) of the electric supply. This is accomplished by suitable apparatus called sub-station.

EX: → \* generation voltage (11 kV / 6.6 kV) at power station is stepped up to high voltage (say 220 kV or 132 kV) for transmission of electric power.

→ The assembly of apparatus (T/F etc) used for this purpose is the sub-station.

→ Near the consumer localities, the voltage may have to be stepped down to utilisation level.

This job is again accomplished by a suitable apparatus called sub-station.

→ A.C to D.C power for traction, electroplating, D.C Motors etc.

### Sub station: →

"The assembly of apparatus used to change some characteristics (e.g. voltage, ac to D.C, frequency, p.f etc) of electric supply is called a sub-station."

The following are the important points which must be kept in view while laying out a sub-station:

(1) It should be located at a proper site.  
(As far as possible, it should be located at the centre of gravity of load.)

(2) It should provide safe and reliable arrangement  
(for safety, consideration must be given to the maintenance of regulation clearance, facilities for carrying out repairs and maintenance, abnormal occurrences such as possibility of explosion or fire).  
For reliability, consideration must be given for good design and construction, the provision of suitable protective gear etc.)



- (iii) It should be easily operated and maintained.
- (iv) It should involve minimum capital cost.

## Classification of sub-stations

There are two most important ways of classifying them, are according to (a) service requirements  
(b) constructional features.

### (a) According to service requirements

A sub-station may be called upon to change voltage level or improve power factor or convert AC power to DC power etc.

According to the service requirements, sub-stations may be classified into: →

#### (1) Transformer sub-station! →

Those sub-stations which change the voltage level of electric supply are called T/f sub-station.

- These sub-stations receive power at some voltage & deliver it at some other voltage.
- ~~These~~ most of the sub-stations in the power system are of this type.

#### (2) Switching sub-station! →

These sub-stations do not change the voltage level. Incoming and outgoing lines have the same voltage.

However, they simply perform the switching operation of power line. (Such sub-stations are meant for switching operation of power lines without transforming the voltage)

#### (iii) Power factor correction sub-station! →

Those sub-stations which improve the power factor of the system are called power factor correction sub-station.

- Such sub-stations are generally located at the receiving end of transmission lines.
- The sub-stations generally use synchronous condensers as the power factor improvement equipment.



(4) Frequency changer sub-station: → Those sub-station which change the supply frequency are known as frequency change sub-station.

→ Such a frequency change may be required for industrial utilisation.

(5) Converting sub-station: → Those sub-station which change a.c power into D.C power are called converting sub-station.  
for such purpose as traction, electroplating, electric welding.

(6) Industrial sub-station: → These sub-stations which supply power to individual industrial concerns are known as industrial sub-stations.

(b) According to constructional features: →  
→ A sub-station has many components (e.g circuit breakers, switches, fuses, instruments etc) which must be housed properly to ensure continuous and reliable service.  
According to constructional features, the sub-stations are classified as:

(1) Indoor sub-station: →

→ for voltage upto 11 kV, the equipment of the sub-station is installed indoor because of economic consideration.

✓ Such sub-stations are usually for a voltage upto 11 kV but can be erected for the 33 kV and 66 kV when the surrounding atmosphere is contaminated with impurities such as metal corroding gases and fumes, conductive dust etc.

(2) Out-door sub-stations: →  
For such sub-stations are usually for voltage above 66 kV.

It is 2 types.



### ① Pole-mounted substation! →

- Such substations are erected for mounting distribution transformer of capacity upto 250 kVA.
- Such substations are cheapest, simple and smallest of substation.

### ② Foundation mounted substation! →

The T/F of capacity above 250 kVA the transformers are heavy for pole mounting. Such substations are usually for voltages of 33 kV and above.

### ③ Underground substation! →

In densely populated areas, the space available for equipment and building is limited and the cost of land is high. Under such situation, the sub-station is created underground.

### Transformer sub-station! →


In transformer sub-station, transformer is the main component employed to change the voltage level. T/F sub-station maybe classified as! →

#### (i) Step-up Transformer sub-station! →

The generated voltage, which is usually low (3.3, 6.6 or 33 kV), is stepped up to primary transmission voltage, so that huge blocks of power can be transmitted over long distances to the load centres economically. (11 kV - 220 kV)
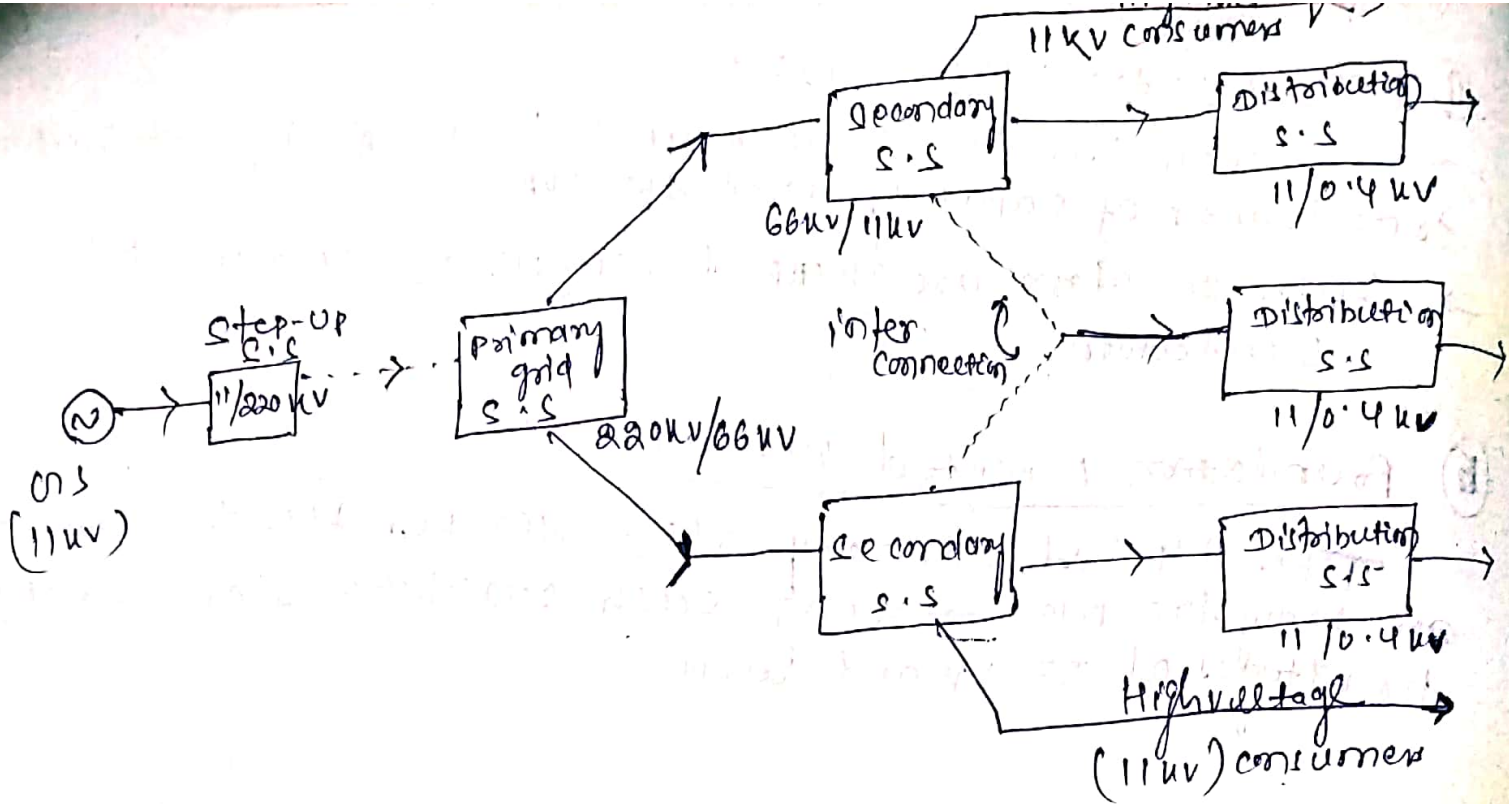
#### (ii) Primary grid substation! →

From the step-up sub-station, electric power at 220 kV is transmitted by 3φ, 3 wire overhead system to the outskirts of the city. Here electric power is received by the primary grid sub-station which reduces the voltage level to 66 kV for secondary transmission. (220 kV - 66 kV)



(iii) Secondary sub-station: → From the primary grid substation, electric power is transmitted at 66 kV by 3φ, 3 wire system to various secondary sub-station located at the strategic points in the city. At the secondary sub-station the voltage is further stepped down to 11 kV.

→ The 11 kV lines run along the important road sides of the city. It may be noted that big consumers (having demand more than 50 kW) are generally supplied power at 11 kV for further handling with their own sub-station.

(iv) Distribution S/S: → The electric power from 11 kV lines is delivered to distribution S/S. These S/S are located near the consumer localities and step-down the voltage to 400 V, 3φ - 4 wire for supplying to the consumers.



## underground S/S

In thickly populated cities, there is scarcity of land as well as the prices of land are very high. This has led to the development of underground S/S. In such S/S, the equipment is placed underground.

While laying out an underground S/S, the following point must be kept in view.

- The size of the station should be minimum as possible.
- There should be reasonable access for both equipment and personnel.
- There should be provision for emergency exits and protection against fire.
- There should be good ventilation.
- There should be provision for remote indication of excessive rise in temp. so that H.V supply can be disconnected.
- The T/F, switches and fuses should be air cooled to avoid bringing oil into the premises.